

Homework 1


Due date: Sep. 27th, 2022, Tuesday

Turn in your hard-copy hand-writing homework in class


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

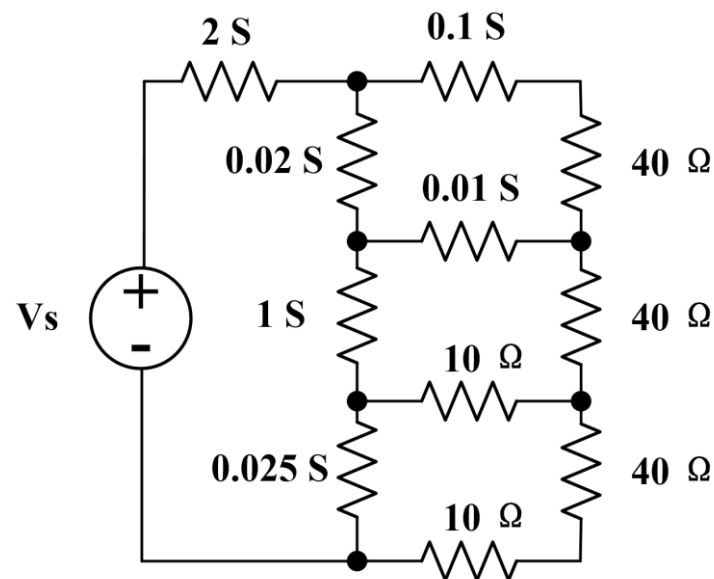
1. (a) Find the resistance seen by the ideal voltage source V_s in the circuit.
(b) If V_s equals 270V, how much power is dissipated in the 1S resistor?



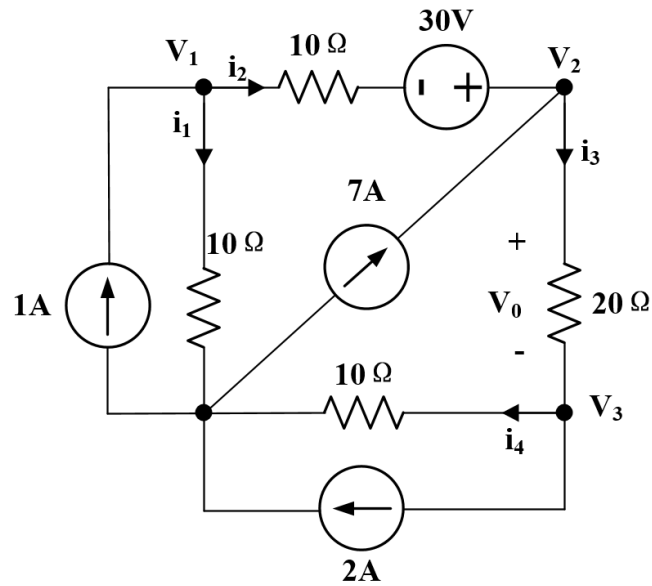
2. Apply nodal analysis method to obtain:
- (a) all the node voltages (V_1 , V_2 , and V_3) if assuming the bottomleft node as the reference node.
 - (b) all the currents (i_1 to i_4) and the voltage on 20Ω resistor (V_0).



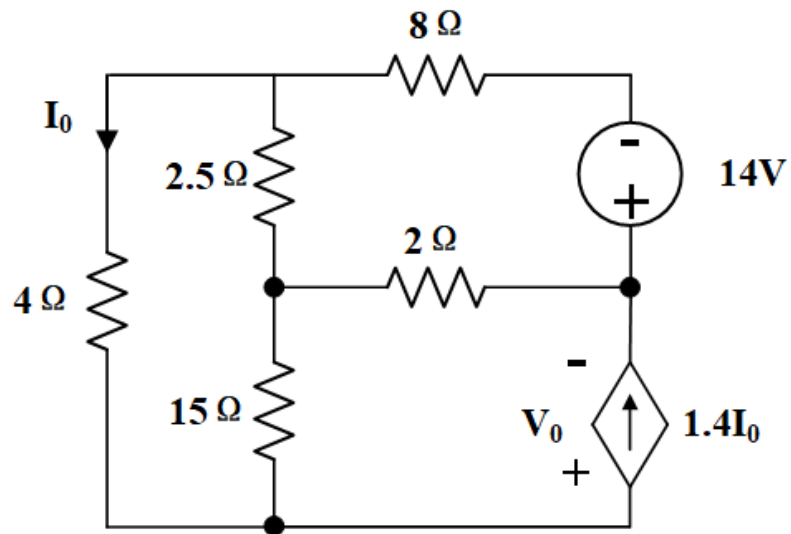3. Apply mesh analysis method to obtain I_0 and V_0 in the following circuit.



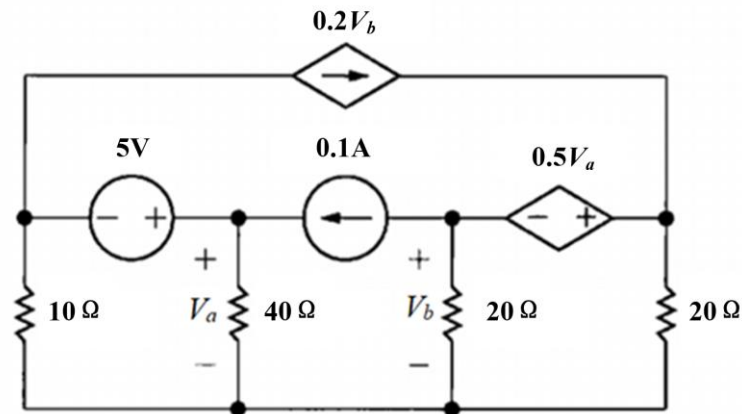4. For the circuit below,
- (a) apply nodal analysis method to find V_a , V_b .
 - (b) apply mesh analysis method to find V_a , V_b .
 - (c) find the power delivered by each source (2 current sources and 2 voltage sources).



5. For the circuit below, $R_1 = 1\Omega$, $R_2 = 2\Omega$,

(a) Apply nodal or mesh analysis method to find i_1

(b) If disconnect the current source from the circuit, try to find the equivalent resistance of **the pure resistor network** between node **a** and **b**.

