

ShanghaiTech University



EE 115B: Digital Circuits

Fall 2022

Lecture 19

Hengzhao Yang
December 13, 2022

 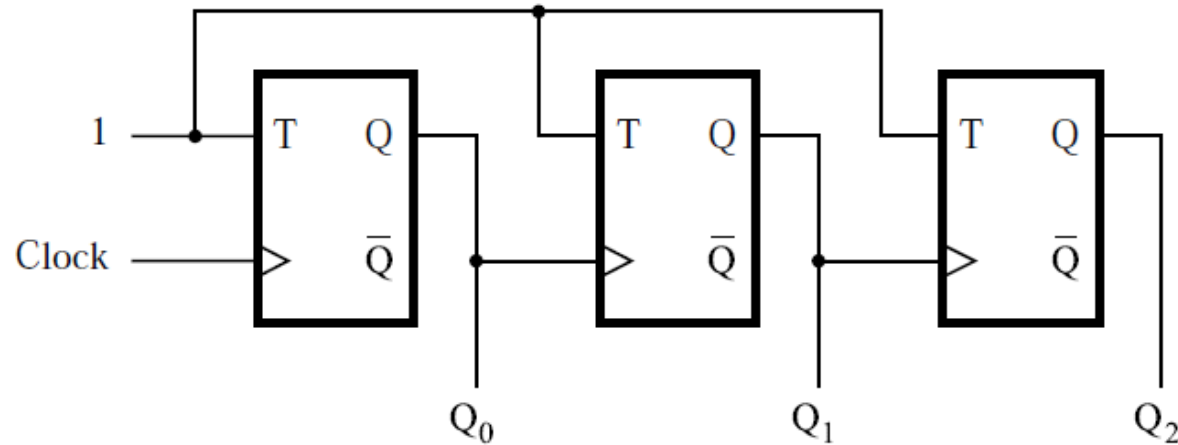Asynchronous down-counter with T flip-flops





Synchronous up-counter with T flip-flops

- Bit pattern: a given stage changes only when all the preceding stages satisfy $Q=1$
 - Q_0 changes at each clock positive edge
 - Q_1 changes only when $Q_0=1$
 - Q_2 changes only when $Q_0=1$ AND $Q_1=1$


- T input
 - $T_0 = 1$
 - $T_1 = Q_0$
 - $T_2 = Q_0Q_1$
 - $T_3 = Q_0Q_1Q_2$
 - .
 - .
 - .
 - $T_n = Q_0Q_1 \cdots Q_{n-1}$

Clock cycle	Q_2	Q_1	Q_0	
0	0	0	0	
1	0	0	1	
2	0	1	0	Q_1 changes
3	0	1	1	
4	1	0	0	Q_2 changes
5	1	0	1	
6	1	1	0	
7	1	1	1	
8	0	0	0	

 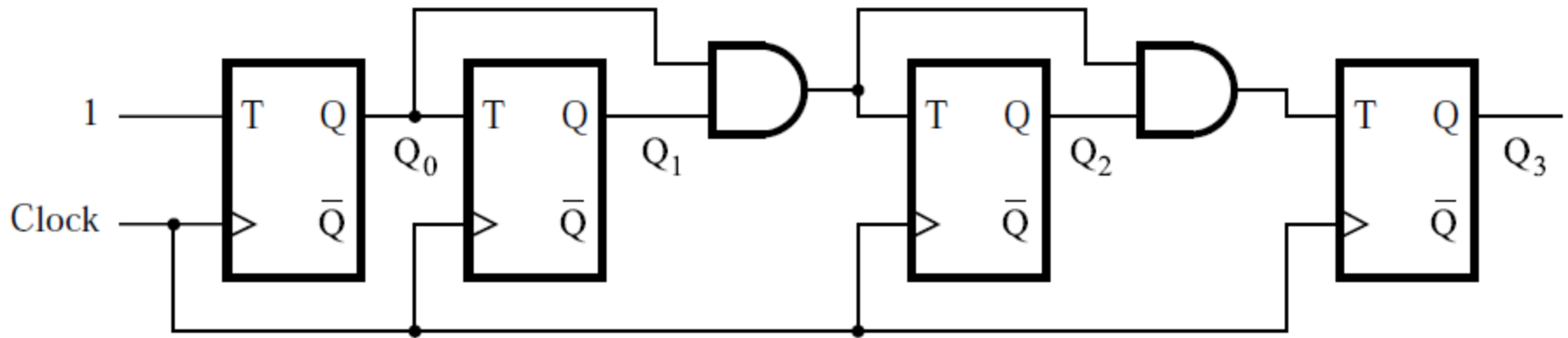4-bit synchronous up-counter with T flip-flops




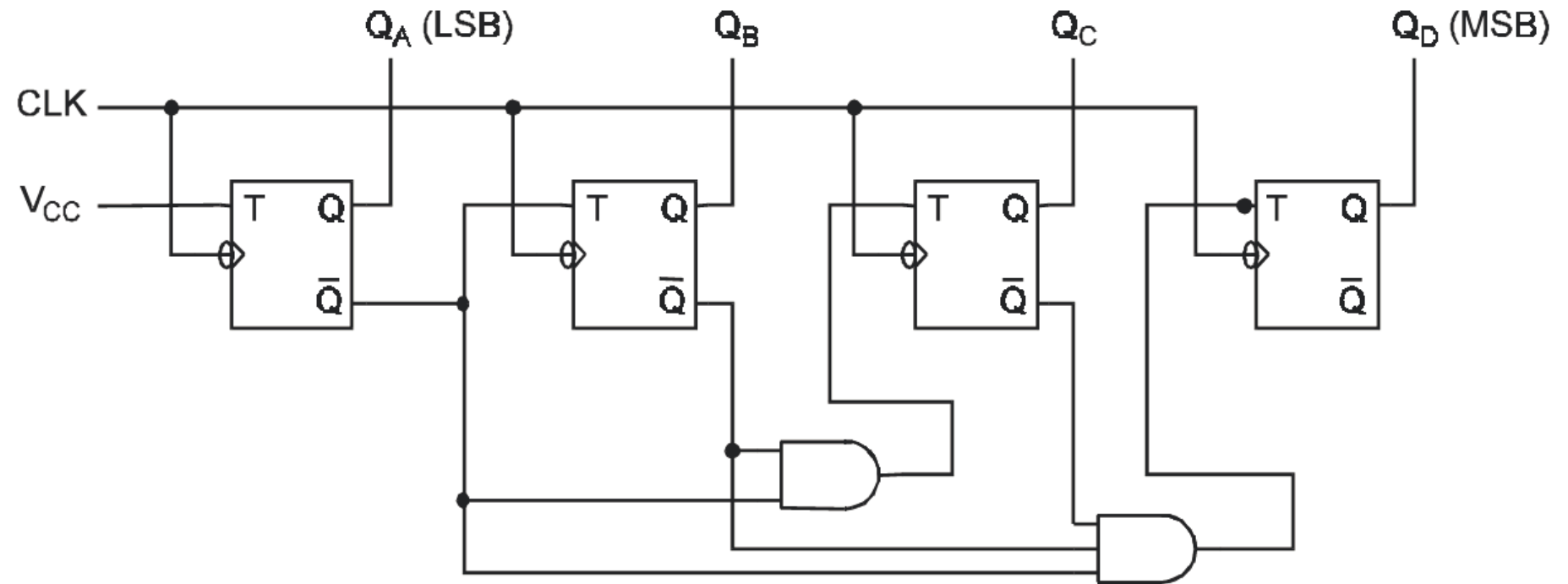4-bit synchronous down-counter with T flip-flops



Enable and clear capabilities

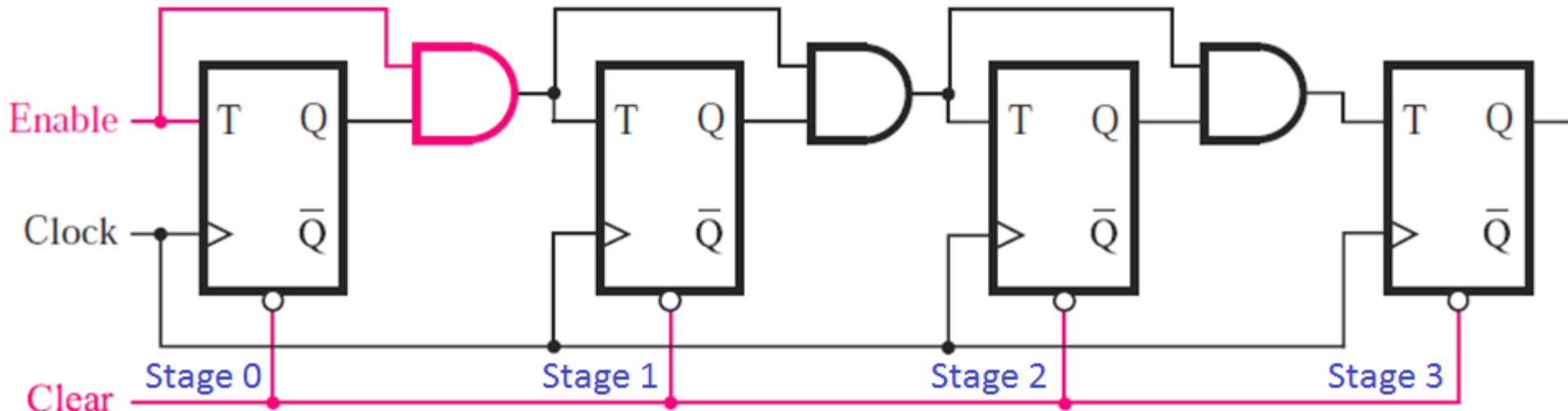- 4-bit synchronous up-counter with T flip-flops
 - Clear=0: reset counter output to 0 (clear is asynchronous)
 - T inputs: $T_0 = \text{Enable}$, $T_1 = Q_0 \cdot \text{Enable}$, $T_2 = Q_1 \cdot Q_0 \cdot \text{Enable}$, $T_3 = Q_2 \cdot Q_1 \cdot Q_0 \cdot \text{Enable}$
 - Enable=1: normal operation as counter
 - Enable=0: hold current state (all T inputs are 0)



Synchronous counter with D flip-flop

- D input

$$D_0 = Q_0 \oplus Enable$$

$$D_1 = Q_1 \oplus Q_0 \cdot Enable$$

$$D_2 = Q_2 \oplus Q_1 \cdot Q_0 \cdot Enable$$

$$D_3 = Q_3 \oplus Q_2 \cdot Q_1 \cdot Q_0 \cdot Enable$$

- Operation (stage 0)


- A=Enable, B=Q₀

- Enable=1

- D₀=Q₀', Q₀ flips


- Enable=0

- D₀=Q₀, Q₀ holds

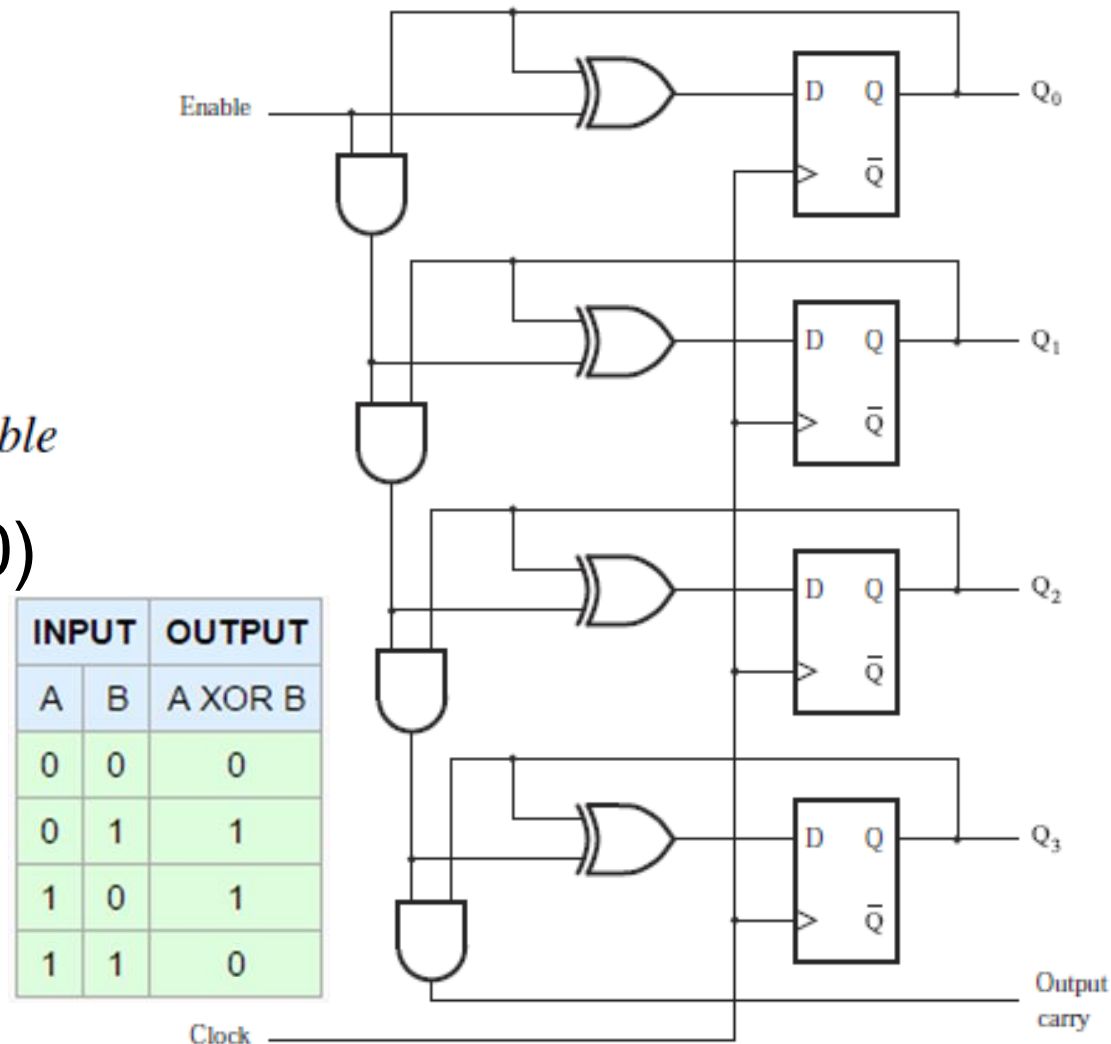

Synchronous counter with parallel loading

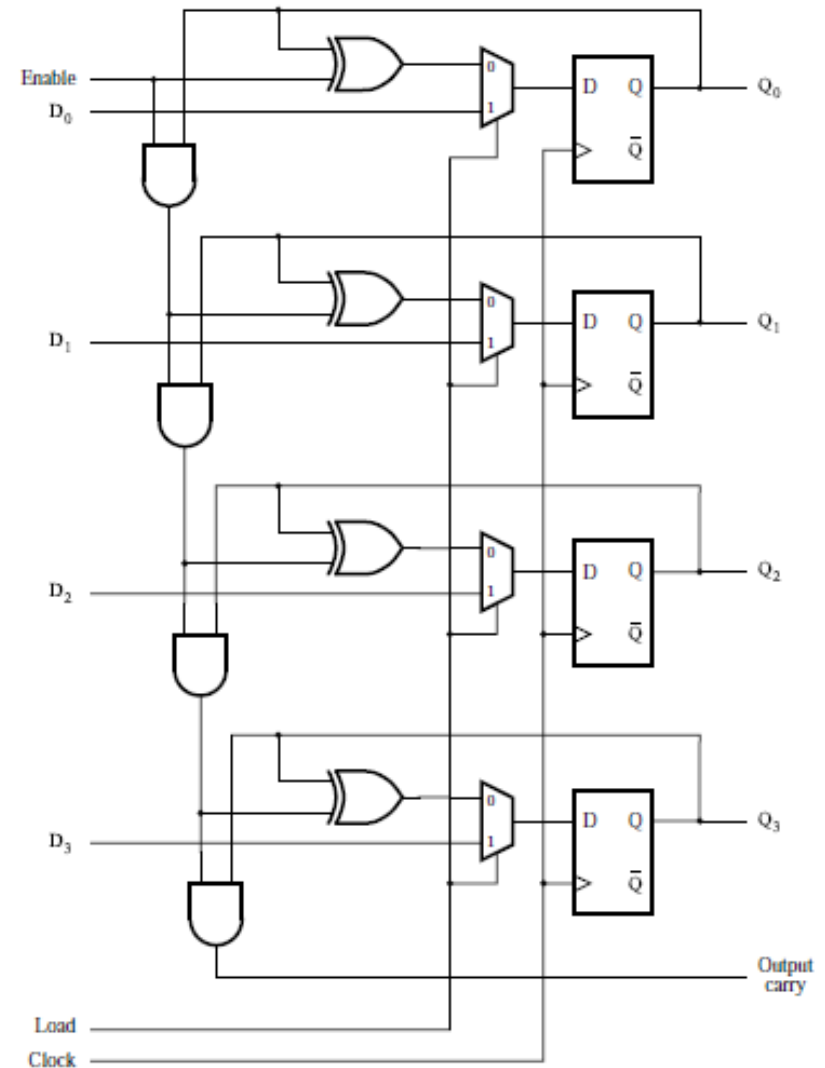- 2-to-1 mux
 - Load: mode selection signal
 - Load=0: normal counter
 - Load=1: load $D_3D_2D_1D_0$





Reset synchronization

- Reset counter during its normal operation
- Modulus (MOD number) of an N-bit counter is NOT always 2^N
- A modulo-6 (MOD-6) counter
 - States (counts): 0, 1, 2, 3, 4, 5
 - Reset is needed when count reaches 5
 - Synchronous reset
 - Asynchronous reset


Synchronous reset

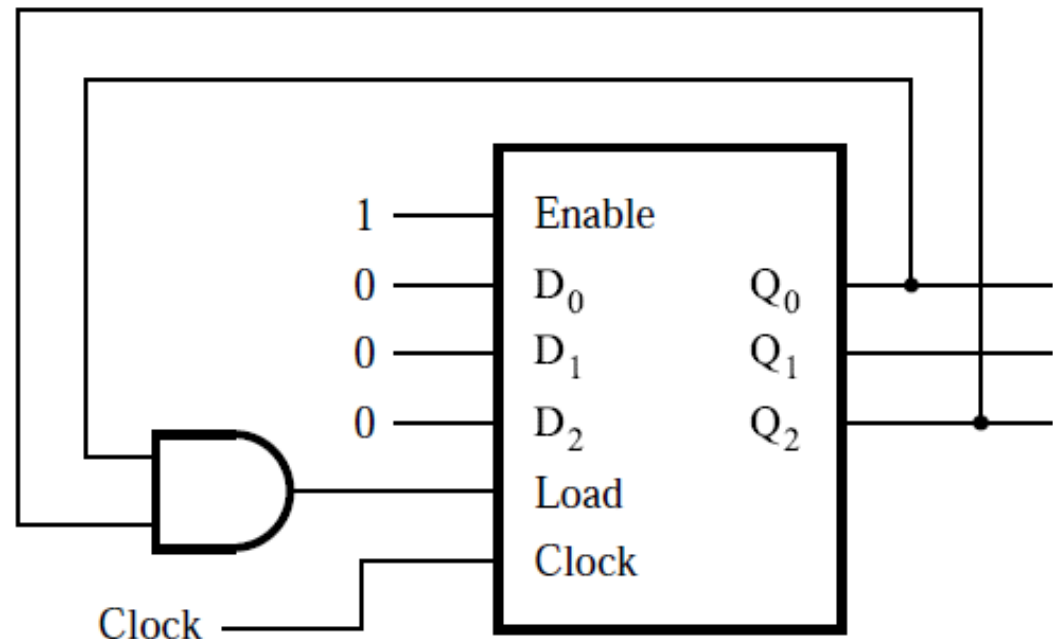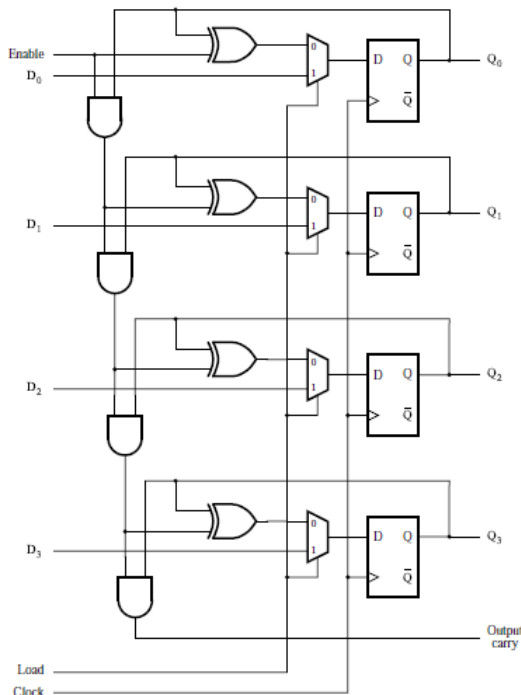- Reset: implemented using parallel loading mode
- Reset condition: $Q_2Q_1Q_0=101$ (count 5)
- Load=1 when $Q_2=Q_0=1$: load $D_2D_1D_0=000$ (reset counter)
- Reset is synchronized by clock



Synchronous reset

- Timing diagram

 


Asynchronous reset


- Reset: implemented using asynchronous clear signal generated by NAND gate
- Reset condition: $Q_2Q_1Q_0=101$ (count 5)
- Circuit modifications
 - NAND gate: use $Q_2=Q_0=1$ to generate asynchronous clear signal (active low)
 - Asynchronous clear: reset flip-flops
- Reset is NOT synchronized by clock

Asynchronous reset

- Original counter (4-bit synchronous)

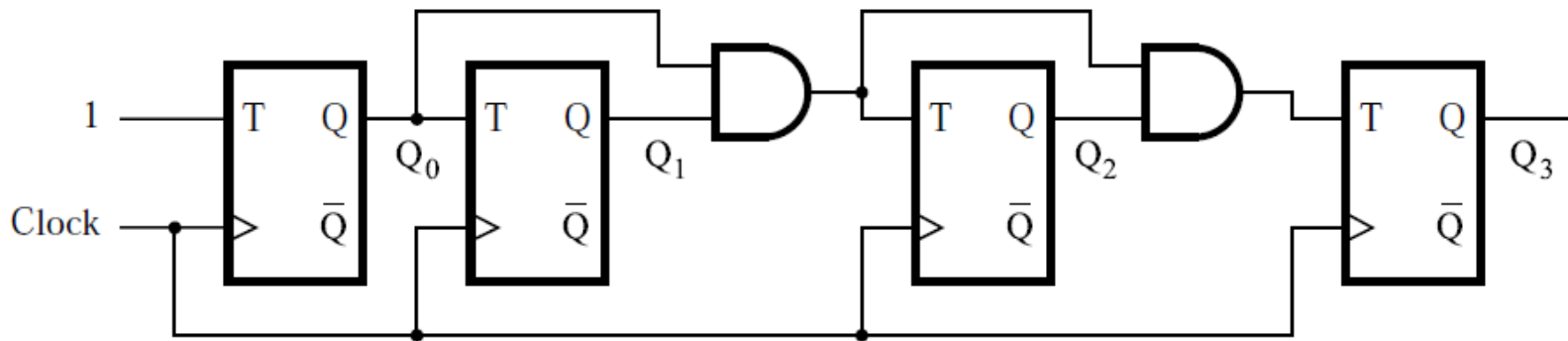


 - Modified counter with asynchronous reset (MOD-6)



Asynchronous reset

 - Timing diagram
 - State “5” duration is shorter than a clock cycle




Code for 4-bit synchronous up-counter with asynchronous reset (clear) and enable

- Ports

- Resetn: clear
- E: Enable

- Signal

- Count: flip-flop outputs

 

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
```

```
ENTITY upcount IS
```

```
    PORT ( Clock, Resetn, E : IN  STD_LOGIC ;
```

```
          Q : OUT STD_LOGIC_VECTOR (3 DOWNT0 0)) ;
```

```
END upcount ;
```

```
ARCHITECTURE Behavior OF upcount IS
```

```
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNT0 0) ;
```

```
BEGIN
```

```
    PROCESS ( Clock, Resetn )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```

```
            Count <= "0000" ;
```

```
        ELSIF (Clock'EVENT AND Clock = '1') THEN
```

```
            IF E = '1' THEN
```

```
                Count <= Count + 1 ;
```

```
            ELSE
```

```
                Count <= Count ;
```

```
            END IF ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
    Q <= Count ;
```

```
END Behavior ;
```

Code for 4-bit synchronous up-counter with asynchronous reset and parallel loading

- L: load
- R: parallel data
- Integer range: 4-bit

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY upcount IS
    PORT ( R          : IN      INTEGER RANGE 0 TO 15 ;
          Clock, Resetn, L : IN      STD_LOGIC ;
          Q          : BUFFER INTEGER RANGE 0 TO 15 ) ;
END upcount ;

ARCHITECTURE Behavior OF upcount IS
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Q <= 0 ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF L = '1' THEN
                Q <= R ;
            ELSE
                Q <= Q + 1 ;
            END IF;
        END IF;
    END PROCESS;
END Behavior;
```


Code for 3-bit down-counter

- Modulus: generic
- E: enable
- L: load
- Initial count: modulus-1

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY downcnt IS
    GENERIC ( modulus : INTEGER := 8 ) ;
    PORT ( Clock, L, E : IN  STD_LOGIC ;
          Q           : OUT INTEGER RANGE 0 TO modulus-1 ) ;
END downcnt ;


ARCHITECTURE Behavior OF downcnt IS
    SIGNAL Count : INTEGER RANGE 0 TO modulus-1 ;
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL (Clock'EVENT AND Clock = '1') ;
        IF L = '1' THEN
            Count <= modulus-1 ;
        ELSE
            IF E = '1' THEN
                Count <= Count-1 ;
            END IF ;
        END IF ;
    END PROCESS;
    Q <= Count ;
END Behavior ;
```

Chapter 8 Synchronous sequential circuits

- Sequential circuits
 - Also called finite state machines (FSMs)
 - Output depends on past behavior and present input


Sequential circuits

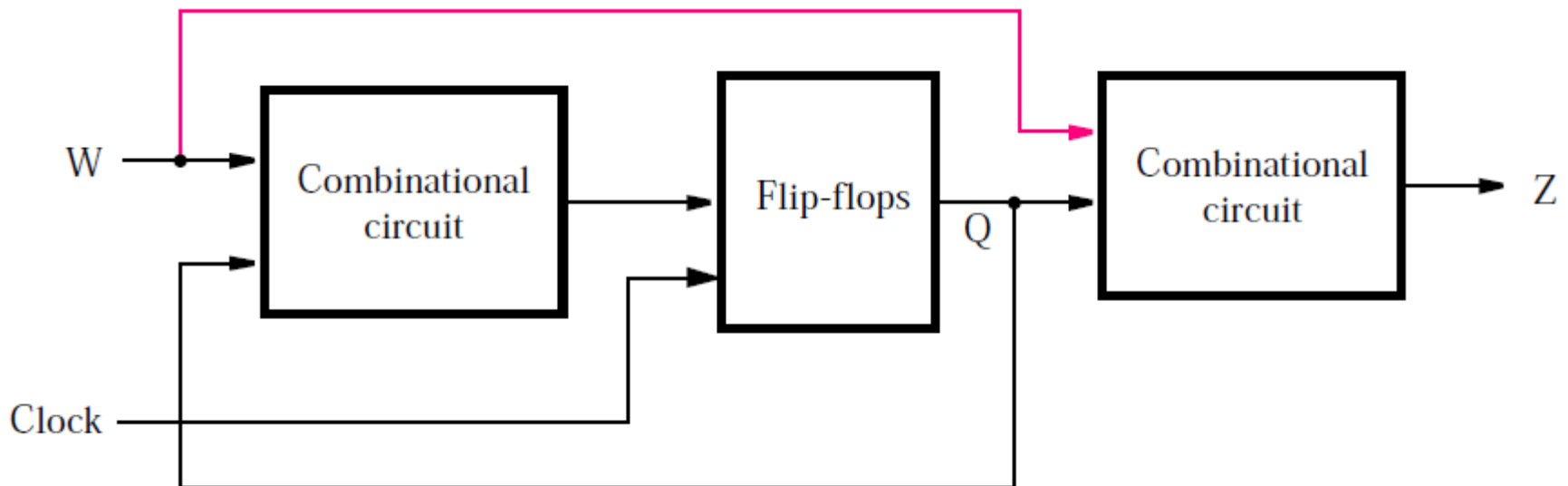- General form
 - Using combinational circuits and flip-flops
 - Input: W , output: Z , state: Q
 - Active clock edge: edge causing state change



Sequential circuits

 - Two types
 - Moore: output depends only on state (without red line)
 - Mealy: output depends on both state and input (with red line)



Synchronous sequential circuits

- Design flow
 - Example: sequence detector
- Moore FSM
- Mealy FSM