

## **Homework 7**


Due date: 8<sup>th</sup> December

Turn in your homework in class

Rules:


- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

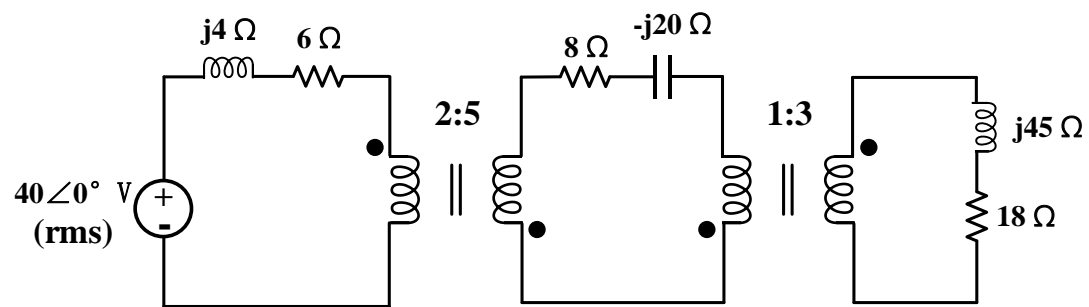1. For the circuit below, please find:
- (a) The complex power released by the source.
  - (b) The average power delivered to the  $18\Omega$  resistor.



2. For the following circuit, please find:

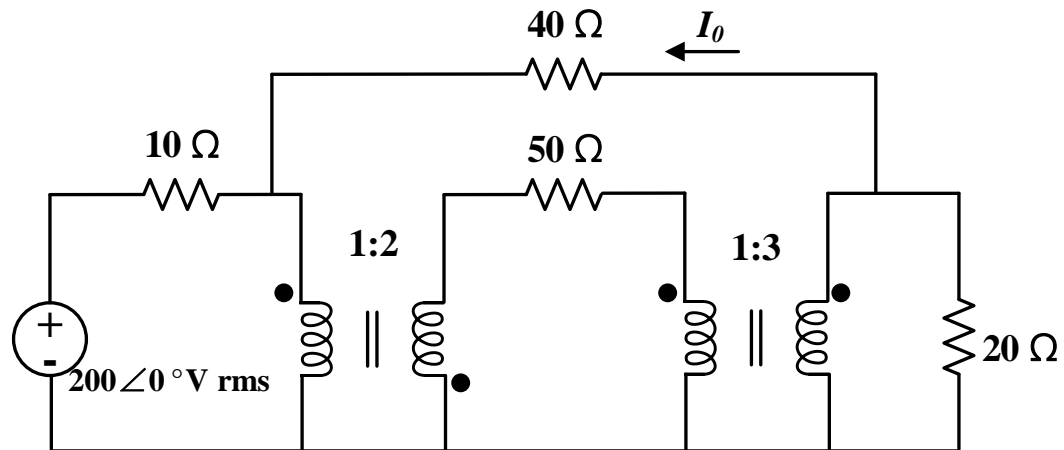- (1) The complex power released by the independent voltage source.
- (2) The average power absorbed by the  $20\Omega$  resistor.
- (3) The current  $I_0$




3. Generate Bode **magnitude and phase** plots for the following voltage transfer functions in (1) and (2).

$$(1) H(\omega) = \frac{4 \cdot 10^4 (60 + j6\omega)}{(j2\omega + 4)(j2\omega + 100)(j4\omega + 400)}$$

$$(2) H(\omega) = \frac{8 \cdot 10^{-2} (10 + j10\omega)}{j\omega (16 - \omega^2 + j4\omega)}$$

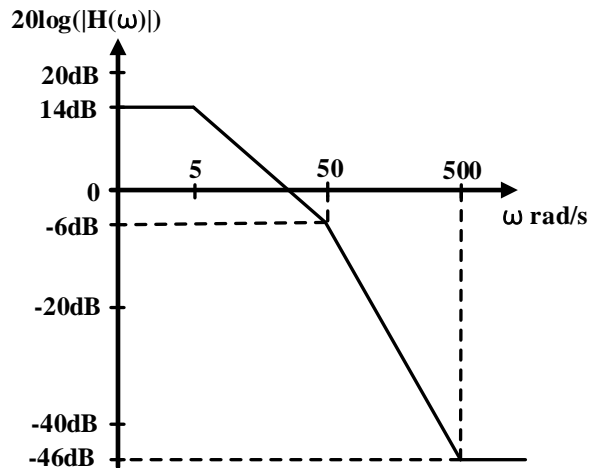(3) Determine the voltage transfer function  $H(\omega)$  corresponding to the Bode magnitude plot shown below. Note that the phase of  $H(\omega)$  is  $0^\circ$  at  $\omega=0$ .



4. For the circuit below, please find the transfer function  $H(\omega) = V_2/V_1$ , **Also** sketch the magnitude and phase frequency relation of bode plot.

