



Outline

- Basic Laws
 - Ohm's Law
 - Kirchhoff's Laws -- KCL, KVL
- Circuit Analysis
 - Nodal Analysis
 - Mesh Analysis



Circuit Analysis

- Two techniques will be presented in this part:
 - Nodal analysis, which is based on **KCL**
 - Mesh analysis, which is based on **KVL**




Nodal Analysis – Three Steps

- Given a circuit with n nodes, the nodal analysis is accomplished via three steps:
 1. Select a node as the reference (i.e., ground) node. Assign the node voltages to the remaining $(n-1)$ nodes. Voltages are relative to the reference node.
 2. Apply KCL to the $(n-1)$ nodes, expressing branch current in terms of the node voltages (using the I - V relationships of branch elements).
 3. Solve the resulting simultaneous equations to obtain the unknown node voltages.





Nodal Analysis: Example #1

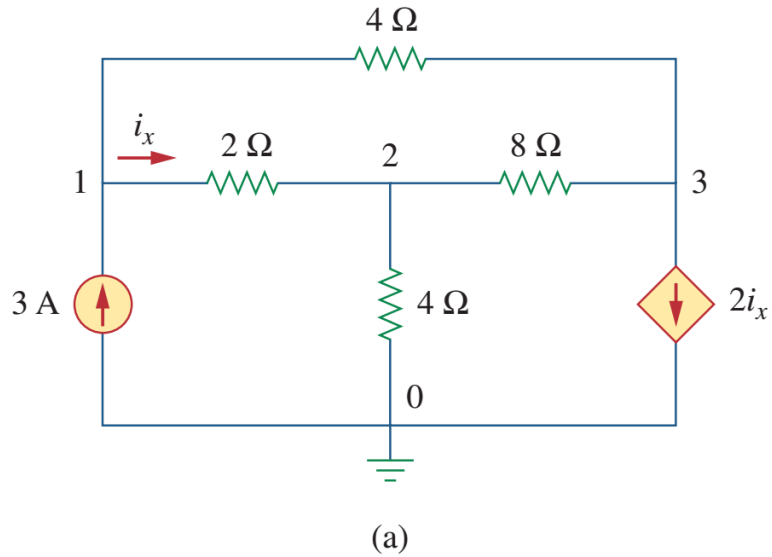




Nodal Analysis: Example #1

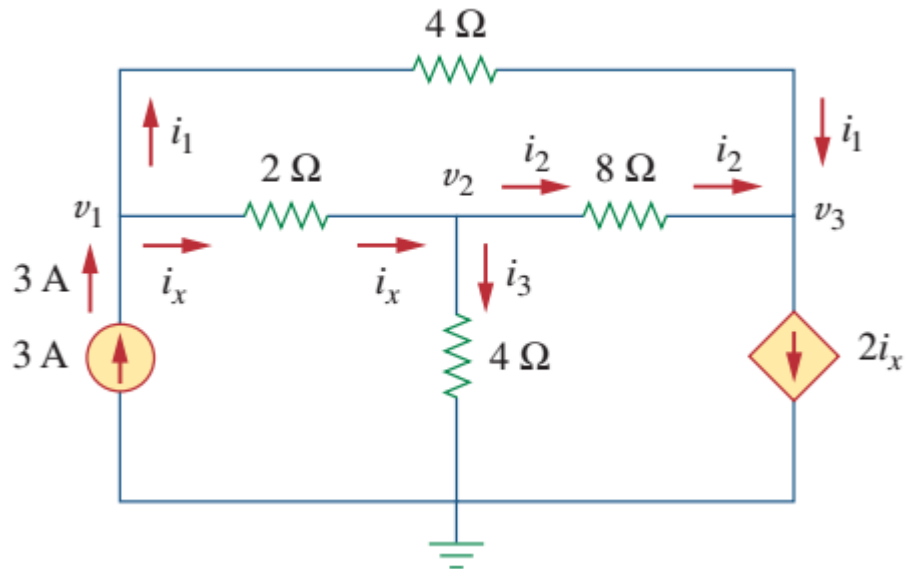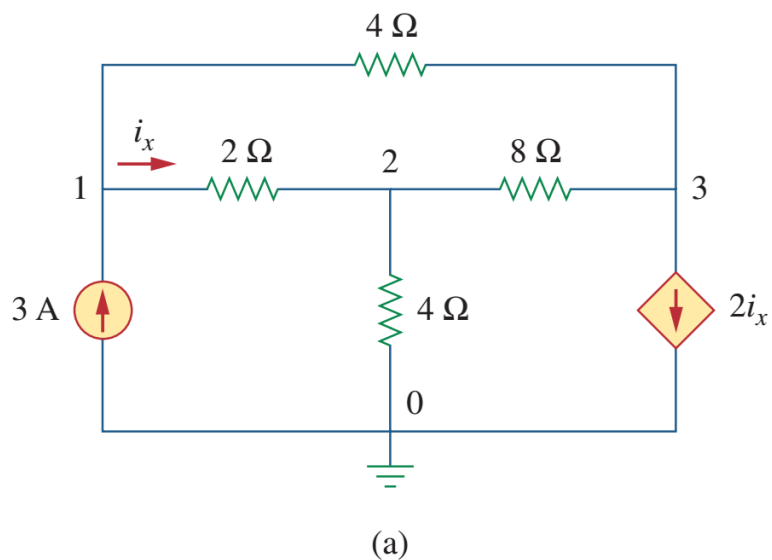



Nodal Analysis with Voltage Sources

Case I:

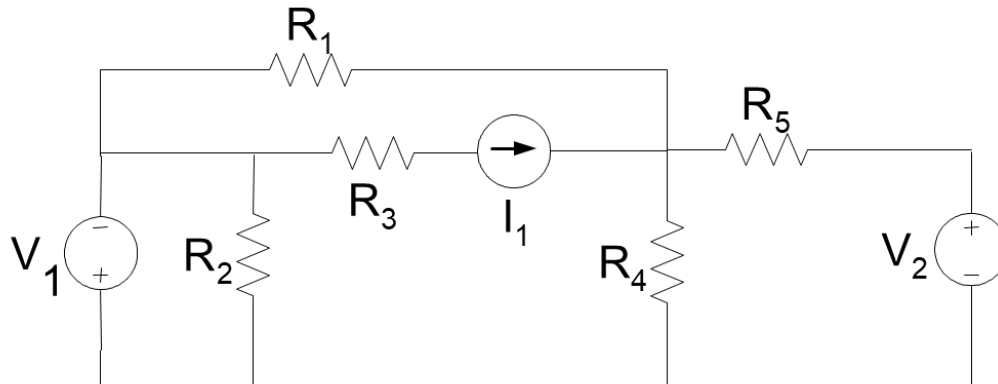




Nodal Analysis: Supernode

Case II

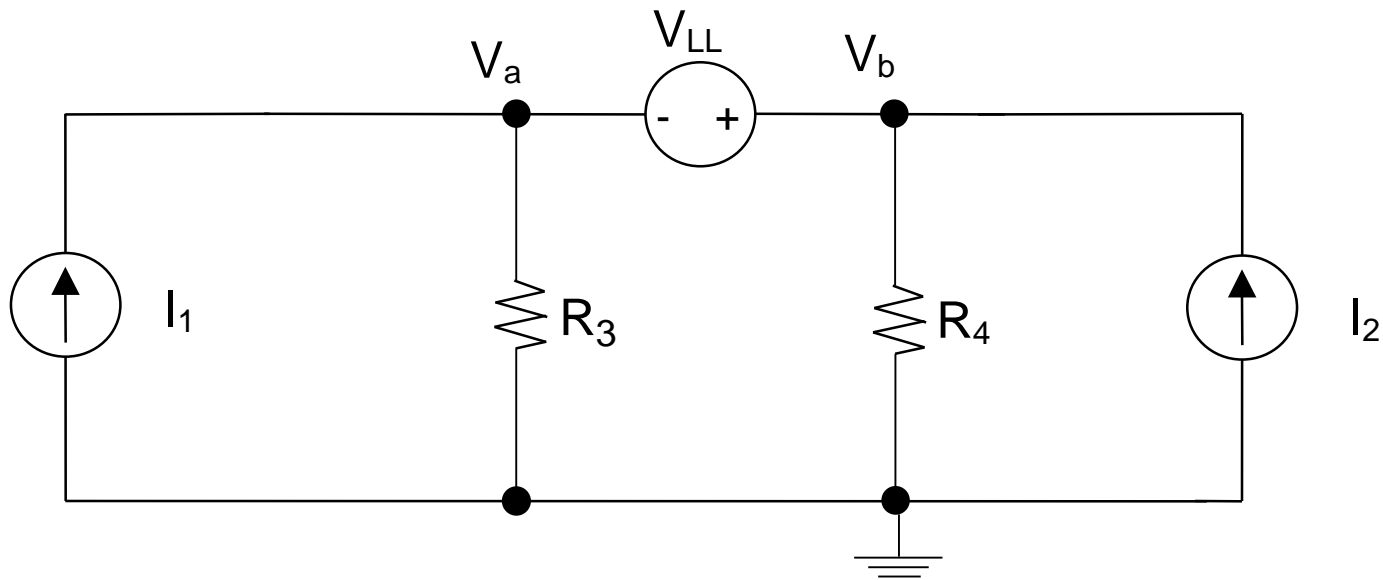A “floating” voltage source is one for which **neither** side is connected to the reference node, e.g. V_{LL} in the circuit below:




A supernode is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.



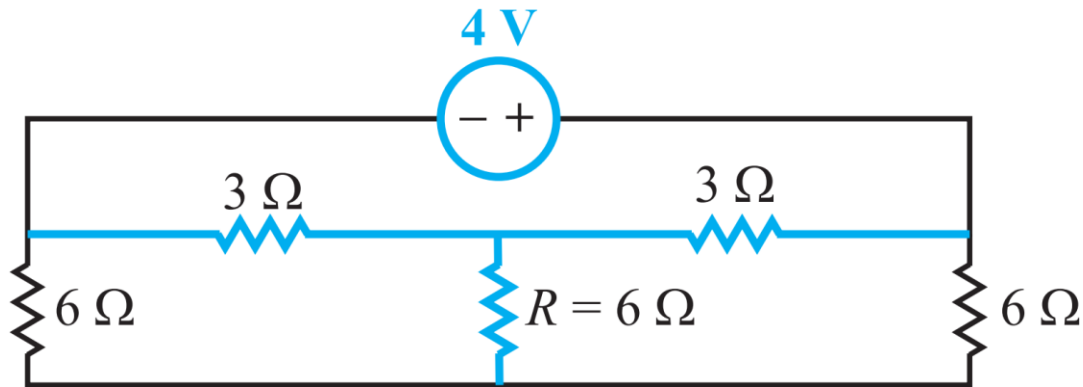Exercise


- Find the power supplied by the voltage source.



Mesh Analysis--Loop, Independent Loop, Mesh

- A loop is a closed path.
- A loop is independent if it contains at least one branch which is not a part of any other independent loop.
- A mesh is a loop that does not contain any other loop within it.

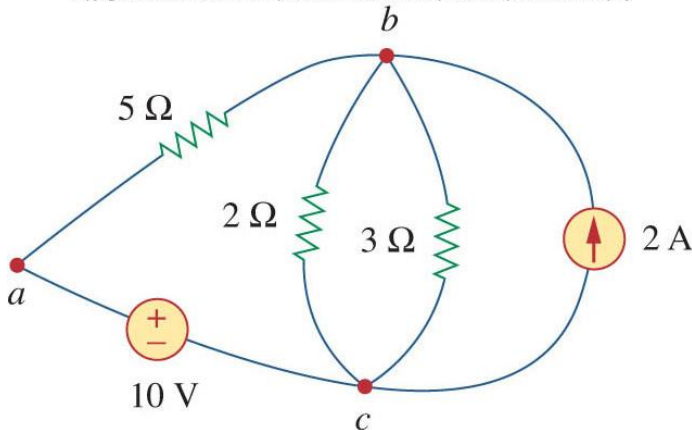Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



- b – number of branches
- n – number of nodes
- l_{ind} – number of ind. loops


Mesh = Independent loop?

$$l_{ind} = b - (n - 1)$$



Mesh Analysis

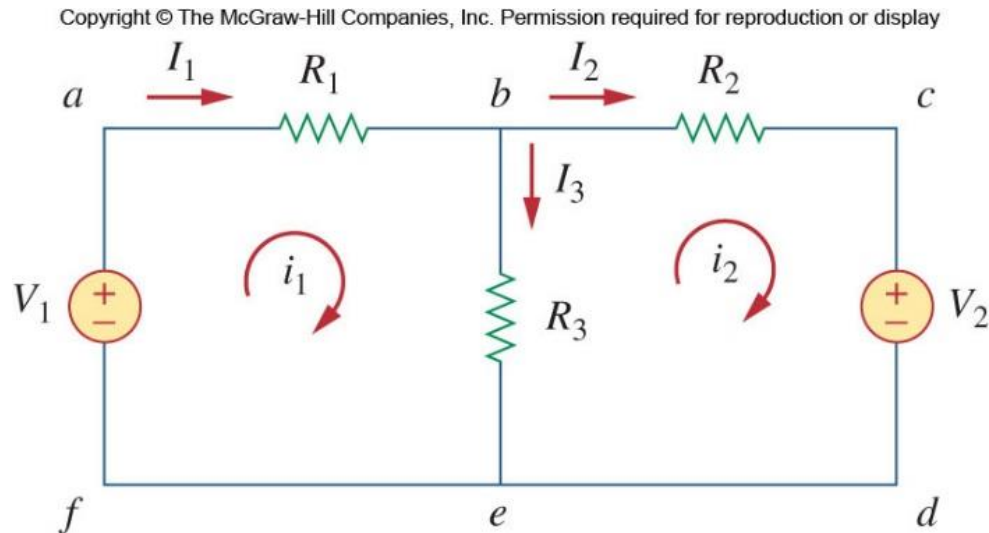- Another general procedure for analyzing circuits is to use the mesh currents as the circuit variables.




- Mesh analysis uses KVL to find unknown currents.




Mesh Analysis Steps

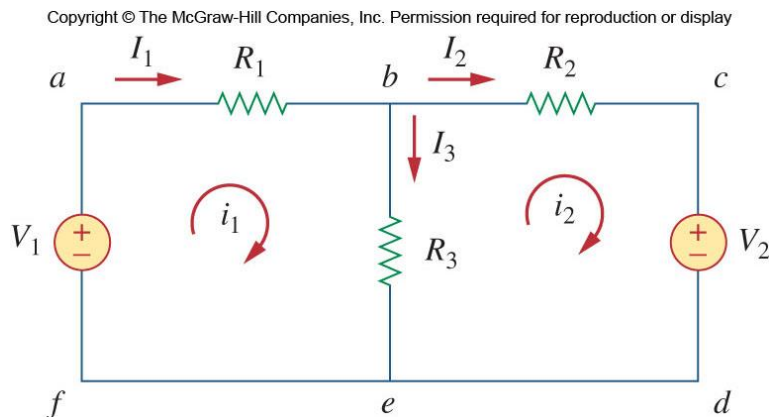- Mesh analysis follows these steps:
 1. Assign mesh currents i_1, i_2, \dots, i_x to the x meshes
 2. Apply KVL to each of the x mesh currents.
 3. Solve the resulting x simultaneous equations to get the mesh currents.






Example

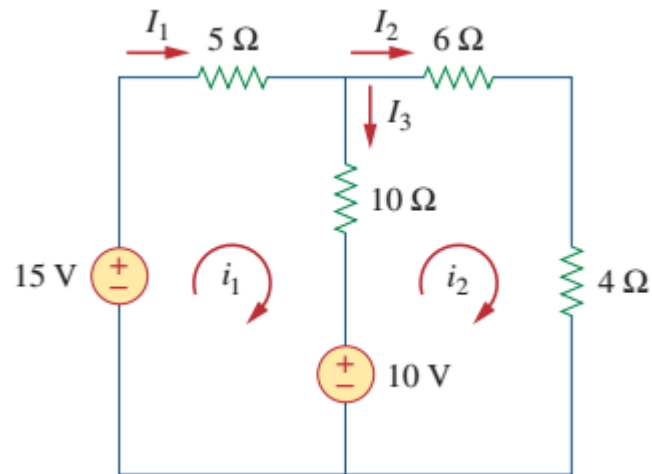


Mesh Analysis with Current Sources

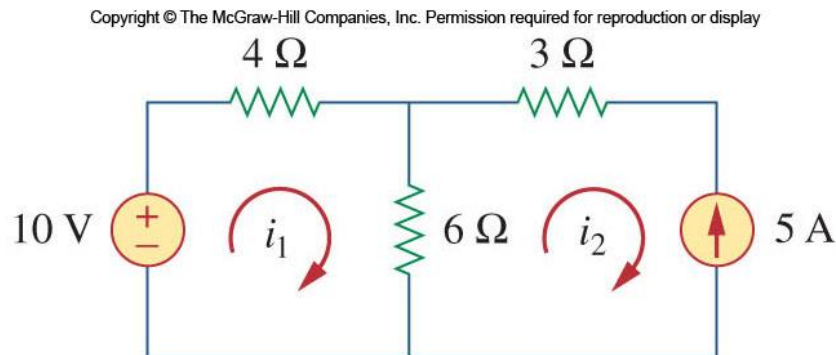- The presence of a current source makes the mesh analysis simpler in that it reduces the number of equations.
 - If the current source is located on only one mesh, the current for that mesh is defined by the source. For example:







If the current source is located...

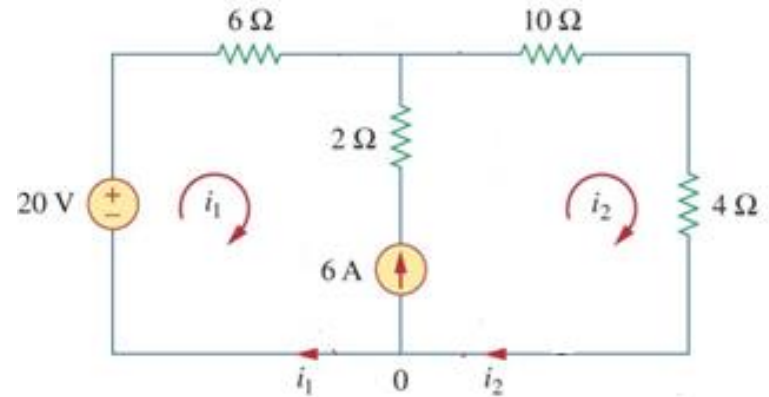




Supermesh

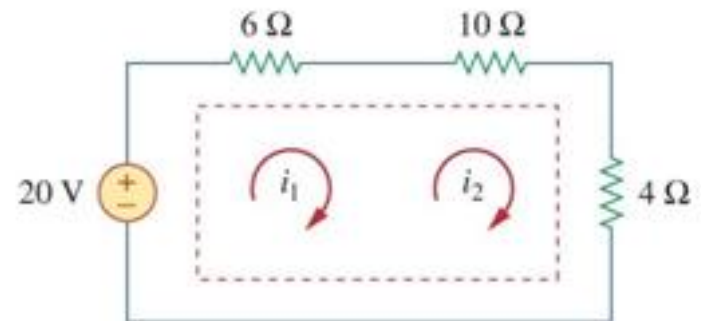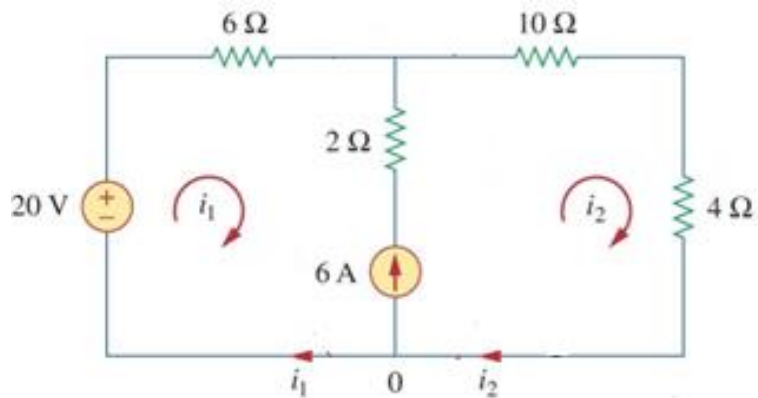

Summary

• Node Analysis

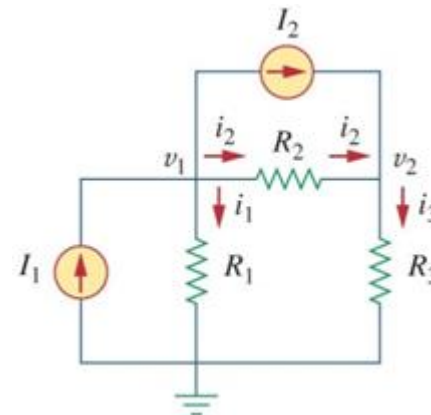- Node voltage is the unknown
- Solve by KCL
- Special case: Floating voltage source



• Mesh Analysis

- Loop current is the unknown
- Solve by KVL
- Special case: Current source

