

Homework 5Due date: May 4th

Turn in your homework online before the class

Rules:

- Please work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1

[16 points]

- (a). The circuit is shown in **Fig 1:a**. Assume steady state of the circuit. Known that $u_S(t) = 1.5\sqrt{2}\cos(10^5t + 60^\circ)\text{V}$. Express $i_R(t)$, $i_L(t)$, $i_C(t)$, $i(t)$, in phasor domain.
- (b). The circuit is shown in **Fig 1:b**. Assume steady state of the circuit. Known that $i(t) = 1\cos(10^7t + 90^\circ)\text{A}$. Express $u_R(t)$, $u_L(t)$, $u_C(t)$, $u_S(t)$ in phasor domain..

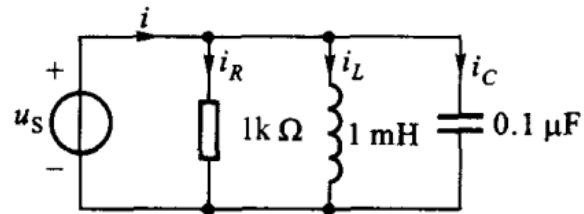


Figure 1: a

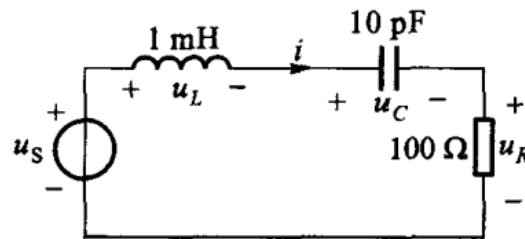


Figure 1: b

2

[12 points] The circuit is shown in **Fig 2**. Use phasor approach to calculate the currents \dot{I}_R , \dot{I}_C , \dot{I}_L , and draw the phasor diagram of the above three currents.

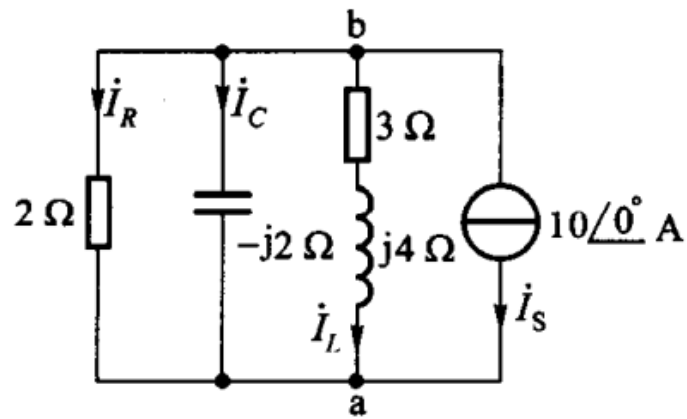


Figure 2

3

[10 points] The circuit is shown in **Fig 3**. $\dot{U}_S = 24\angle 60^\circ \text{V}$, $\dot{I}_S = 6\angle 0^\circ \text{A}$. Use mesh analysis to calculate \dot{I}_1 and \dot{I}_2 .

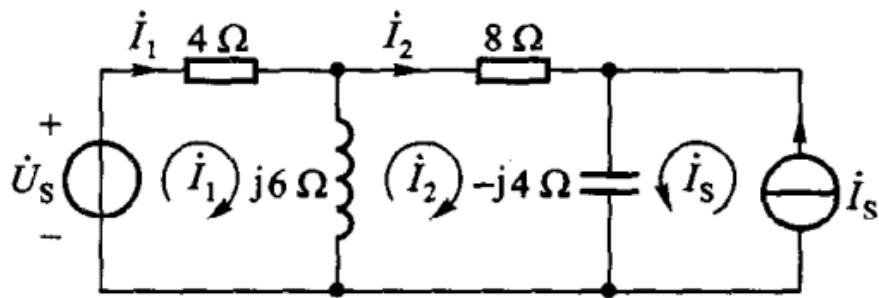


Figure 3

4

[10 points] The circuit is shown in **Fig 4**. $\dot{U}_S = 10\angle 0^\circ \text{V}$, $\mu = 0.5$. Use nodal analysis to calculate \dot{U}_2 .

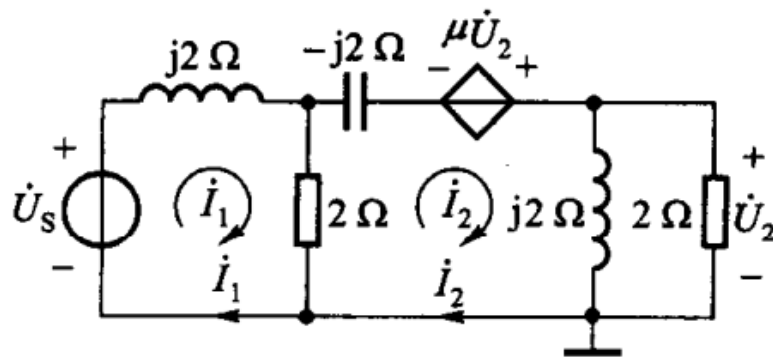


Figure 4

5

[12 points] The circuit is shown in **Fig 5**. The circuit is under sinusoidal steady state. Known that $i_S(t) = 30\sqrt{2}\cos 20t$ A. For the circuit excluding the 30Ω resistance, find the Thevenin equivalence (phasor domain) at the terminals a-b. Afterwards, use the Thevenin equivalence to calculate $u_k(t)$.

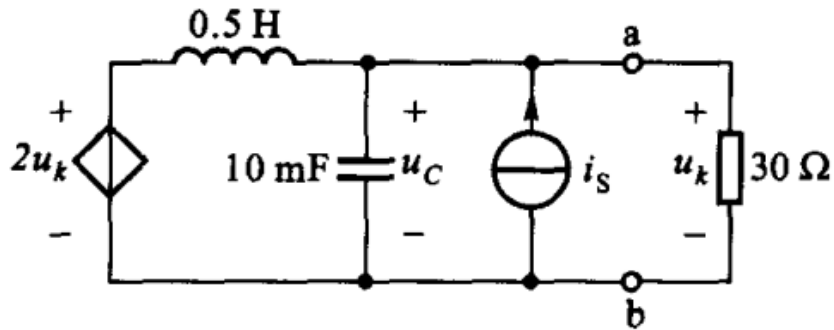


Figure 5

6

[14 points] The circuit is shown in **Fig 6**. The circuit is under sinusoidal steady state. Known that $i_S(t) = 10\sqrt{2}\cos 100t$ A, $u_S(t) = 100\sqrt{2}\cos 1000t$ V. Find $i_L(t)$. (Note: you should be careful about the operating frequency of the system when applying phasor domain equivalence)

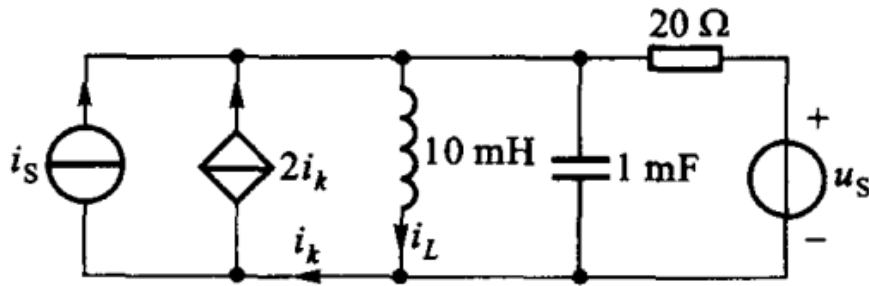


Figure 6

7

[12 points]

- (a). The circuit is shown in **Fig 7:a**. All of the elements are working in Sinusoidal Steady-state. Find out the relationship that the values of the elements satisfy to make the equivalent impedance (between a and b) pure resistive at any frequency. (Please make sure that you write down all of the conditions).
- (b). The circuit is shown in **Fig 7:b**. All of the elements are working in Sinusoidal Steady-state. Try to figure out what conditions the values of the elements and ω have to meet to make sure that $\frac{\dot{U}_1}{\dot{U}_2}$ has nothing to do with Z (Z is the value of the impedance of the element), and write down the ratio.

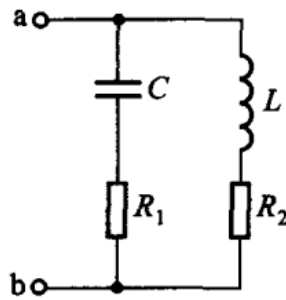


Figure 7: a

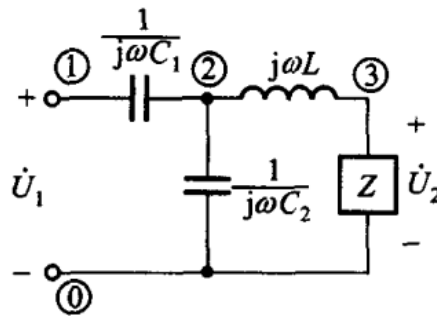


Figure 7: b

8

[14 points]

- (a). Known that the sinusoidal voltage has an amplitude of 100V. The instantaneous value of the voltage at $t=0$ is 10V, and the period is 1ms. Please write down the expression of the voltage as a cosine function.
- (b). $i_1(t) = 4\cos(\omega t - 80^\circ)A$, $i_2(t) = 10\cos(\omega t + 20^\circ)A$, $i_3(t) = 8\sin(\omega t - 20^\circ)A$. Please express these currents in phasor domain.