

 


Can we build the button now?

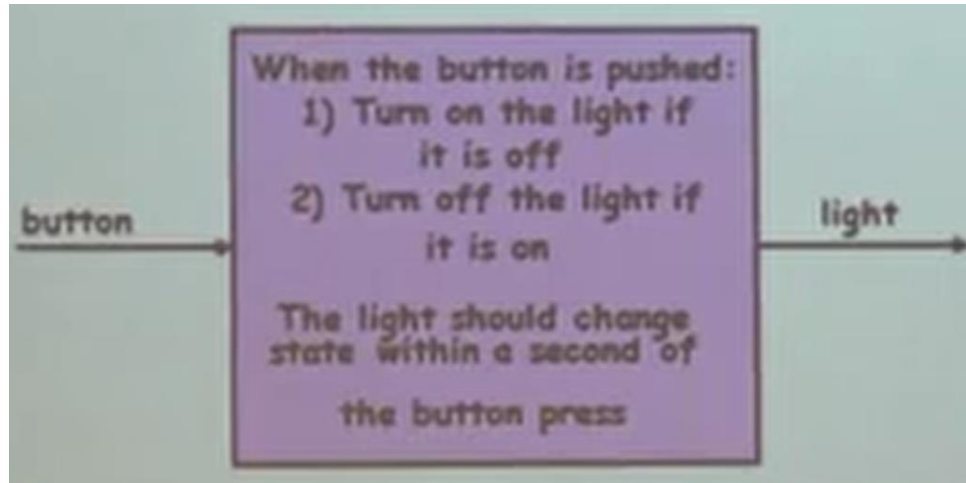

- One needs to press the button precisely the propagation delay of an inverter!




Pulse Trigger S-R Flip-Flops

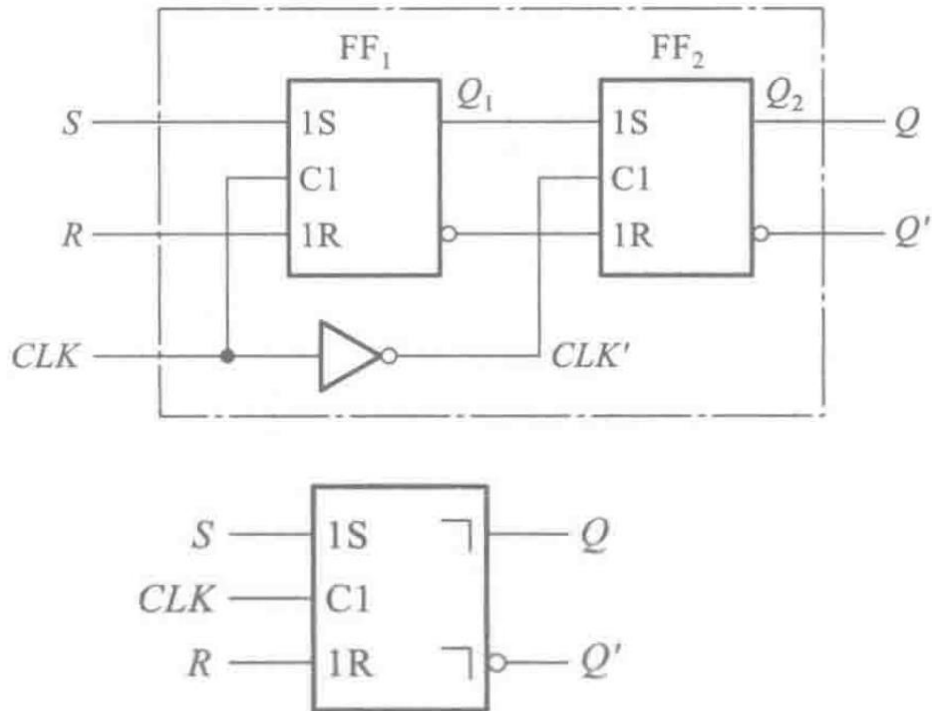

CLK	S	R	Q	Q^*
\times	\times	\times	\times	Q
	0	0	0	0
	0	0	1	1
	1	0	0	1
	1	0	1	1
	0	1	0	0
	0	1	1	0
	1	1	0	1 ⁽¹⁾
	1	1	1	1 ⁽¹⁾



- Compared to the level-sensitive latch, the Flip-Flops changes state only on the edge of CLK.
- “ \neg ” denotes the pulse trigger
- Triggered at the falling edge

Pulse Trigger S-R Flip-Flops

 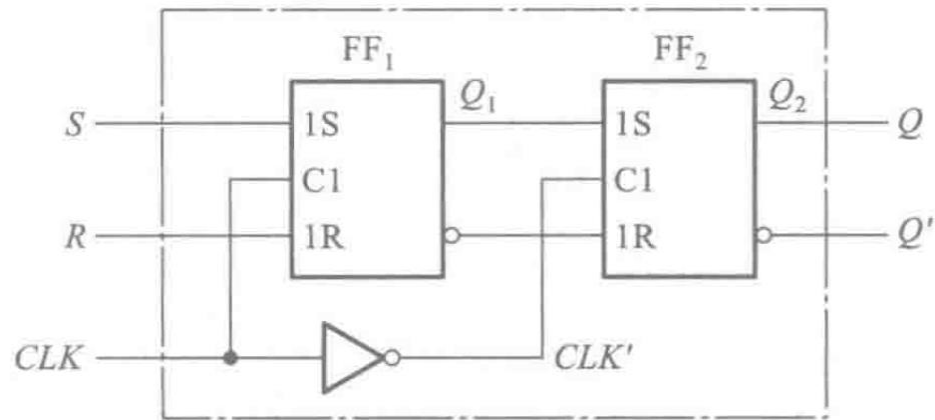 



Question: plot the waveform of Q and Q' , assume the initial Q and Q_1 is 0

Pulse Trigger J-K Flip-Flops

  


CLK	J	K	Q	Q^*
\times	\times	\times	\times	Q
	0	0	0	0
	0	0	1	1
	1	0	0	1
	1	0	1	1
	0	1	0	0
	0	1	1	0
	1	1	0	1
	1	1	1	0

Pulse Trigger J-K Flip-Flops

  


Question: plot the waveform of Q and Q', assume the initial Q and the output of the master stage are 0

Pulse Trigger J-K Flip-Flops


 


 Question: plot the waveform of Q and Q' , assume the initial Q and the output of the master stage are 0




- When $CLK=1$, the output of the master stage can only change once. This is different from the S-R flip flop.



Can we build the button now?

 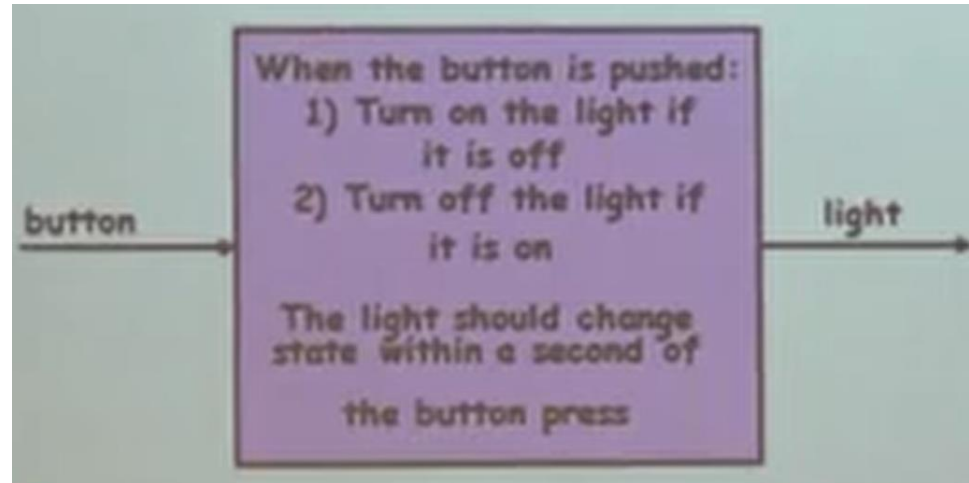

Edge Trigger Flip-Flops


 


CLK	D	Q	Q'
\times	\times	\times	Q
\uparrow	0	0	0
\uparrow	0	1	0
\uparrow	1	0	1
\uparrow	1	1	1

 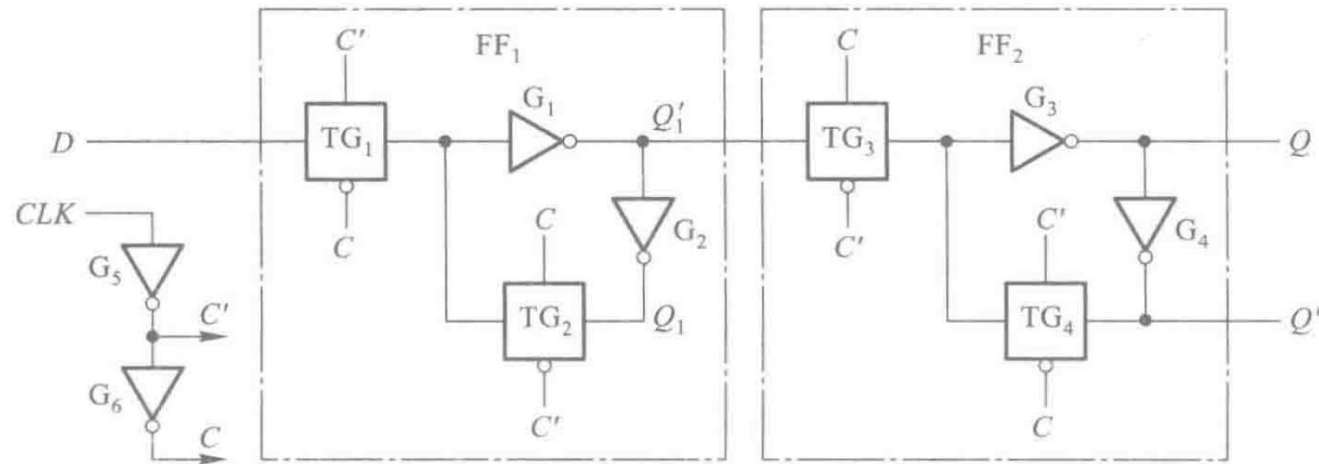


- To improve the noise tolerance, it is desired to have an edge trigger FF rather than the pulse trigger FF.
- ">" denotes the edge trigger
- Triggered at the rising edge

Edge Trigger Flip-Flops

  

Question: plot the waveform of Q ,
assume the initial Q is 0

The asynchronous Edge Trigger Flip-Flops

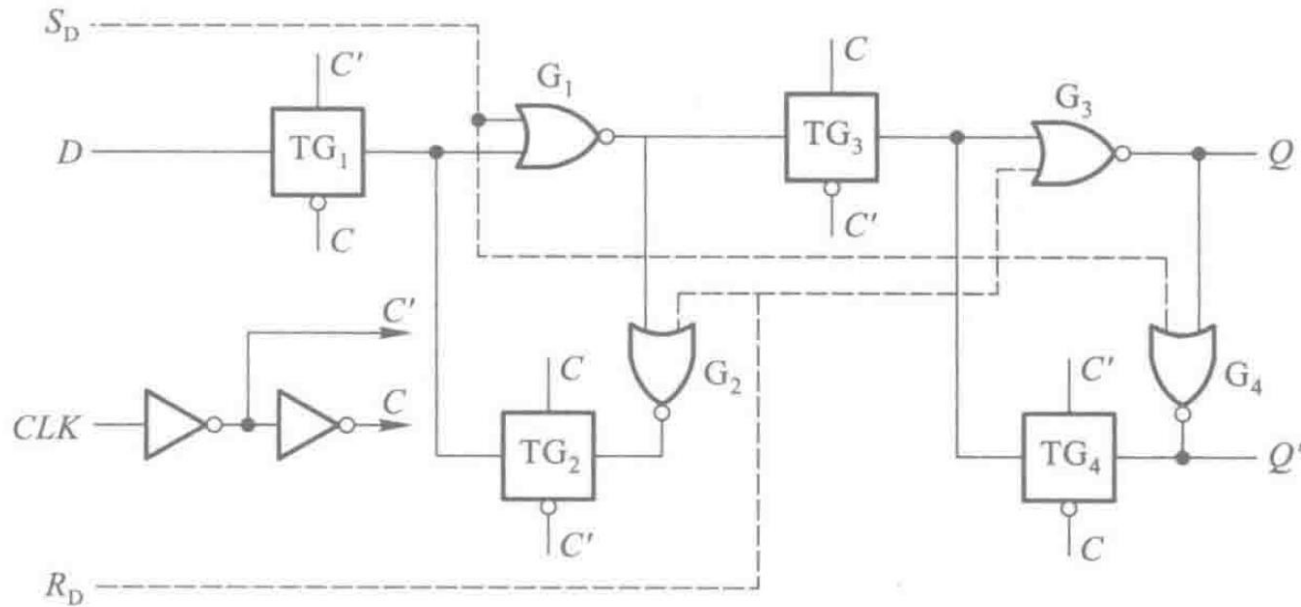

- The asynchronous set or reset should apply to both the master and slave stage



Content

Classification based on the functionality

Timing analysis

S-R Flip-Flops

S	R	Q	Q^*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	不定
1	1	1	不定

  


$$\begin{cases} Q^* = S'R'Q + SR'Q' + SR'Q = SR' + S'R'Q \\ SR = 0 \quad (\text{约束条件}) \end{cases}$$

$$\begin{cases} Q^* = S + R'Q \\ SR = 0 \quad (\text{约束条件}) \end{cases}$$

J-K Flip-Flops


J	K	Q	Q^*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 

$$Q^* = JQ' + K'Q$$

T Flip-Flops

T	Q	Q^*
0	0	0
0	1	1
1	0	1
1	1	0

 


➡ $Q^* = TQ' + T'Q$

D Flip-Flops

D	Q	Q^*
0	0	0
0	1	0
1	0	1
1	1	1

 $Q^* = D$

 


Content



Classification based on the functionality

Timing analysis

Setup time

 

 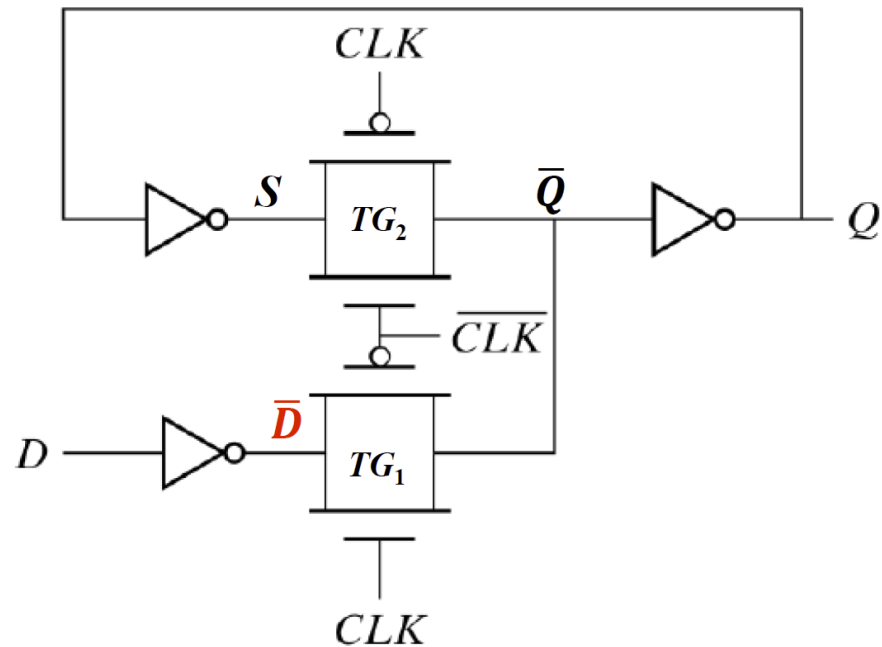
- Set-up time t_{su} is the minimum interval required for the logic levels to be maintained prior to the triggering edge of CLK



$$t_{su} = t_{TG1} + 3t_{INV}$$

Setup time and hold time

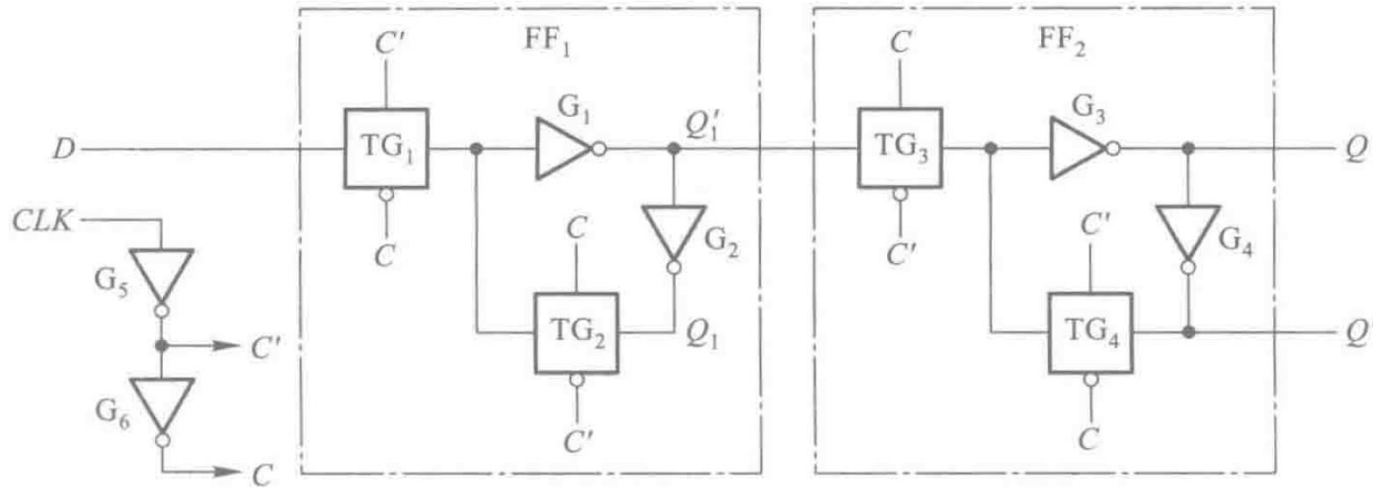- Assume the propagation delay of both the inverter and transmission gate is t_d



$$t_{su} = 2t_{INV} + t_{TG} - t_{INV} = t_{INV} + t_{TG}$$

$$t_h = 2t_{INV}$$

