

ShanghaiTech University

**EE 115B: Digital Circuits**

Fall 2022

Lecture 20

Hengzhao Yang  
December 15, 2022

# Sequence detector

- Design specifications (problem statement)
  - Circuit has one input ( $w$ ) and one output ( $z$ )
  - All changes occur at positive clock edges
  - Operation:  $z=1$  if  $w=1$  during two immediately preceding clock cycles;  $z=0$ , otherwise


Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

# State diagram

- Identify states to describe circuit behavior
  - State A (starting state): when a reset signal is applied or  $w=0$ , circuit enters this state,  $z=0$
  - State B:  $w=1$  for one clock cycle,  $z=0$
  - State C:  $w=1$  for two clock cycles,  $z=1$
 
# State diagram

- State diagram
  - Nodes: states
  - Directed arcs: state transitions



# State table

- Convert state diagram to state table
  - First state is starting state (state A)
  - Present state, next state, and state transitions
  - Output is specified with respect to present state


Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

# State assignment

- Each state is represented by a combination of state variables
- Each state variable is implemented by a flip-flop
- Three states (A, B, C) need two state variables ( $y_1, y_2$ )
- Moore type: output only depends on state
- Present-state variables:  $y_1, y_2$
- Next-state variables:  $Y_1, Y_2$

# State assignment

- Circuit block diagram

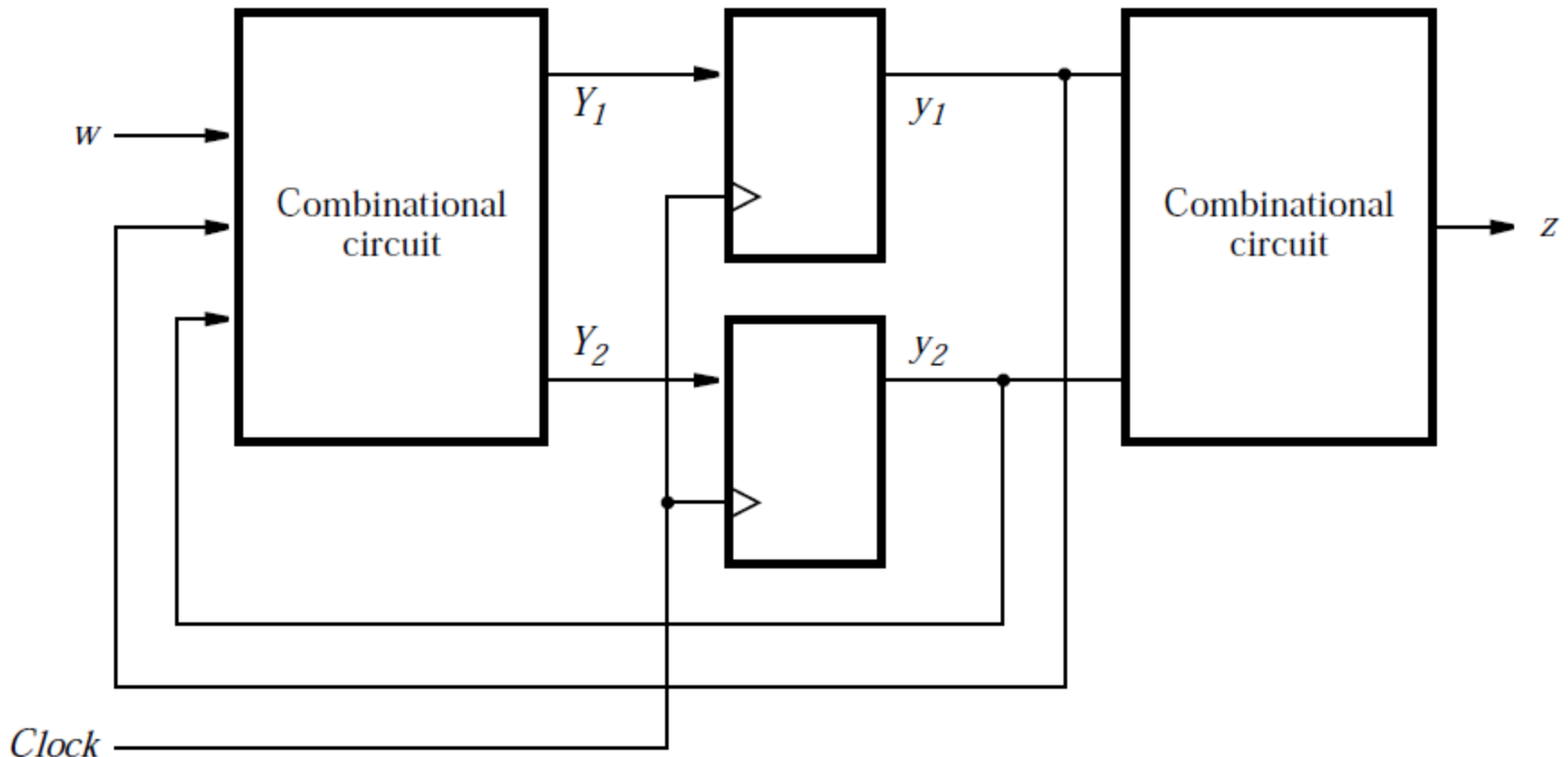

# State-assigned table

- Assign binary values to states
  - A: 00, B: 01, C: 10
  - “11” is not used

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

	Present state $y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	$dd$	$dd$	$d$



# Choice of flip-flops

- D flip-flops: transfer  $Y_1$  and  $Y_2$  to  $y_1$  and  $y_2$

	Present state $y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	$dd$	$dd$	$d$


# Output expression

- Output expression:  $z$

- Ignoring don't cares:  $z = \bar{y}_1 y_2$

- Using don't cares:  $z = y_2$

$y_2$	$y_1$	$z$
0	0	0
0	1	0
1	0	1
1	1	d

 

	Present state $y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	$dd$	$dd$	$d$

# Next-state expressions

- Next-state expression:  $Y_1$ 
  - Ignoring don't cares:  $Y_1 = w\bar{y}_1\bar{y}_2$
  - Using don't cares:  $Y_1 = w\bar{y}_1\bar{y}_2$

w	y2	y1	Y <sub>1</sub>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	d
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	d

		$y_2y_1$			
		00	01	11	10
$w$	0	0	0	d	0
	1	1	0	d	0

A  
B  
C

	Present state $y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2Y_1$	$Y_2Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	$dd$	$dd$	$d$

# Next-state expressions

- Next-state expression:  $Y_2$ 
  - Ignoring don't cares:  $Y_2 = wy_1\bar{y}_2 + w\bar{y}_1y_2$
  - Using don't cares:  $Y_2 = wy_1 + wy_2$   
 $= w(y_1 + y_2)$

w	y <sub>2</sub>	y <sub>1</sub>	Y <sub>2</sub>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	d
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	d

		$y_2y_1$			
		00	01	11	10
$w$	0	0	0	d	0
	1	0	1	d	1

A  
B  
C

	Present state $y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2Y_1$	$Y_2Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	$dd$	$dd$	$d$

# Circuit (using don't cares)


- Output

$$z = y_2$$


- Next-state

$$Y_1 = w\bar{y}_1\bar{y}_2$$
 
$$\begin{aligned} Y_2 &= wy_1 + wy_2 \\ &= w(y_1 + y_2) \end{aligned}$$



# Timing diagram

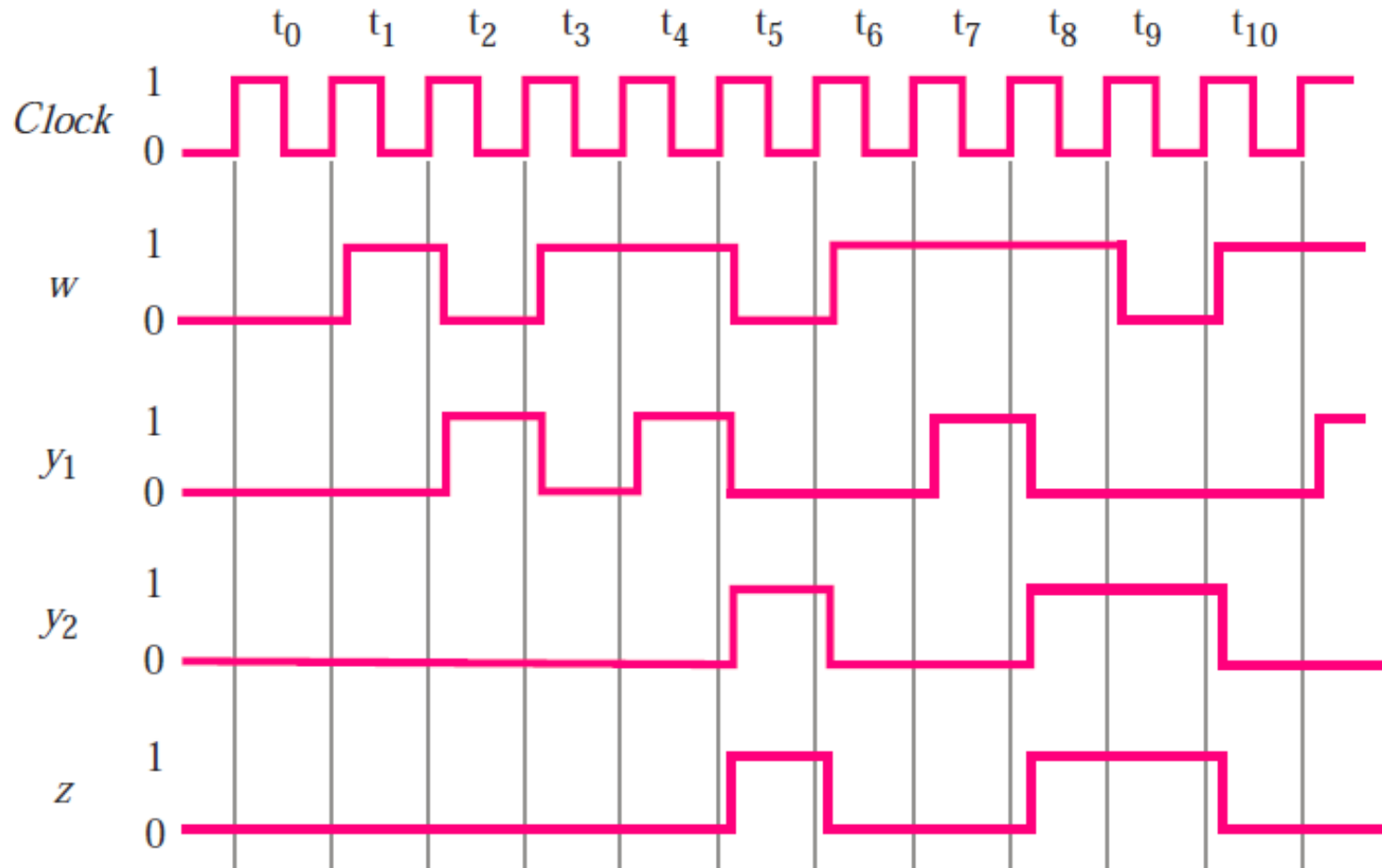

# Summary

- Design steps
  - Understand design specifications
  - Identify states to describe circuit behavior and draw state diagram for states and transitions
  - Convert state diagram to state table
  - Assign state variables
  - Choose flip-flops and determine output and next-state expressions
  - Implement circuit

# State-assignment issue

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

- Original state assignment
  - A: 00, B: 01, C: 10
  - “11” is not used
- Alternative state assignment
  - A: 00, B: 01, C: 11
  - “10” is not used

	Present state	Next state		Output $z$
		$w = 0$	$w = 1$	
	$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	$dd$	$dd$	$d$

	Present state	Next state		Output $z$
		$w = 0$	$w = 1$	
	$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	$dd$	$dd$	$d$



# Output and next-state expressions

- Expressions

$$Y_1 = D_1 = w$$

$$Y_2 = D_2 = wy_1$$

$$z = y_2$$

	Present state $y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2Y_1$	$Y_2Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	$dd$	$dd$	$d$


# Circuit (with a lower cost)

- Expressions

$$Y_1 = D_1 = w$$

$$Y_2 = D_2 = wy_1$$

$$z = y_2$$

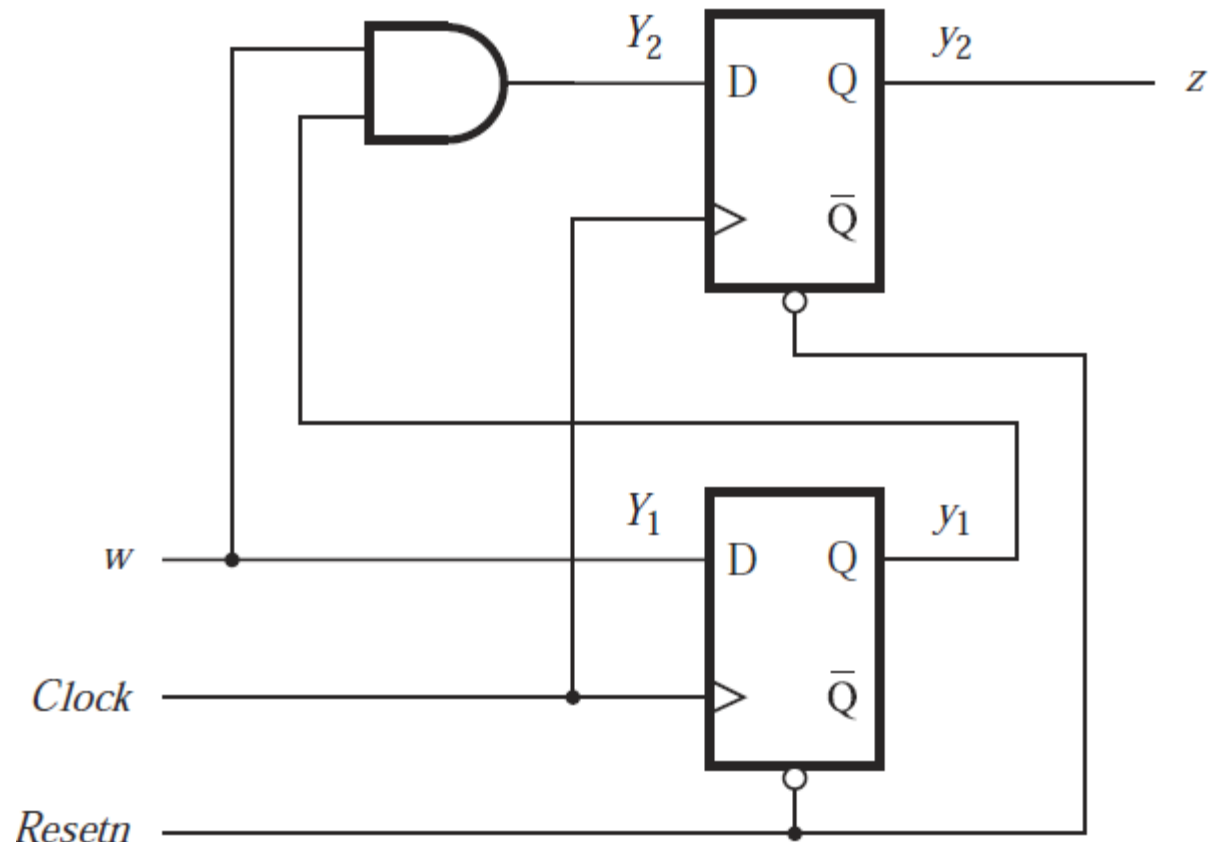

# One-hot encoding

- One-hot encoding
  - Another approach to assign states
  - Number of states equals number of state variables
  - For each state, only ONE state variable is “hot”: its value is “1”. The values of all the other state variables are “0”.

# Example

- State table
  - Three states: A, B, C
- One-hot state assignment
  - Three state variables:  $y_3, y_2, y_1$
  - A: 001, B: 010, C: 100
  - Other combinations of state variables are don't cares

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

	Present state $y_3 y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_3 Y_2 Y_1$	$Y_3 Y_2 Y_1$	
A	0 0 1	0 0 1	0 1 0	0
B	0 1 0	0 0 1	1 0 0	0
C	1 0 0	0 0 1	1 0 0	1

# Example

- Output and next-state expressions

$$Y_1 = \overline{w}$$

$$Y_2 = wy_1$$

$$Y_3 = w\overline{y}_1$$


$$z = y_3$$

	Present state $y_3 y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_3 Y_2 Y_1$	$Y_3 Y_2 Y_1$	
A	0 0 1	0 0 1	0 1 0	0
B	0 1 0	0 0 1	1 0 0	0
C	1 0 0	0 0 1	1 0 0	1

- Circuit is not simpler for this example
- One-hot encoding is useful in many cases
 
# VHDL code for Moore FSMs

- Design input: state diagram
- Example: “11” sequence detector



# Moore type: code 1

- **TYPE** keyword
  - User-defined signal type
  - Name: State\_type
  - Values: A, B, C
- Signal **y**
  - Type: State\_type
  - Describes FSM state
  - Takes values (A, B, C)
- Initial state A by Resetn
- CASE statement
  - State transitions

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;

3  ENTITY simple IS
4      PORT ( Clock, Resetn, w      : IN    STD_LOGIC ;
5              z                      : OUT  STD_LOGIC ) ;
6  END simple ;

7  ARCHITECTURE Behavior OF simple IS
8      TYPE State_type IS (A, B, C) ;
9      SIGNAL y : State_type ;
10 BEGIN
11     PROCESS ( Resetn, Clock )
12     BEGIN
13         IF Resetn = '0' THEN
14             y <= A ;
15         ELSIF (Clock'EVENT AND Clock = '1') THEN
16             CASE y IS
17                 WHEN A =>
18                     IF w = '0' THEN
19                         y <= A ;
20                     ELSE
21                         y <= B ;
22                     END IF ;
```

# Moore type: code 1 (continued)

- WHEN statement
  - Output expression
- Summary
  - One signal (y) for state
  - One PROCESS block

```
23      WHEN B =>
24          IF w = '0' THEN
25              y <= A ;
26          ELSE
27              y <= C ;
28          END IF ;
29      WHEN C =>
30          IF w = '0' THEN
31              y <= A ;
32          ELSE
33              y <= C ;
34          END IF ;
35      END CASE ;
36  END IF ;
37  END PROCESS ;
38  z <= '1' WHEN y = C ELSE '0' ;
39  END Behavior ;
```