

Homework 2

Total points : 90

Due date: 11th Oct, 2022


Turn in your homework in class

Rules:





- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

10'

1. For the circuit below,





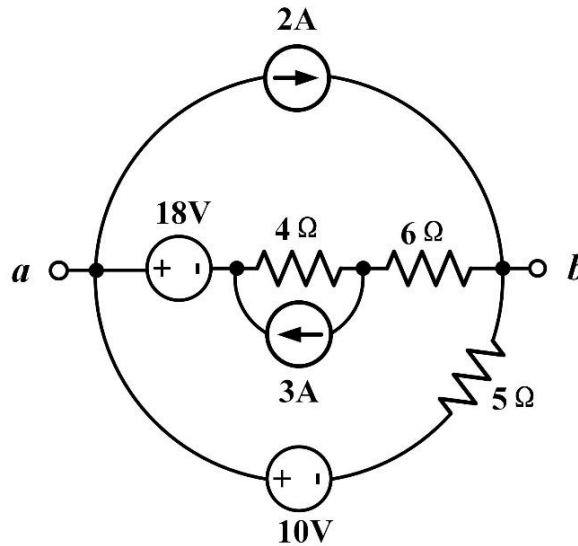
(a) Use superposition theorem to find the voltage drop between *a* and *b*, namely V_{ab} (b) Use source transformation (at least twice) to find V_{ab} (c) Find the Norton equivalent circuit at terminals *a* and *b*

a)

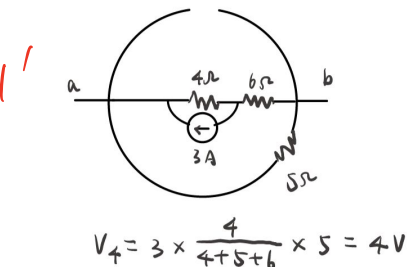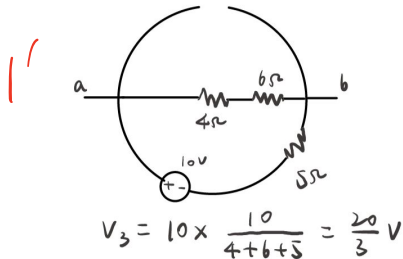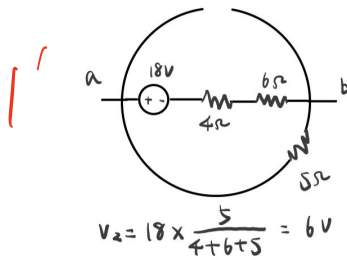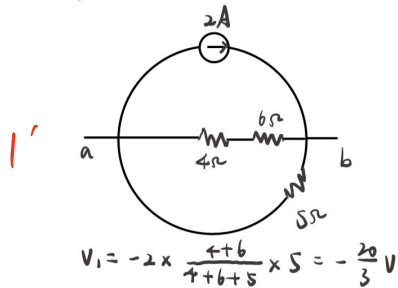


$$V_{ab} = V_1 + V_2 + V_3 + V_4 = 10 \text{ V}$$

b)

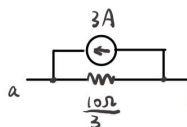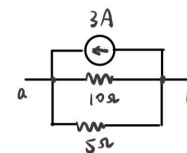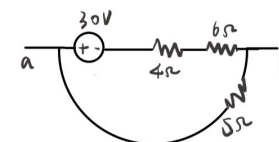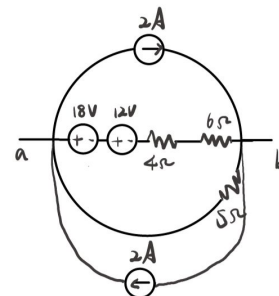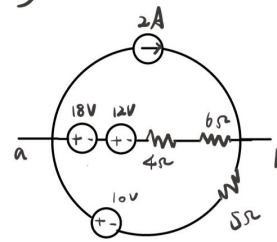

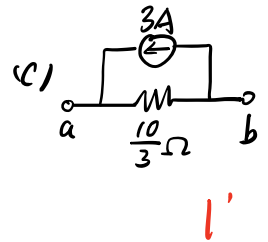
$$V_{ab} = 3 \times \frac{10 \text{ V}}{3} = 10 \text{ V}$$





1.5' } twice
1.5'

20 pts

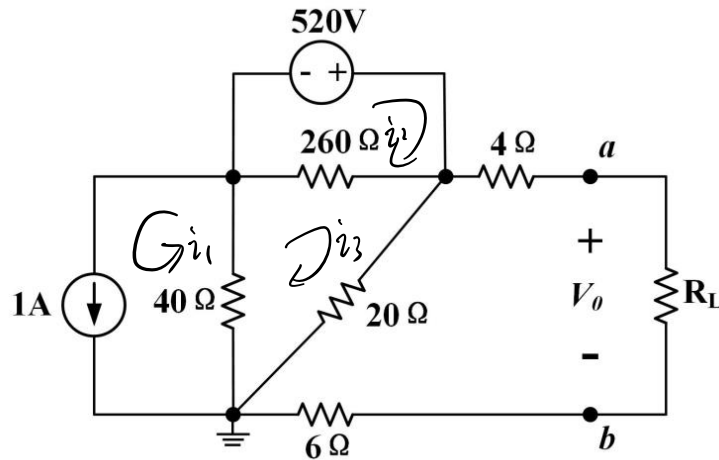2. (a) Apply superposition to find V_o in the circuit below when $R_L = 250\Omega$.
 (b) Find the Thevenin equivalent circuit for the left hand side circuit of node a and node b .
 (c) Determine the value of R_L when maximum power could be transferred to it.
 (d) for the situation in (c), find the power absorbed by the $520V$ voltage source and the $1A$ current source, **respectively**.



(a) keep 1A current source :

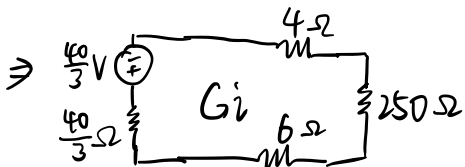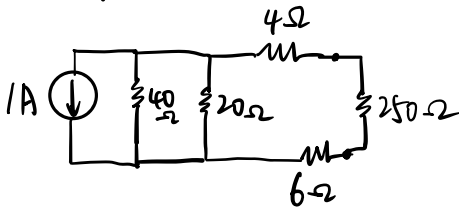


$$i = \frac{40}{3} / (250 + 10 + 40/3)$$

$$= \frac{2}{41} A$$

$$V_{o1} = -\frac{2}{41} \times 250V = -\frac{500}{41} V$$

keep 520V Voltage source

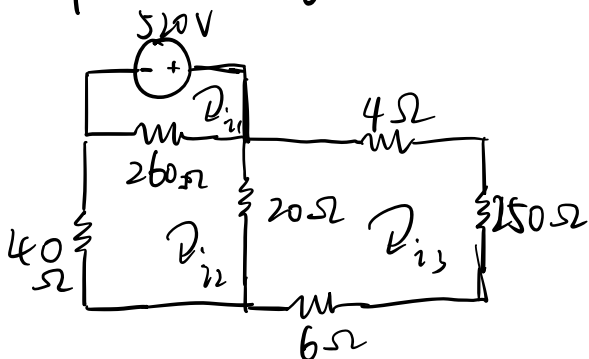


$$\begin{cases} -520 + (i_1 - i_2)260 = 0 \\ 260(i_2 - i_1) + 20(i_2 - i_3) + 40i_2 = 0 \\ 20(i_3 - i_2) + 260i_3 = 0 \end{cases}$$

$$\begin{cases} 260(i_2 - i_1) + 20(i_2 - i_3) + 40i_2 = 0 \\ 20(i_3 - i_2) + 260i_3 = 0 \end{cases}$$


$$i_3 = \frac{26}{41} A \Rightarrow V_{o2} = i_3 R_L = \frac{6500}{41} V$$

$$\Rightarrow \text{Superposition} = V_o = V_{o1} + V_{o2} = \frac{6000}{41} V$$

(b)

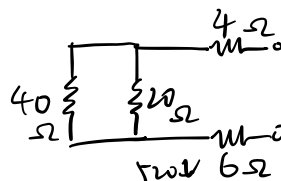

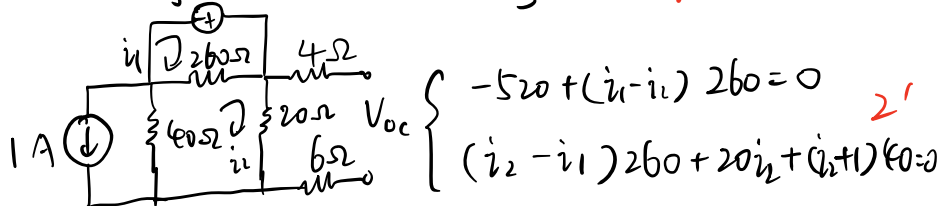
$$\Rightarrow R_{TH} = 4\Omega + 6\Omega + 40\Omega \parallel 20\Omega = \frac{70}{3} \Omega$$




$$\Rightarrow -520 + 60i_2 + 40 = 0 \Rightarrow i_2 = 8A$$

$$\Rightarrow V_{oc} = 8 \cdot 20 = 160V$$
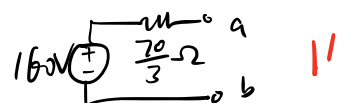
$$(c) R_L = R_{TH} = \frac{70}{3} \Omega$$



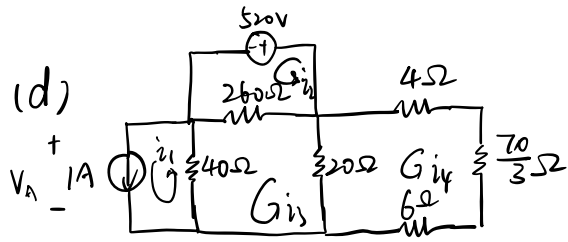

$$2' \quad \begin{cases} i_1 = 1 \text{ A} \\ (i_2 - i_3) 260 + 520 = 0 \\ 260(i_3 - i_2) + 40(i_3 - i_1) + 20(i_3 - i_4) = 0 \\ i_4(10 + \frac{70}{3}) + 20(i_4 - i_3) = 0 \end{cases}$$

$$\Rightarrow \begin{cases} i_1 = 1 \text{ A} \\ i_2 = -\frac{78}{7} \text{ A} \\ i_3 = -\frac{64}{7} \text{ A} \\ i_4 = -\frac{24}{7} \text{ A} \end{cases}$$

$$\Rightarrow P_{520V, \text{absor.}} = -\frac{78}{7} \cdot 520 = -\frac{40560}{7} \text{ W} \quad 2'$$

$$(i_1 - i_3) 40 + V_A = 0 \Rightarrow V_A = (i_3 - i_1) 40$$

$$= -\frac{71}{7} \times 40 \text{ V}$$

$$= -\frac{2840}{7} \text{ V}$$


$$\Rightarrow \begin{array}{c} \downarrow i_1 = 1 \text{ A} \\ \text{---} \text{---} \text{---} \\ \uparrow \text{---} \text{---} \text{---} \\ \text{---} \text{---} \text{---} \end{array} \quad \begin{array}{c} - \\ + \end{array} \quad \frac{2840}{7} \text{ V} \quad P_{1A, \text{absor.}} = -\frac{2840}{7} \text{ V} \times 1 \text{ A} = -\frac{2840}{7} \text{ W}$$

$P < 0$ means the source generates power. 2'

3. (a) Find the Thevenin equivalent circuit at the terminals **a** and **b**.


20 pts

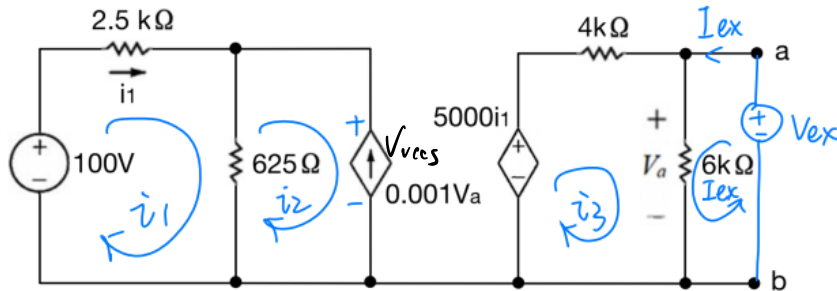(b) If a load resistor R_L is connected at terminals **a** and **b**, what is the maximum power that could be transferred to it by this circuit, and what is the value of R_L in this situation? Also, find the power absorbed by the three sources, **respectively**.




$$\begin{aligned} V_{oc}: \quad & \begin{cases} 100 = 2500i_1 + 625(i_1 - i_2) \\ i_2 = -0.001V_a \\ 5000i_1 = 4000i_3 + 6000i_3 \\ V_a = 6000i_3 \end{cases} \Rightarrow \begin{cases} i_1 = 0.02 \text{ A} \\ i_2 = -0.06 \text{ A} \\ i_3 = 0.01 \text{ A} \\ V_a = 60 \text{ V} = V_{ex} \end{cases} \end{aligned}$$
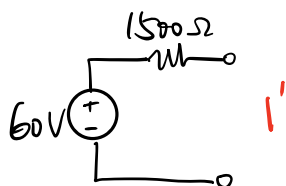
$$\begin{aligned} R_{Th}: \quad & \begin{cases} 2500i'_1 + 625(i'_1 - i'_2) = 0 \\ i'_2 = -0.001 \times 60 \\ 5000i'_1 = 4000i'_3 + 60 \\ 60 = 6000(I_{ex} + i'_3) \end{cases} \Rightarrow \begin{cases} 3125i'_1 - 625i'_2 = 0 \\ 5i'_1 = i'_2 = -0.06 \text{ A} \\ i'_1 = -0.012 \text{ A} \\ i'_3 = -0.03 \text{ A} \end{cases} \end{aligned}$$



$$I_{ex} = 0.04 \text{ A} \\ R_{Th} = \frac{V_{ex}}{I_{ex}} = 1500 \Omega$$

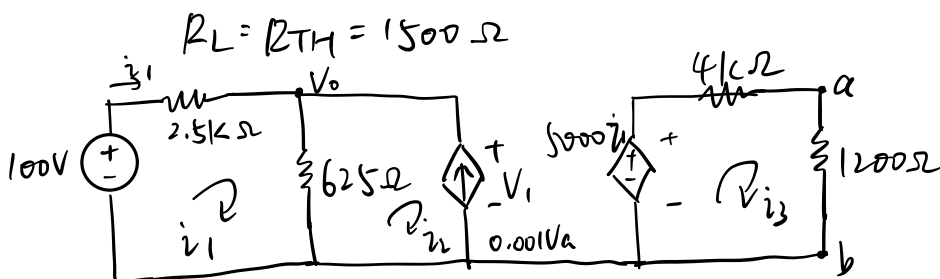(b) $P_{max} = \frac{60^2}{4 \times 1500} \text{ W} = 0.6 \text{ W}$



$$V_{ab} = 60 \text{ V} \cdot \frac{1}{2} = 30 \text{ V}$$

$$i_1 = \frac{100 - 35}{2500} \text{ A} = \frac{65}{2500} \text{ A}$$

$$\frac{100 - V_o}{2500} + 0.001V_a = V_o / 625$$

$$\Rightarrow V_o = 35 \text{ V} = V_1$$


$$\Rightarrow P_{VCCS, \text{absorbe}} = -0.001V_a \cdot 35 = -1.05 \text{ W}$$

$$P_{100V, \text{absorbe}} = \frac{-65}{2500} \times 100 = -2.6 \text{ W}$$

$$P_{CCVS, \text{absorbe}} = -5000i_1 \cdot \frac{5000i_1 - V_a}{4000} = -3.25 \text{ W}$$

4. For the circuit below, find the Norton equivalent with respect to the terminals **a**, **b**.

10 pts

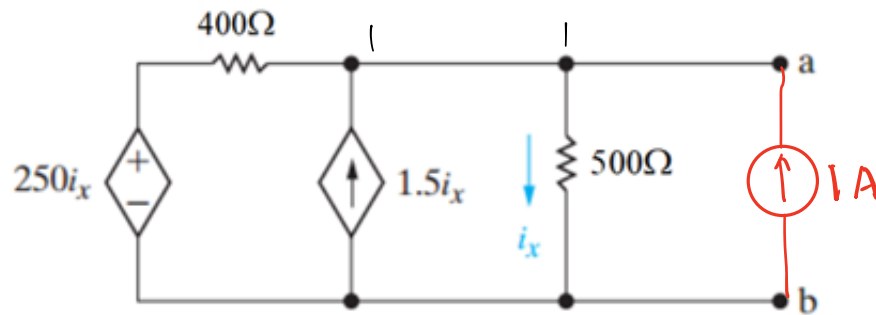

↵

Solution: ↵

Because there are no independent sources in the circuit, ↵

$$i_N = 0 \quad 2'$$

To calculate R_N , we write no de-voltage equation, and place an independent 1A current source between nodes a and b with the current going from node b to node a. ↵

$$\frac{v - 250i_x}{400} - 1.5i_x + i_x = 1 \quad 2'$$


$$v = 500 * i_x \quad ↵$$

Now we can calculate ↵

$$i_x = 8A \quad 2'$$

$$v = 4000V \quad ↵$$

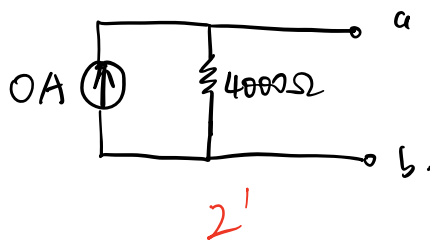Now we can calculate $R_N = 4000/1 = 4000\Omega$ ↵ 2'





5. The values of V_S , R_1 , R_2 , R_3 , R_4 are known positive constants.

Use them to find:

(a) The Thevenin equivalent circuit between node a and b .

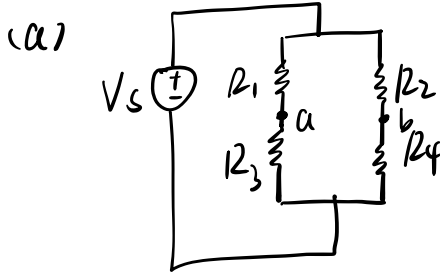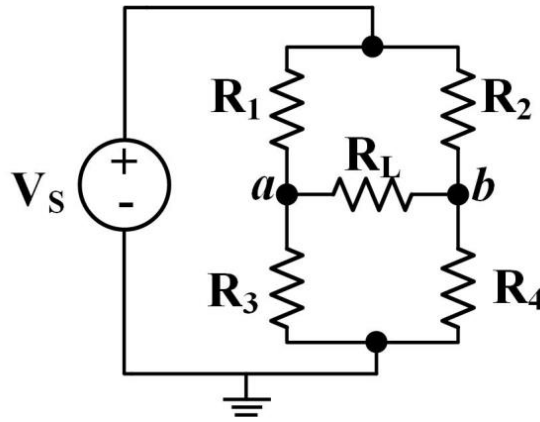
(b) The resistance of R_L that absorbs the maximum power, and the maximum power P_{\max} absorbed by the load R_L .



$$V_a = V_S \cdot \frac{R_3}{R_1 + R_3} \Rightarrow V_{ab} = V_a - V_b$$


$$V_b = V_S \cdot \frac{R_4}{R_2 + R_4} \quad V_{ab} = V_{oc} = V_S \left(\frac{R_3}{R_1 + R_3} - \frac{R_4}{R_2 + R_4} \right) \quad 2'$$

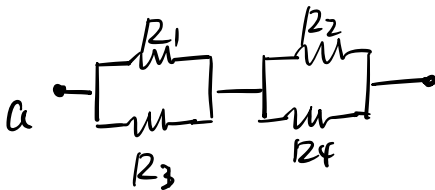When finding R_{TH} , short circuit V_S , the equivalent circuit is



$$R_{TH} = R_1 \parallel R_3 + R_2 \parallel R_4$$
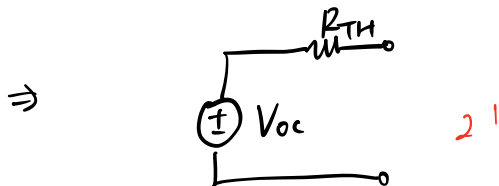
$$= \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4} \quad 2'$$




(b) $R_L = R_{TH} = R_1 \parallel R_3 + R_2 \parallel R_4 \quad 2'$

$$P_{\max} = \frac{V_{oc}^2}{4R_L} = \frac{V_S^2 \left(\frac{R_3}{R_1 + R_3} - \frac{R_4}{R_2 + R_4} \right)^2}{4(R_1 \parallel R_3 + R_2 \parallel R_4)} \quad 2'$$

10pts.

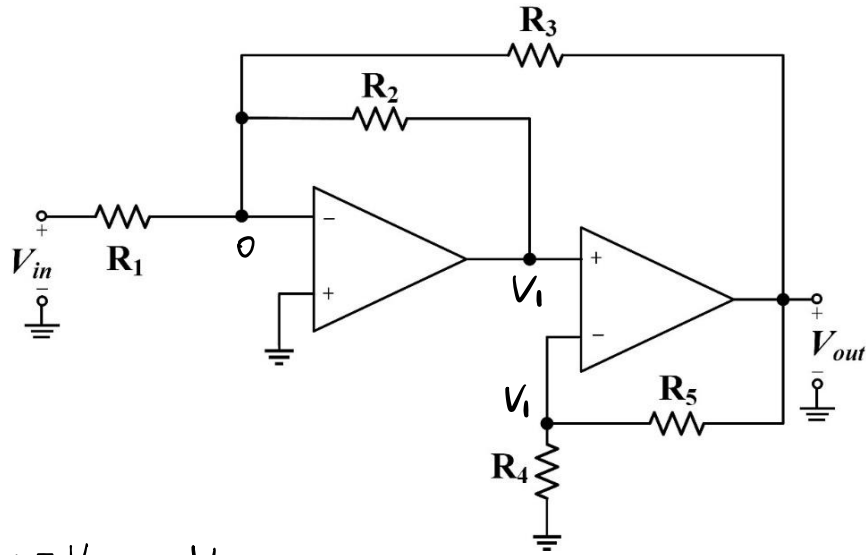6. Find the voltage gain V_{out}/V_{in} of the following circuit, if $R_1=1\text{k}\Omega$, $R_2=R_3=2\text{k}\Omega$, $R_4=R_5=4\text{k}\Omega$.




Solutions:

$$\begin{cases} \frac{V_{out} - V_1}{R_5} = \frac{V_1}{R_4} & 4' \\ \frac{V_{in}}{R_1} + \frac{V_1}{R_2} + \frac{V_{out}}{R_3} = 0 & 4' \end{cases}$$

$$\frac{V_{out}}{V_{in}} = -\frac{4}{3} \quad 2'$$

10 pts.

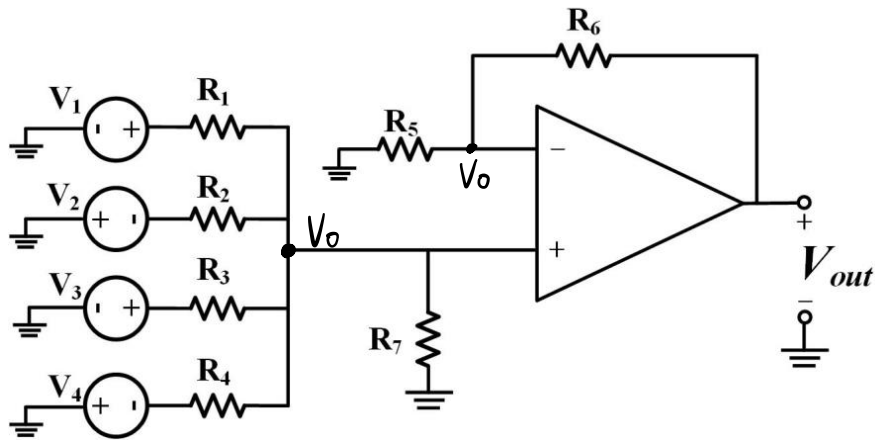7. For the following circuit, find the output voltage V_{out} in terms of V_1 to V_4 . Note that all the resistors in the circuit have the same resistance of $1\text{k}\Omega$. (Also, please pay attention to the given reference direction of the independent voltage sources)



$$\left\{ \begin{array}{l} \frac{V_{out} - V_o}{R_6} = \frac{V_o}{R_5} \quad \dots \textcircled{1} \end{array} \right. \quad 4'$$

$$\left\{ \begin{array}{l} \frac{V_1 - V_o}{R_1} + \frac{-V_2 - V_o}{R_2} + \frac{V_3 - V_o}{R_3} + \frac{-V_4 - V_o}{R_4} = \frac{V_o}{R_7} \quad \dots \textcircled{2} \end{array} \right. \quad 4'$$

$$\Rightarrow V_{out} = \frac{2}{5} (V_1 - V_2 + V_3 - V_4) \quad 2'$$