

ShanghaiTech University

**EE 115B: Digital Circuits**

Fall 2022

Lecture 16

Hengzhao Yang  
November 29, 2022

# Flip-Flops


- Edge triggered circuits
  - Output only changes at **clock edges** (i.e., clock changes from one value to the other)
  - **Positive edge**: clock changes from 0 to 1
  - **Negative edge**: clock changes from 1 to 0
  - Output value changes **no more than once** during one clock cycle
- Examples
  - D flip-flop
  - T flip-flop
  - JK flip-flop

# D flip-flops

- Operation
  - Output follows input at active clock edge
- Implementations
  - Master-slave D flip-flop
    - Output changes at negative edge of clock
    - Output changes at positive edge of clock
  - Edge-triggered D flip-flop
    - Positive-edge-triggered
    - Negative-edge-triggered
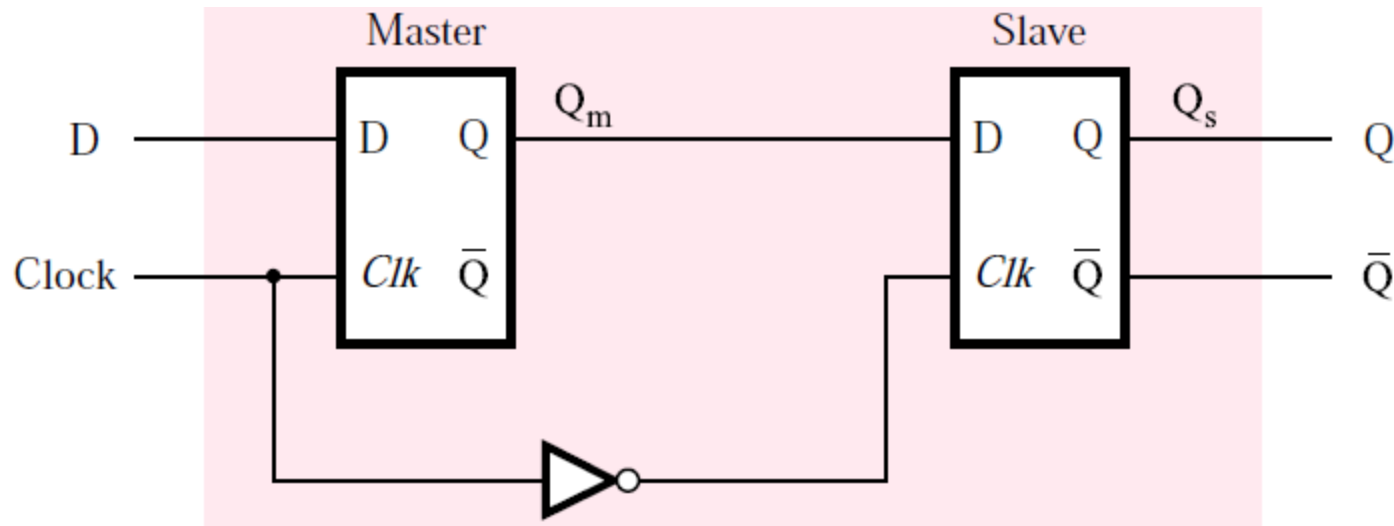
# Master-slave D flip-flop: negative edge

- Master-slave D flip-flop: negative edge
  - Built on 2 gated D latches: master and slave
  - Clock: original for master and complement for slave
  - Output changes at negative edge of clock



# Master-slave D flip-flop: negative edge



- Operation and timing diagram

- While Clock=1

- Master is active
    - $Q_m$  follows D
    - $Q_s$  remains unchanged


- While Clock=0

 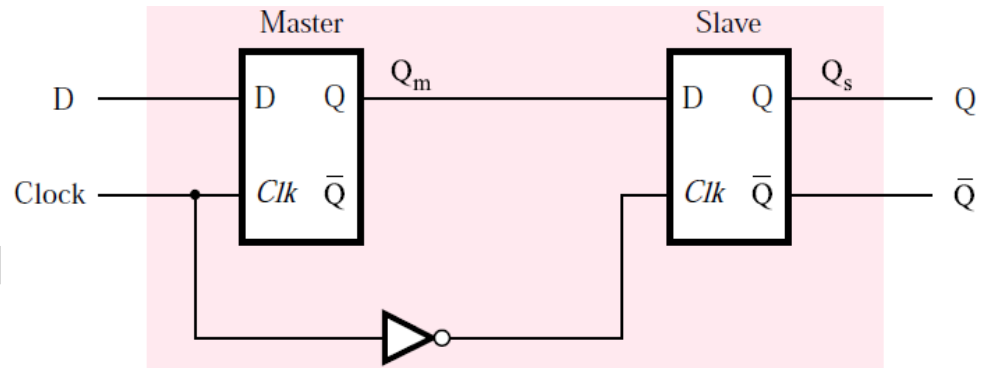- Slave is active
    - $Q_s$  responds to  $Q_m$ , Q (final output) changes at negative edge



 
# Master-slave D flip-flop: negative edge

- Circuit symbol
  - Symbol “>” denotes active edge of clock
  - Bubble on clock indicates negative edge


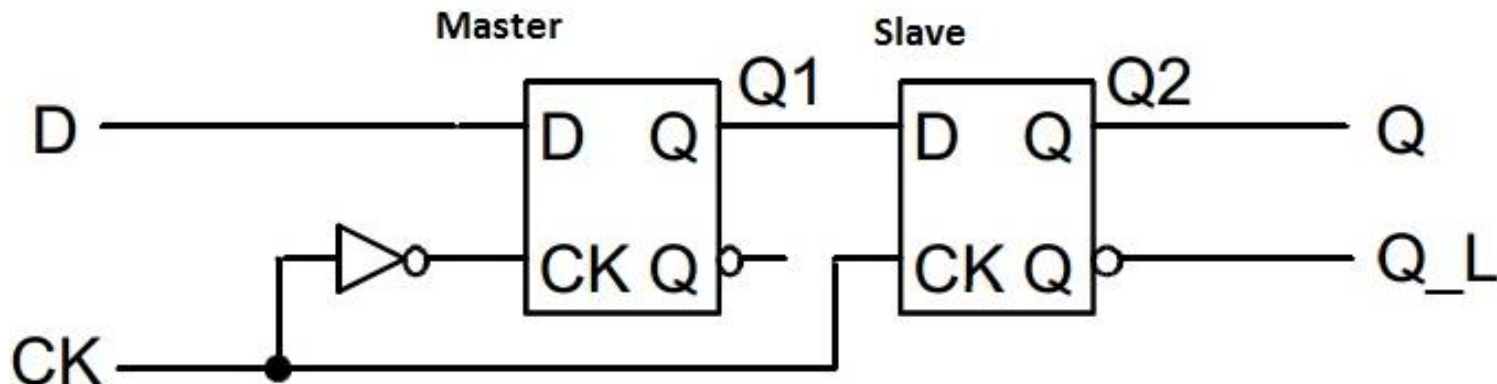
# Master-slave D flip-flop: positive edge



- Master-slave D flip-flop: positive edge
  - Built on 2 gated D latches: master and slave
  - Clock: complement for master and original for slave
  - Output changes at positive edge of clock



Source: <https://allthingsvlsi.files.wordpress.com/2013/04/master-slave-dff.jpg>

# Edge-triggered D flip-flop: positive


- Circuit and circuit symbol

 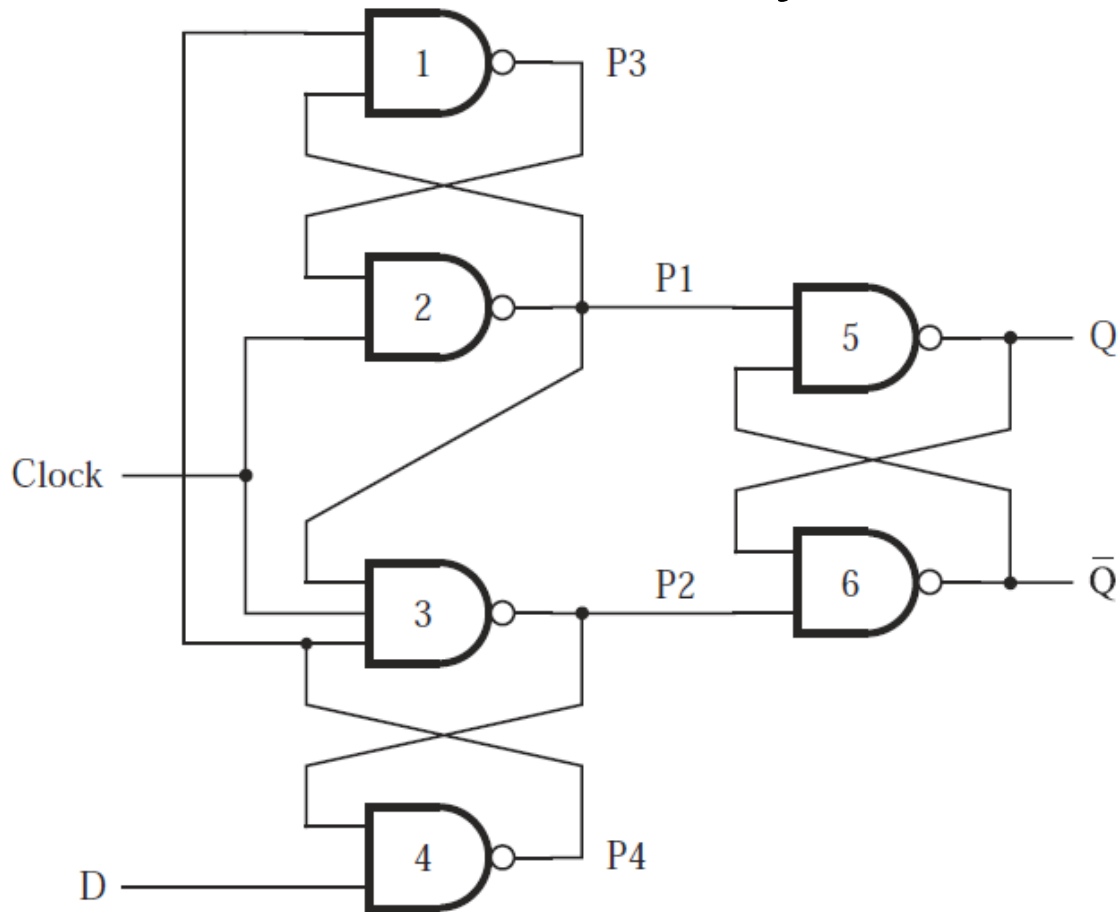


 
# Edge-triggered D flip-flop: positive

- Clock=0
  - P1=1, P2=1, basic S'R' latch holds
  - P4=D', P3=D
- Positive edge
  - P1=(P3 AND Clock)'=D'
  - P2=(P1 AND Clock AND P4)'=D
  - Q=P1'=D, Q'=P2'=D' (latch: S'=P1, R'=P2)



SR latch operation		
S	R	Action
0	0	Not allowed
0	1	Q = 1
1	0	Q = 0
1	1	No change

