




# Lecture 9

## - Sinusoidal Steady-State Analysis


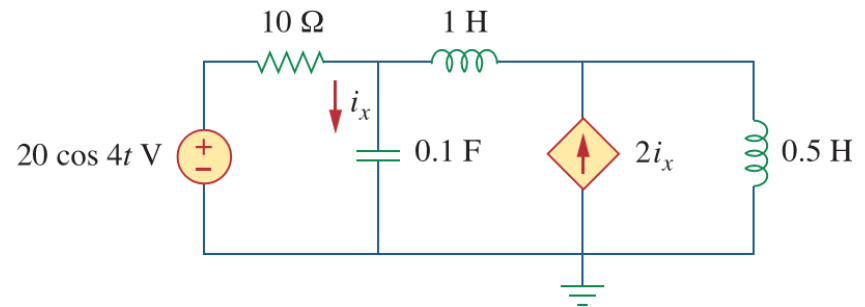
# Outline

- Kirchhoff's laws in phasor domain
- Generalized impedance
- General AC phasor analysis
- Phasor diagram





## Kirchhoff's Laws in the Phasor Domain

- Let  $v_1, v_2, \dots, v_n$  be the voltages around a closed loop.  
Then according to KVL

$$v_1 + v_2 + \dots + v_n = 0$$

$$\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n = 0$$

Similarly, KCL holds for phasors:

$$i_1 + i_2 + \dots + i_n = 0$$

$$\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0,$$



# Proof

If

$$v_1 + v_2 + \cdots + v_n = 0$$

where  $v_i$  are sinusoidal voltages of the same frequency, then

$$\mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n = 0$$

$$v_1 + v_2 + \cdots + v_n = 0$$



$$V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \cdots + V_{mn} \cos(\omega t + \theta_n) = 0$$



$$\operatorname{Re}(V_{m1} e^{j\theta_1} \cdot e^{j\omega t}) + \cdots + \operatorname{Re}(V_{mn} e^{j\theta_n} \cdot e^{j\omega t}) = 0$$



$$\operatorname{Re}((\mathbf{V}_1 + \cdots + \mathbf{V}_n) \cdot e^{j\omega t}) = 0 \quad \text{Where } \mathbf{V}_k = V_{mk} e^{j\theta_k}$$



$$\mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n = 0$$



# Outline

- Kirchhoff's laws in phasor domain
- Generalized impedance
- General AC phasor analysis
- Phasor diagram



## Review: Impedance and Admittance

Resistor	$\mathbf{Z} = R$	$\mathbf{Y} = 1 / R$
Inductor	$\mathbf{Z} = j \omega L$	$\mathbf{Y} = 1 / j \omega L$
Capacitor	$\mathbf{Z} = 1 / j \omega C$	$\mathbf{Y} = j \omega C$

Impedance is  
voltage/current

$$\mathbf{Z} = R + jX$$

$R$  = resistance =  $\text{Re}(\mathbf{Z})$

$X$  = reactance =  $\text{Im}(\mathbf{Z})$

Admittance is  
current/voltage


$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = G + jB$$

$G$  = conductance =  $\text{Re}(\mathbf{Y})$

$B$  = susceptance =  $\text{Im}(\mathbf{Y})$
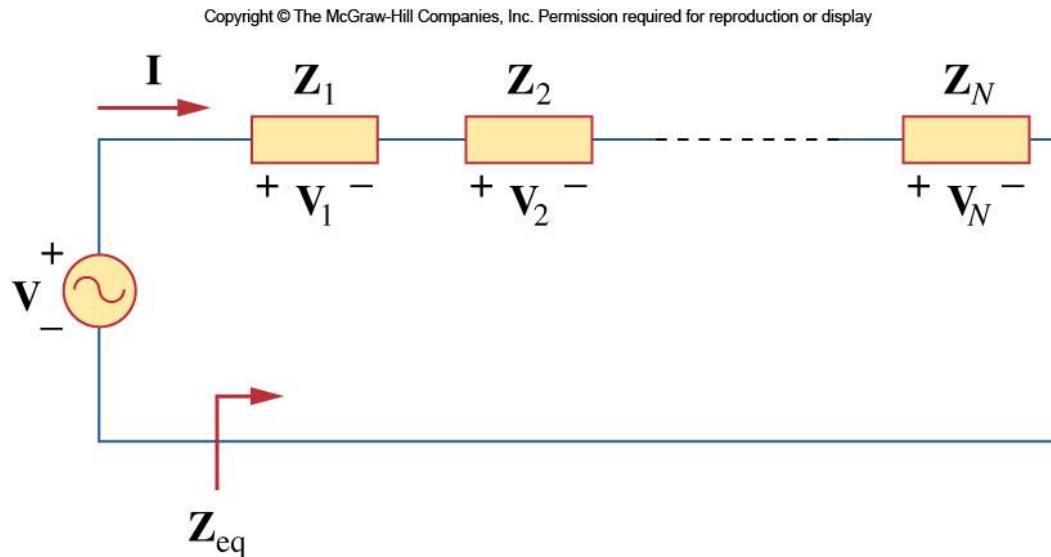
# Series Impedance

- Once in frequency domain, the impedance elements are generalized, combinations will follow the rules for resistors:




$$Z_{eq} = Z_1 + Z_2 + Z_3 + \cdots + Z_N$$



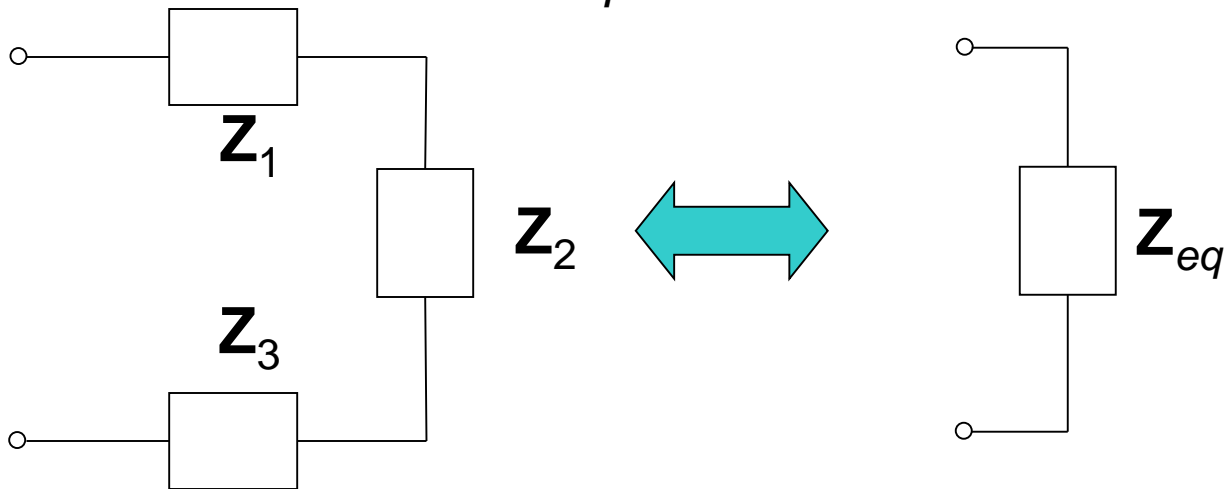
## Series Impedance


$$\mathbf{Z}_{eq} = \mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3$$



For example:

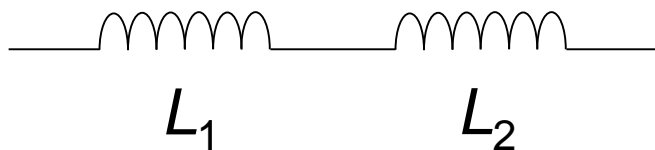

$$\mathbf{Z}_{eq} =$$

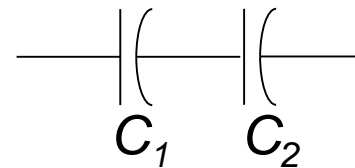


$$\mathbf{Z}_{eq} =$$







# Impedance combination for RLC Circuit

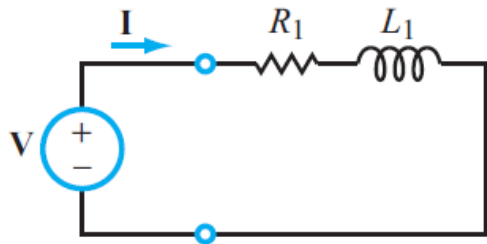

(a) RL

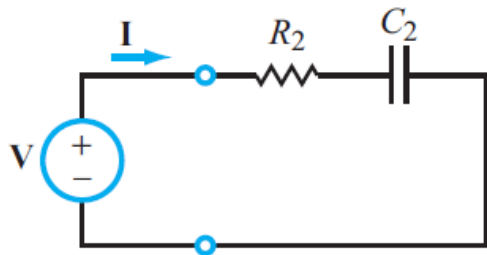

(b) RC

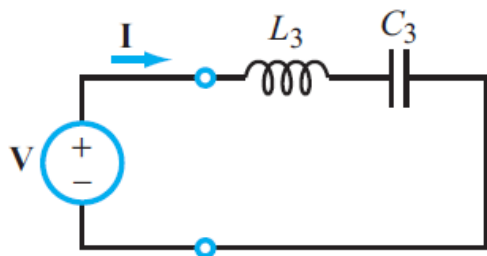


(c) LC


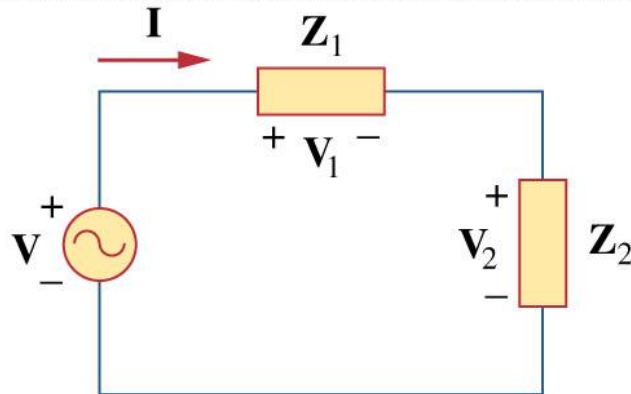
# Voltage Divider


- Two elements in series can act like a voltage divider

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\dot{V}_1 = \frac{Z_1}{Z_1 + Z_2} \dot{V} \quad \dot{V}_2 = \frac{Z_2}{Z_1 + Z_2} \dot{V}$$

## Example

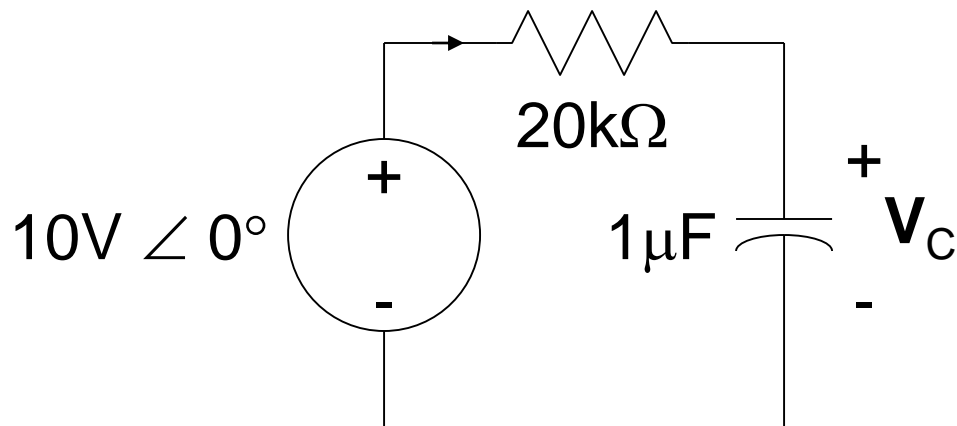


1.  $f=60$  Hz,  $V_C=?$

First compute impedances for resistor and capacitor:

$$\mathbf{Z}_R = R = 20k\Omega = 20k\Omega \angle 0^\circ$$
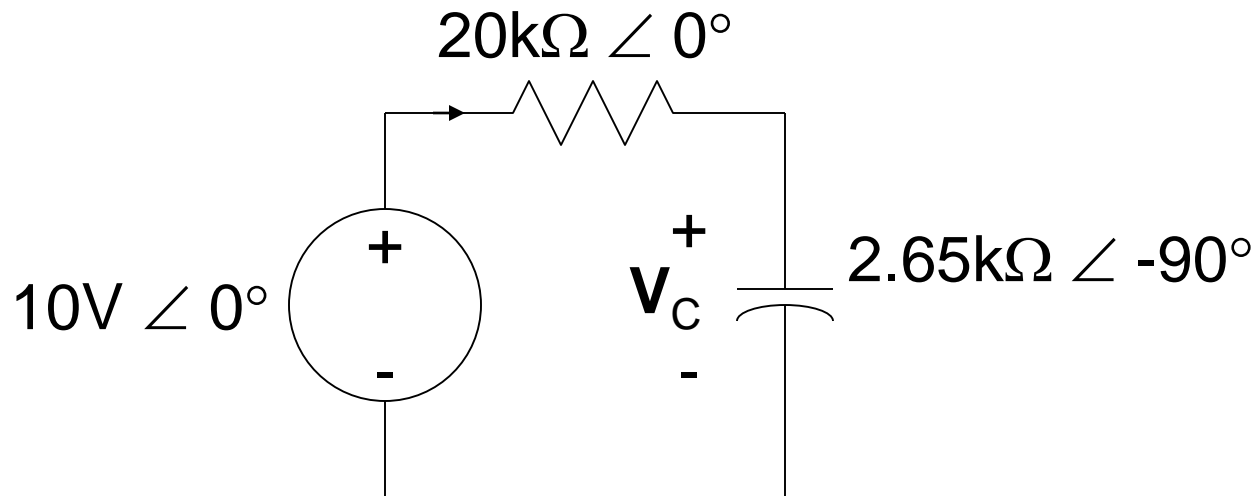
$$\mathbf{Z}_C = 1/j(2\pi f \times 1\mu F) = 2.65k\Omega \angle -90^\circ$$



Now use the voltage divider to find  $V_C$ :


$$V_C = 10V \angle 0^\circ \left( \frac{2.65k\Omega \angle -90^\circ}{2.65k\Omega \angle -90^\circ + 20k\Omega \angle 0^\circ} \right)$$

$$V_C = 1.31V \angle -82.4^\circ$$

What if  $\omega = 10$ , find  $V_C$
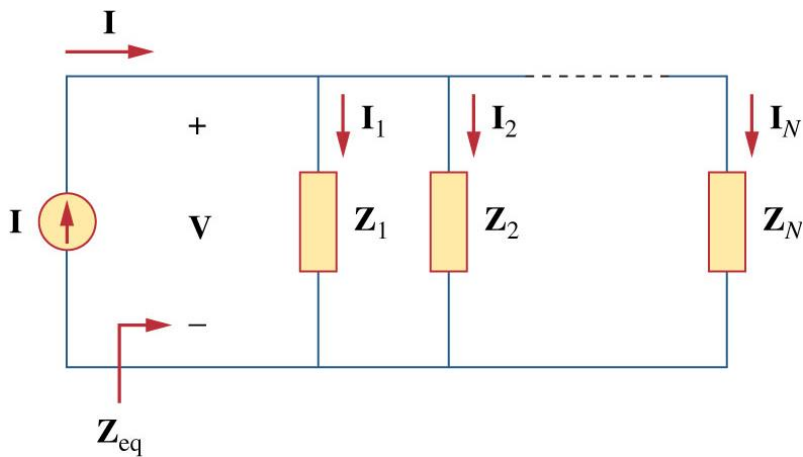
## Parallel Combination

- Likewise, elements combined in parallel will combine in the same fashion as resistors in parallel:



$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_N}$$

$$Y_{eq} = Y_1 + Y_2 + Y_3 + \dots + Y_N$$


$$I_1 = \frac{Y_1}{Y_1 + \dots + Y_N} I$$

$$I_2 = \frac{Y_2}{Y_1 + \dots + Y_N} I$$

.....




# Parallel Impedance

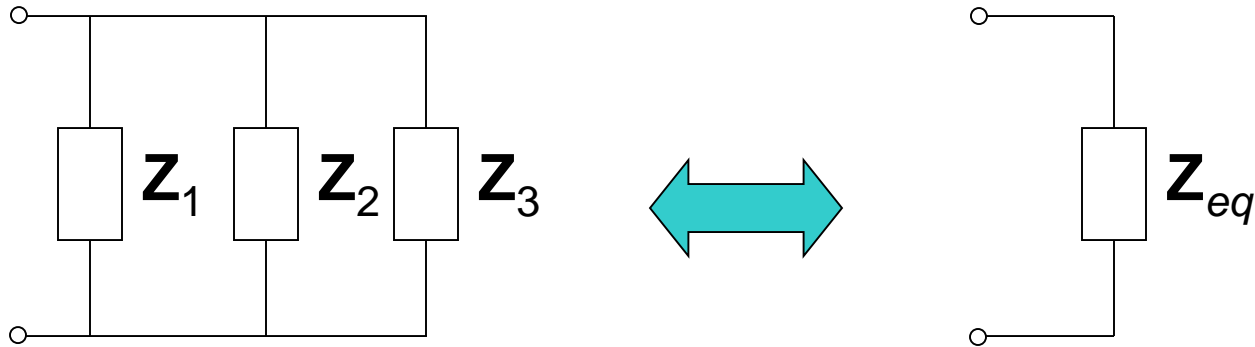


For example:

$$1/Z_{eq} = 1/Z_1 + 1/Z_2 + 1/Z_3$$

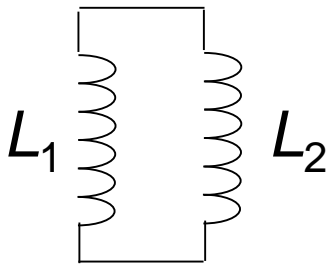

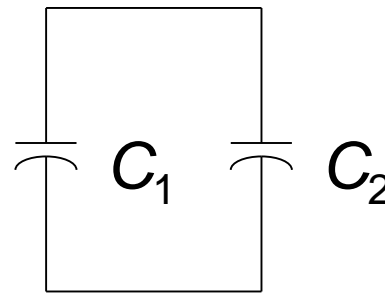
$$Z_{eq} = j\omega \frac{L_1 L_2}{(L_1 + L_2)}$$




$$Z_{eq} = \frac{1}{j\omega(C_1 + C_2)}$$




## Example

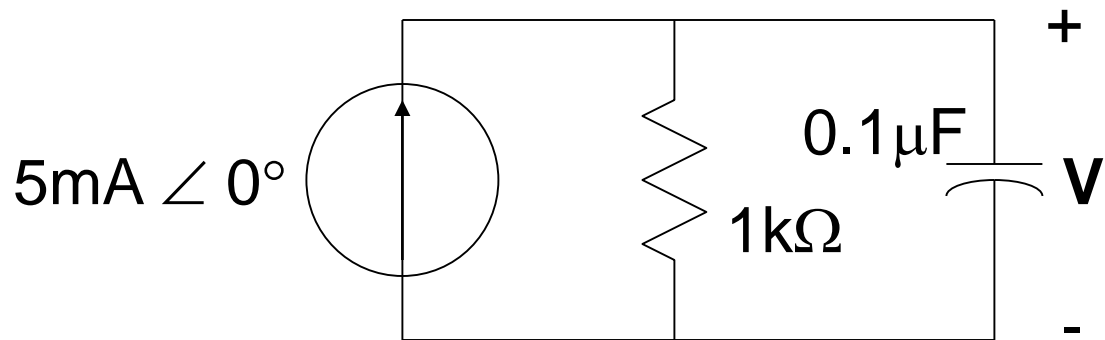

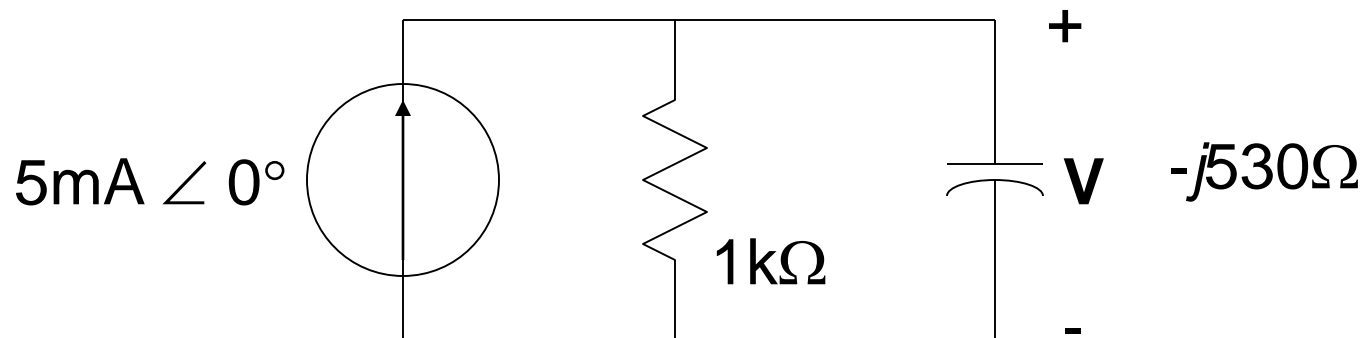Find  $v(t)$  for  $\omega = 2\pi \times 3000$



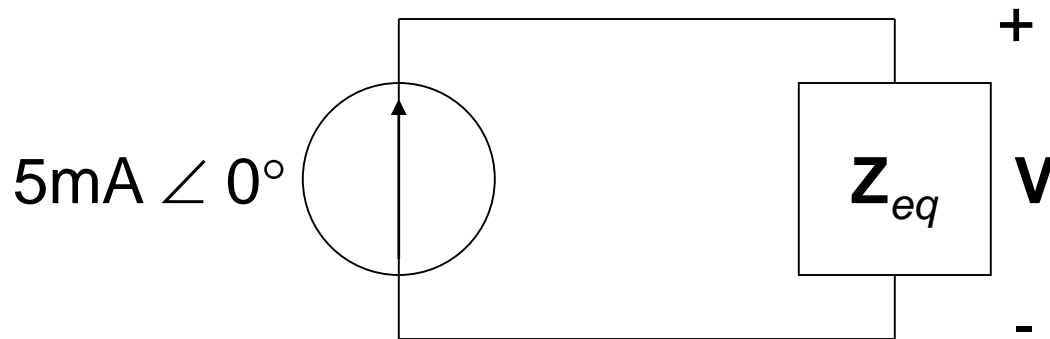

$$\mathbf{Z}_{eq} = \frac{1000 \times (-j530)}{1000 - j530} = \frac{10^3 \angle 0^\circ \times 530 \angle -90^\circ}{1132 \angle -27.9^\circ}$$

$$\mathbf{Z}_{eq} = 468.2\Omega \angle -62.1^\circ$$

$$\mathbf{V} = \mathbf{I}\mathbf{Z}_{eq} = 5\text{mA} \angle 0^\circ \times 468.2\Omega \angle -62.1^\circ$$


$$\mathbf{V} = 2.34\text{V} \angle -62.1^\circ$$

$$v(t) = 2.34 \cos(2\pi 3000t - 62.1^\circ) \text{V}$$







## Change the Frequency

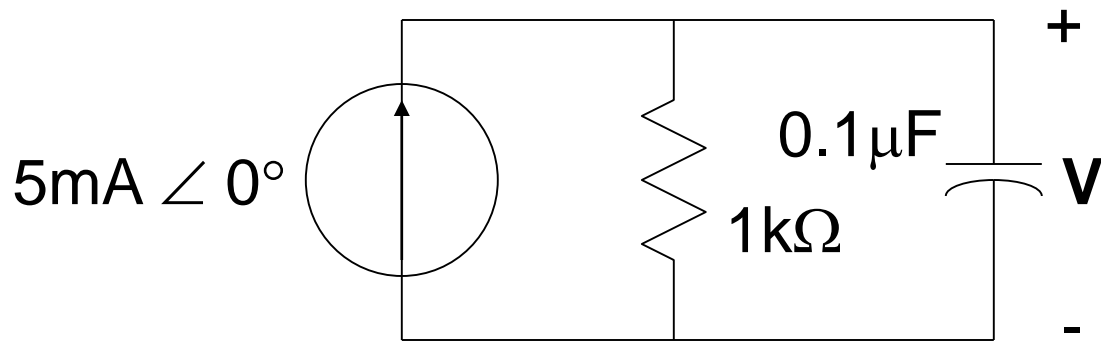

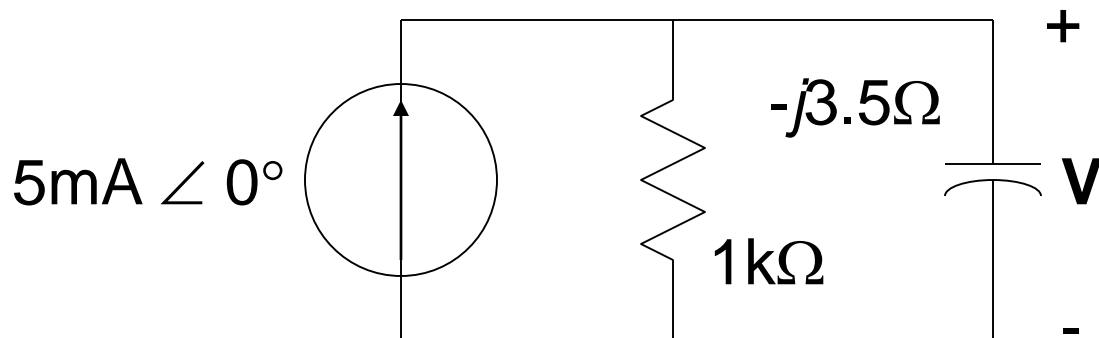Find  $v(t)$  for  $\omega = 2\pi \cdot 455000$



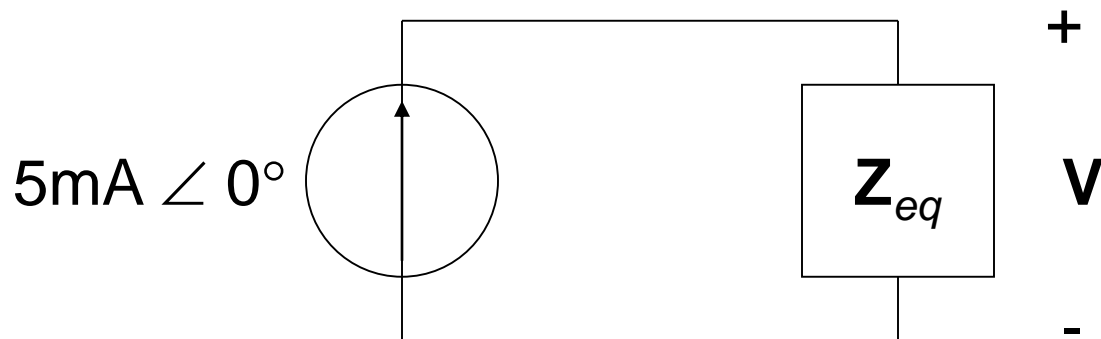

$$\mathbf{Z}_{eq} = \frac{1000 \times (-j3.5)}{1000 - j3.5} = \frac{10^3 \angle 0^\circ \times 3.5 \angle -90^\circ}{1000 \angle -0.2^\circ}$$



$$\mathbf{Z}_{eq} = 3.5 \angle -89.8^\circ \Omega$$

$$\mathbf{V} = \mathbf{I} \mathbf{Z}_{eq} = 5 \angle 0^\circ \text{mA} \times 3.5 \angle -89.8^\circ \Omega \quad \mathbf{V} = 17.5 \angle -89.8^\circ \text{mV}$$

$$v(t) = 17.5 \cos(2\pi 455000t - 89.8^\circ) \text{mV}$$




# Summary: Voltage & Current Division

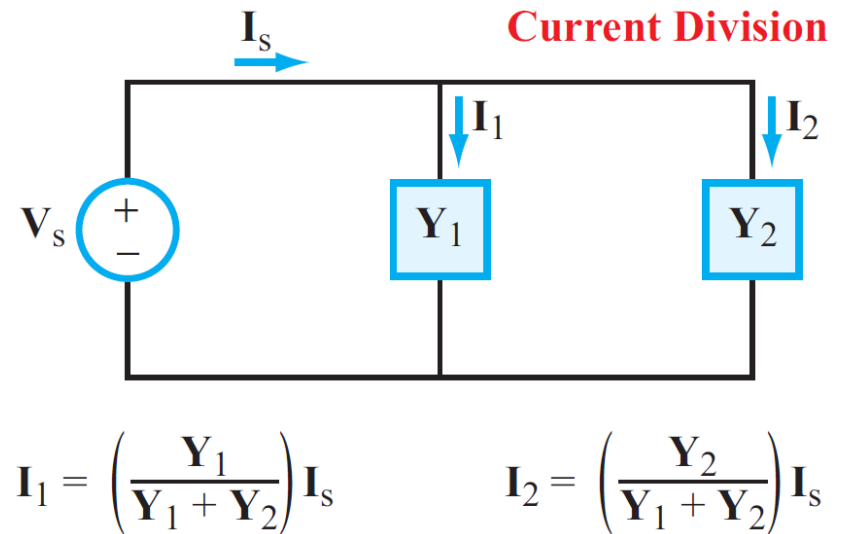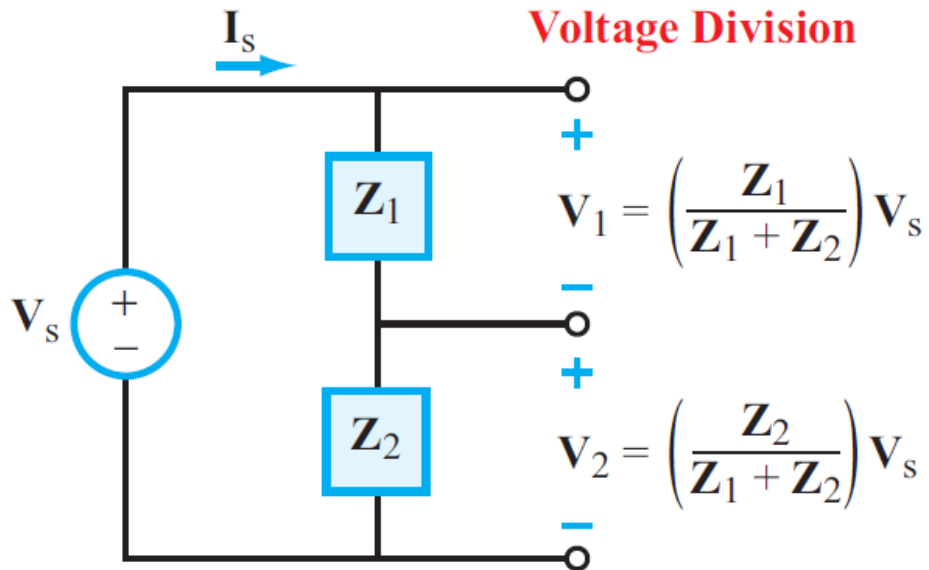


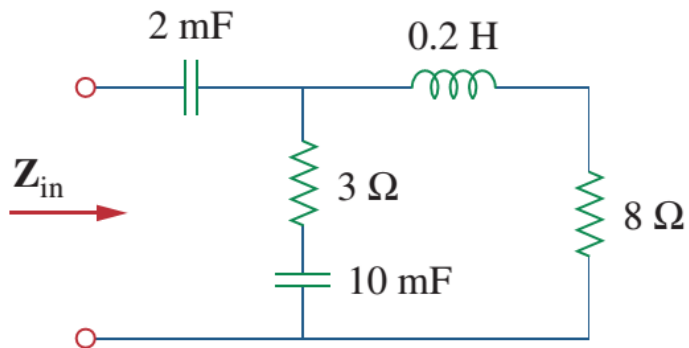
## Exercise

- Find the input impedance of the circuit below.  $\omega = 50$  rad/s.





# Outline

- Kirchhoff's laws in phasor domain
- Generalized impedance
- General AC phasor analysis
  - Nodal/mesh analysis
  - Superposition
  - Source transformation/Thevenin/Norton
- Phasor diagram



# AC Phasor Analysis General Procedure

## Step 1: Adopt cosine reference

$$\begin{aligned} v_s(t) &= 12 \sin(\omega t - 45^\circ) \\ &= 12 \cos(\omega t - 45^\circ - 90^\circ) = 12 \cos(\omega t - 135^\circ) \text{ V.} \\ \mathbf{V}_s &= 12e^{-j135^\circ} \text{ V.} \end{aligned}$$

## Step 2: Transform circuit to phasor domain

## Step 3: Cast KCL and/or KVL equations in phasor domain

$$\mathbf{Z}_R \mathbf{I} + \mathbf{Z}_C \mathbf{I} = \mathbf{V}_s,$$

which is equivalent to

$$\left( R + \frac{1}{j\omega C} \right) \mathbf{I} = 12e^{-j135^\circ}.$$

### Step 1

Adopt Cosine Reference  
(Time Domain)



### Step 2



Transfer to Phasor Domain

$$\begin{aligned} i &\rightarrow \mathbf{I} \\ v &\rightarrow \mathbf{V} \\ R &\rightarrow \mathbf{Z}_R = R \\ L &\rightarrow \mathbf{Z}_L = j\omega L \\ C &\rightarrow \mathbf{Z}_C = 1/j\omega C \end{aligned}$$



### Step 3

Cast Equations in  
Phasor Form

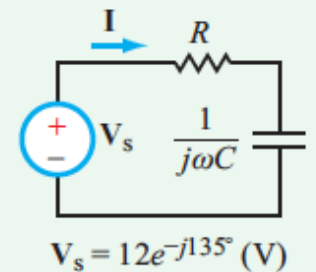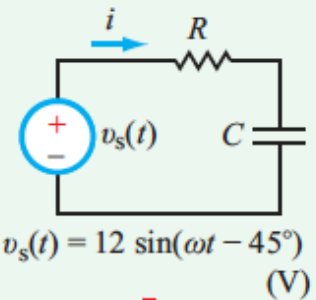

$$\mathbf{I} \left( R + \frac{1}{j\omega C} \right) = \mathbf{V}_s$$



# AC Phasor Analysis General Procedure

## Step 4: Solve for unknown variable

$$\mathbf{I} = \frac{12e^{-j135^\circ}}{R + \frac{1}{j\omega C}} = \frac{j12\omega C e^{-j135^\circ}}{1 + j\omega RC}.$$

Using the specified values, namely  $R = \sqrt{3} \text{ k}\Omega$ ,  $C = 1 \text{ }\mu\text{F}$ , and  $\omega = 10^3 \text{ rad/s}$ ,

$$\mathbf{I} = \frac{j12 \times 10^3 \times 10^{-6} e^{-j135^\circ}}{1 + j10^3 \times \sqrt{3} \times 10^3 \times 10^{-6}} = \frac{j12e^{-j135^\circ}}{1 + j\sqrt{3}} \text{ mA.}$$

$$\mathbf{I} = \frac{12e^{-j135^\circ} \cdot e^{j90^\circ}}{2e^{j60^\circ}} = 6e^{j(-135^\circ+90^\circ-60^\circ)} = 6e^{-j105^\circ} \text{ mA.}$$


## Step 5: Transform solution back to time domain

To return to the time domain, we apply the fundamental relation between a sinusoidal function and its phasor counterpart, namely

$$i(t) = \Re[\mathbf{I}e^{j\omega t}] = \Re[6e^{-j105^\circ} e^{j\omega t}] = 6 \cos(\omega t - 105^\circ) \text{ mA.}$$

### Step 1


Adopt Cosine Reference  
(Time Domain)

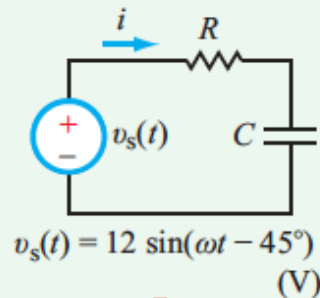
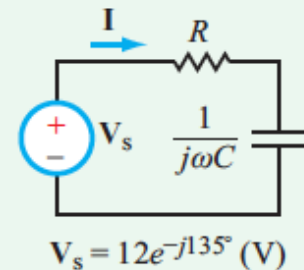
### Step 2

Transfer to Phasor Domain

$$\begin{aligned} i &\rightarrow \mathbf{I} \\ v &\rightarrow \mathbf{V} \\ R &\rightarrow \mathbf{Z}_R = R \\ L &\rightarrow \mathbf{Z}_L = j\omega L \\ C &\rightarrow \mathbf{Z}_C = 1/j\omega C \end{aligned}$$



### Step 3

Cast Equations in  
Phasor Form

$$\mathbf{I} \left( R + \frac{1}{j\omega C} \right) = \mathbf{V}_s$$

### Step 4

Solve for Unknown Variable  
(Phasor Domain)

$$\mathbf{I} = \frac{\mathbf{V}_s}{R + \frac{1}{j\omega C}}$$

### Step 5

Transform Solution  
Back to Time Domain

$$\begin{aligned} i(t) &= \Re[\mathbf{I}e^{j\omega t}] \\ &= 6 \cos(\omega t - 105^\circ) \text{ (mA)} \end{aligned}$$

# Example: RL Circuit

$$v_s(t) = 15 \sin(4 \times 10^4 t - 30^\circ) \text{ V.}$$

Also,  $R = 3 \Omega$  and  $L = 0.1 \text{ mH}$ . Obtain an expression for the voltage across the inductor.

## Solution:

**Step 1:** Convert  $v_s(t)$  to the cosine reference


$$v_s(t) = 15 \sin(4 \times 10^4 t - 30^\circ) = 15 \cos(4 \times 10^4 t - 120^\circ) \text{ V,}$$

$$\mathbf{V}_s = 15e^{-j120^\circ} \text{ V.}$$


**Step 2:** Transform circuit to the phasor domain

**Step 3:** Cast KVL in phasor domain
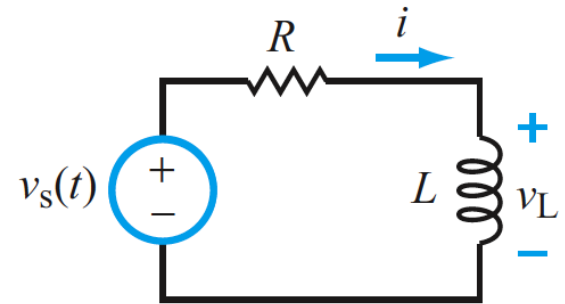
$$R\mathbf{I} + j\omega L\mathbf{I} = \mathbf{V}_s.$$



(a) Time domain

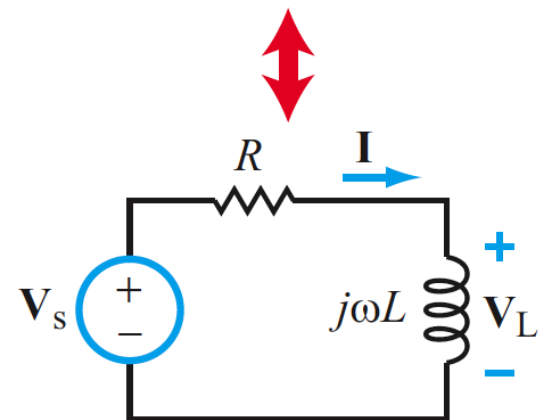

(b) Phasor domain





Step 4: Solve for unknown variable

$$\begin{aligned}\mathbf{I} &= \frac{\mathbf{V}_s}{R + j\omega L} = \frac{15e^{-j120^\circ}}{3 + j4 \times 10^4 \times 10^{-4}} \\ &= \frac{15e^{-j120^\circ}}{3 + j4} = \frac{15e^{-j120^\circ}}{5e^{j53.1^\circ}} = 3e^{-j173.1^\circ} \text{ A.}\end{aligned}$$


The phasor voltage across the inductor is related to  $\mathbf{I}$  by

$$\begin{aligned}\mathbf{V}_L &= j\omega L \mathbf{I} \\ &= j4 \times 10^4 \times 10^{-4} \times 3e^{-j173.1^\circ} \\ &= j12e^{-j173.1^\circ} \\ &= 12e^{-j173.1^\circ} \cdot e^{j90^\circ} = 12e^{-j83.1^\circ} \text{ V,}\end{aligned}$$


where we replaced  $j$  with  $e^{j90^\circ}$ .

Step 5: Transform solution to the time domain
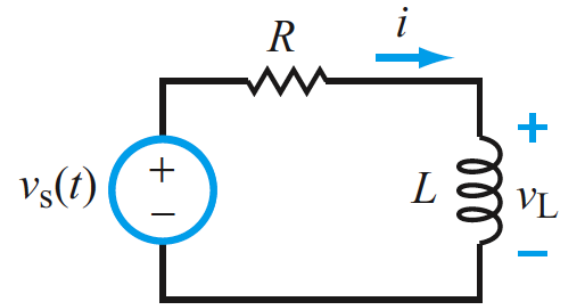
$$\begin{aligned}v_L(t) &= \Re\{\mathbf{V}_L e^{j\omega t}\} \\ &= \Re[12e^{-j83.1^\circ} e^{j4 \times 10^4 t}] \\ &= 12 \cos(4 \times 10^4 t - 83.1^\circ) \text{ V.}\end{aligned}$$



(a) Time domain

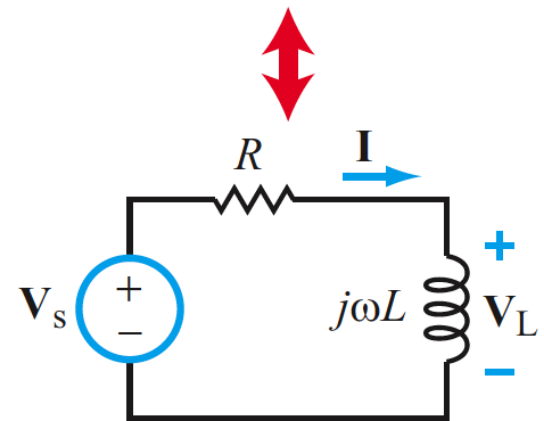



(b) Phasor domain



# Nodal Analysis

- Example---Find  $i_x$

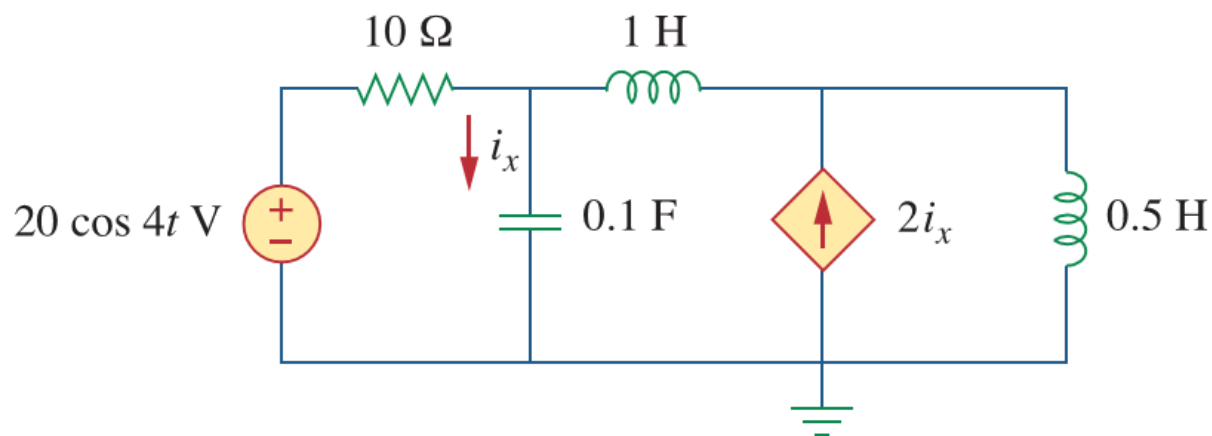

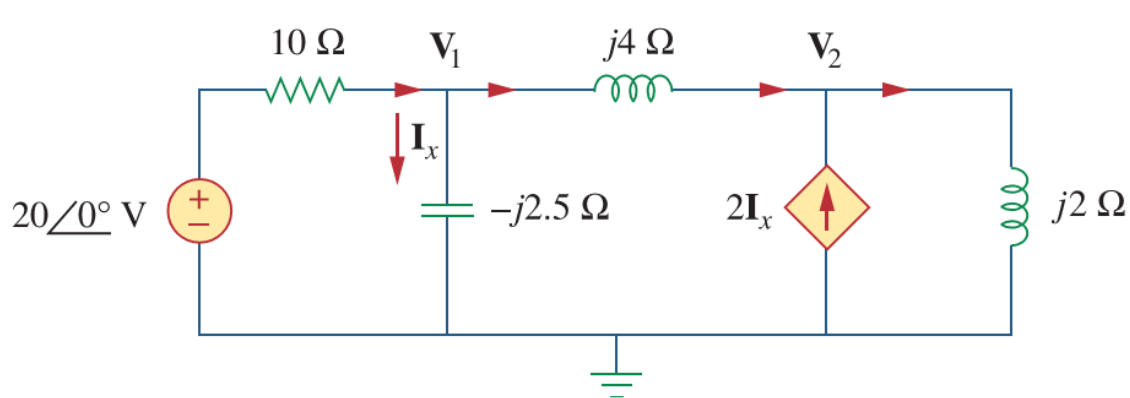


$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$
$$2\mathbf{I}_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$



10.5 Find  $i_o$  in the circuit of Fig. 10.54.

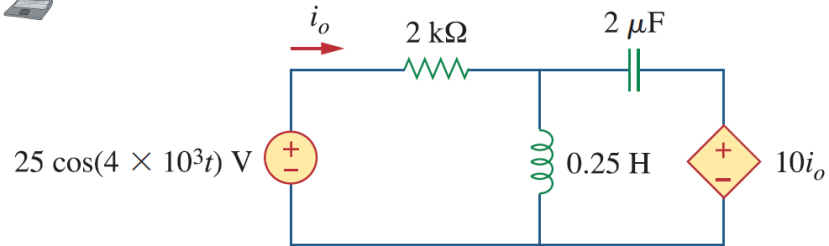


**Figure 10.54**

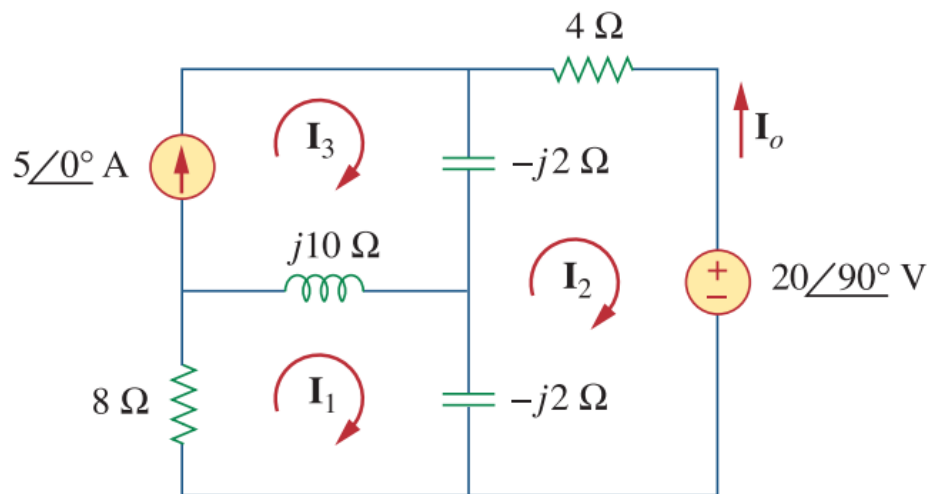For Prob. 10.5.




# Mesh Analysis





# Mesh Analysis

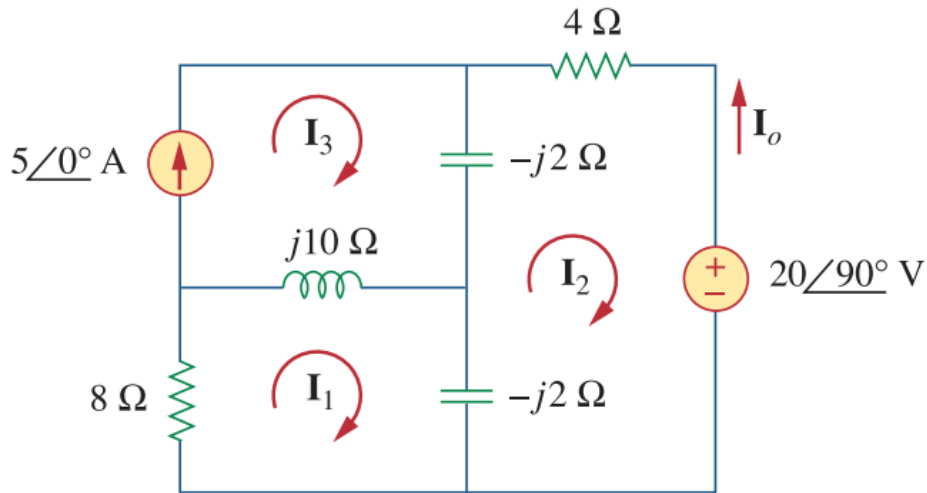

Applying KVL to mesh 1, we obtain

$$(8 + j10 - j2)\mathbf{I}_1 - (-j2)\mathbf{I}_2 - j10\mathbf{I}_3 = 0 \quad (10.3.1)$$

For mesh 2,

$$(4 - j2 - j2)\mathbf{I}_2 - (-j2)\mathbf{I}_1 - (-j2)\mathbf{I}_3 + 20\angle 90^\circ = 0 \quad (10.3.2)$$

For mesh 3,  $\mathbf{I}_3 = 5$ . Substituting this in Eqs. (10.3.1) and (10.3.2), we get

$$(8 + j8)\mathbf{I}_1 + j2\mathbf{I}_2 = j50 \quad (10.3.3)$$

$$j2\mathbf{I}_1 + (4 - j4)\mathbf{I}_2 = -j20 - j10 \quad (10.3.4)$$




**10.27** Using mesh analysis, find  $\mathbf{I}_1$  and  $\mathbf{I}_2$  in the circuit of



Fig. 10.75.

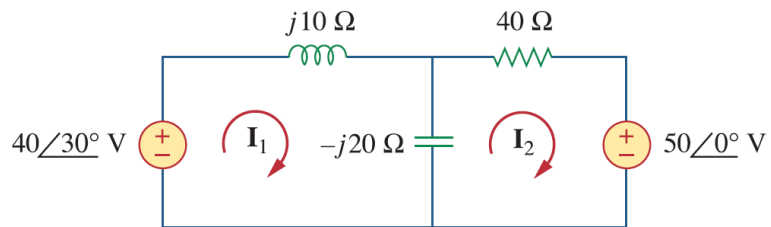**ML**



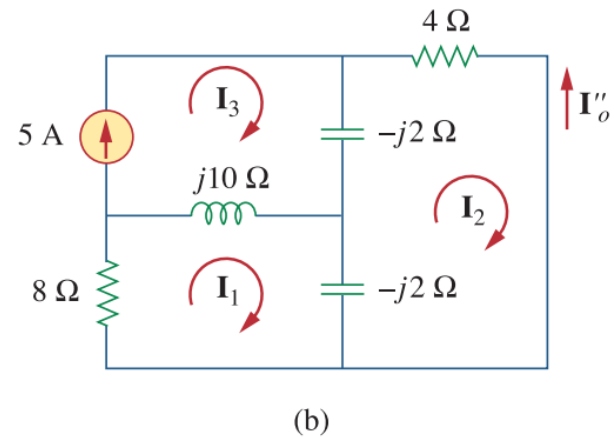


**Figure 10.75**

For Prob. 10.27.

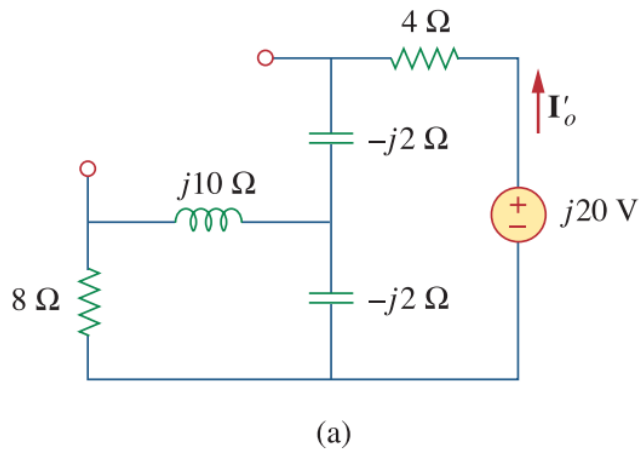

# Superposition-Example

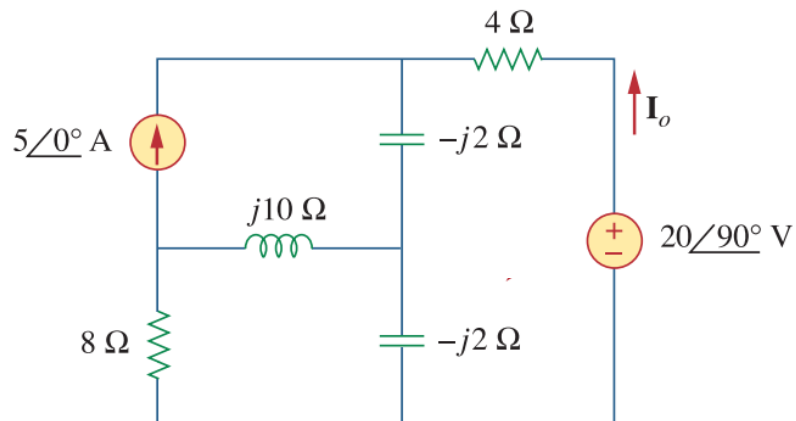






# Multiple Frequencies

**10.46** Solve for  $v_o(t)$  in the circuit of Fig. 10.91 using the superposition principle.

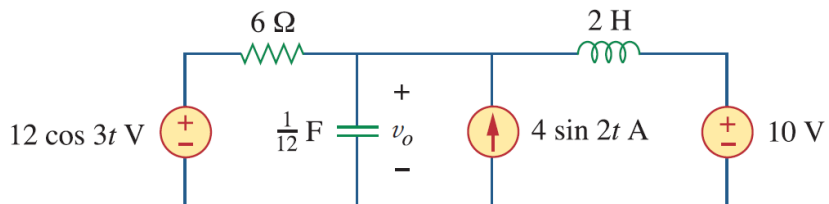


**Figure 10.91**

For Prob. 10.46.



10.48 Find  $i_o$  in the circuit of Fig. 10.93 using superposition.

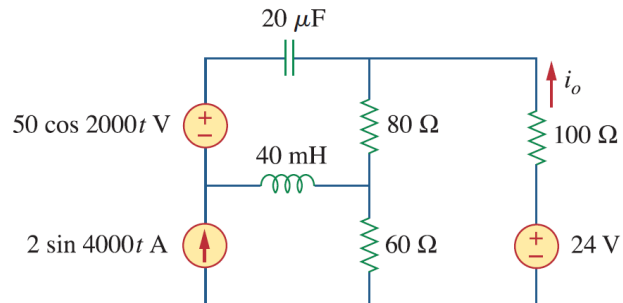


**Figure 10.93**

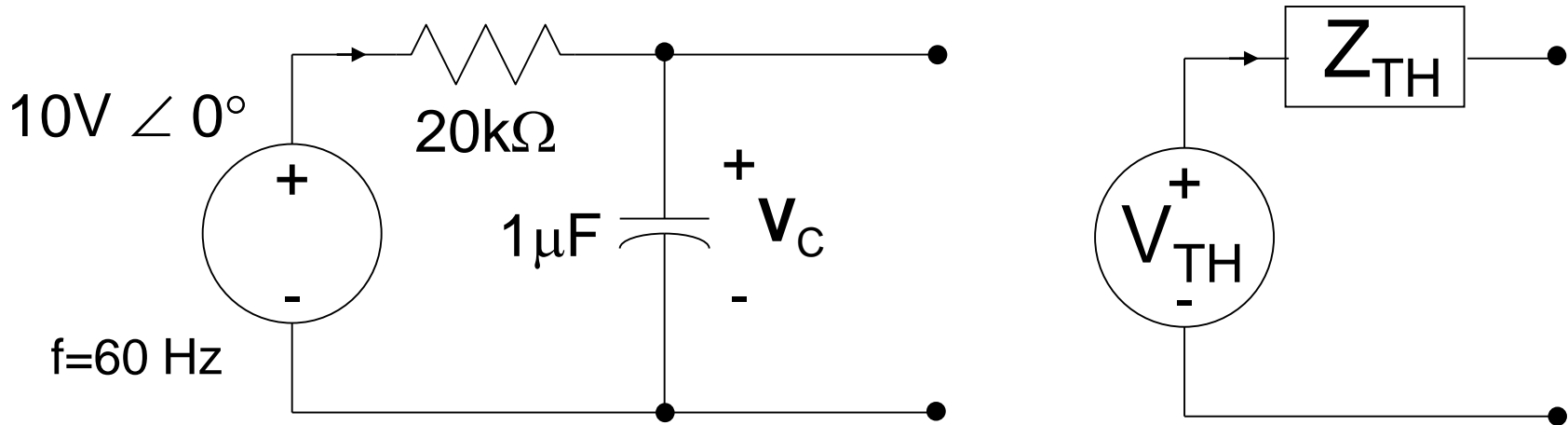For Prob. 10.48.



# Thevenin Equivalent



$$\mathbf{Z}_R = R = 20\text{k}\Omega = 20\text{k}\Omega \angle 0^\circ$$

$$\mathbf{Z}_C = 1/j(2\pi f \times 1\mu\text{F}) = 2.65\text{k}\Omega \angle -90^\circ$$

$$\mathbf{V}_{TH} = \mathbf{V}_{OC} = 10\text{V} \angle 0^\circ \left( \frac{2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 1.31 \angle -82.4$$


$$\mathbf{Z}_{TH} = \mathbf{Z}_R \parallel \mathbf{Z}_C = \left( \frac{20\text{k}\Omega \angle 0^\circ \cdot 2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 2.62 \angle -82.4$$



10.67 Find the Thevenin and Norton equivalent circuits at terminals  $a$ - $b$  in the circuit of Fig. 10.110.



ML

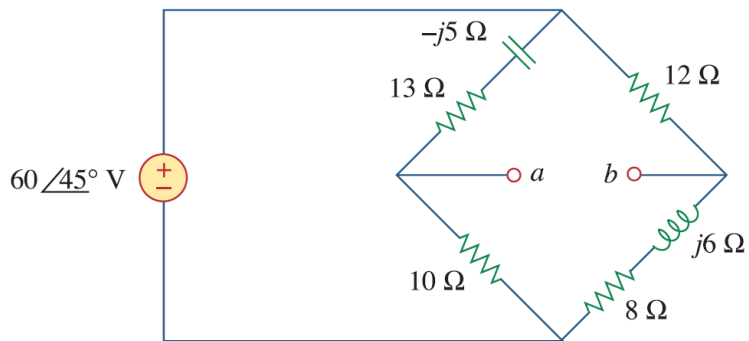


**Figure 10.110**

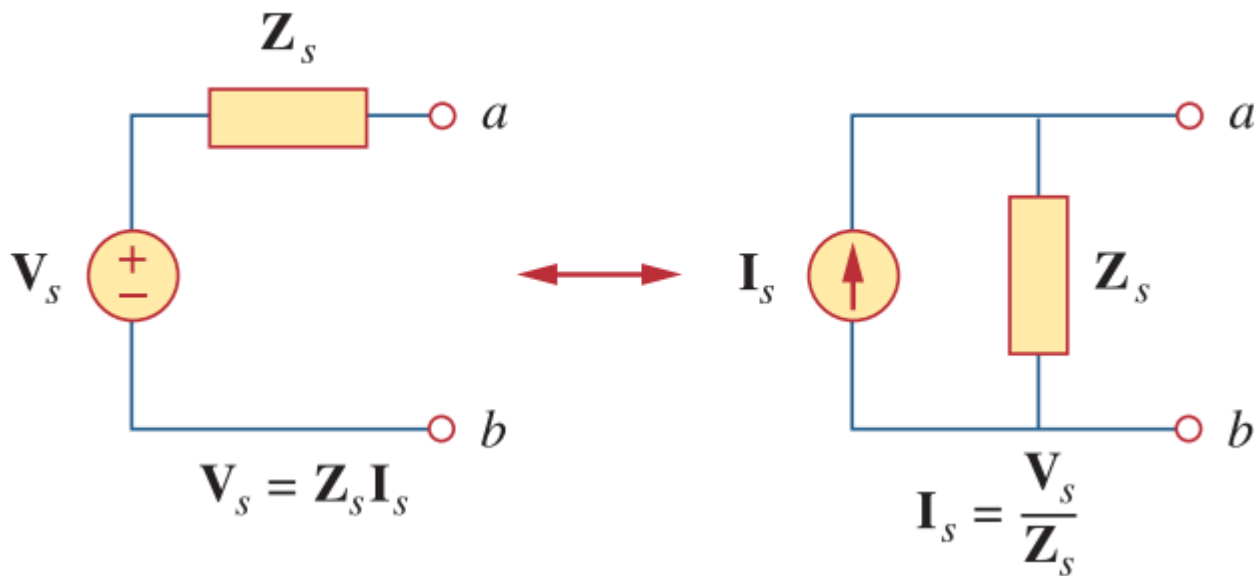For Prob. 10.67.



# Source transformation/Norton



$$V_s = Z_s I_s \quad \Leftrightarrow \quad I_s = \frac{V_s}{Z_s}$$


# AC Op Amp Circuits

**Question 1:** Are op amps used in ac circuits?

**Answer 1:** Yes.


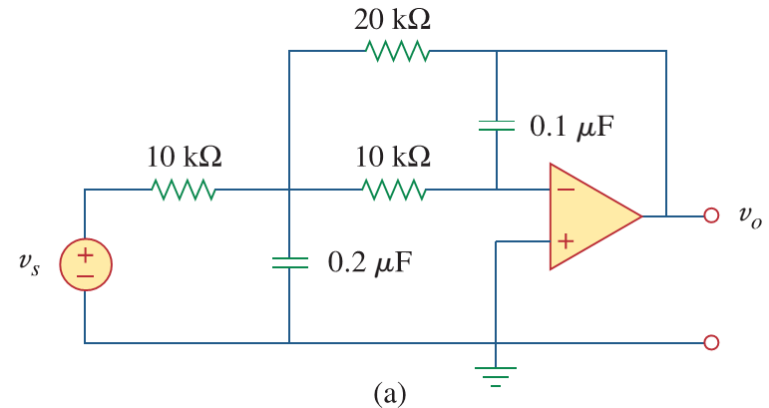
**Question 2:** Is the ideal op-amp model applicable to ac circuits?

**Answer 2:** The ideal op-amp model is based on the assumption that the open-loop gain  $A$  is very large ( $> 10^4$ ), which is true at dc and low frequencies, but not necessarily so at high frequencies. The range of frequencies over which  $A$  is large depends on the specific op-amp design.






## Example –find $v_o$

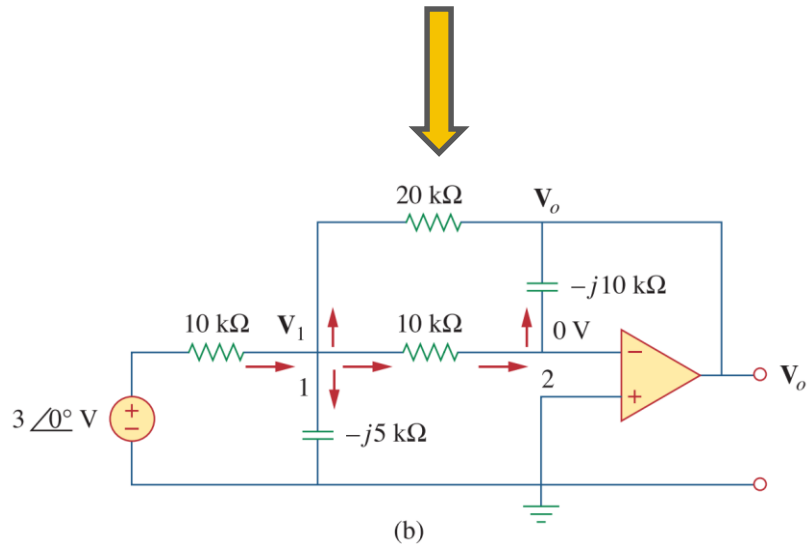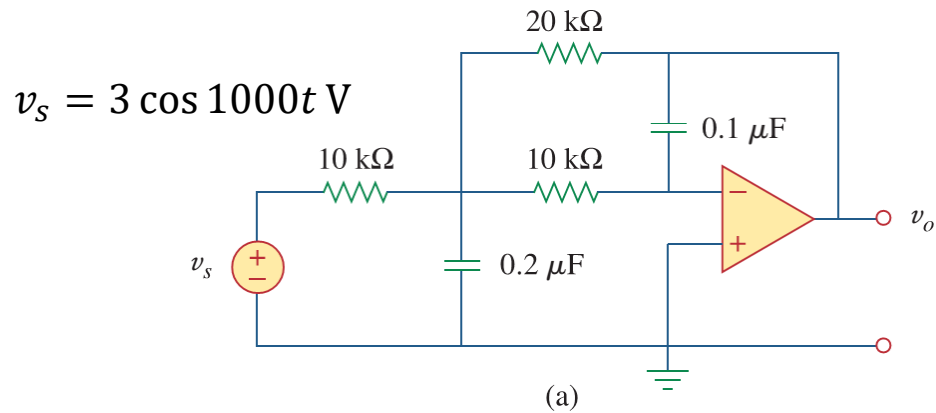



**10.74** Evaluate the voltage gain  $A_v = V_o/V_s$  in the op amp circuit of Fig. 10.117. Find  $A_v$  at  $\omega = 0$ ,  $\omega \rightarrow \infty$ ,  $\omega = 1/R_1C_1$ , and  $\omega = 1/R_2C_2$ .

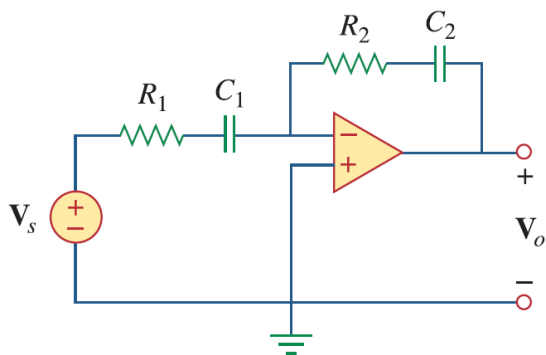

**Figure 10.117**

For Prob. 10.74.






# Outline

- Kirchhoff's laws in phasor domain
- Generalized impedance
- General AC phasor analysis
- Phasor diagram





# Phasor Diagrams

## Capacitor

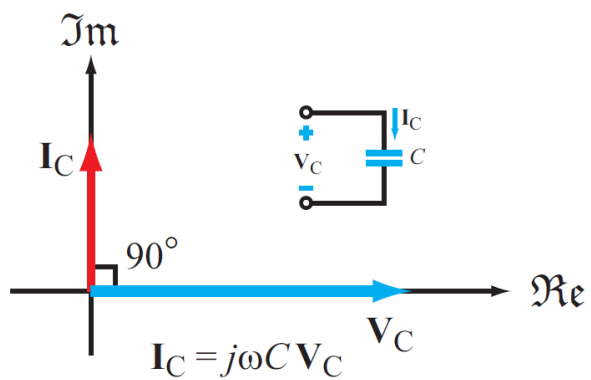


## Inductor

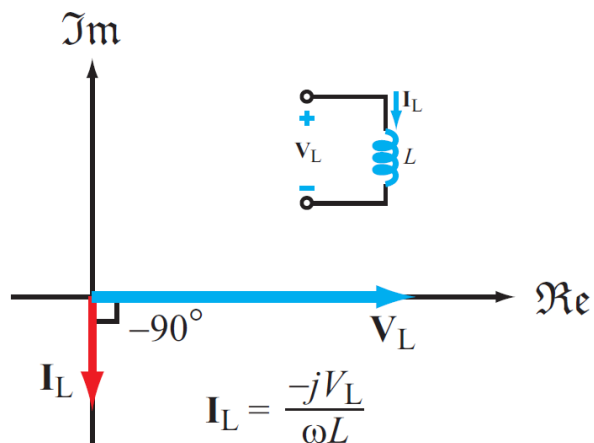

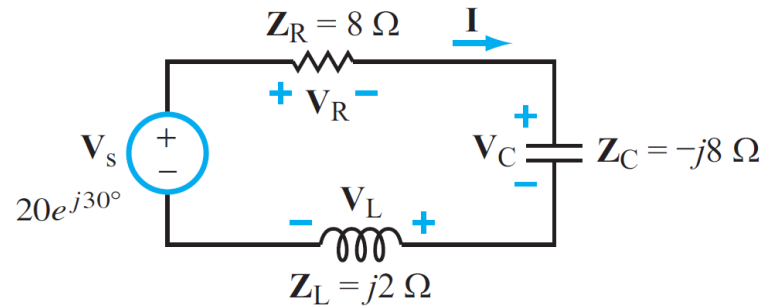

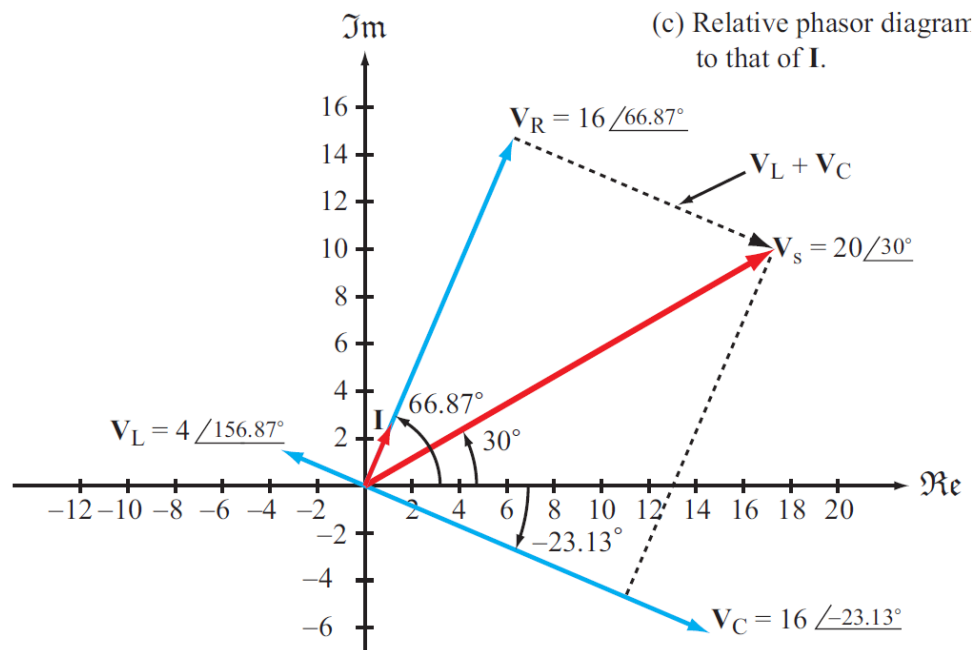
$$\mathbf{I} = \frac{\mathbf{V}_s}{R + j\omega L - \frac{j}{\omega C}} = \frac{20e^{j30^\circ}}{8 + j2 - j8} = \frac{20e^{j30^\circ}}{8 - j6} = \frac{20e^{j30^\circ}}{10e^{-j36.87^\circ}} = 2e^{j66.87^\circ} \text{ A}$$





**10.79** For the op amp circuit in Fig. 10.122, obtain  $v_o(t)$ .

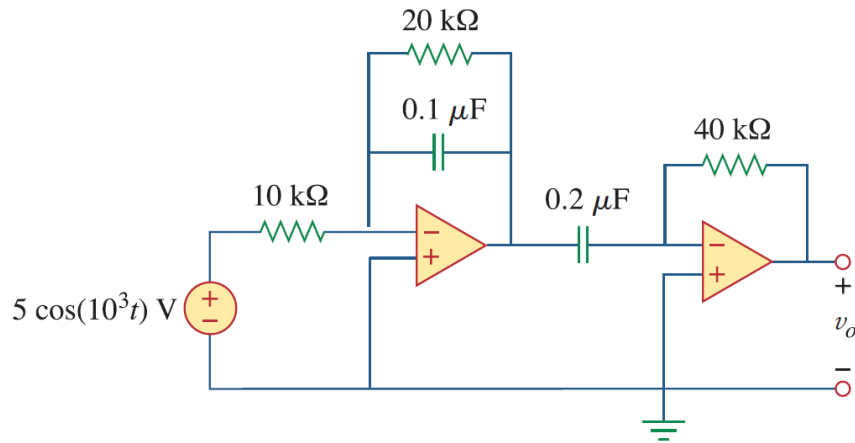

**Figure 10.122**


For Prob. 10.79.

**10.89** The op amp circuit in Fig. 10.131 is called an *inductance simulator*. Show that the input impedance is given by

$$\mathbf{Z}_{\text{in}} = \frac{\mathbf{V}_{\text{in}}}{\mathbf{I}_{\text{in}}} = j\omega L_{\text{eq}}$$

where

$$L_{\text{eq}} = \frac{R_1 R_3 R_4}{R_2} C$$

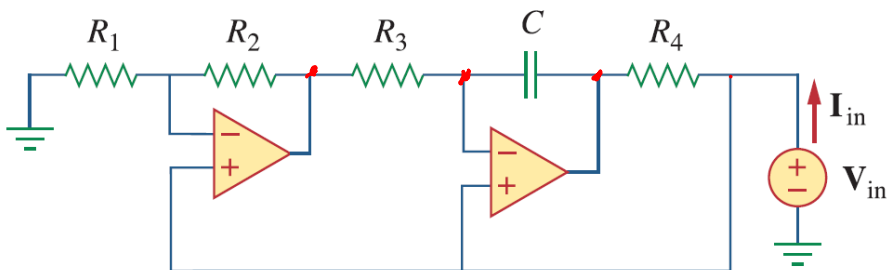


**Figure 10.131**

For Prob. 10.89.



**10.91** Consider the oscillator in Fig. 10.133.

- (a) Determine the oscillation frequency.
- (b) Obtain the minimum value of  $R$  for which oscillation takes place.

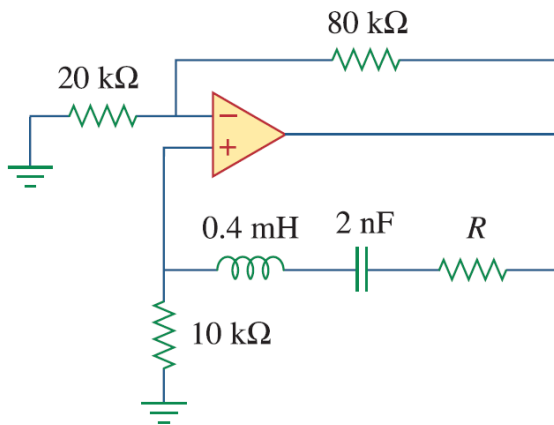


**Figure 10.133**

For Prob. 10.91.



**10.91** Consider the oscillator in Fig. 10.133.

- (a) Determine the oscillation frequency.
- (b) Obtain the minimum value of  $R$  for which oscillation takes place.

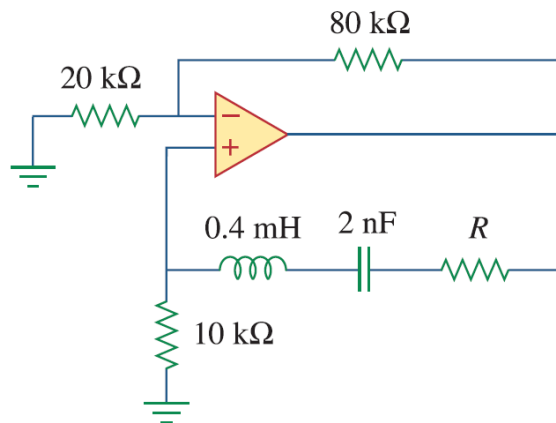

**Figure 10.133**

For Prob. 10.91.