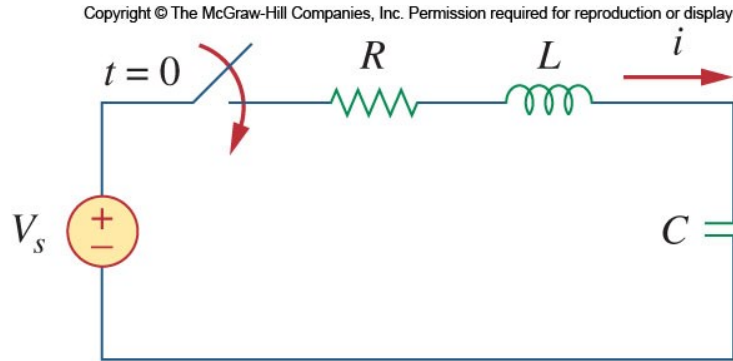




Step Response of a Series RLC Circuit



$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}$$

- The solution

$$v(t) = v_t(t) + v_{ss}(t)$$

- The complete solutions for the three conditions of damping are:

$$v(t) = V_s + (A_1 e^{s_1 t} + A_2 e^{s_2 t}) \quad (\text{Overdamped})$$

$$v(t) = V_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically Damped})$$

$$v(t) = V_s + (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$





Example

- Find $v(t)$ and $i(t)$ for $t > 0$.

Consider three cases:

- $R = 5\Omega$
- $R = 4\Omega$
- $R = 1\Omega$


When $R = 5\Omega$,


- For $t < 0$, switch closed, capacitor open, inductor shorted.
- For $t > 0$, switch open, a series RLC network

- $v(0) = 4V$ $i(0) = 4A = C \frac{dv(0)}{dt}$, $\frac{dv(0)}{dt} = 16$

$$\alpha = \frac{R}{2L} = 2.5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2, \quad s_{1,2} = -1, -4 \quad \text{Overdamped.}$$
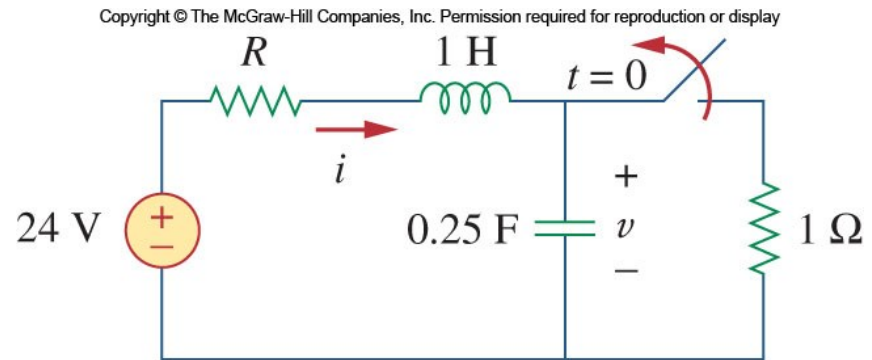
$$v(t) = v_s + (A_1 e^{-t} + A_2 e^{-4t})$$



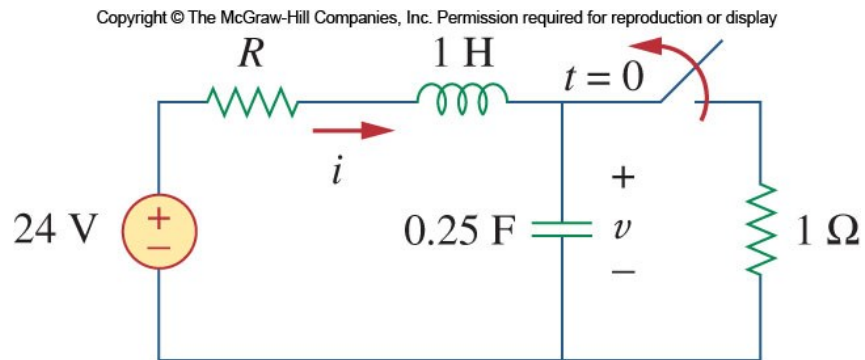


When $R = 4\Omega$,

- For $t < 0$, switch closed, capacitor open, inductor shorted.
- For $t > 0$, switch open, a series RLC network
- $v(0) = 4.8V, i(0) = 4.8A = C \frac{dv(0)}{dt}, \frac{dv(0)}{dt} = 19.2$

$$\alpha = \frac{R}{2L} = 2, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2, \quad s_{1,2} = -2 \quad \text{Critically damped}$$

$$v(t) = v_s + (A_1 + A_2 t)e^{-2t}$$

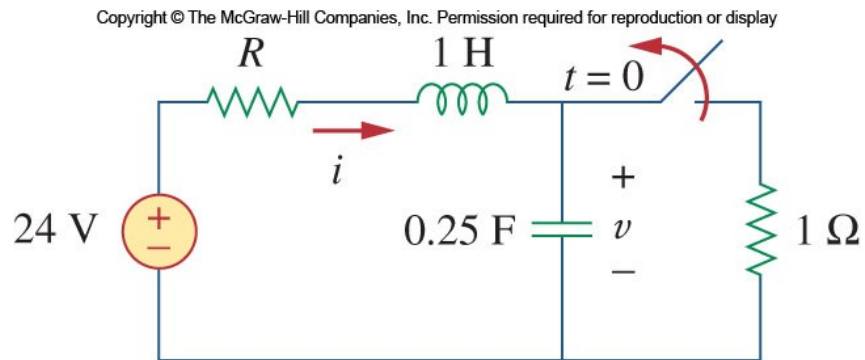

When $R = 1\Omega$,


- For $t < 0$, switch closed, capacitor open, inductor shorted.
- For $t > 0$, switch open, a series RLC network
- $v(0) = 12V$, $i(0) = 12A = C \frac{dv(0)}{dt}$, $\frac{dv(0)}{dt} = 48$

$$\alpha = \frac{R}{2L} = 0.5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2, \quad s_{1,2} = -0.5 \pm j1.936 \quad \text{Underdamped}$$

$$v(t) = v_s + (B_1 \cos 1.936t + B_2 \sin 1.936t)e^{-0.5t}$$



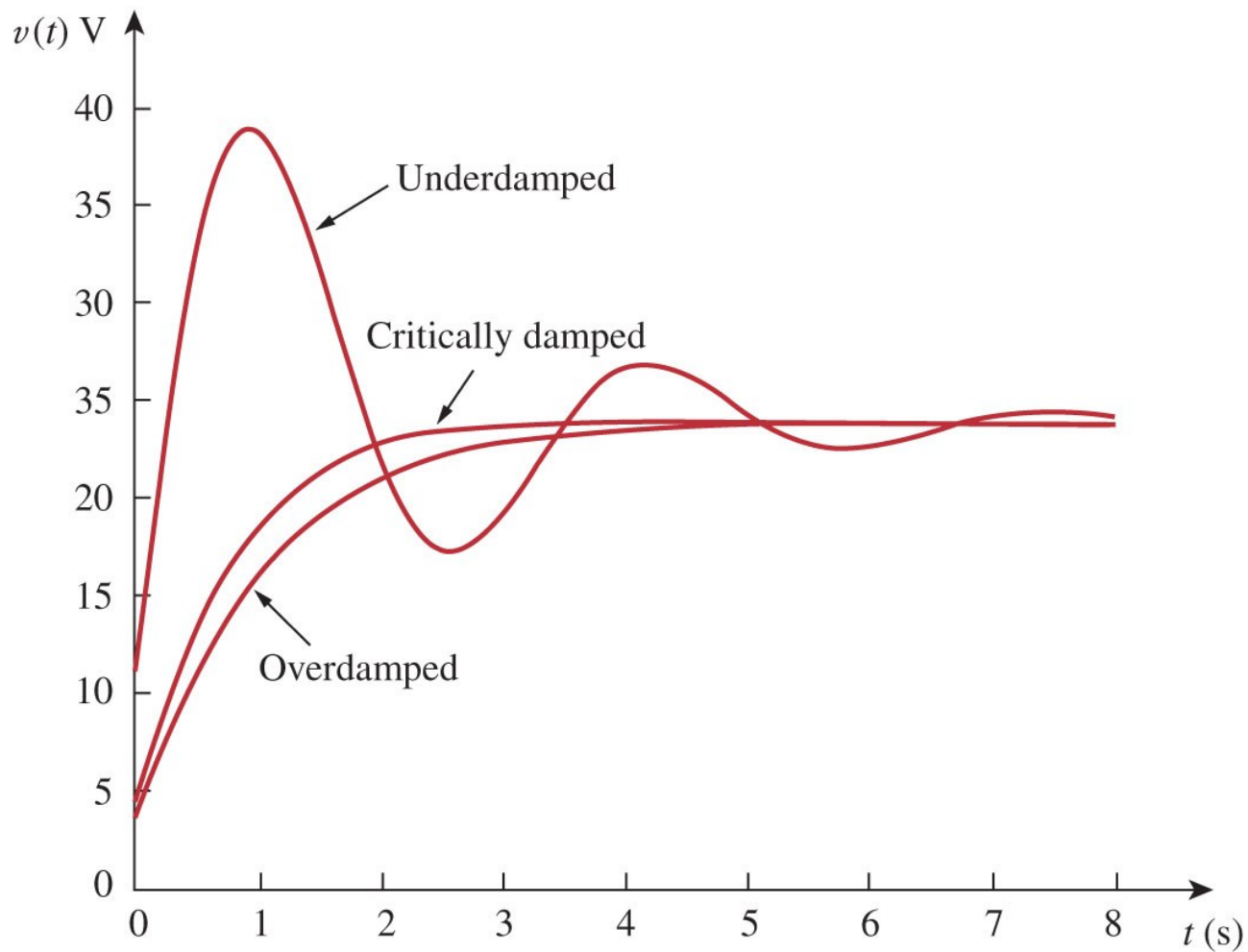Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display








Step Response of a Parallel RLC Circuit

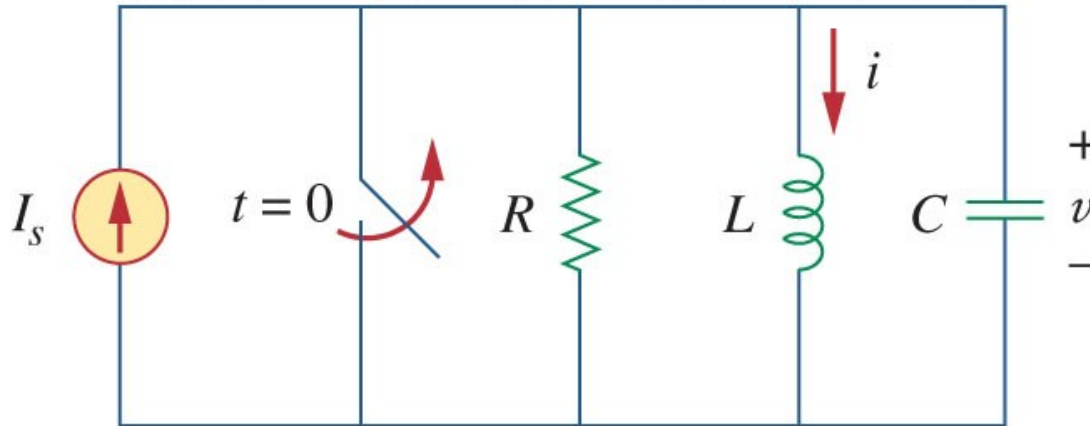Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Apply KCL,

$$\frac{v}{R} + i + C \frac{dv}{dt} = I_s$$

$$\& \quad v = L \frac{di}{dt}$$

So we get

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$



Step Response of a Parallel RLC Circuit

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

- The total response is a combination of **steady state responses and transient response**:

$$i(t) = I_s + (A_1 e^{s_1 t} + A_2 e^{s_2 t}) \text{ (Overdamped)}$$

$$i(t) = I_s + (A_1 + A_2 t) e^{-\alpha t} \text{ (Critically Damped)}$$

$$i(t) = I_s + (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t} \text{ (Underdamped)}$$


Here the variables A_1/A_2 B_1/B_2 are obtained from the initial conditions, $i(0)$ and $di(0)/dt$.





Example

- Find $i(t)$ and $i_R(t)$ for $t > 0$.

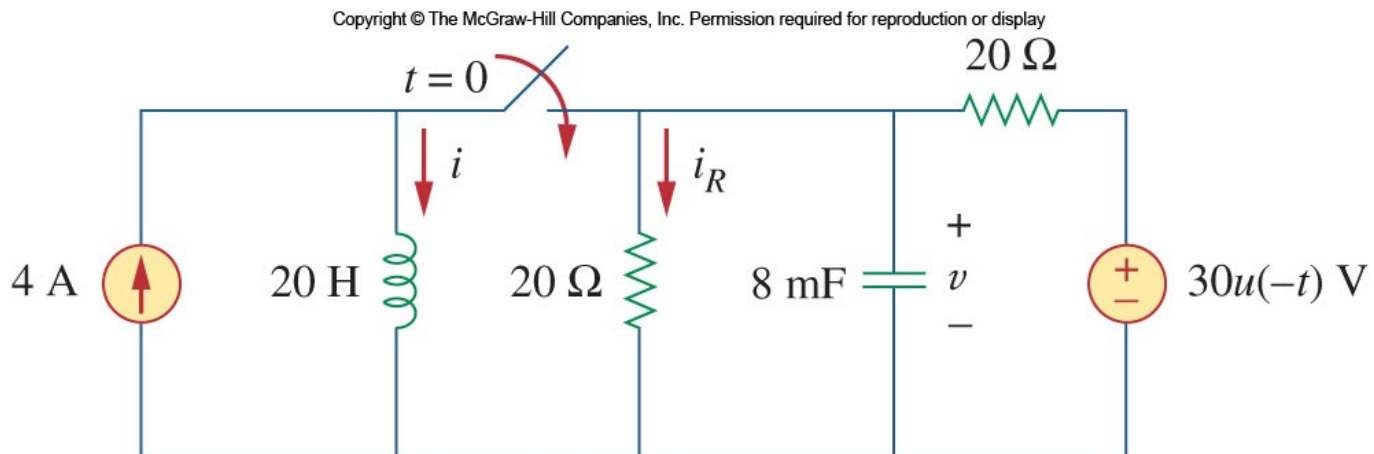




General Second-Order Circuits

- An example

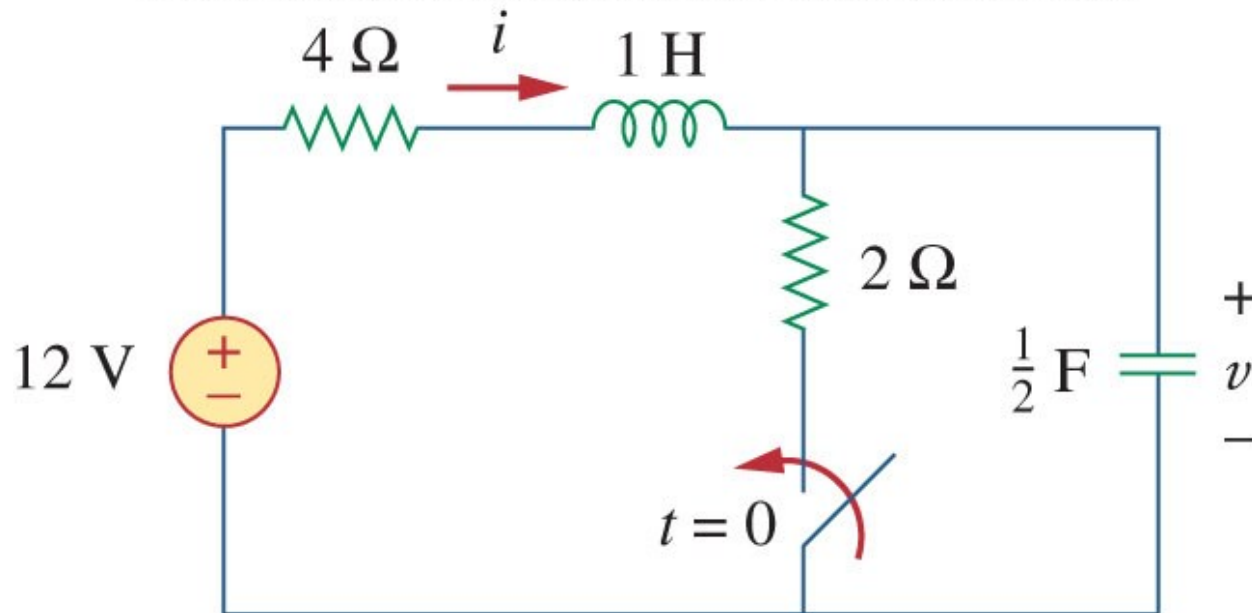Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





General Second-Order Circuits

- The principles of solving the series/parallel forms of RLC circuits can **be applied** to **general second-order circuits**, by taking the following six steps:
 1. First determine the initial conditions, $x(0)$ and $dx(0)/dt$.
 2. **Applying KVL and KCL**, to find the **general** second-order differential equation to describe $x(t)$.
 3. **Depending on the roots of C.E. , the form of the general solution $x_{g.s.}(t)$ (3 cases) of homogeneous equation can be determined.**
 4. We obtain the **particular solution** by observation/calculation, **specially** for a DC/step response

$$x_{p.s.}(t) = x(\infty)$$

5. The total response = general solution + particular solution.

$$x(t) = x_{p.s.}(t) + x_{g.s.}(t)$$

6. Using the initial conditions to determine the constants of $x(t)$.





General RLC Circuits

- Find the complete response $v(t)$ for $t > 0$ in the circuit.

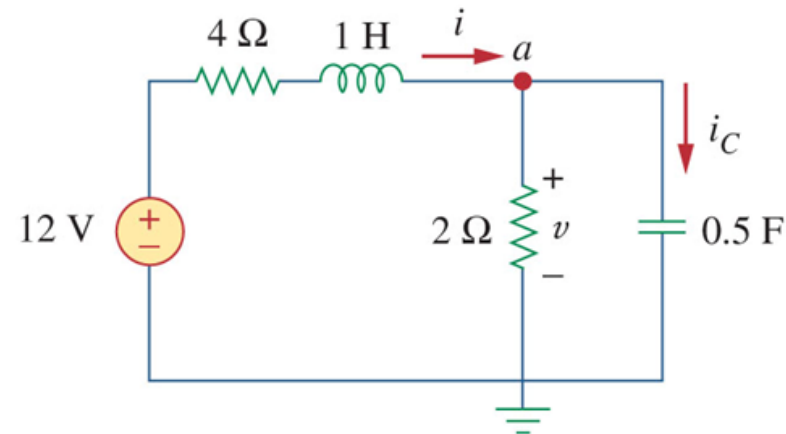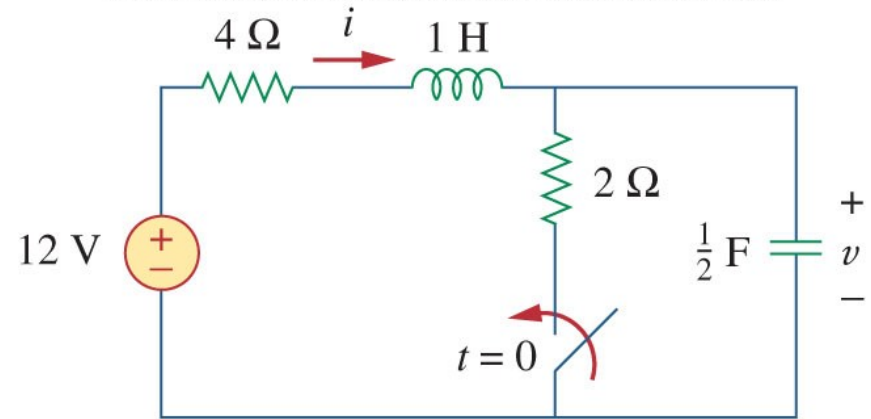1. Initial conditions

$$v(0^+) = v(0^-) = 12V, i(0^+) = i(0^-) = 0$$


$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = \frac{-12/2}{0.5} = -12 V/s$$





General RLC Circuits

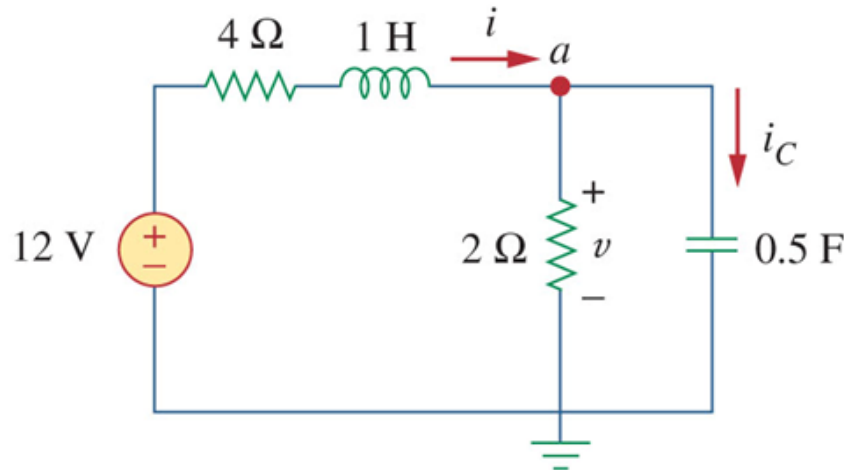- Find the complete response $v(t)$ for $t > 0$ in the circuit.




2. KCL at node a : $i = \frac{v}{2} + 0.5 \frac{dv}{dt}$

KVL on left mesh: $4i + 1 \frac{di}{dt} + v = 12$

➔ $\frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 6v = 24$

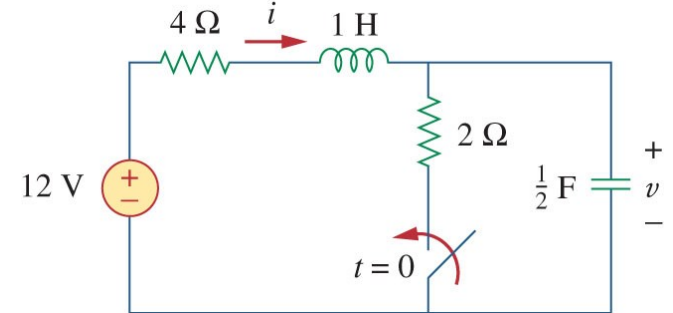Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





$$\frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 6v = 24$$

3. General Solution:

➡ General Solution $v_t(t) = A_1 e^{-2t} + A_2 e^{-3t}$

4. Particular Solution : Steady-state response $v_{ss}(t) = 4V$

5. Put together : $v(t) = 4 + A_1 e^{-2t} - A_2 e^{-3t}$

6. Using initial conditions to determine A_1 , A_2



Self-test-General RLC Circuit

- Find the complete response $i(t)$ for $t > 0$ in the circuit.

