




# Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits  
阶跃
- Others
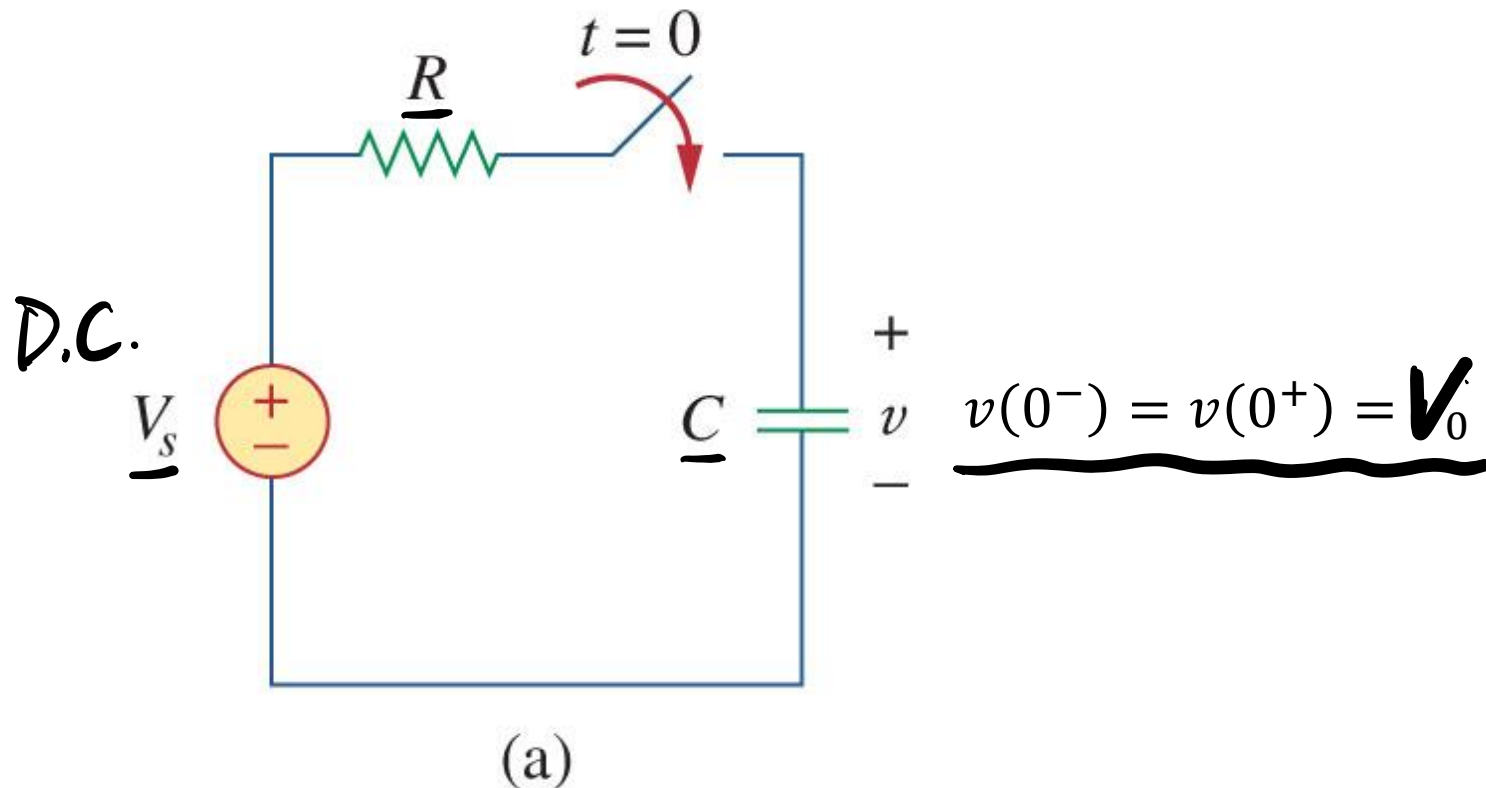
# Step Response of RC Circuit

- When a DC source is suddenly applied to a RC circuit, the circuit response is known as the step response.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





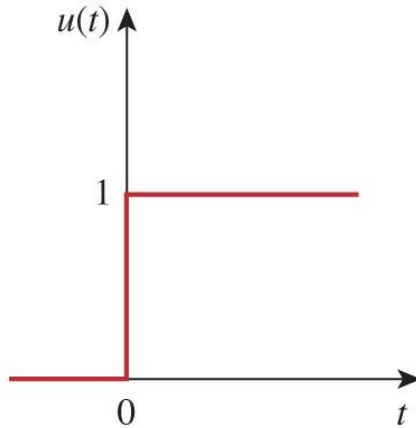
# The Unit Step $u(t)$ function $u(t)$

- A step function is one that maintains a constant value before a certain time and then changes to another constant afterwards.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$


switching time may be shifted to  $t = t_0$  by
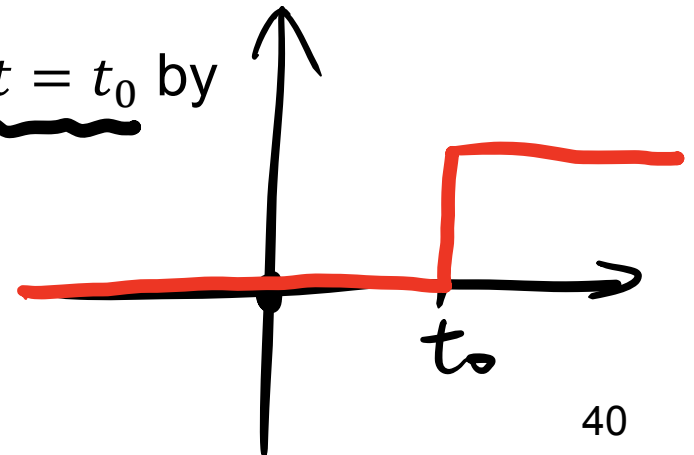
$$\underline{u(t - t_0)} = \begin{cases} 0, & t < \underline{t_0} \\ 1, & t > \underline{t_0} \end{cases}$$



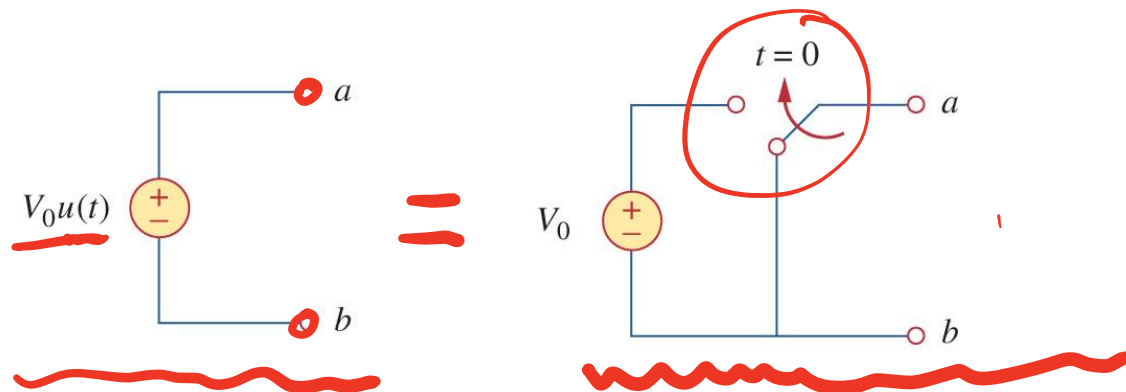
# Equivalent Circuit of Unit Step

- The unit step function has an equivalent circuit to represent when it is used **to switch on** a source.



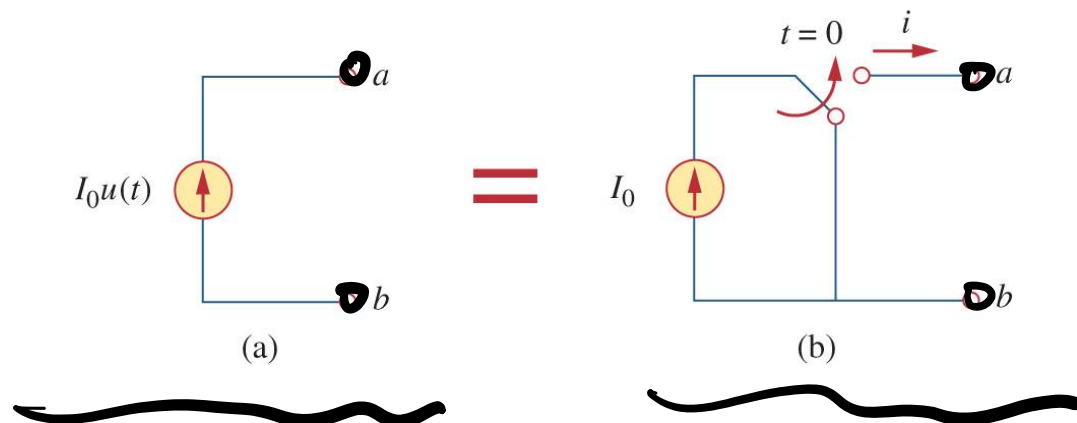
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




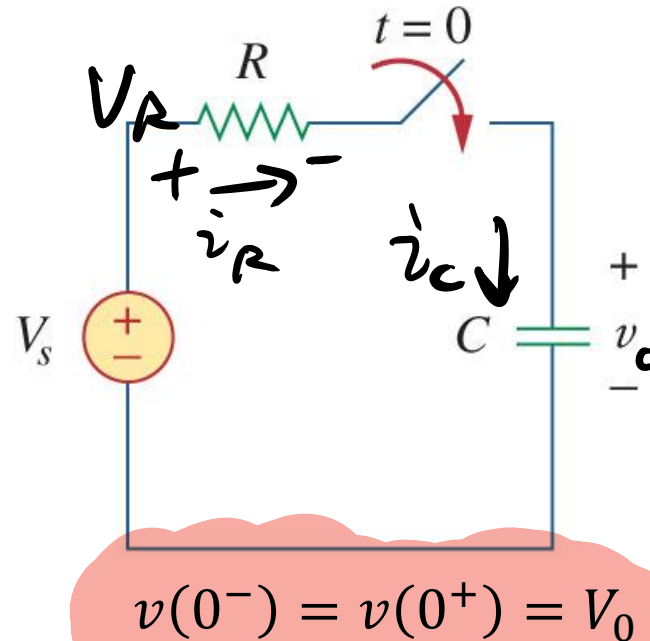
# Step Response of the RC Circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\underline{V_c(t > 0)}$$

$$\underline{V_s > V_0} \quad t \rightarrow \infty$$

$$V_c(t \rightarrow \infty) ? = \begin{cases} \langle 1 \rangle & 0 \\ \langle 2 \rangle & V_0 \\ \langle 3 \rangle & V_s \quad \checkmark \end{cases}$$



$$C \frac{dV_c}{dt} = \dot{V}_c = \dot{V}_R = \frac{V_R}{R} = \frac{V_s - V_c}{R}$$

$$\frac{dV_c}{dt} + \frac{1}{RC} \cdot V_c = \frac{V_s}{RC}$$

G.S. :  $V_c' = A \cdot e^{-\frac{1}{RC} \cdot t}$

P.S. :  $\underline{V_c'' = V_s}$


$\therefore V_c(t) = A \cdot e^{-\frac{1}{RC} t} + V_s$

$$\hookrightarrow V_c(t=0) = V_0 = A + V_s \quad \downarrow$$

$$\Rightarrow A = V_0 - V_s$$

$$\underline{V_c(t) = V_s + (V_0 - V_s) \cdot e^{-t/\tau_{RC}}, t > 0} \quad (2)$$


$$V_s > V_0$$

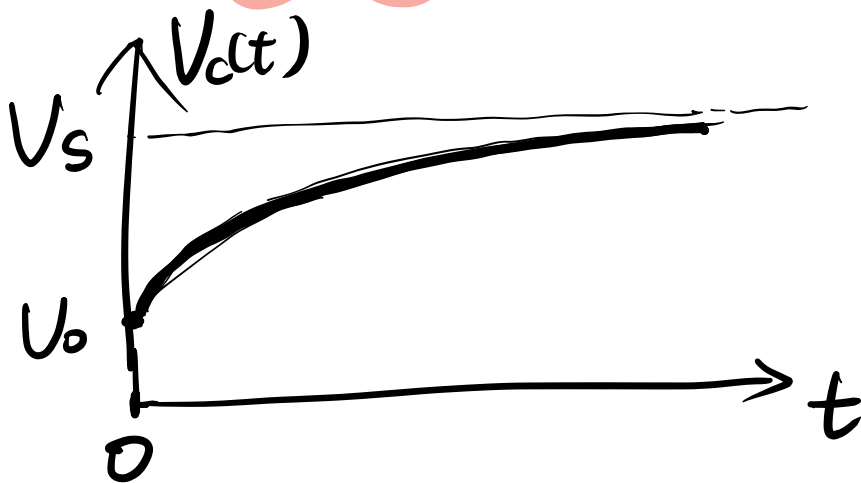



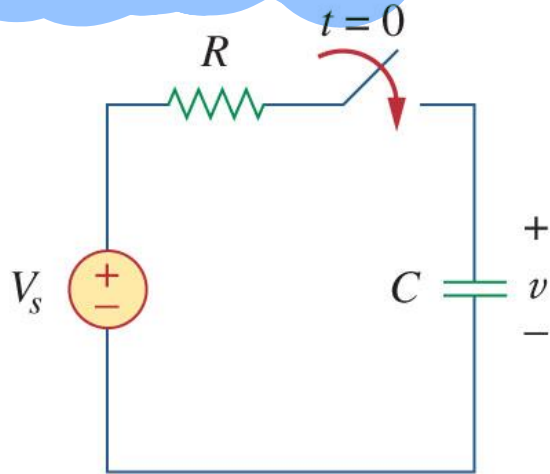
# Step Response of the RC Circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$v(0^-) = v(0^+) = V_0$$

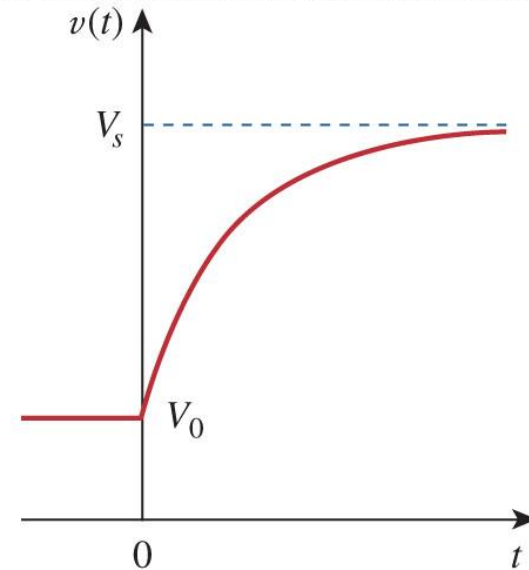Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

$$\tau = RC$$


- This is known as the complete response, or total response.




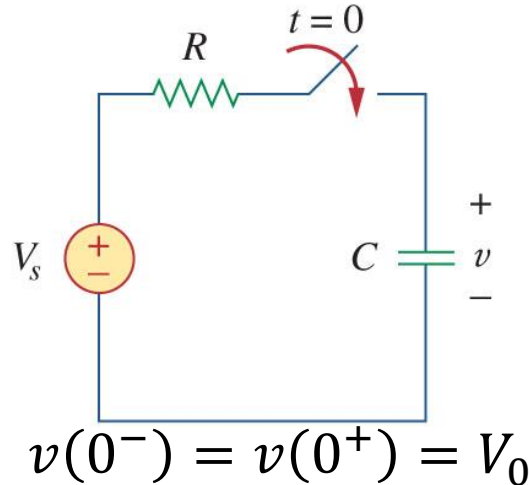
# Complete response

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- The complete response

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$

can be written as:

$$v = v_n + v_f$$

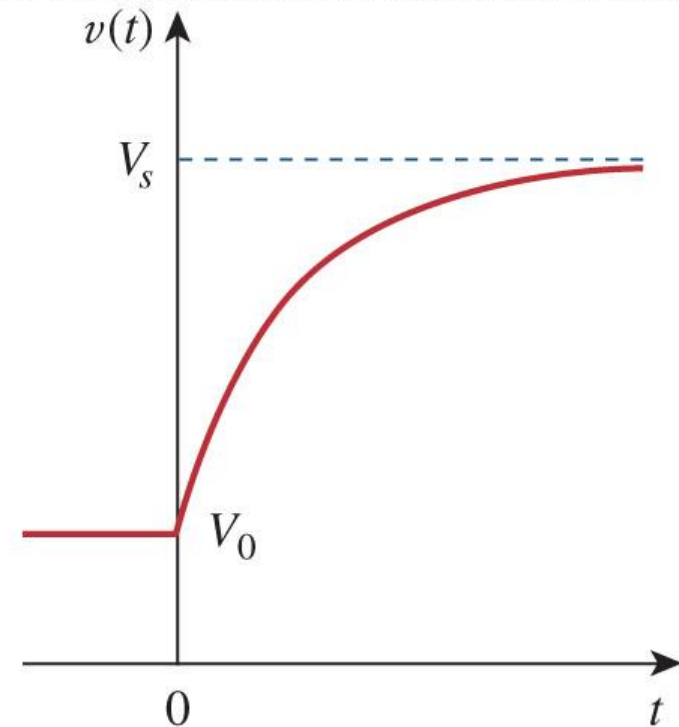Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





$$V_s + (V_0 - V_s)e^{-t/\tau} = \underbrace{V_0 \cdot e^{-t/\tau}}_{\text{natural response}} + \underbrace{V_s(1 - e^{-t/\tau})}_{\text{forced response}}$$

Complete response = natural response + forced response  
stored energy                      independent source

or


$$v = v_n + v_f$$

where

$$\rightarrow v_n = V_0 e^{-t/\tau}$$

and

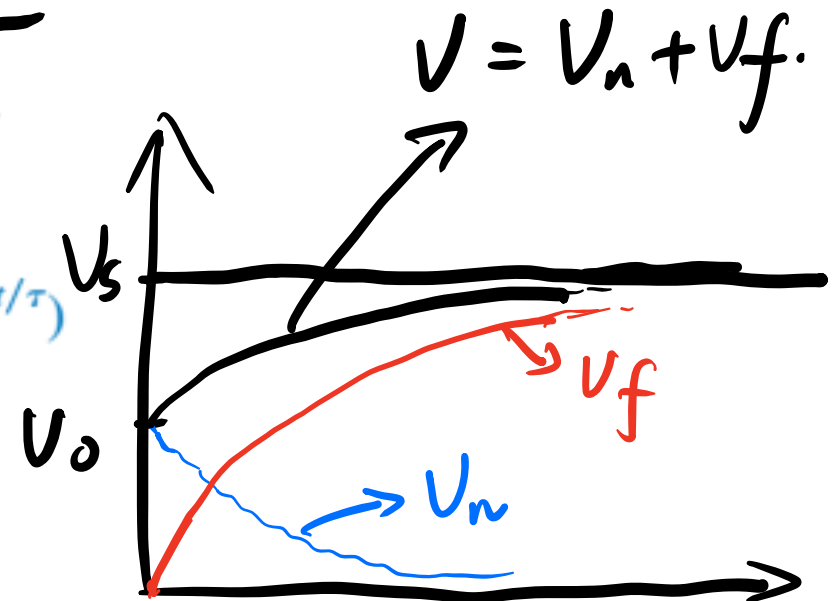
$$\rightarrow v_f = V_s(1 - e^{-t/\tau})$$





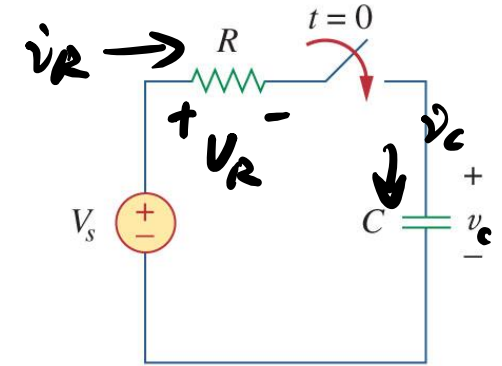
## Another Perspective

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$




- Another way to look at the response is to break it up into the transient response and the steady state response:
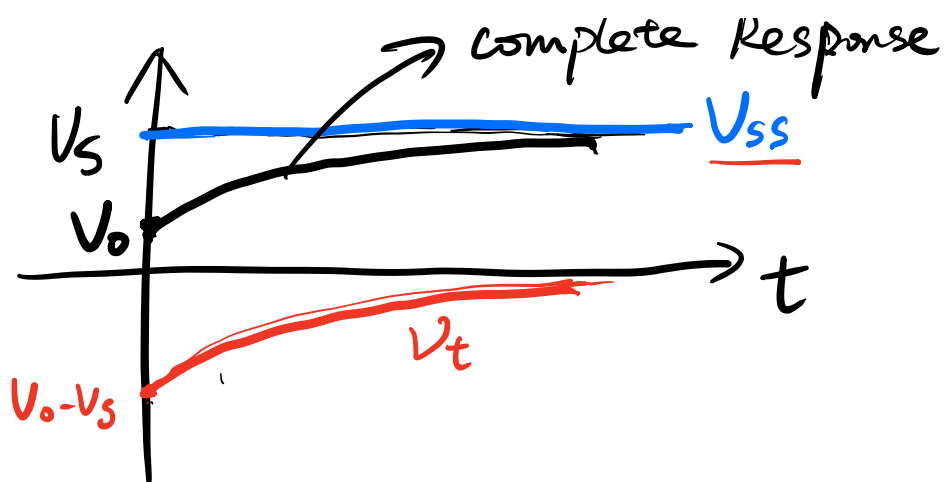
$$\rightarrow \underline{v(t)} = \underbrace{v(\infty)}_{\text{steady } v_{ss} \parallel V_s} + \underbrace{[v(0) - v(\infty)]e^{-t/\tau}}_{\text{transient } v_t \parallel \underbrace{V_0}_{\text{initial}} \parallel V_s} \quad \tau = RC$$



$$V_c(t) \longrightarrow \underline{\dot{i}_c(t)} = C \cdot \frac{dV_c(t)}{dt}$$

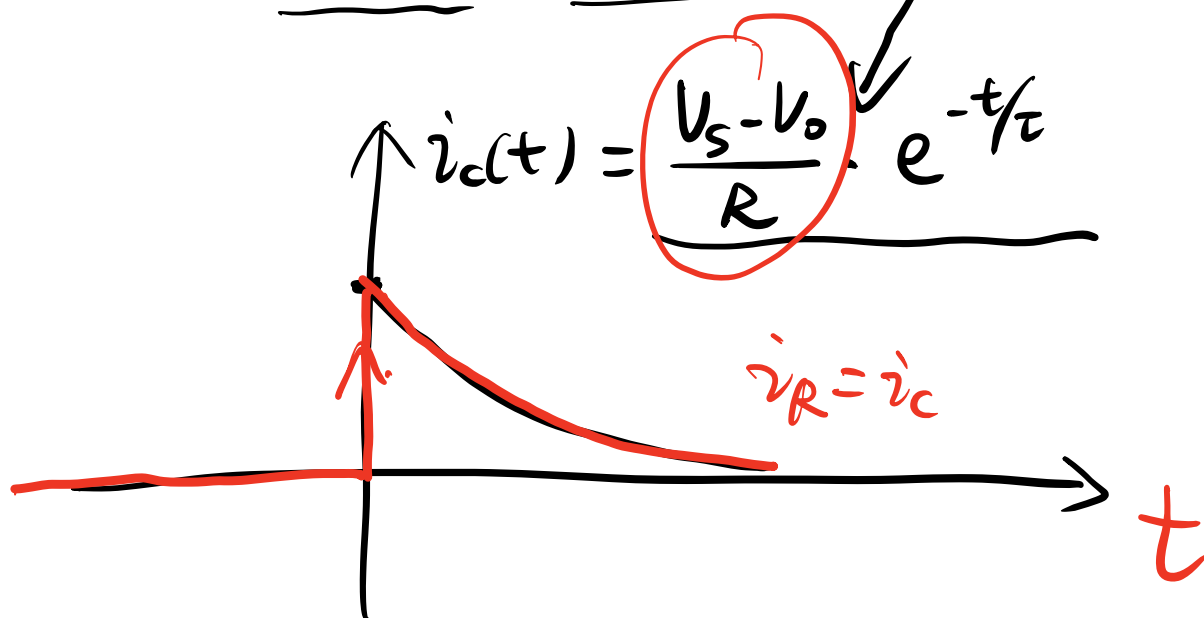
$$\underline{\dot{V}_R(t)} = \underline{\dot{i}_c(t)}$$




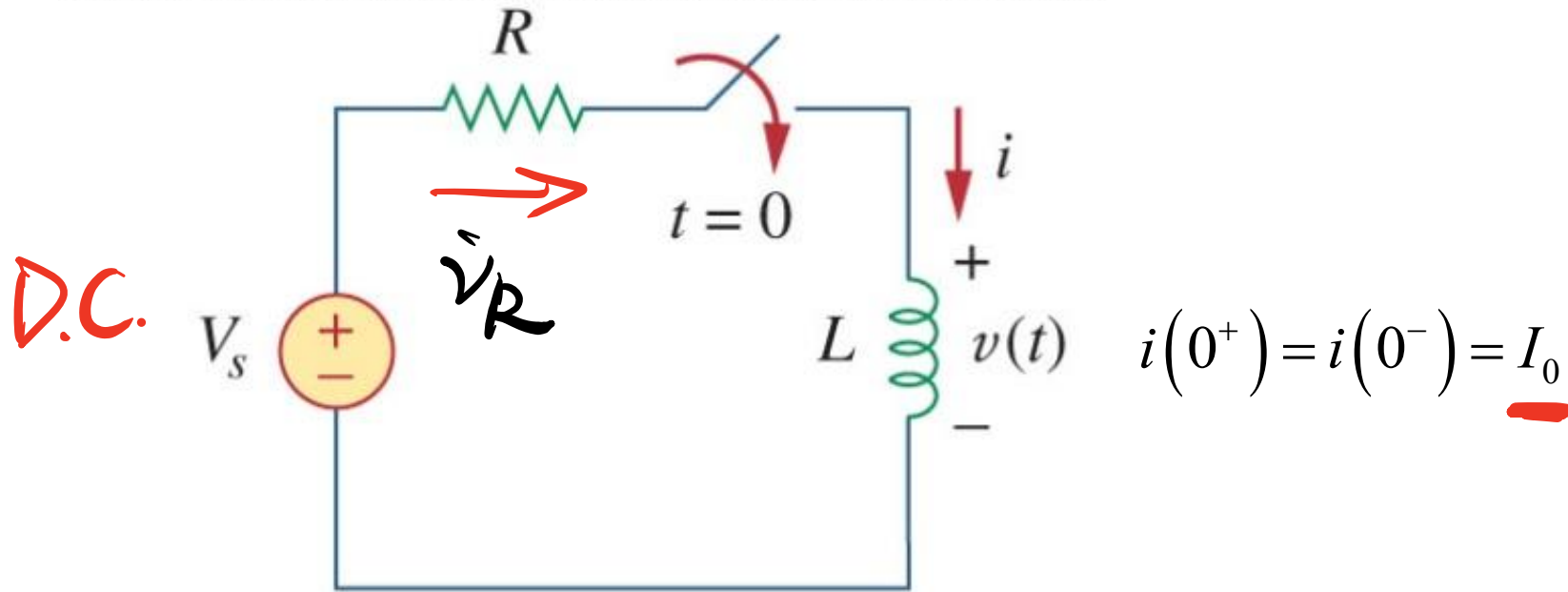
# Step Response of the RL Circuit


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$t \rightarrow \infty \quad i_L(t) = \begin{cases} 0 \\ I_0 \\ ?? \end{cases} = \frac{V_s}{R}$$



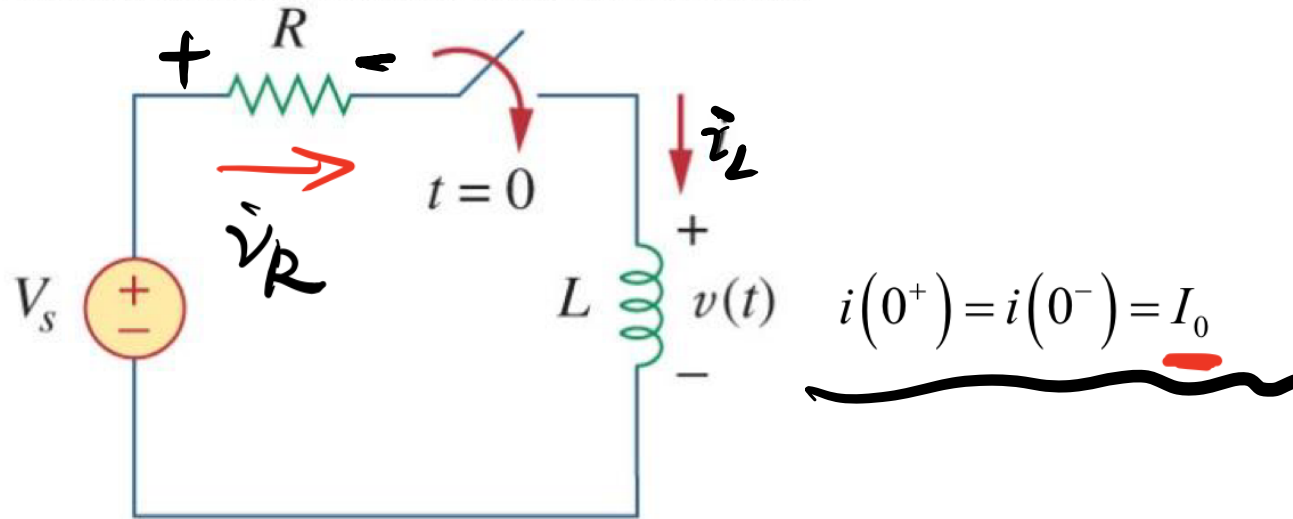Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$L \frac{d\dot{i}_L}{dt} = V_L = V_s - V_R = V_s - \dot{i}_L R$$

$$\frac{d\dot{i}_L}{dt} + \frac{R}{L} \cdot \dot{i}_L = \frac{V_s}{L} \quad (1)$$


$$\text{G.S.} \quad \underline{\frac{di_L}{dt} + \frac{R}{L} \cdot i_L = 0} \quad \therefore i_L' = A \cdot e^{-\frac{R}{L} \cdot t}$$

$$\text{P.S.} \quad \underline{i_L'' = \frac{V_s}{R}}$$

$$\underline{i_L(t) = A \cdot e^{-\frac{R}{L} \cdot t} + \frac{V_s}{R}} \quad (2)$$

$$i_L(t=0) = I_0 = A + \frac{V_s}{R} \Rightarrow A = I_0 - \frac{V_s}{R}$$
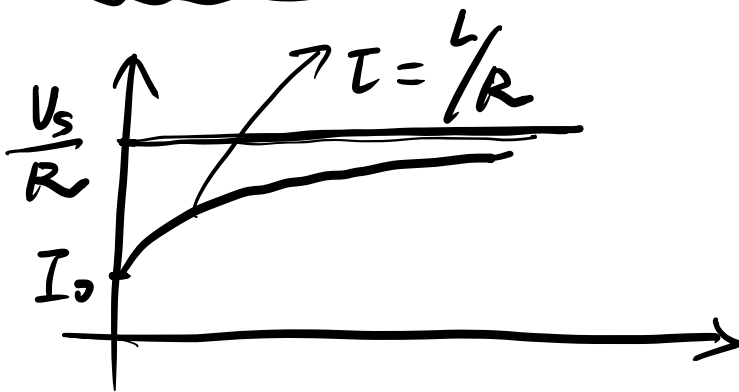
$$i_L(t) = \frac{V_s}{R} + \left( I_0 - \frac{V_s}{R} \right) e^{-\frac{R}{L} \cdot t}, \quad t > 0$$



$$\begin{aligned} i_L(t) &= \underline{i_n} + \underline{i_f} \\ &= \underset{\uparrow}{I_0} \cdot e^{-t/\tau} + \underline{\frac{V_s}{R} (1 - e^{-t/\tau})} \end{aligned}$$



$$i_L(t) = \underbrace{\frac{\downarrow V_s}{R}}_{\text{S.S.}} + \underbrace{\left( I_0 - \frac{V_s}{R} \right) e^{-\frac{R}{L} \cdot t}}_{\text{transient}}, t > 0$$

$$= \underline{I(\infty)} + \underline{[I(0) - I(\infty)]} e^{-t/\tau}, t > 0$$

$$\underline{\tau = L/R}$$

# Step Response of the RL Circuit



- We will use the transient and steady state response approach.
- We know that the transient response will be an exponential:

$$i_t = Ae^{-t/\tau}$$

- After a sufficiently long time, the current will reach the steady state:

$$i_{ss} = \frac{V_s}{R}$$

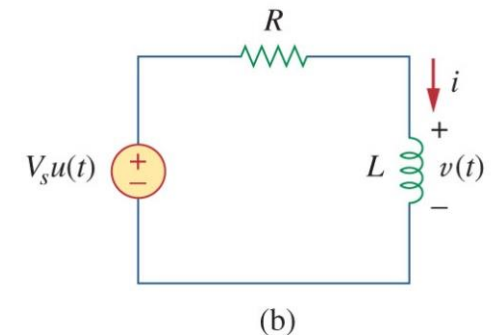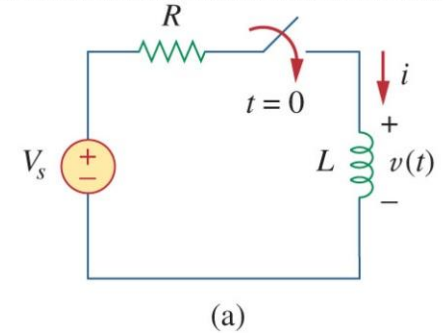
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display


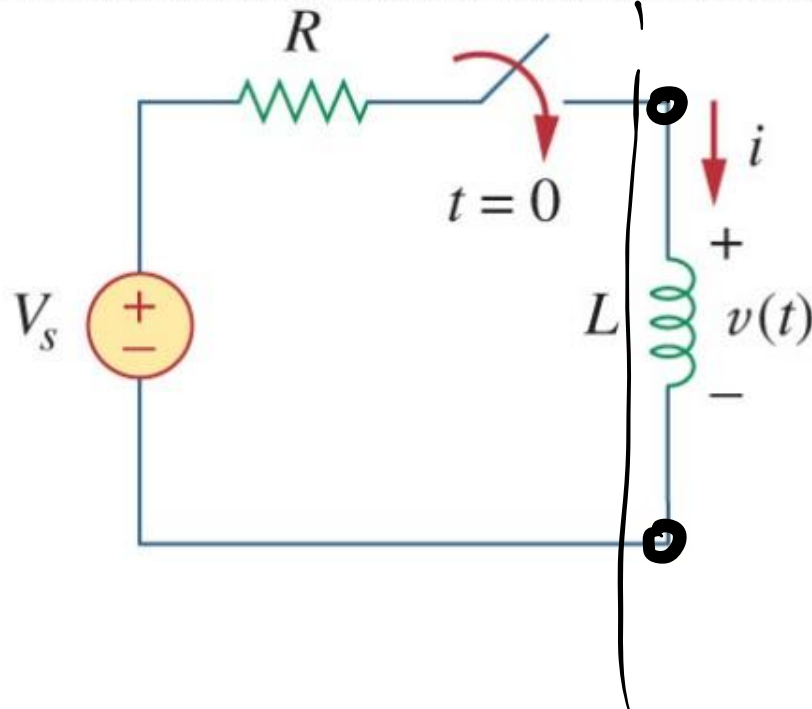
# Step Response of RL Circuit

- This yields an overall response of:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$i = Ae^{-t/\tau} + \frac{V_s}{R}$$

$$i(0^+) = i(0^-) = I_0 \quad A = I_0 - \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} + \left( I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$



# General Procedure of Finding RC/RL Response with D.C. sources

## 1. Identify the variable of interest

- For RL circuits, it is usually the inductor current  $\underline{i_L(t)}$ .
- For RC circuits, it is usually the capacitor voltage  $\underline{v_c(t)}$ .

## 2. Determine the initial value of the variable at $\underline{T_0}$

- Recall that  $i_L(t)$  and  $v_c(t)$  are continuous variables:

$$\rightarrow i_L(T_0^+) = i_L(T_0^-) \text{ and } v_c(T_0^+) = v_c(T_0^-) \leftarrow$$

## 3. Determine the final value of the variable (as $t \rightarrow \infty$ )



If needed, recall an inductor behaves like a short circuit in steady state ( $t \rightarrow \infty$ ) & that a capacitor behaves like an open circuit in steady state ( $t \rightarrow \infty$ ). <sup>eg.</sup> <sup>eg.</sup>

## 4. Calculate the time constant for the circuit

- $\tau = CR$  for an RC circuit where  $R$  is the Thévenin equivalent resistance “seen” by the capacitor.
- $\tau = L/R$  for an RL circuit, where  $R$  is the Thévenin equivalent resistance “seen” by the inductor.




# Response Form of Basic First-Order Circuits
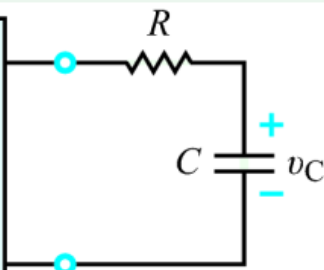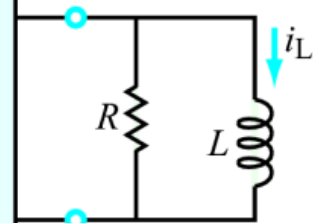
| Circuit | Diagram   | Response   |
|---------|---|--|
| RC      | <p><b>Input: dc circuit with switch action @ <math>t = T_0</math></b></p>   | <p><math>v_C(t) = \left\{ v_C(\infty) + [v_C(T_0) - v_C(\infty)] e^{-\frac{(t-T_0)}{\tau}} \right\}</math></p> <p><math>(\tau = RC)</math></p> <p><i>Handwritten notes: "time shift" with arrows pointing to <math>(t-T_0)</math> and <math>T_0</math>. Numbered arrows 1, 2, 3 point to <math>v_C(\infty)</math>, <math>v_C(T_0)</math>, and <math>v_C(\infty)</math> respectively.</i></p> |
| RL      | <p><b>Input: dc circuit with switch action @ <math>t = T_0</math></b></p>  | <p><math>i_L(t) = \left\{ i_L(\infty) + [i_L(T_0) - i_L(\infty)] e^{-\frac{(t-T_0)}{\tau}} \right\}</math></p> <p><math>(\tau = L/R)</math></p> <p><i>Handwritten note: "time shift" with an arrow pointing to <math>(t-T_0)</math>.</i></p>   |
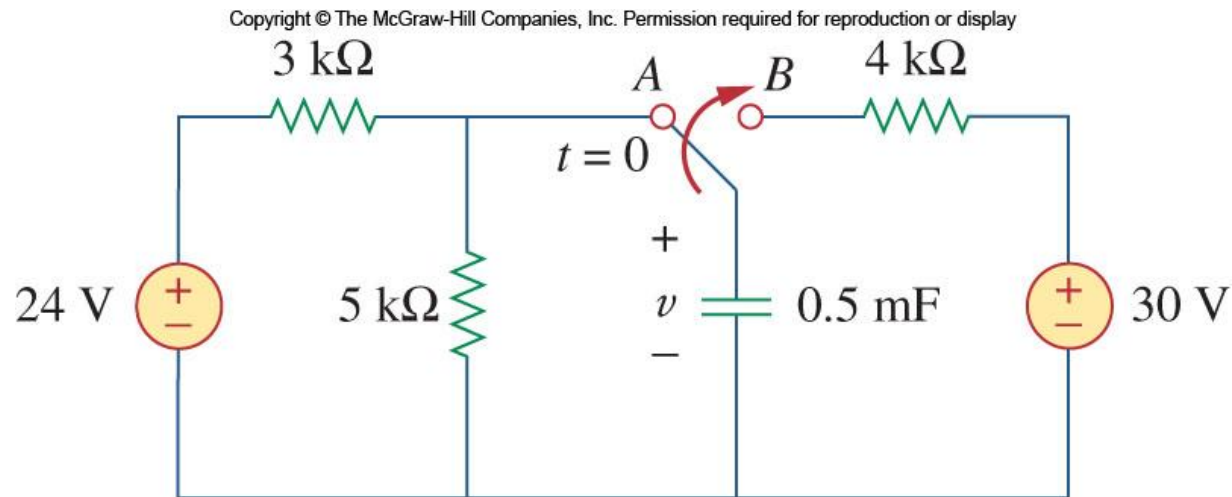
## Example

- The switch has been in position A for a long time. At  $t = 0$ , the switch moves to B. Find  $v(t)$ .



## Example

- Find  $i(t)$  in the circuit for  $t > 0$ . Assume that the switch has been closed for a long time.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

