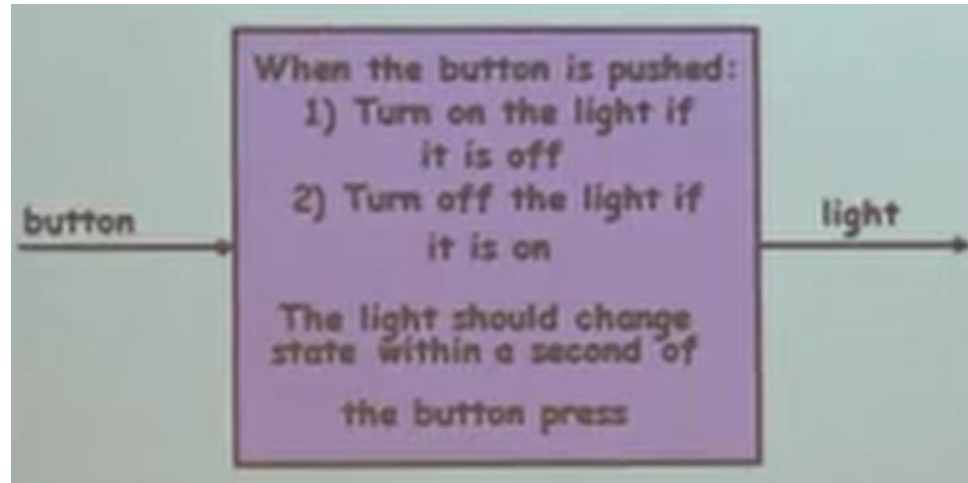


# Something We Cannot Build




Think about it:


- Can we built the circuit using the combinational logic?
- If not, what is missing here?
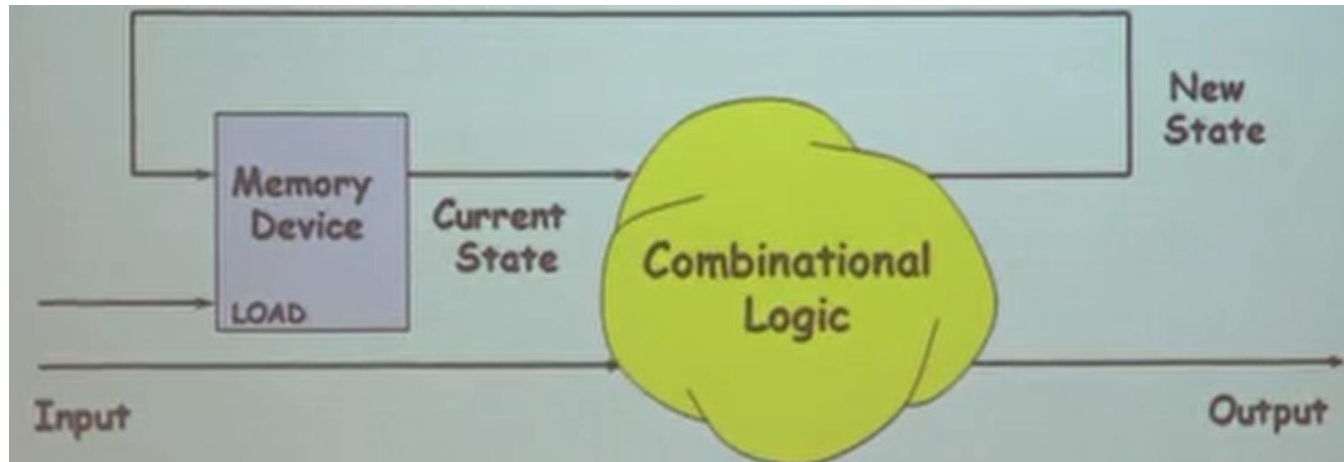
# Something We Cannot Build


- One needs the storage unit
- The output is triggered by an event instead of a value.



# Use feedback to store a bit

 


Add control terminals

 

Question: if we want to maintain the state, what voltage should be applied to  $v_{I1}$  and  $v_{I2}$ ?

# S-R (SET-RESET) Latch

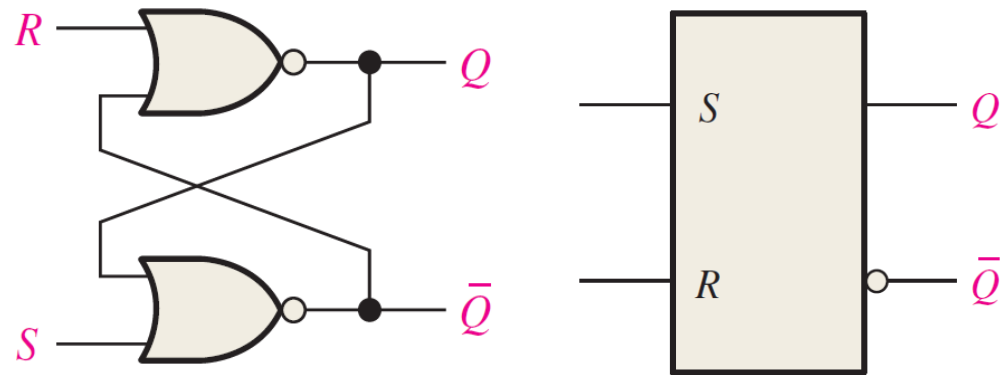


- The output of each gate is connected to an input of the opposite gate to provide a feedback.
- Even the input is removed, the output state is still maintained.
- This is the active high input SR latch

$S_D$	$R_D$	$Q$	$Q^*$
0	0	0	0
0	0	1	1
1	0	0	1
1	0	1	1
0	1	0	0
0	1	1	0
1	1	0	0 <sup>Ⓢ</sup>
1	1	1	0 <sup>Ⓢ</sup>

① The state is undetermined when  $S$  and  $R$  are removed simultaneously




# S-R (SET-RESET) Latch

Active low input SR latch

 


$S'_D$	$R'_D$	$Q$	$Q^*$
1	1	0	0
1	1	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
0	0	0	1 <sup>(1)</sup>
0	0	1	1 <sup>(1)</sup>

# S-R (SET-RESET) Latch

   


Question: plot the waveform of  $Q$  and  $Q'$
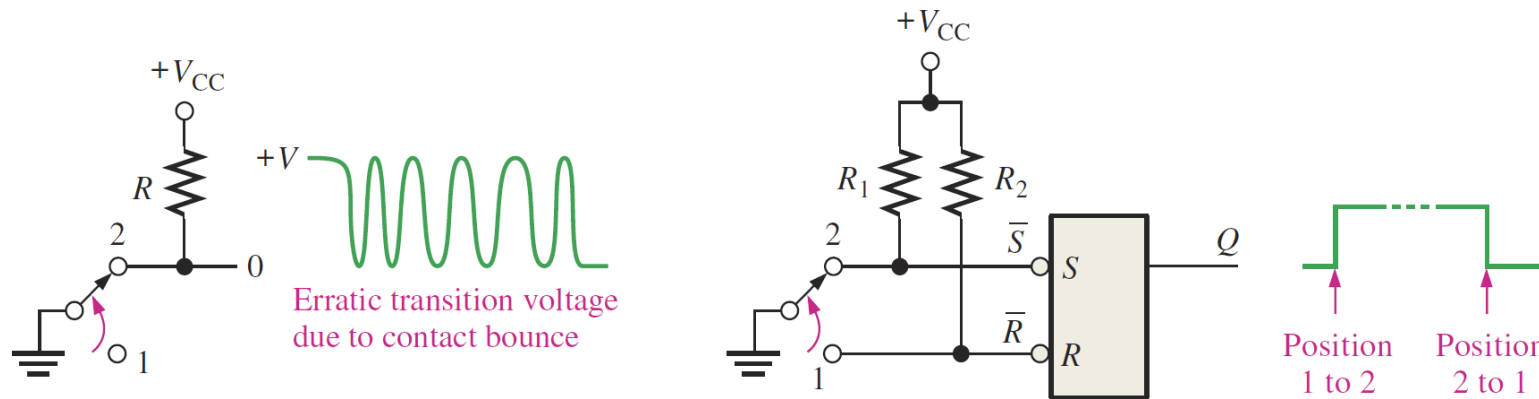
# S-R Latch as a Contact-Bounce Eliminator



- The closure of a mechanical switch is accompanied by the contact bounce
- An S-R latch can be used to eliminate the effects of switch bounce.
- The 1 to 2 transition sets the latch. Any further voltage spikes on the S input do not affect the latch.
- Similarly, a clean transition from HIGH to LOW is made for a 2 to 1 transition .

# The gated S-R Latch


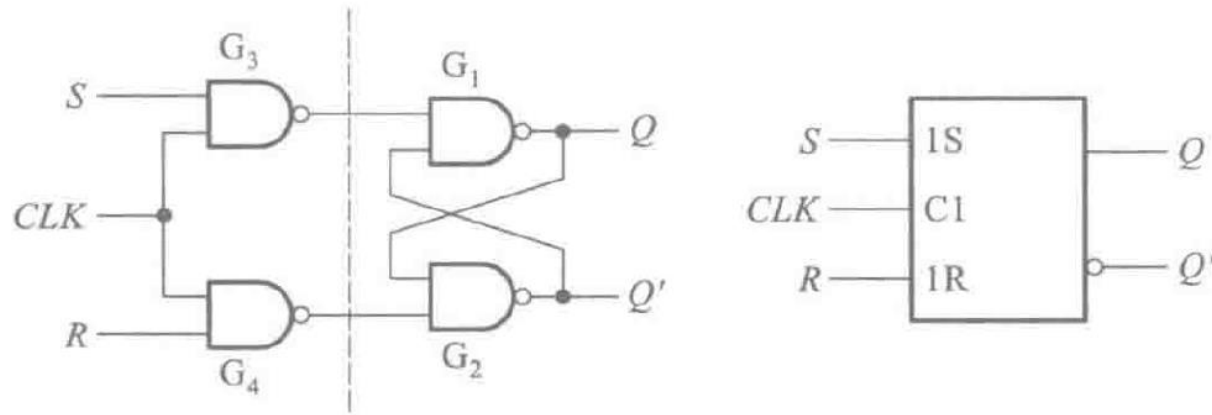


- $C1$  denotes that  $CLK$  is a control signal with the numbering 1
- $1S$  and  $1R$  denotes that  $S$  and  $R$  are controlled by  $C1$
- The gated latch is a level-sensitive device

$CLK$	$S$	$R$	$Q$	$Q'$
0	×	×	0	0
0	×	×	1	1
1	0	0	0	0
1	0	0	1	1
1	1	0	0	1
1	1	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	1	0	$1^{(1)}$
1	1	1	1	$1^{(1)}$




# The gated S-R Latch

  


Question: plot the waveform of  $Q$  and  $Q'$ ,  
assume the initial  $Q$  is 0

# The asynchronous gated S-R Latch

 

- When  $S'_D$  and  $R'_D$  are not used for asynchronous set and reset, one should set them to 1
- When they are used,  $CLK$  should be set to 0



# The gated D Latch

 

$CLK$	$D$	$Q$	$Q'$
0	$\times$	0	0
0	$\times$	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


- Compared to the S-R latch, it lost the keep function

# The gated D Latch

  


Question: plot the waveform of  $Q$  and  $Q'$ ,  
assume the initial  $Q$  is 0

# The gated D Latch

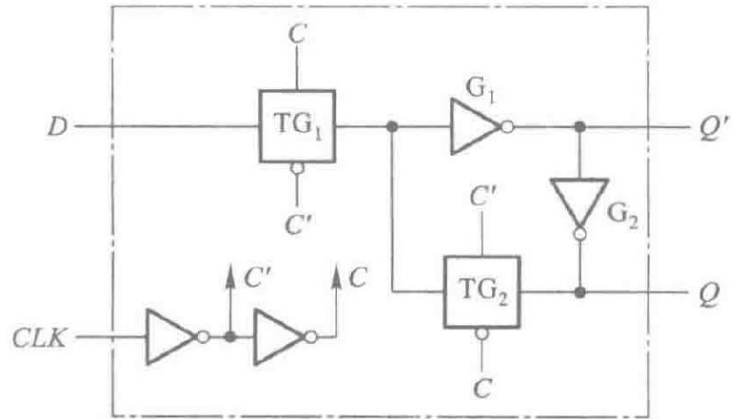

D latch using transmission gate

 

D latch using MUX