

My signature below indicates that I understand and have complied with the Academic Integrity Policy of ShanghaiTech University. I have neither received nor given any unauthorized aid.

Print Name: 朱子恒 Signature: [Signature]

1. Short questions. (28 points. 2 points each.)

1) Convert  $(17.25)_{10}$  to binary.

$$\begin{array}{r} 2 \overline{) 17} \\ \underline{2 \times 8} \\ 2 \overline{) 9} \\ \underline{2 \times 4} \\ 2 \overline{) 5} \\ \underline{2 \times 2} \\ 2 \overline{) 1} \\ \underline{2 \times 0} \\ 0 \end{array} \quad \begin{array}{l} 1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 1 \end{array}$$

$$\begin{array}{r} 0.25 \\ \times 2 \\ \hline 0.5 \\ \hline \end{array} \quad \begin{array}{r} 0.5 \\ \times 2 \\ \hline 1.0 \\ \hline \end{array}$$

$$(17.25)_{10} = (10001.01)_2$$

2) Convert  $(101.11)_2$  to decimal.

$$\begin{aligned} (101.11)_2 &= 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-2} \\ &= (5.75)_{10} \end{aligned}$$

3) Convert  $(2E.A)_{16}$  to octal.

$$\begin{array}{ccc} 2 & E & A \\ \hline 0010 & 1110 & 1010 \\ \downarrow & \downarrow & \downarrow \\ 5 & 6 & 5 \end{array}$$

$$(2E.A)_{16} = (56.5)_8$$

4) Convert  $(000110010010)_{BCD}$  to decimal.

$$\begin{array}{ccc} 0001 & 1001 & 0010 \\ \hline \downarrow & \downarrow & \downarrow \\ 1 & 9 & 2 \end{array}$$

$$(000110010010)_{BCD} = (192)_{10}$$

5) Determine the even parity bit for 11010.

Three 1's  $\Rightarrow$  Even parity bit is '1'.

6) (True or False) The XOR gate is also called the equivalence gate.

False

7) (True or False) The POS form of a logic function is written with minterms.

False

8) (True or False) If the value of a logic variable is 0, it appears in the complemented form in a maxterm.

False

9) What does "VHDL" stand for?

VHSIC (Very High Speed Integrated Circuits)  
Hardware Description Language

10) What does "FPGA" stand for?

Field Programmable Gate Array

11) (True or False) The VHDL code is case sensitive.

False

12) (True or False) A signal has three possible values: 0, 1, and Z. It is fine to use BIT as the type of this signal.

False

13) Given the following VHDL code, determine the value of A(6 downto 3).

signal A: std\_logic\_vector (7 downto 0);

A <= "11001010";

A(6 downto 3) = 1001

14) Given the following VHDL code, write the logic function for F.

F <= A and B or C and D;

F = (A B + C) D

2. Derive the standard SOP and POS expressions for the following function. Write the results in two forms: (a) explicit expressions with minterms/maxterms (e.g.,  $Y=ABC$ ) and (b) compact expressions with indexes of minterms/maxterms (e.g.,  $Y=\sum m(7)$  for  $Y=ABC$ ). (12 points. 3 points each.)

$$Y(A, B, C) = (A + \bar{C})(\bar{A} + B)$$

$$Y = (A + \bar{C})(\bar{A} + B)$$

$$= (A + \bar{C} + B\bar{B})(\bar{A} + B + C\bar{C})$$

pos explicit

$$= (A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + B + C)(\bar{A} + B + \bar{C})$$

$$= M_1 M_3 M_4 M_5$$

pos compact

$$= \prod M(1, 3, 4, 5)$$

sop compact

$$= \sum m(0, 2, 6, 7)$$

$$= m_0 + m_2 + m_6 + m_7$$


sop explicit

$$= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + AB\bar{C} + ABC$$

3. Develop the minimum SOP and POS expressions for the following function using Karnaugh map. (20 points. 10 points each.)

$$Y(A, B, C, D) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$

> SOP

 

Red:  $A\bar{B}$

Green:  $\bar{A}B$

Blue:  $CD$

Yellow:  $B\bar{C}\bar{D}$  or  $A\bar{C}\bar{D}$  } PIs


} EPIs

$$Y = A\bar{B} + \bar{A}B + CD + B\bar{C}\bar{D}$$

or

$$Y = A\bar{B} + \bar{A}B + CD + A\bar{C}\bar{D}$$

> POS

 

Red:  $A+B$

Green:  $C+\bar{D}$

Blue:  $\bar{A}+\bar{B}+\bar{C}+D$

} EPIs

$$Y = (A+B)(C+\bar{D})(\bar{A}+\bar{B}+\bar{C}+D)$$

4. Convert the following AND-OR expression to NAND, AND-OR-Invert (AOI), and NOR expressions. (12 points. 4 points each.)

$$Y(A, B, C) = AB + BC + AC$$

> NAND

$$Y = AB + BC + AC = \overline{\overline{AB + BC + AC}} = \overline{\overline{AB} \cdot \overline{BC} \cdot \overline{AC}}$$

> AOI

|   |    |    |    |    |
|---|----|----|----|----|
|   | BC |    |    |    |
|   | 00 | 01 | 11 | 10 |
| A | 0  | 0  | 1  | 0  |
|   | 0  | 1  | 1  | 1  |

Red:  $\overline{A}\overline{B}$

Green:  $\overline{B}\overline{C}$

Blue:  $\overline{A}\overline{C}$

$$Y = \overline{\overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}\overline{C}}$$

> NOR

$$Y = \overline{\overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}\overline{C}}$$

$$= \overline{\overline{A+B} + \overline{B+C} + \overline{A+C}}$$

5. Design a 1-bit half-adder using AND, OR, and NOT gates. The inputs are A and B. The outputs are S and C: S is the sum and C is the carry out. You need to (a) build the truth table, (b) write the logic expressions for S and C, and (c) draw the circuit diagram. (12 points. 4 points each.)


> Truth table

| A | B | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

$$S = \bar{A}B + A\bar{B}$$

$$C = AB$$

> Circuit diagram

 

6. Plot the output ( $Y_0$  through  $Y_7$ ) waveforms given the following inputs to the 3-8 decoder (also a DEMUX) 74LS138. The enable inputs  $G_{2A}$  and  $G_{2B}$  are set as LOW all the time. (16 points. 2 points each.)

