

ShanghaiTech University

EE 115B: Digital Circuits


Fall 2022

Lecture 9

Hengzhao Yang
October 25, 2022

Digital Fundamentals


ELEVENTH EDITION

 

CHAPTER 5

Combinational Logic Analysis

AND-OR logic for SOP expressions

 

(a) Logic diagram (ANSI standard distinctive shape symbols)

FIGURE 5-1 An example of AND-OR logic.

AND-OR-Invert (AOI) logic for POS expressions

 


FIGURE 5-3 An AND-OR-Invert circuit produces a POS output.

$$X = (\overline{A} + \overline{B})(\overline{C} + \overline{D}) = (\overline{AB})(\overline{CD}) = \overline{\overline{\overline{AB}}(\overline{CD})} = \overline{\overline{AB} + \overline{CD}} = \overline{AB} + \overline{CD}$$

Implementing combinational logic: From a Boolean expression

 


FIGURE 5-9 Logic circuit for $X = AB + CDE$.

Implementing combinational logic: From a truth table

TABLE 5-3

Inputs			Output	Product Term
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\overline{A}BC$
1	0	0	1	$A\overline{B}\overline{C}$
1	0	1	0	
1	1	0	0	
1	1	1	0	


 



FIGURE 5-11 Logic circuit for $X = \bar{A}BC + A\bar{B}\bar{C}$.

NAND-only and NOR-only circuits

 - CMOS implementations
 - 2-input AND/OR gate (6 transistors)
 - 2-input NAND/NOR gate (4 transistors)
 - NOT gate (2 transistors)




NAND

 


NOT

NAND-only and NOR-only circuits

- NAND and NOR gates (two symbols)

 

 
$$(a) \overline{x_1 x_2} = \bar{x}_1 + \bar{x}_2$$



$$(b) \overline{x_1 + x_2} = \bar{x}_1 \bar{x}_2$$

FIGURE 5-18 Universal application of NAND gates.

 

(a) One NAND gate used as an inverter



(b) Two NAND gates used as an AND gate

FIGURE 5-18 Universal application of NAND gates.



 
 
 


FIGURE 5-19 Universal application of NOR gates.

 


(a) One NOR gate used as an inverter

 


(b) Two NOR gates used as an OR gate



FIGURE 5-19 Universal application of NOR gates.

 

(c) Three NOR gates used as an AND gate

 

(d) Four NOR gates used as a NAND gate

NAND-only logic

【例 2.9.1】 试用 2 输入端与非门产生如下的逻辑函数

$$Y = AC + BC' \quad (2.9.4)$$

解： 为了全部用 2 输入端与非门实现这个电路,就必须将式(2.9.4)变换成全部由两变量与非运算组成的形式。为此,利用摩根定理将式(2.9.4)变换为

$$\begin{aligned} Y &= AC + BC' \\ &= ((AC + BC')')' \\ &= ((AC)'(BC')')' \end{aligned} \quad (2.9.5)$$

根据上式就得到了图 2.9.4 的电路。

 


图 2.9.4 按照式(2.9.5)接成的逻辑电路

输入端C'应为:C级联NAND

NOR-only logic

【例 2.9.2】 试用 2 输入端或非门产生式 (2.9.4) 给出的逻辑函数。

解： 为了全部用 2 输入端或非门实现这个电路,则需要将式 (2.9.4) 变换成全部由两变量或非运算组成的形式。为此,用摩根定理将式 (2.9.4) 变换为

$$\begin{aligned} Y &= AC + BC' \\ &= ((AC)'(BC')')' \\ &= ((A' + C')(B' + C))' \\ &= (B'C' + A'C)' \\ &= ((B + C)' + (A + C')')' \end{aligned} \quad (2.9.6)$$

按照式 (2.9.6) 接成的逻辑电路如图 2.9.5 所示。


 


图 2.9.5 按照式 (2.9.6) 接成的逻辑电路

Boolean relationship for steps 3 and 4: $AB + A'C + BC = AB + A'C$


Convert AND to NAND

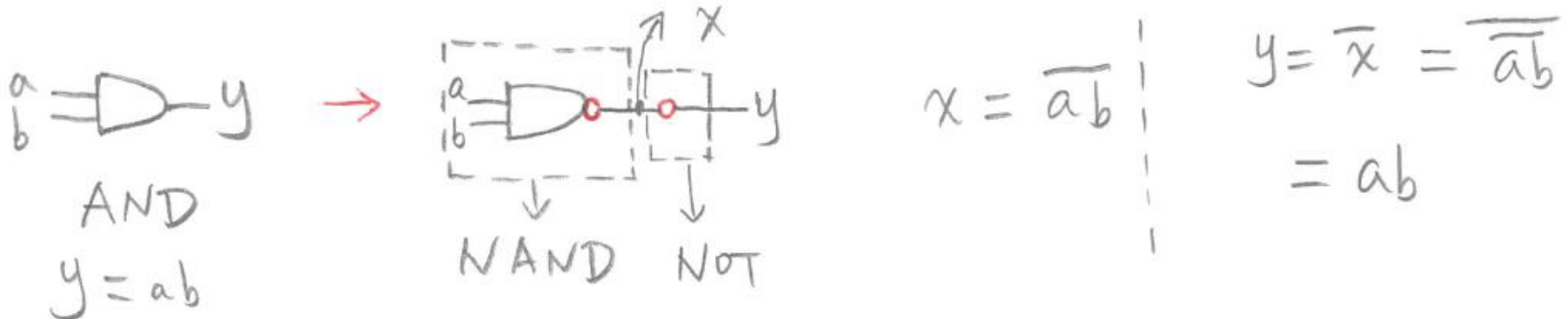- General rules
 - Logic function (circuit functionality) should NOT be changed after conversions
 - A bubble means an inverter (NOT)
 - Add bubbles in pairs
- Convert AND to NAND




Convert OR/NOT to NAND

- Convert OR to NAND

 

$$\begin{array}{l|l} x_1 = \bar{a} & y = \overline{x_1 x_2} = \overline{\bar{a} \bar{b}} \\ x_2 = \bar{b} & = a + b \end{array}$$


- Convert NOT to NAND

 

$$\begin{array}{l|l} x_1 = a & y = \overline{x_1 x_2} = \overline{a a} \\ x_2 = a & = \bar{a} \end{array}$$

Convert AND to NOR

 
- General rules
 - Logic function (circuit functionality) should NOT be changed after conversions
 - A bubble means an inverter (NOT)
 - Add bubbles in pairs
- Convert AND to NOR



$$\begin{aligned} x_1 &= \overline{a} & y &= \overline{x_1 + x_2} \\ x_2 &= \overline{b} & &= \overline{\overline{a} + \overline{b}} \\ & & &= ab \end{aligned}$$

Convert OR/NOT to NOR

- Convert OR to NOR

 


$$x = \overline{a + b} \quad \left| \quad y = \overline{x} \right.$$

$$= \overline{\overline{a + b}}$$

$$= a + b$$

- Convert NOT to NOR

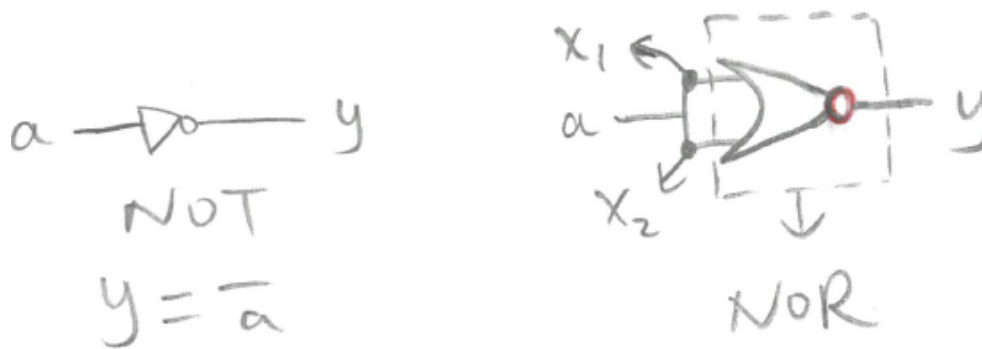

$$x_1 = a \quad \left| \quad y = \overline{x_1 + x_2} \right.$$

$$x_2 = a \quad \left| \quad = \overline{a + a} \right.$$


$$= \overline{a}$$

Convert circuits with AND/OR/NOT to NAND-only or NOR-only circuits

- Convert AND/OR to NAND (NOR if NOR-only) by adding bubbles
- If necessary, add bubbles to keep logic function unchanged
- Convert single bubbles to NAND/NOR

NAND-only


- Example

 

(a) Circuit with AND and OR gates

NAND-only


- Convert AND/OR to NAND, add bubbles

 

(b) Inversions needed to convert to NANDs

NAND-only


- Convert single bubbles to NAND

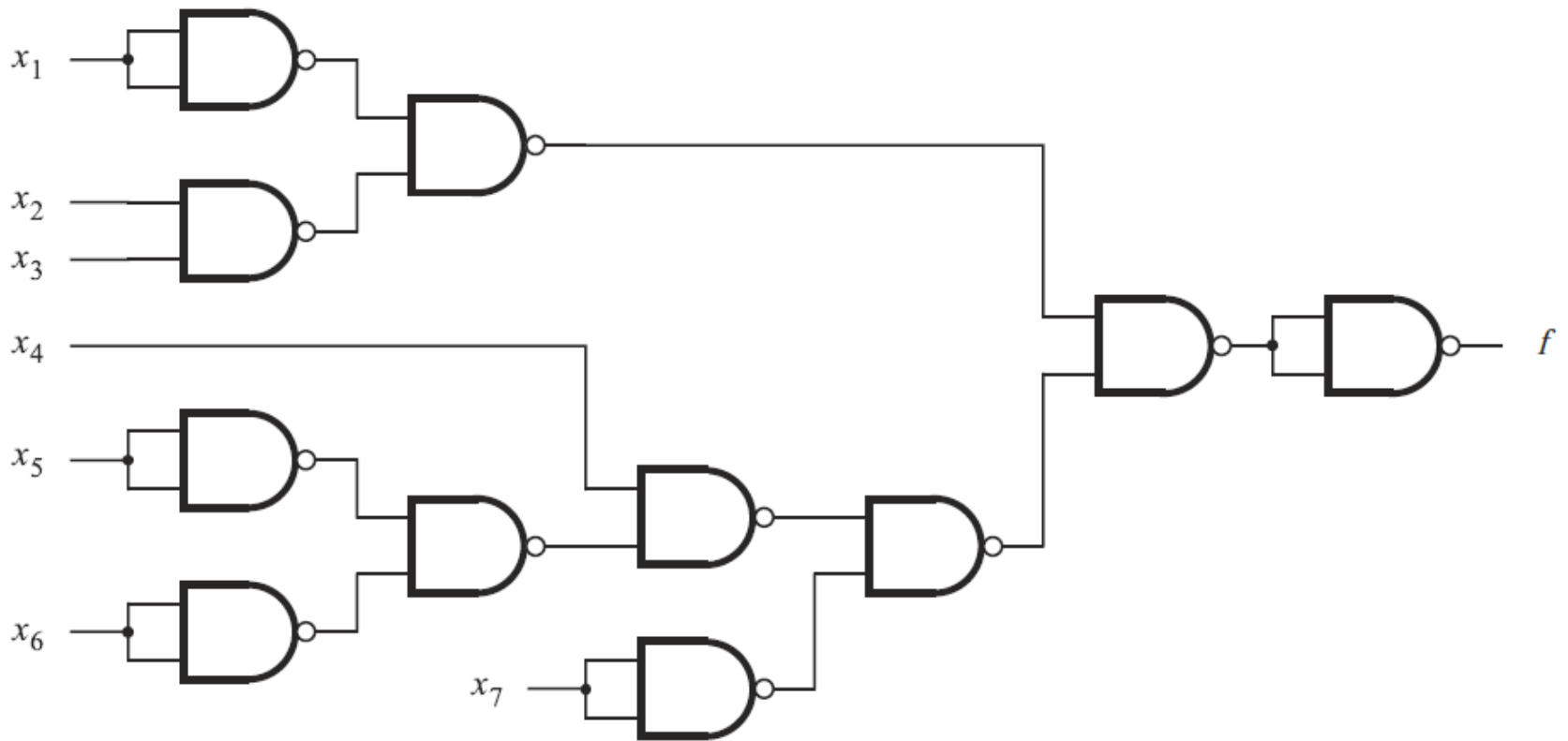

(c) NAND-gate circuit

NOR-only


- Example

 

(a) Circuit with AND and OR gates

NOR-only


- Convert AND/OR to NOR, add bubbles

 

(a) Inversions needed to convert to NORs

NOR-only

- Convert single bubbles to NOR

 

(b) NOR-gate circuit