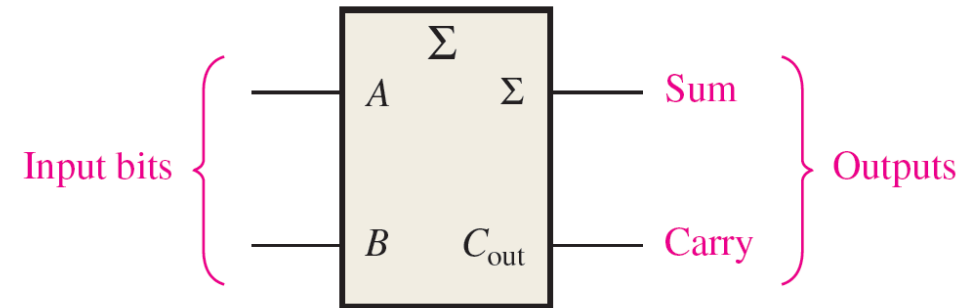


Half Adder

- The half-adder accepts two binary digits on its inputs and produces a sum bit and a carry bit.

A	B	C_{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0




- C_{out} is a 1 only when both A and B are 1s.

$$C_{out} = AB$$

- Σ is a 1 only if A and B are not equal.

$$\Sigma = A \oplus B$$

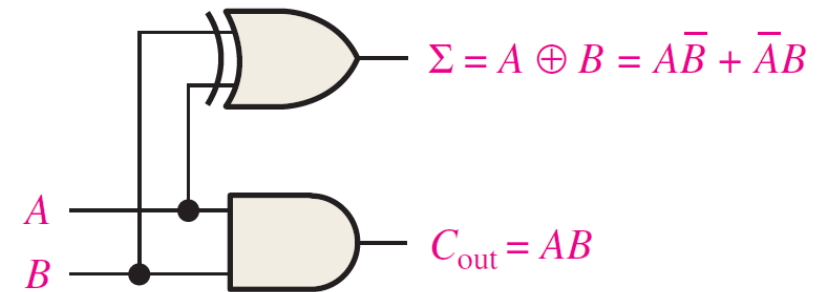

Full Adder

The full-adder (FA) accepts two bits and a carry and generates a sum and a carry.

A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$\begin{cases} S = (A'B'CI' + AB'CI + A'BCI + ABCI')' \\ CO = (A'B' + B'CI' + A'CI')' \end{cases}$$

$AB \backslash CI$	00	01	11	10
0	0	1	0	1
1	1	0	1	0

S



$AB \backslash CI$	00	01	11	10
0	0	0	1	0
1	0	1	1	1

CO

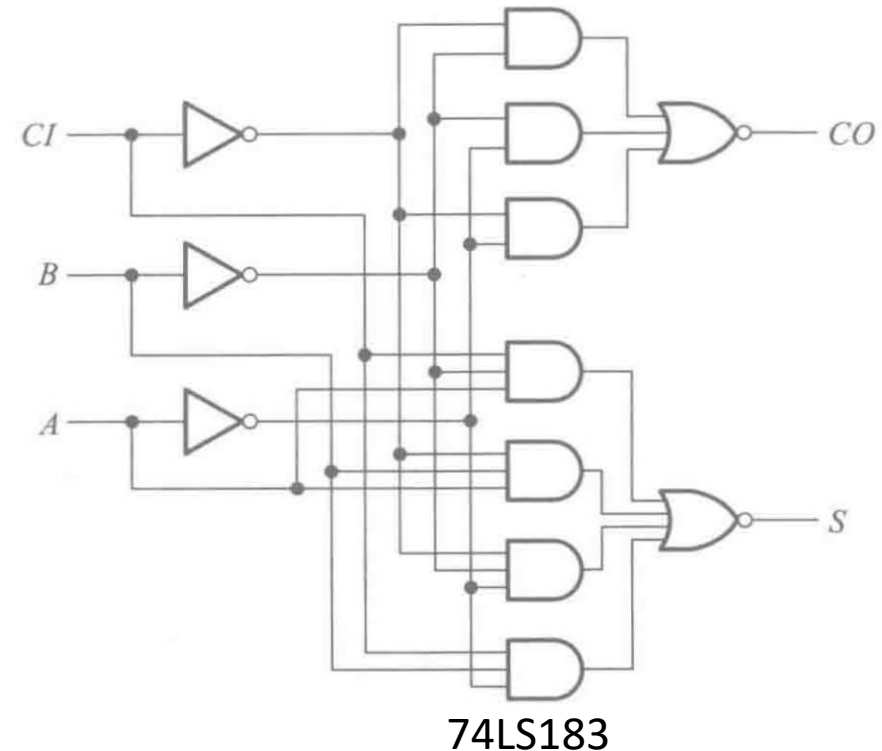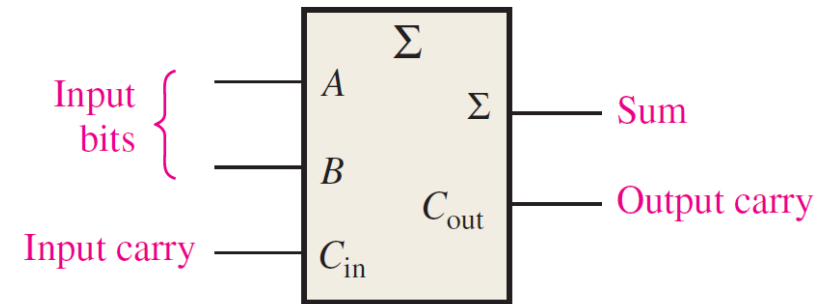


Ripple Carry Adder

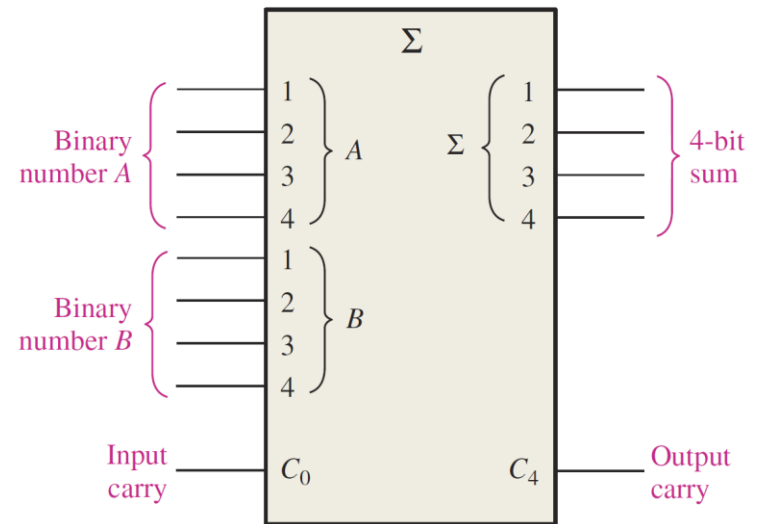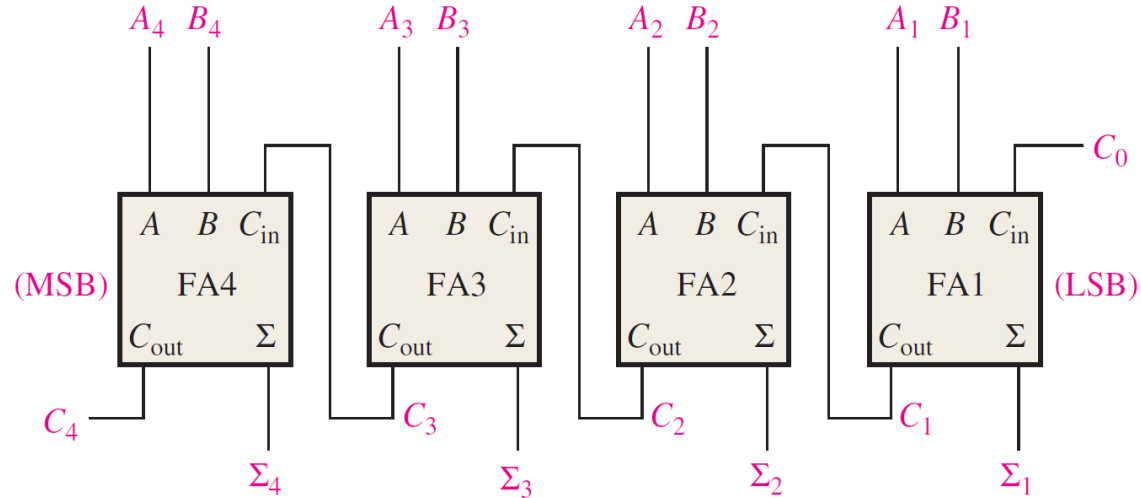- To add binary numbers with more than one bit, more full-adders are connected




Ripple Carry Adder

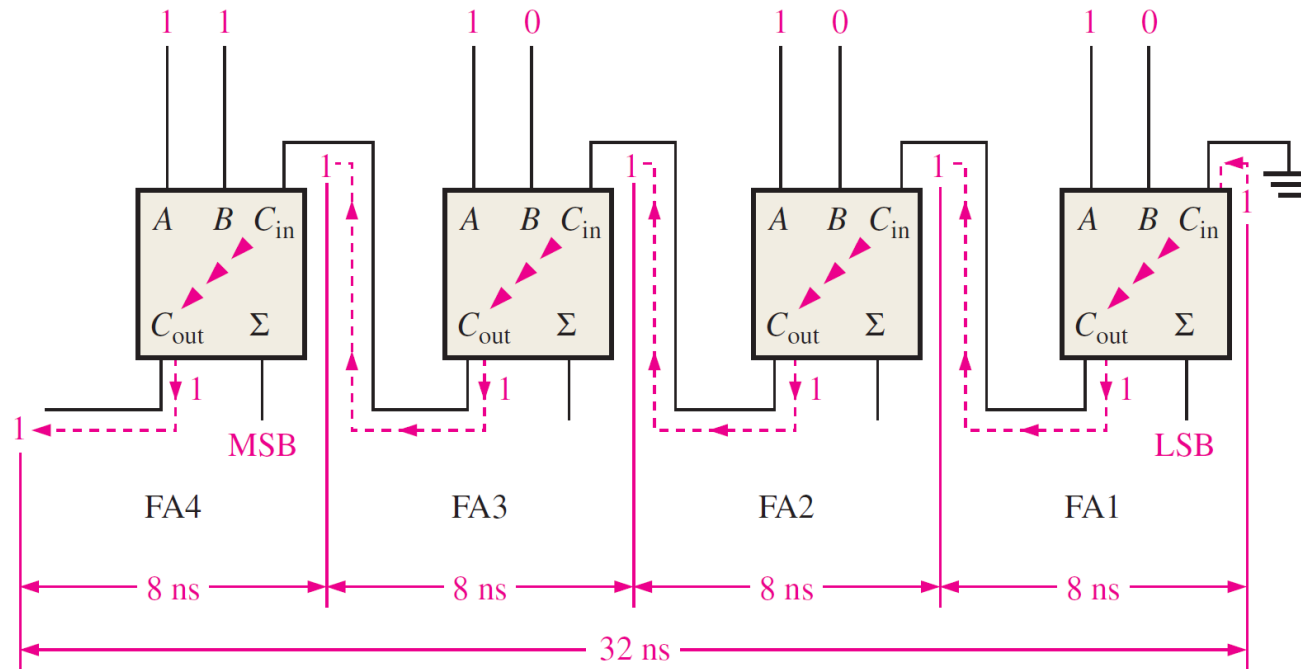- The sum and the output carry of any stage cannot be produced until the input carry occurs.



Full Adder – Another Look

A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

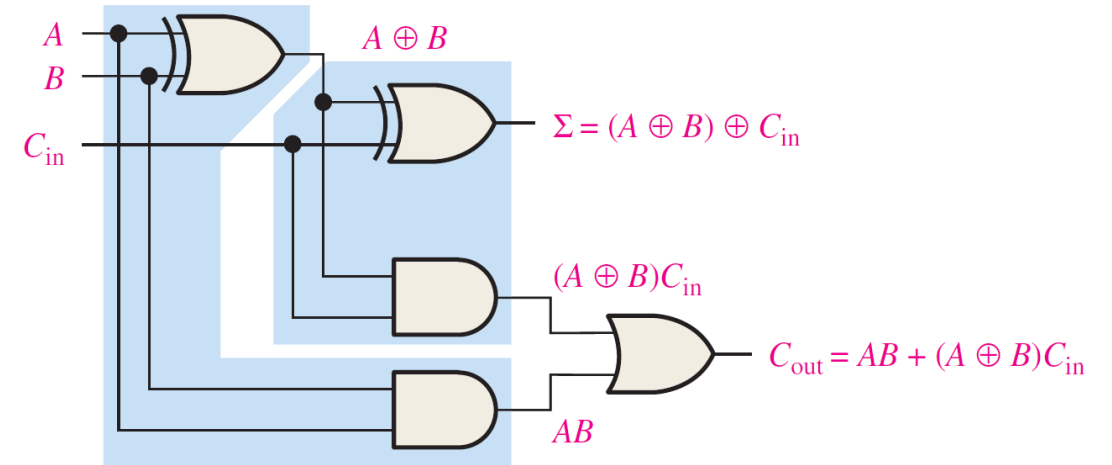

$$\Sigma = (A \oplus B) \oplus C_{in}$$


- A carry is generated only when both input bits are 1s.

$$C_g = AB$$

- A carry is propagated when either or both of the input bits are 1s.


$$C_p = A \oplus B \text{ or } C_p = A + B$$

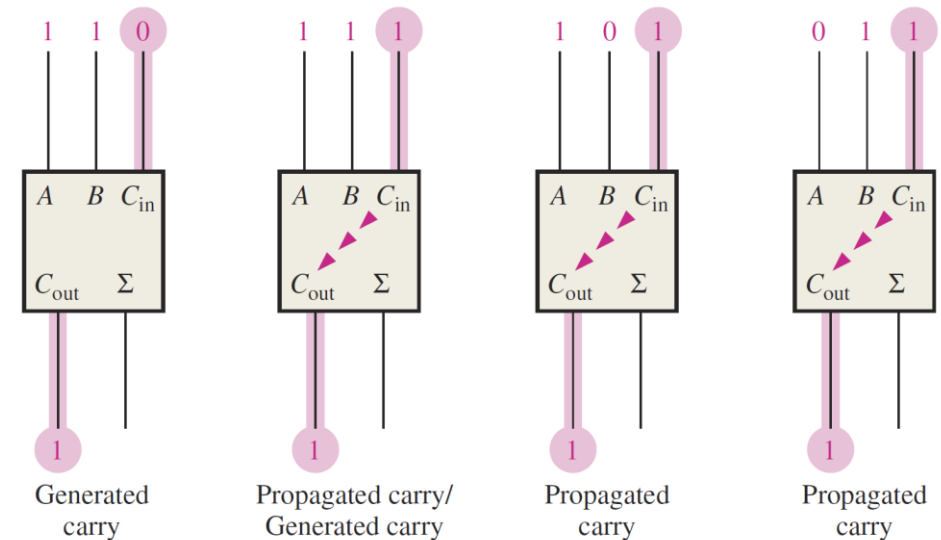➔ $C_{out} = C_g + C_p C_{in} = AB + (A \oplus B)C_{in} = AB + (A+B)C_{in}$



Look-Ahead Carry Adder

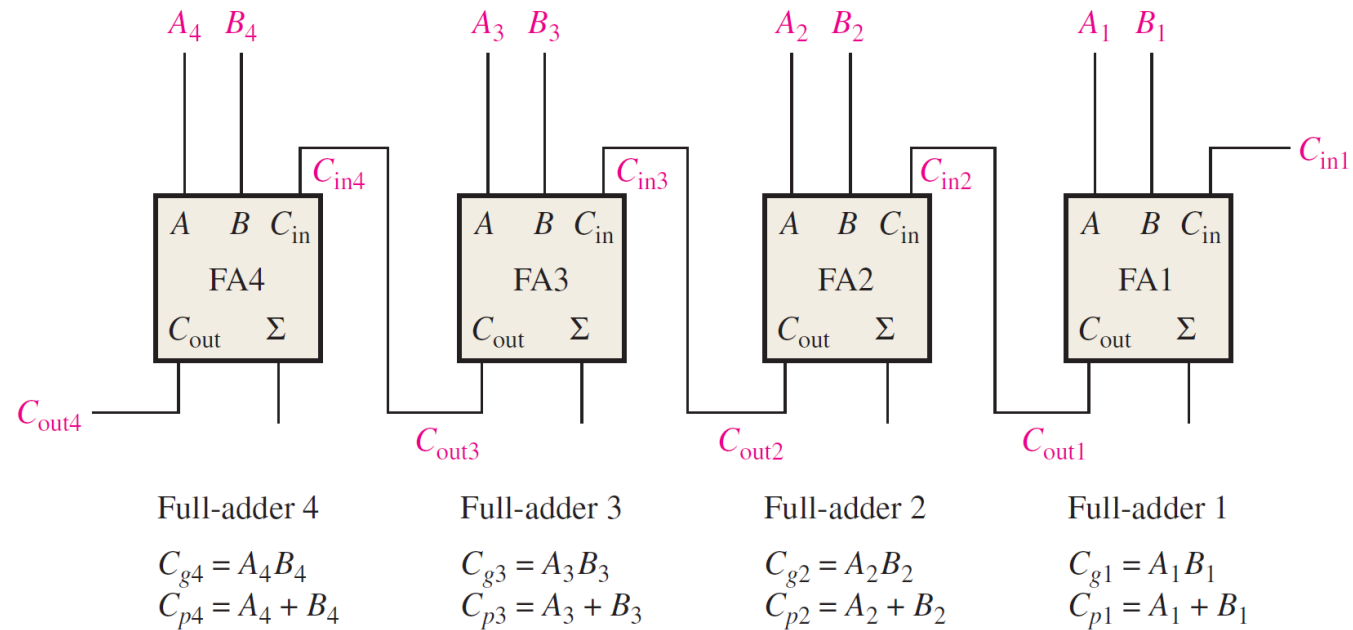- The look-ahead carry adder produces C_{out} by either carry generation or carry propagation, i.e., $C_{out} = C_g + C_p C_{in}$
- C_g and C_p for each stage are immediately available.



Look-Ahead Carry Adder

Full-adder 1:

$$C_{\text{out}1} = C_{g1} + C_{p1}C_{\text{in}1}$$

- Based on $C_{\text{out}} = C_g + C_p C_{\text{in}}$, we can build the look-ahead carry adder
- C_g and C_p for each stage are immediately available.
- It only takes $3t_{\text{pd}}$ to get the C_{out}

Full-adder 2:

$$C_{\text{in}2} = C_{\text{out}1}$$

$$\begin{aligned} C_{\text{out}2} &= C_{g2} + C_{p2}C_{\text{in}2} = C_{g2} + C_{p2}C_{\text{out}1} = C_{g2} + C_{p2}(C_{g1} + C_{p1}C_{\text{in}1}) \\ &= C_{g2} + C_{p2}C_{g1} + C_{p2}C_{p1}C_{\text{in}1} \end{aligned}$$

Full-adder 3:

$$C_{\text{in}3} = C_{\text{out}2}$$


$$\begin{aligned} C_{\text{out}3} &= C_{g3} + C_{p3}C_{\text{in}3} = C_{g3} + C_{p3}C_{\text{out}2} = C_{g3} + C_{p3}(C_{g2} + C_{p2}C_{g1} + C_{p2}C_{p1}C_{\text{in}1}) \\ &= C_{g3} + C_{p3}C_{g2} + C_{p3}C_{p2}C_{g1} + C_{p3}C_{p2}C_{p1}C_{\text{in}1} \end{aligned}$$

Full-adder 4:



$$C_{\text{in}4} = C_{\text{out}3}$$

$$\begin{aligned} C_{\text{out}4} &= C_{g4} + C_{p4}C_{\text{in}4} = C_{g4} + C_{p4}C_{\text{out}3} \\ &= C_{g4} + C_{p4}(C_{g3} + C_{p3}C_{g2} + C_{p3}C_{p2}C_{g1} + C_{p3}C_{p2}C_{p1}C_{\text{in}1}) \\ &= C_{g4} + C_{p4}C_{g3} + C_{p4}C_{p3}C_{g2} + C_{p4}C_{p3}C_{p2}C_{g1} + C_{p4}C_{p3}C_{p2}C_{p1}C_{\text{in}1} \end{aligned}$$

Look-Ahead Carry Adder

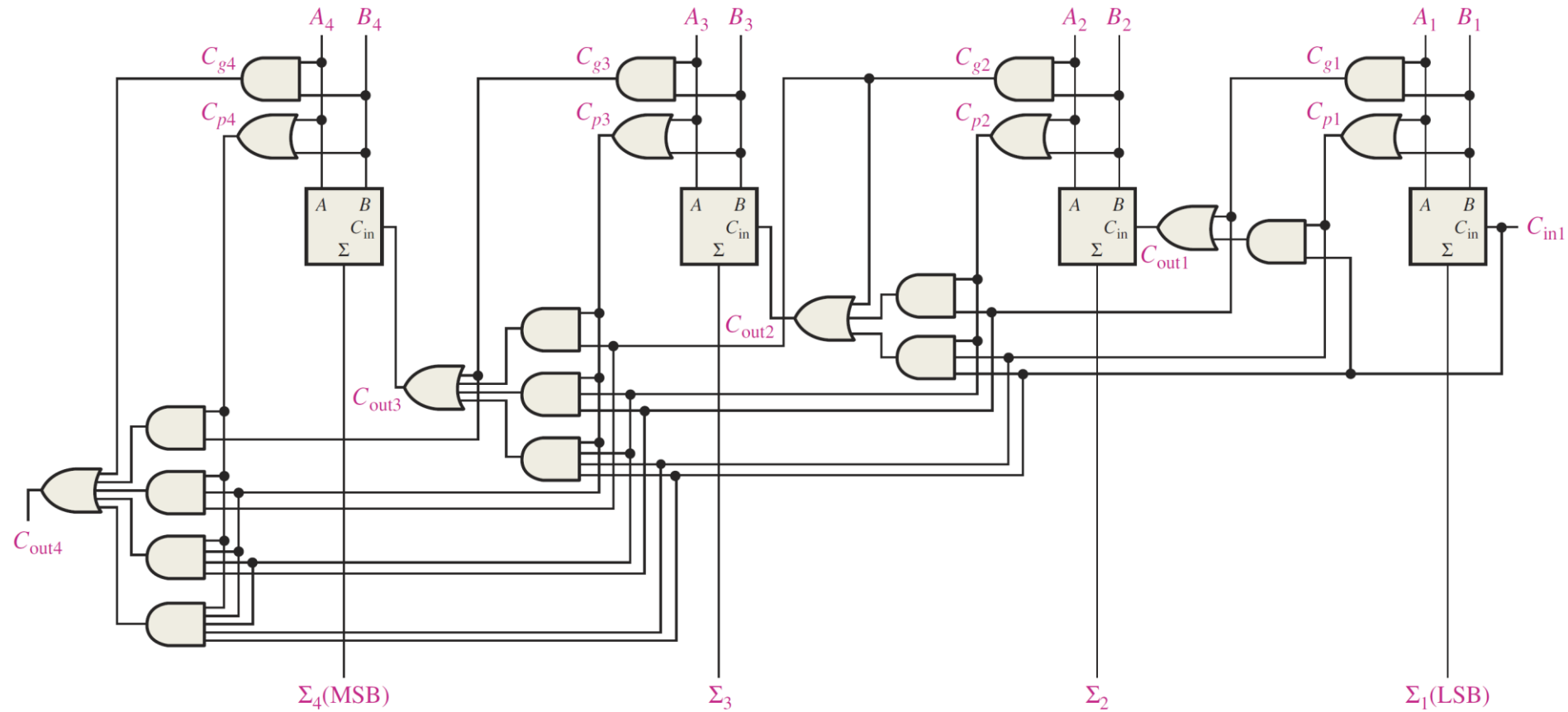

Look-Ahead Carry Adder

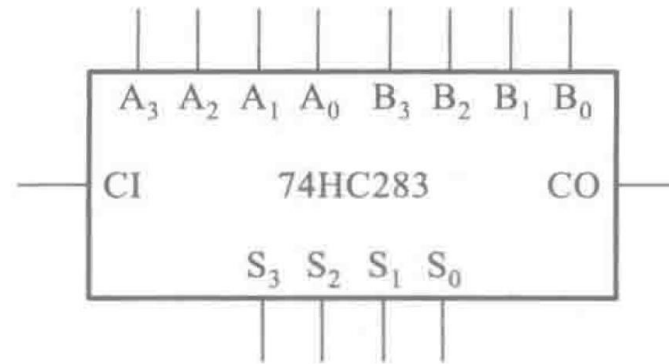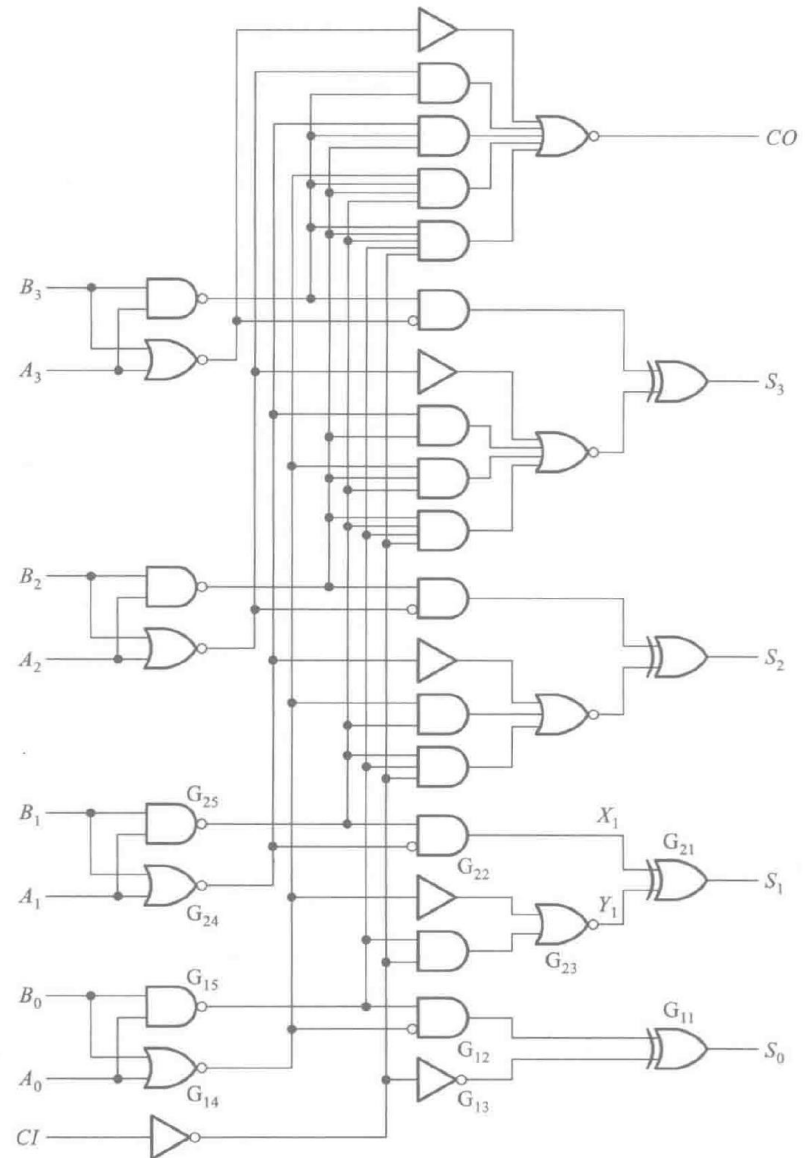

Reading materials

- Chapter 6 of Floyd book
- Chapter 4 of 阎石 book