



Lecture 2

Basic Laws & Circuit Analysis




Outline

- Terminology: Branches, Nodes, and Loops
- Basic Laws
 - Ohm's Law
 - Kirchhoff's Laws -- KCL, KVL
- Circuit Analysis
 - Nodal Analysis
 - Mesh Analysis


Terminology: Branch, Node, and Loop

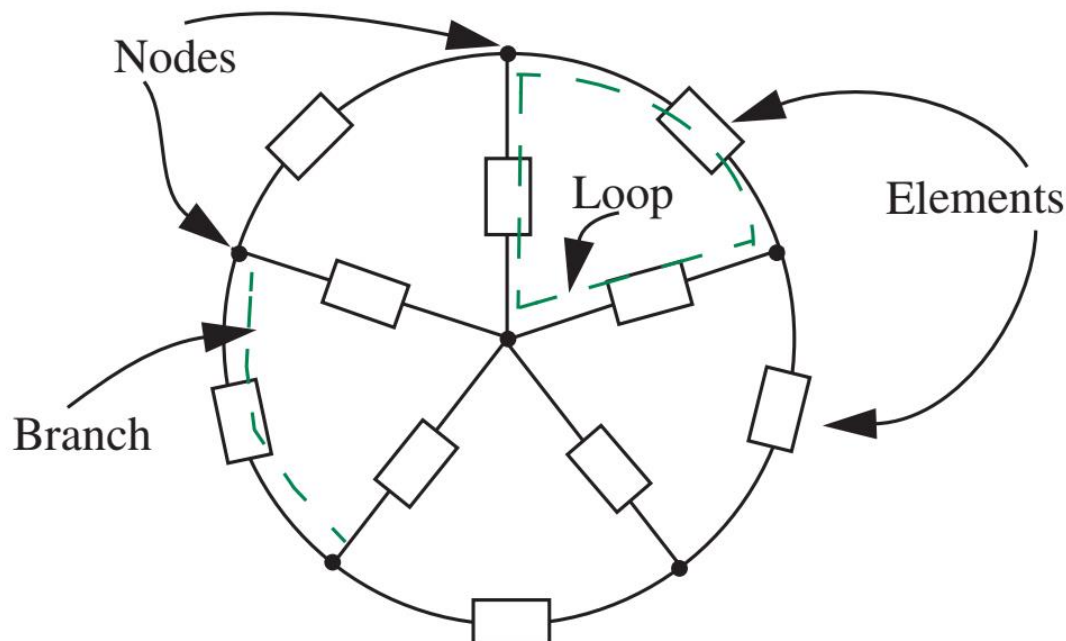- **Branch**: represents a single element;
- **Node**: a point of connection between two or more branches;
- **Loop**: **Any** closed path in a circuit.





Example

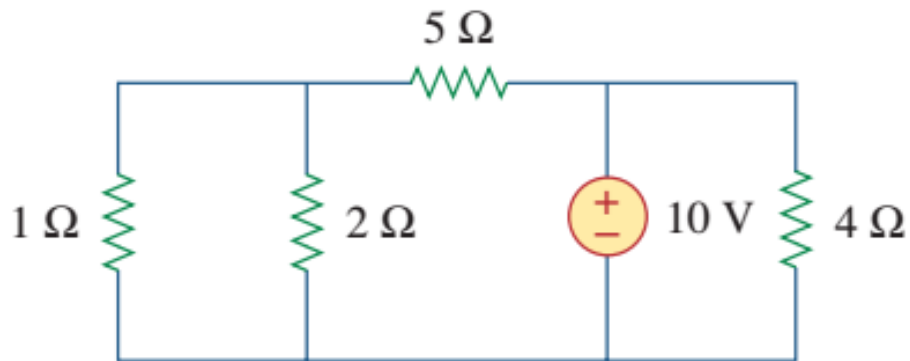

- b – number of branches
- n – number of nodes
- l – number of loops



Ohm's Law

- Resistance: the ratio of voltage drop and current. The circuit element used to model this behavior is the resistor.

Circuit symbol: 


- The current flowing in the resistor is proportional to the voltage across the resistor:

$$V = I * R$$

(Ohm's Law)

- Conductance** is the reciprocal of resistance

$$G = \frac{1}{R} = \frac{I}{V}$$

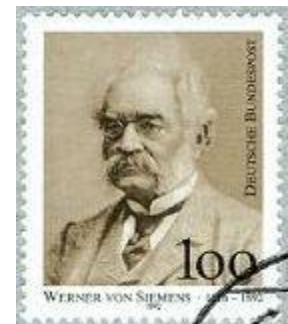


Werner von Siemens
1816-1892

Kirchhoff's Laws

- Kirchhoff's Current Law (KCL):
 - The algebraic sum of all the **currents** entering any **node** in a circuit equals zero.
 - Why?

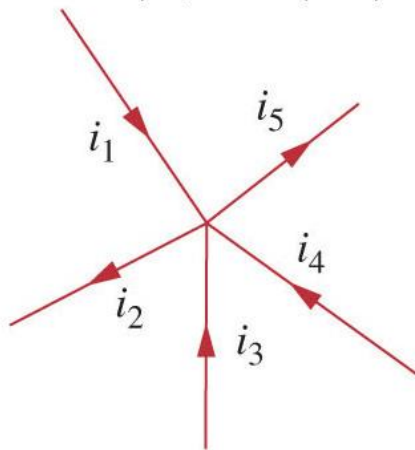
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Gustav Robert Kirchhoff
1824-1887


KCL

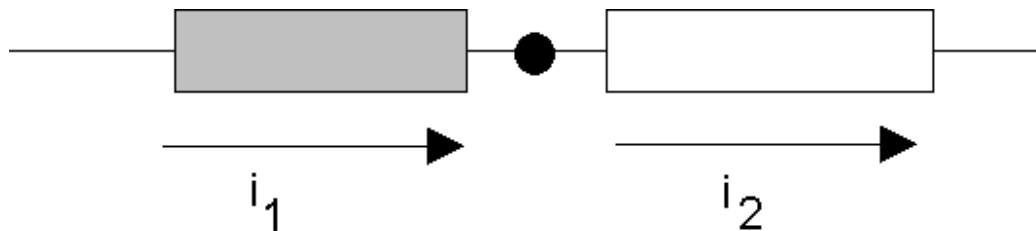- KCL tells us that **all of the elements that are connected *in series* carry the same current.**



Current entering node = Current leaving node

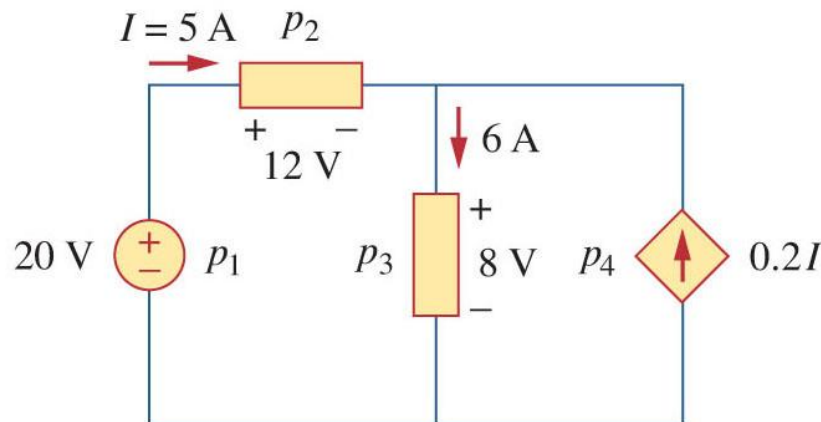
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Generalization of KCL



- The sum of currents entering/leaving a **closed surface** is zero.
 - Circuit branches can be inside this surface, *i.e.* the surface can enclose more than one node!

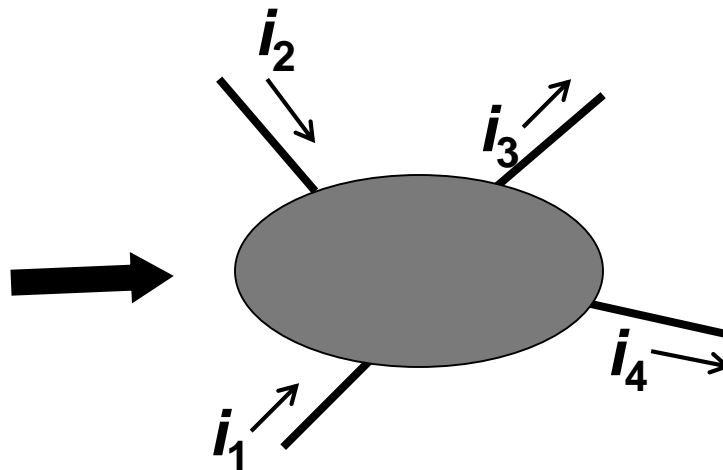This could be a big chunk of a circuit, *e.g.* a “black box”





Generalized KCL Examples

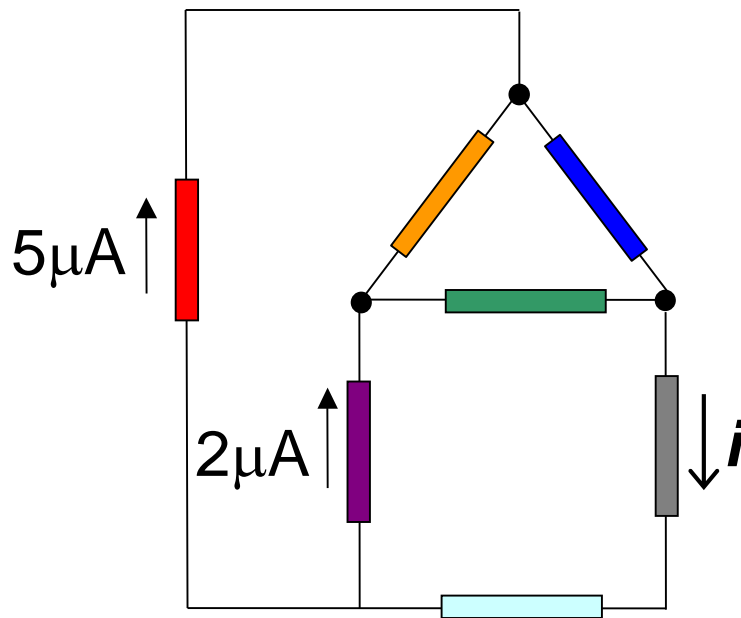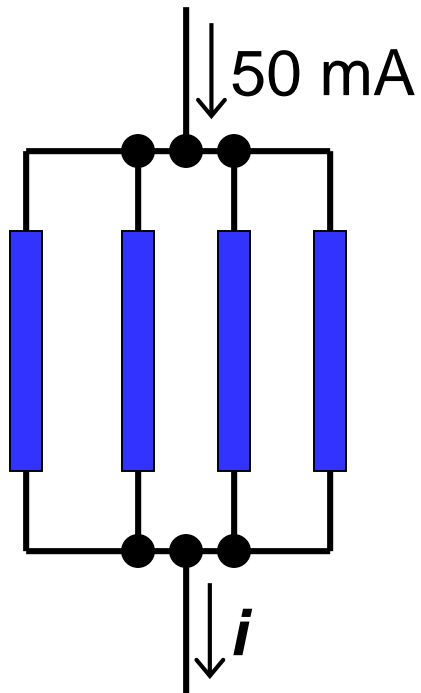




Kirchhoff's Voltage Law (KVL)

- The algebraic sum of all the **voltages** around any **loop** in a circuit equals zero.
- Why?

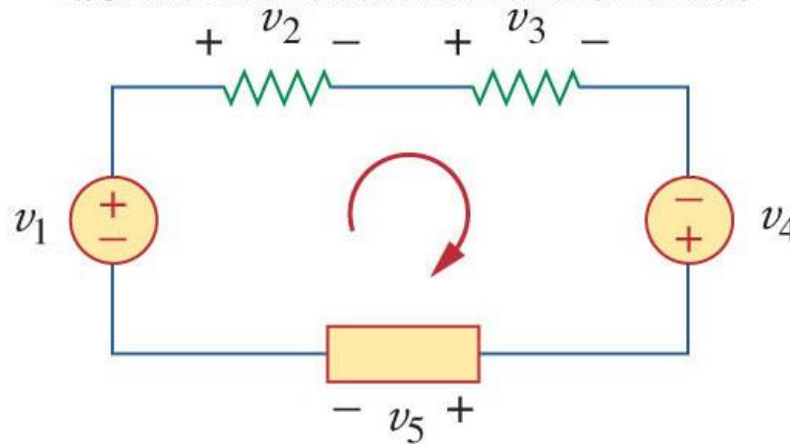
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





KVL

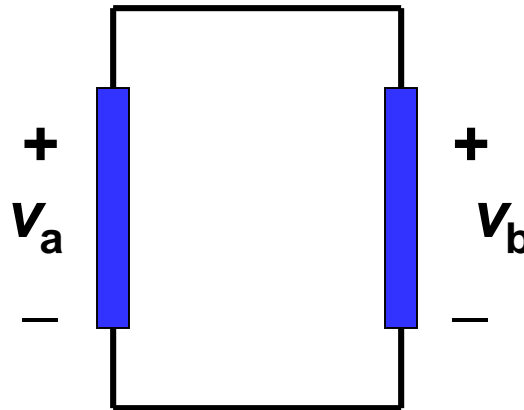
- KVL tells us that **any set of elements which are connected at both ends carry the same voltage.**
- We say these elements are connected **in parallel.**





KVL Example

Three closed paths:

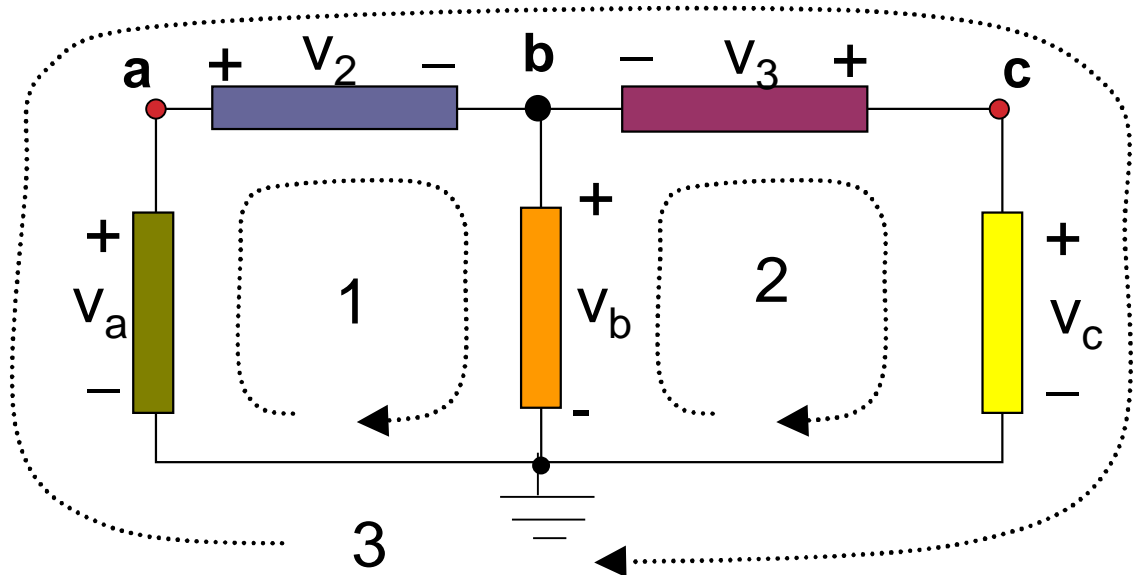


Path 1:

Path 2:


Path 3:



Series Resistors

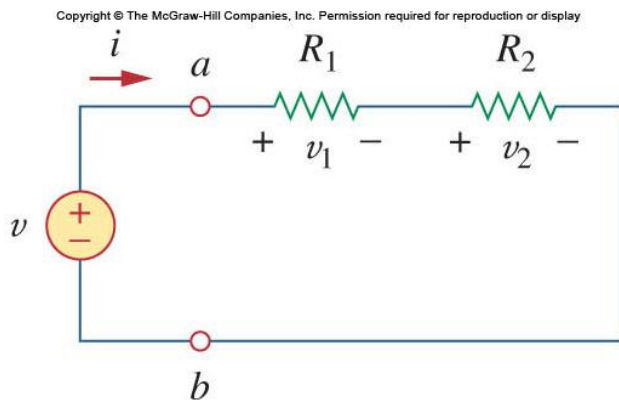

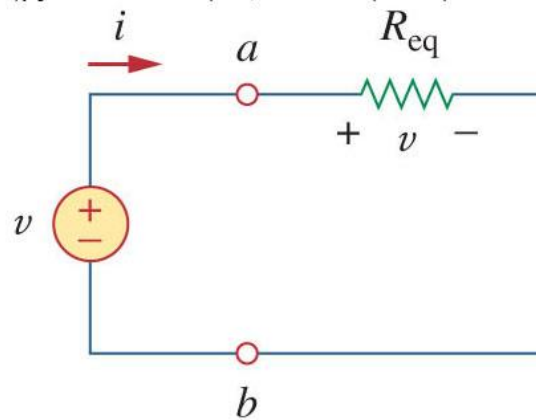
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Voltage Division

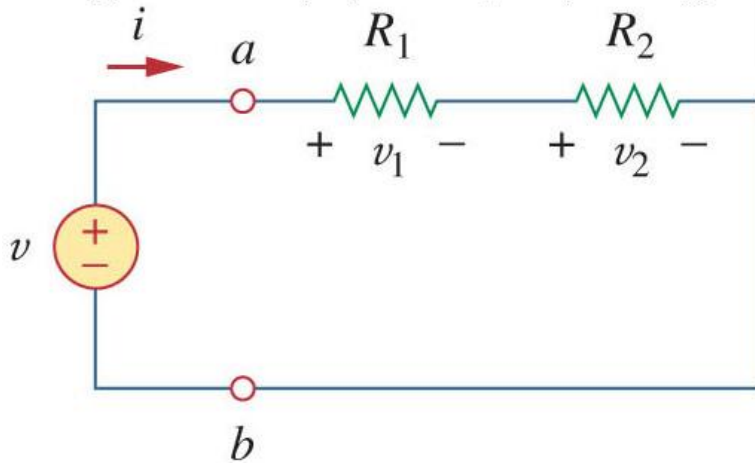Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




Three-terminal rheostat




Parallel Resistors

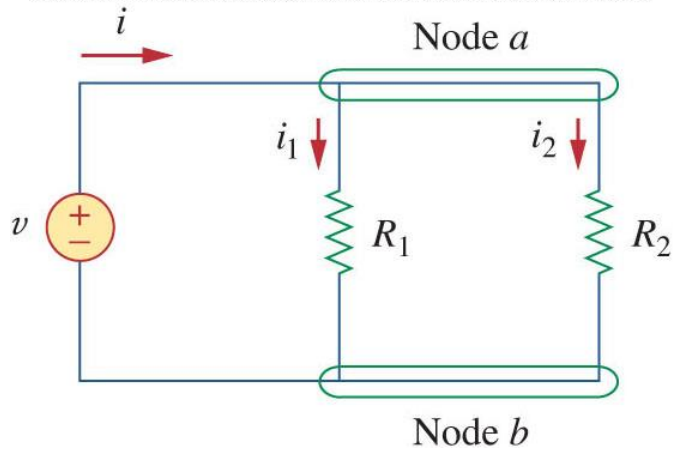Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



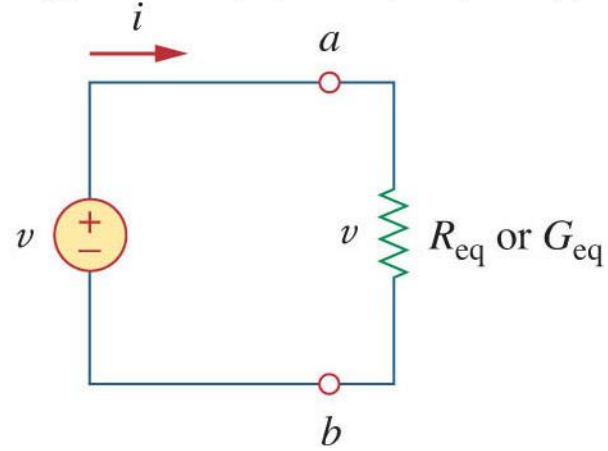
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Current Division

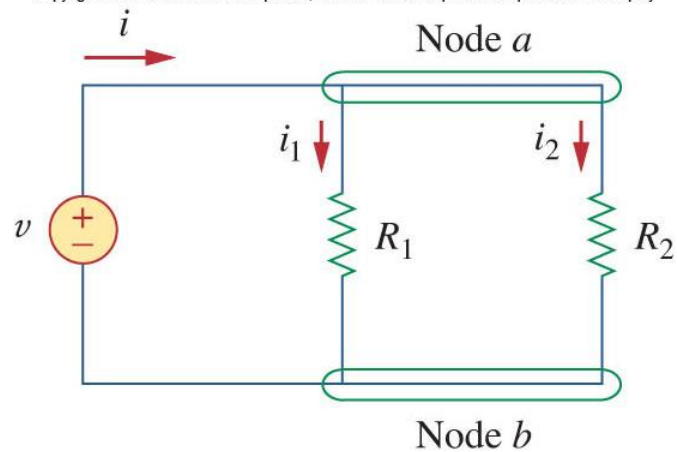Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






Summary-1

- KCL and KVL


$$\sum_{n=1}^N i_n = 0$$

$$\sum_{m=1}^M v_m = 0$$

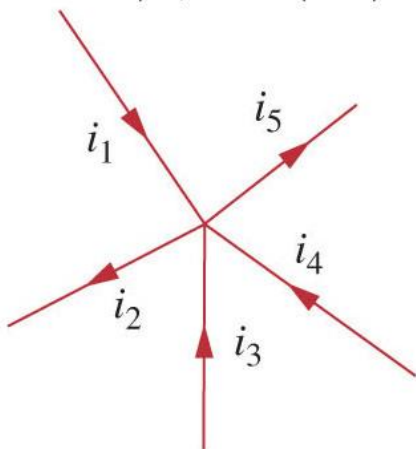Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display







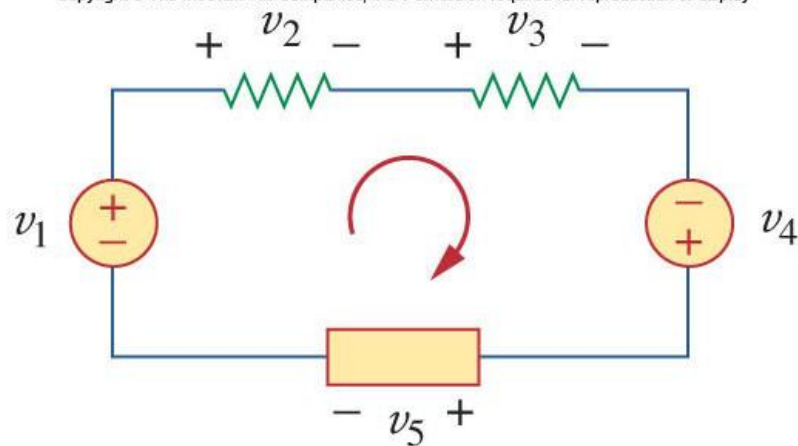Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






Summary-2

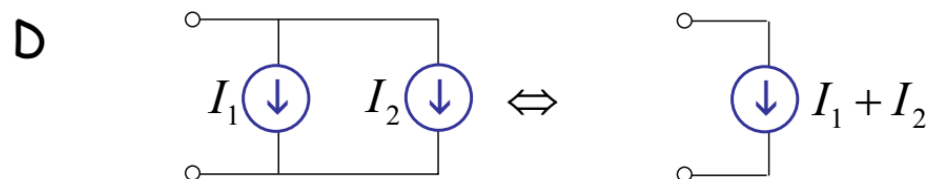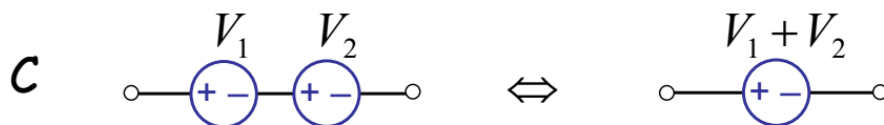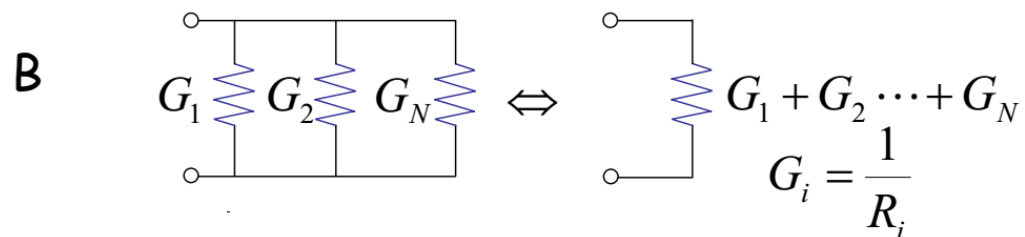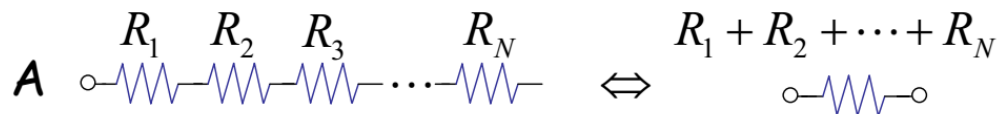







Example

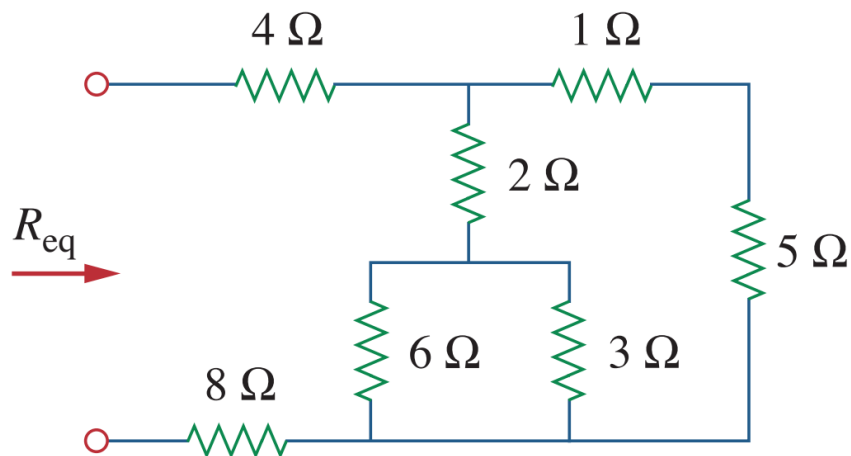




Practice

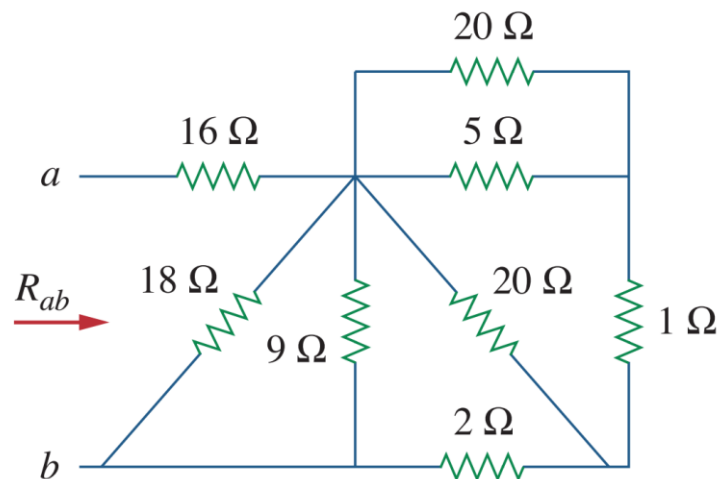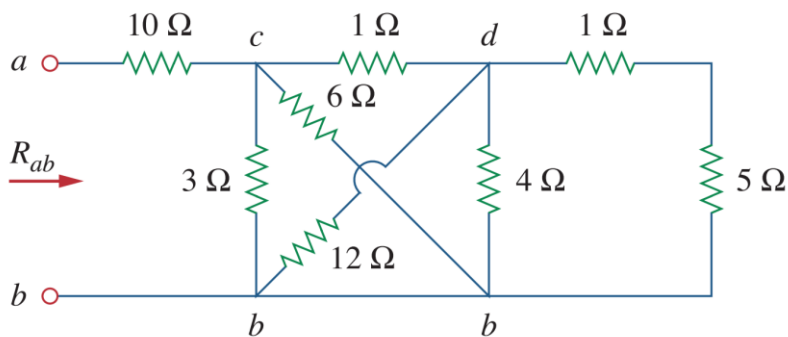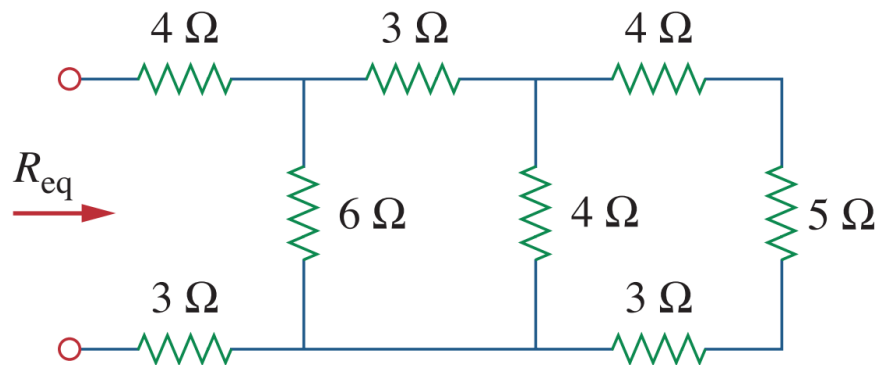

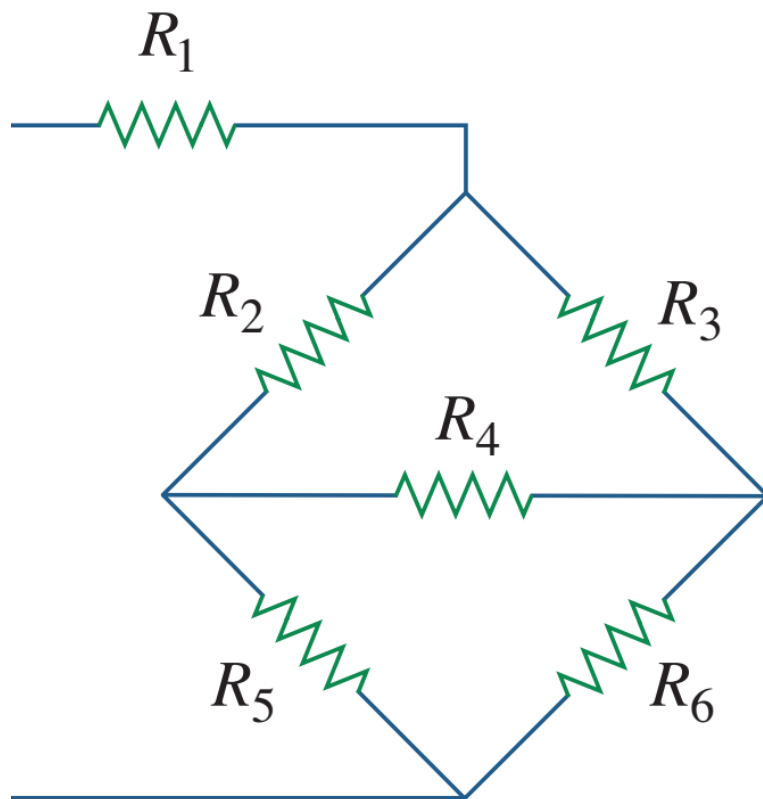



Delta-wye conversion

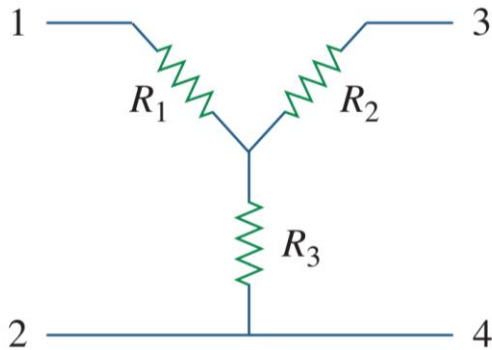

$$R_{12}(Y) = R_1 + R_3 \quad (2.46)$$

$$R_{12}(\Delta) = R_b \parallel (R_a + R_c)$$

Setting $R_{12}(Y) = R_{12}(\Delta)$ gives

$$R_{12} = R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c} \quad (2.47a)$$

Similarly,

$$R_{13} = R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} \quad (2.47b)$$

$$R_{34} = R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} \quad (2.47c)$$


Subtracting Eq. (2.47c) from Eq. (2.47a), we get

$$R_1 - R_2 = \frac{R_c(R_b - R_a)}{R_a + R_b + R_c} \quad (2.48)$$

Adding Eqs. (2.47b) and (2.48) gives


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad (2.49)$$
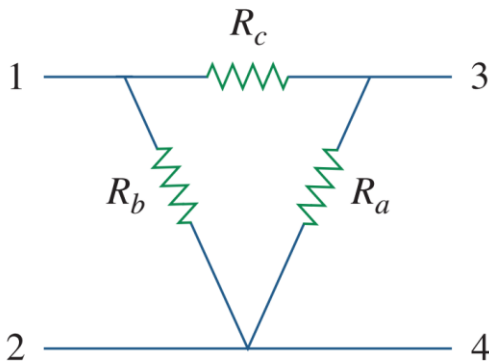
$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$





Wye-delta conversion

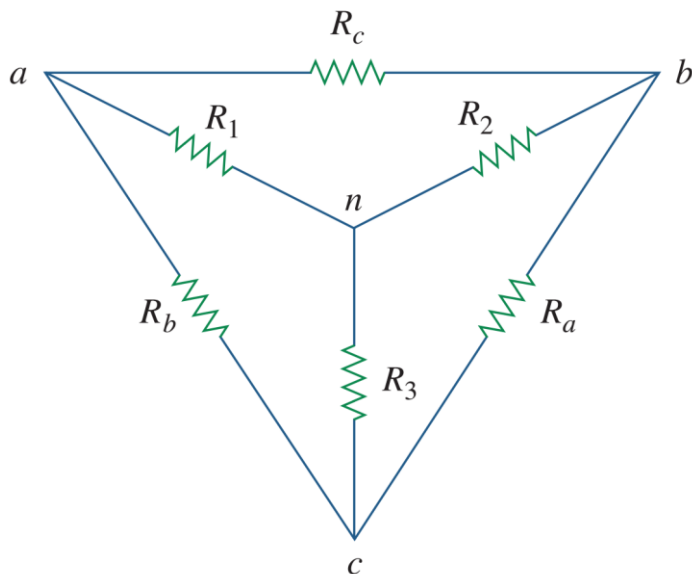

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

The Y and Δ networks are said to be *balanced* when

$$R_1 = R_2 = R_3 = R_Y, \quad R_a = R_b = R_c = R_\Delta \quad (2.56)$$

Under these conditions, conversion formulas become

$$R_Y = \frac{R_\Delta}{3} \quad \text{or} \quad R_\Delta = 3R_Y \quad (2.57)$$