

Homework 8


Due date: 18:00, 23rd, Dec.

Turn in your homework to room 3-305, SIST


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

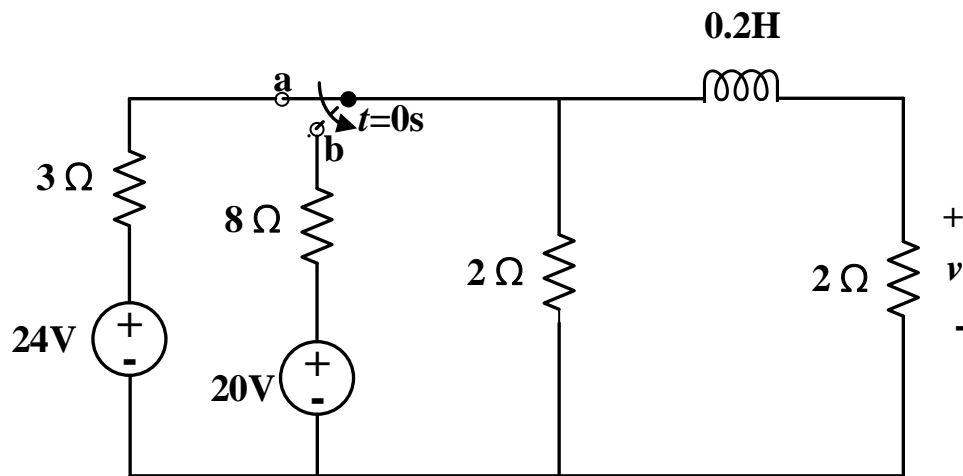
1. For the following circuit, the switch had been at node **a** for a long time before $t=0$ s. At $t=0$ s, the switch was turned to node **b** immediately. Please find the voltage on the 2Ω resistor for $t>0$ s by using **time domain method AND Laplace domain method, respectively.**



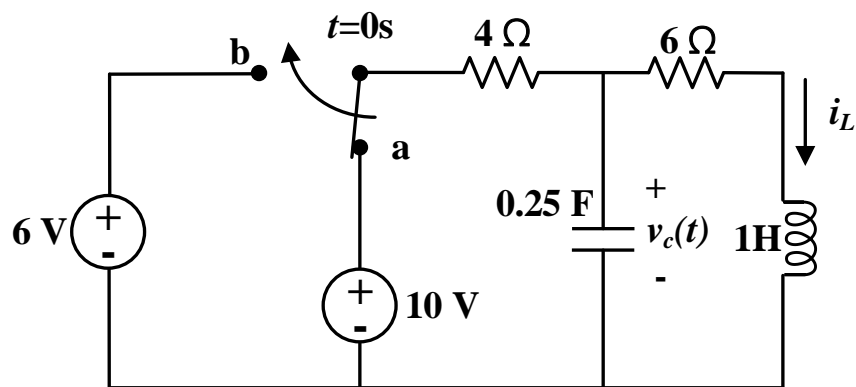2. For the following circuit, the switch had been at node *a* for a long time before $t=0$ s. When $t=0$ s, the switch was turned to node *b* immediately. Please use **Laplace domain method** to find $i_L(t)$ for $t>0$ s.



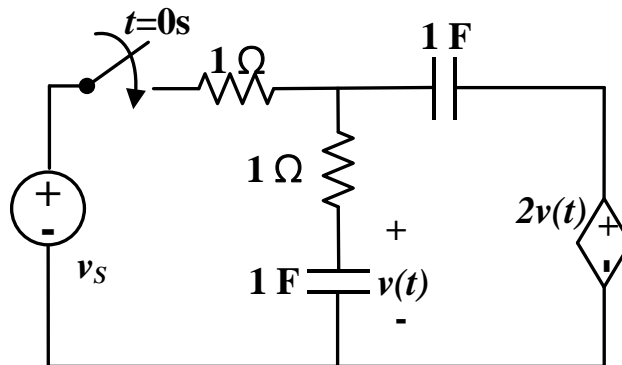3. For the circuit below, the switch closed immediately at $t=0$ s, and $v_s(t)=e^{-t}\sin(t)$ V. Please find the voltage $v(t)$ shown in the circuit for $t>0$ s by using **Laplace domain method**. Note that there is no energy stored in this circuit before $t=0$ s.



4. For the following circuit, $v_s(t)=10\cos t$ V, and the switch closed immediately at $t=0$ s. There is no energy stored in the circuit before $t=0$ s. Please
- (a) Use **phasor method** to find the **steady-state** for the voltage of $v(t)$.
 - (b) Use **Laplace domain method** to find $v(t)$ for $t>0$ s and compare the results from (a).

