

ShanghaiTech University

**EE 115B: Digital Circuits**


Fall 2022

Lecture 17

Hengzhao Yang  
December 1, 2022
 
# D: latch vs. flip-flop

- Top to bottom
  - Gated D latch (level sensitive)
  - Positive-edge-triggered flip-flop
  - Negative-edge-triggered flip-flop




# D flip-flops with CLEAR and PRESET

- Control signals: CLEAR and PRESET
  - Use CLEAR to set initial condition  $Q=0$
  - Use PRESET to set initial condition  $Q=1$
- Implementations
  - Based on master-slave D flip-flop
  - Based on edge-triggered D flip-flop

 
# Master-slave D flip-flop with CLEAR and PRESET

- CLEAR and PRESET are active low
  - CLEAR=0: Q=0
  - PRESET=0: Q=1
  - CLEAR=1 or PRESET=1: no effect
- Circuit symbol (negative edge)




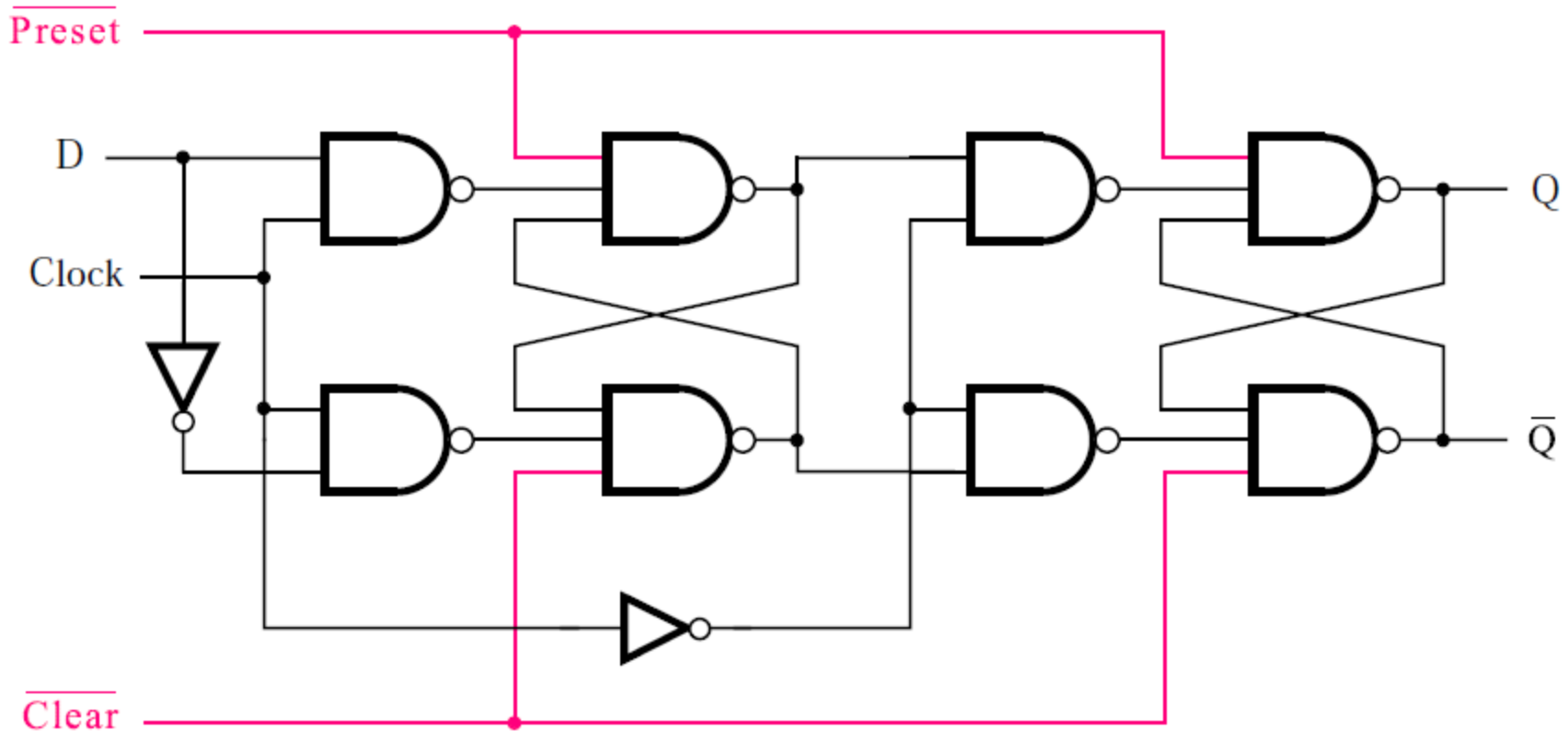
# Master-slave D flip-flop with CLEAR and PRESET

- Circuit: modified master-slave D flip-flop


  
# Edge-triggered D flip-flop with CLEAR and PRESET

- Circuit and circuit symbol (positive edge)




# Asynchronous vs. synchronous CLEAR

- Asynchronous CLEAR
  - If  $CLEAR=0$ , flip-flop will be cleared to  $Q=0$  immediately without regard to clock
- Synchronous CLEAR
  - If  $CLEAR=0$ , flip-flop will be cleared to  $Q=0$  at the next clock edge (positive or negative)

# Synchronous CLEAR


- Circuit

 


 
# T flip-flop


- T flip-flop
  - $T=0$ : state does not change
  - $T=1$ : state is reversed
- Circuit




# T flip-flop

- Characteristic table and circuit symbol

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

 


- Timing diagram

 

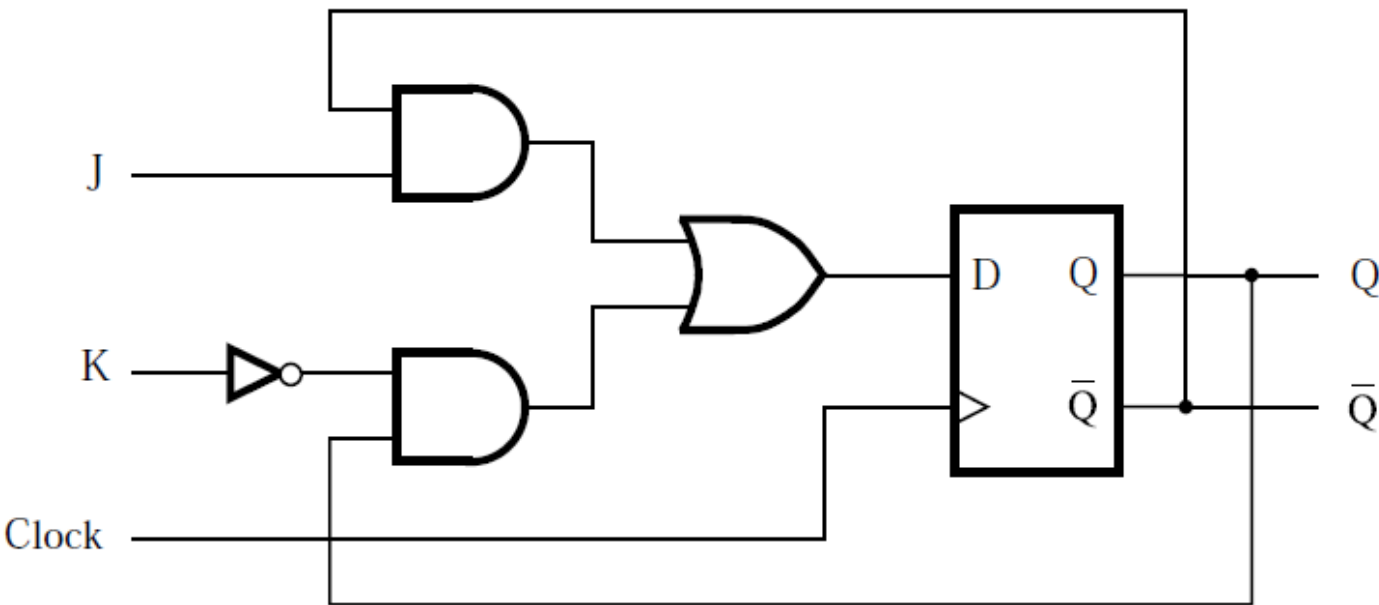
# JK flip-flop

- JK flip-flop
  - Combines behaviors of basic SR latch and T flip-flop
  - J: set, K: reset
- Circuit, characteristic table, and circuit symbol




J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

 
 
# Code for D flip-flop (positive edge)

- Code

- Sensitivity list: Clock
- 'EVENT: signal attribute
- Clock'EVENT: any change in the Clock signal
- Clock'EVENT AND Clock='1': clock signal value has changed and the value is now 1 (positive edge)




```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN    STD_LOGIC ;
          Q          : OUT  STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```
 
# Comparison: VHDL code for gated D latch



Clk	D	$Q(t + 1)$
0	x	$Q(t)$
1	0	0
1	1	1

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY latch IS
    PORT ( D, Clk : IN  STD_LOGIC ;
          Q       : OUT STD_LOGIC) ;
END latch ;
```

```
ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

# Alternative code for D flip-flop (positive edge)

- Alternative code
  - Sensitivity list: omitted
  - **WAIT UNTIL**: implying that sensitivity list only includes clock signal
  - Some VHDL tools accept a simplified WAIT UNTIL statement (i.e., Clock'EVENT is redundant and removed): WAIT UNTIL Clock='1'

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY flipflop IS
    PORT ( D, Clock : IN    STD_LOGIC ;
          Q         : OUT STD_LOGIC ) ;
END flipflop;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        Q <= D ;
    END PROCESS ;
END Behavior ;
```


# Code for D flip-flop with asynchronous reset (clear)

- Asynchronous reset (clear): active low

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN  STD_LOGIC ;
          Q                  : OUT STD_LOGIC) ;
END flipflop ;

 ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



# Code for D flip-flop with synchronous reset (clear)

- Synchronous reset (clear) acts at clock edge

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN  STD_LOGIC ;
          Q                  : OUT STD_LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSE
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

