



# Lecture 11

## - Transformers/Three-Phase Circuits





# Outline

- Mutual Inductance
- Transformers
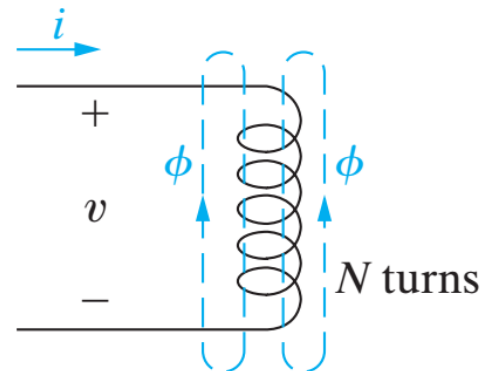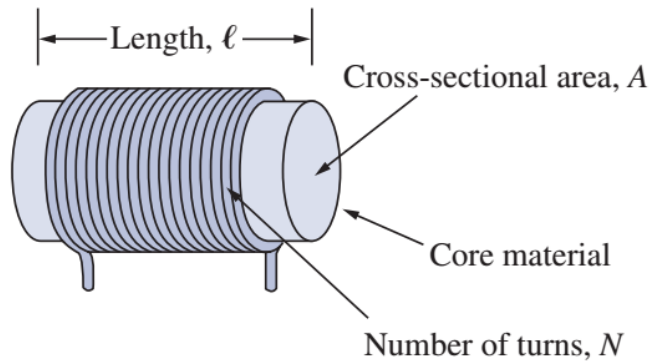
# Review: Self Inductance



- Self inductance: reaction of the inductor to the change in current through itself.



$$v = L \frac{di}{dt}$$
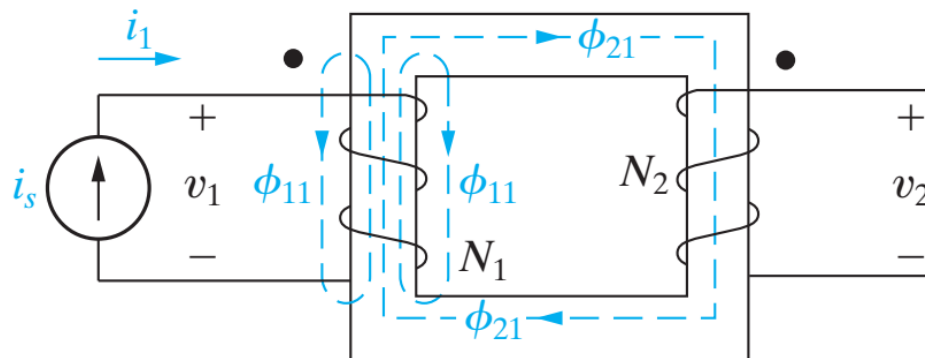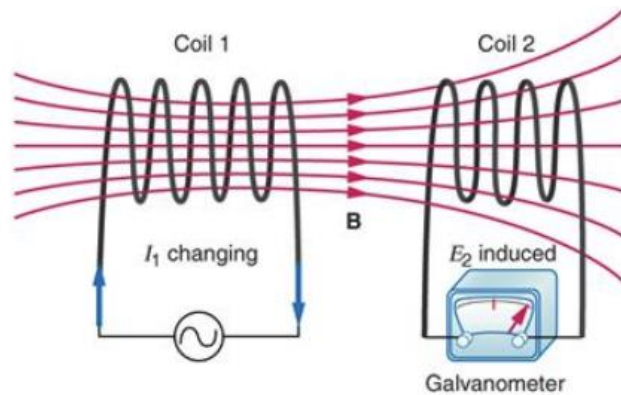
# Mutual Inductance

- Mutual inductance: reaction of the inductor to change in current through another inductor.



$$\Phi_{11} = L_1 i_1$$


$$\Phi_{21} = M i_2$$

$$\begin{aligned} v_1 &= \frac{d\Phi_1}{dt} \\ &= \frac{d\Phi_{11}}{dt} + \frac{d\Phi_{21}}{dt} \\ &= L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \end{aligned}$$

$$v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$



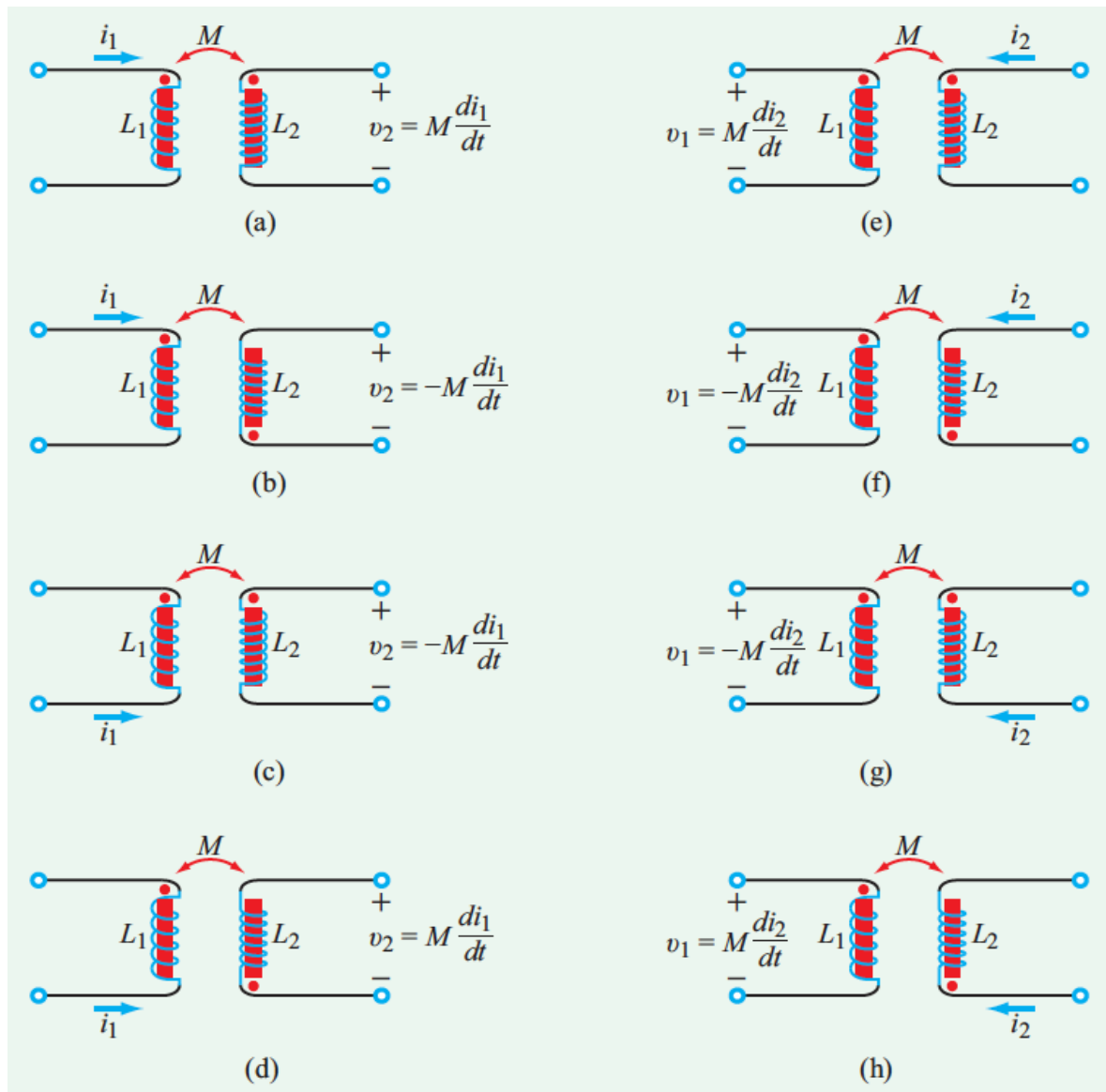
# Dot Convention: Defines Directions of Windings



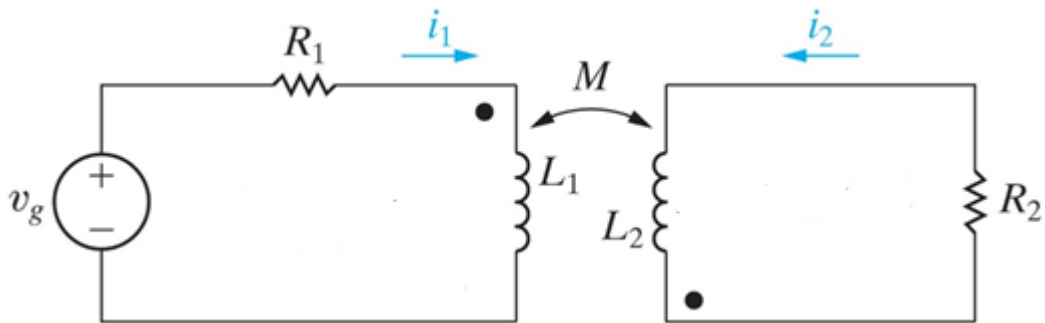
# Mutual Inductance: General Case


- Two circuits lined by a magnetic field
  - $L_1, L_2$ : self-inductances
  - $M$ : mutual inductance
  - Dots: indicating polarity of mutually induced voltages.



## Exercise

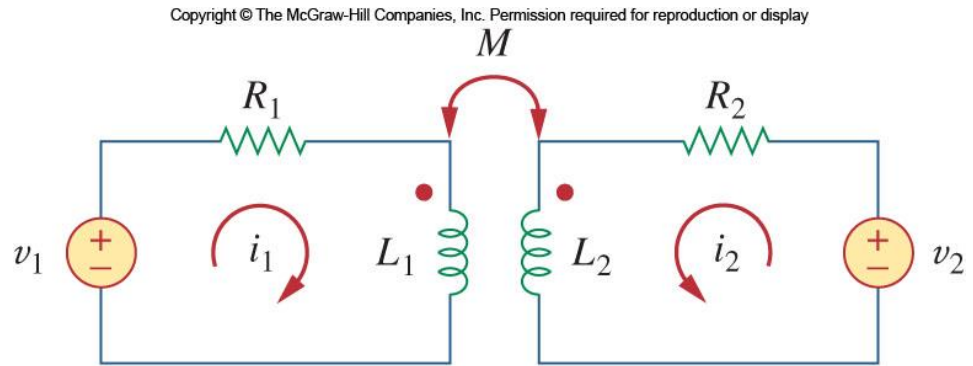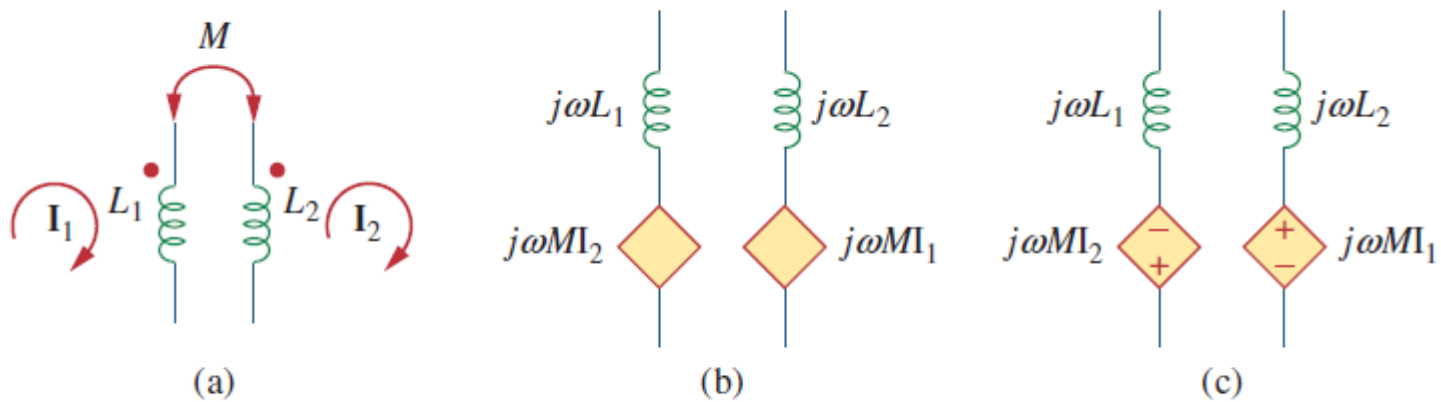- Relate  $v_1, v_2$  with  $i_1$  and  $i_2$ .
  - In time domain
  - In phasor domain


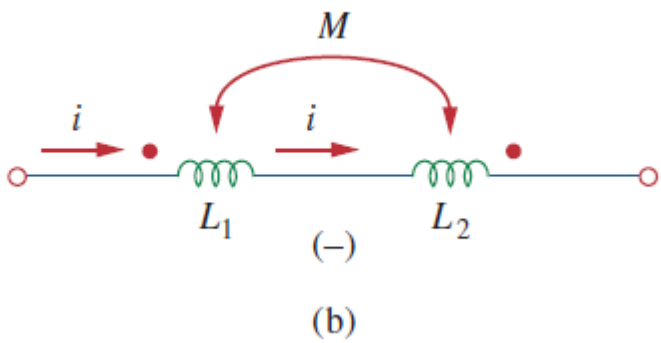


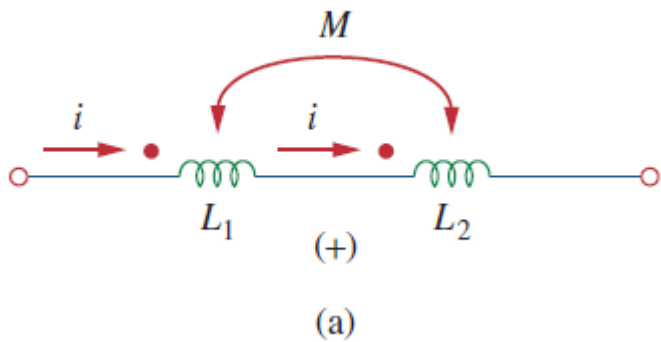

**Figure 13.8**


Model that makes analysis of mutually coupled easier to solve.







Calculate the mesh currents in the circuit of Fig. 13.11.

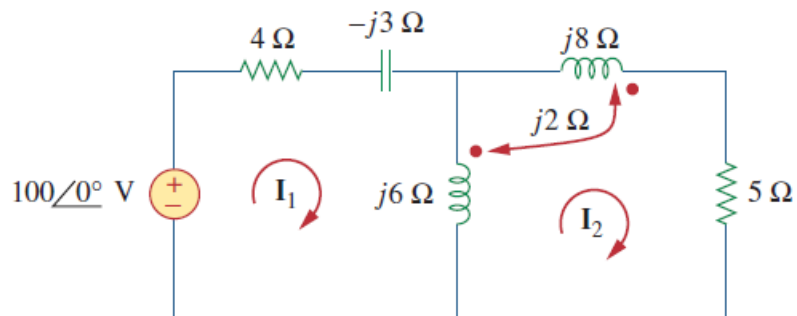


**Figure 13.11**  
For Example 13.2.

# Energy in a Coupled Circuit


- The energy stored in an inductor is
- For coupled inductors, the total energy stored is

$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

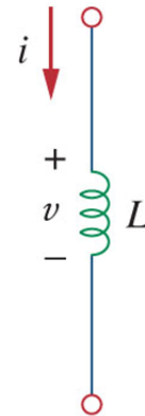- The positive sign is selected when the currents both enter or leave the dotted terminals.



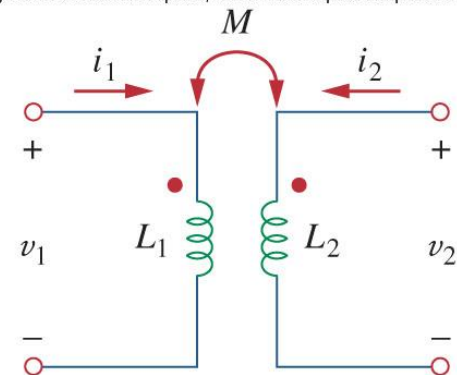Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



# Coupling Coefficient $k$


- The system cannot have negative energy

$$\frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 - Mi_1i_2 \geq 0 \quad \Rightarrow \quad M \leq \sqrt{L_1L_2}$$

- Define a parameter describes how closely  $M$  approaches upper limit.


$$k = \frac{M}{\sqrt{L_1L_2}}$$

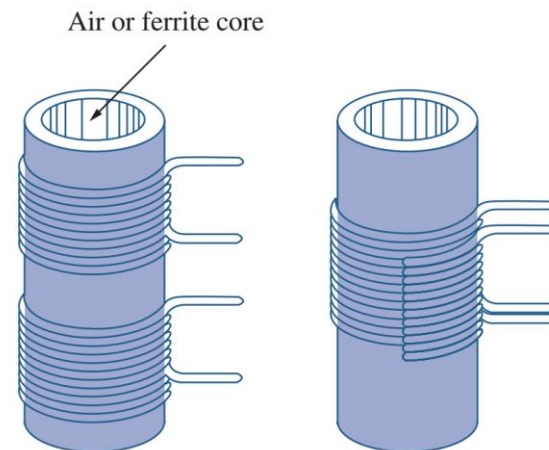- Coupling coefficient,  $0 \leq k \leq 1$ .
- determined by the physical configuration of the coils.


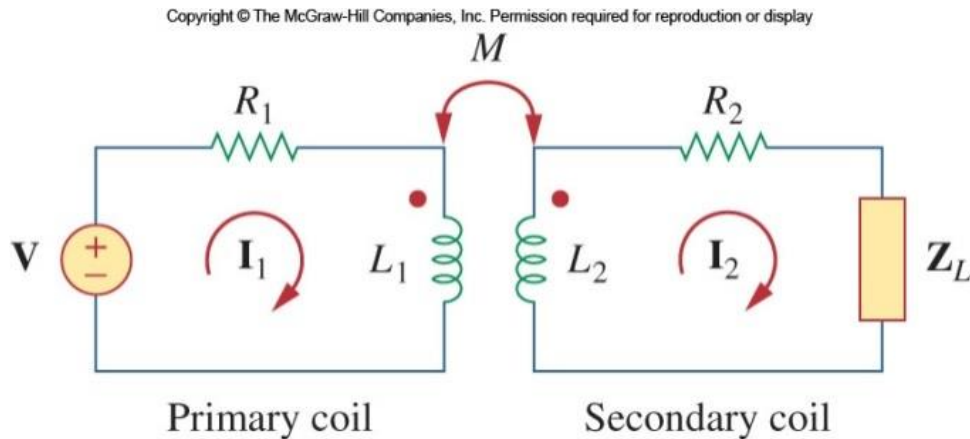
# Linear Transformers


- A transformer is a magnetic device that takes advantage of mutual inductance.
  - Called linear if the coils are wound on a magnetically linear material, i.e. permeability  $\mu$  is constant.


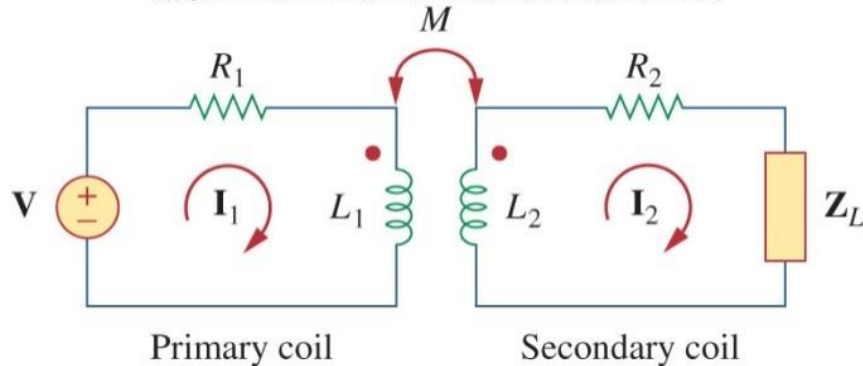
# Transformer Impedance

- An important parameter to know for a transformer is how the input impedance  $Z_{in}$  is seen from the source.
  - $Z_{in}$  is important because it governs the behavior of the primary circuit.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




$$Z_{in} = \frac{V}{I_1} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$


Reflected impedance from secondary to primary
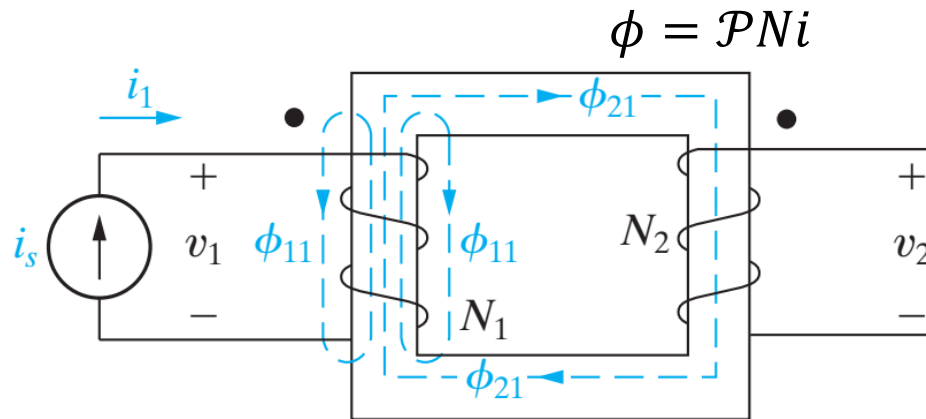
# Ideal Transformers

- The ideal transformer has:
  - Coils with very large reactance  
( $L_1, L_2, M \rightarrow \infty$ )
  - Coupling coefficient  $k=1$ .
  - Primary and secondary coils are lossless,  $R_1 = R_2 = 0$ .



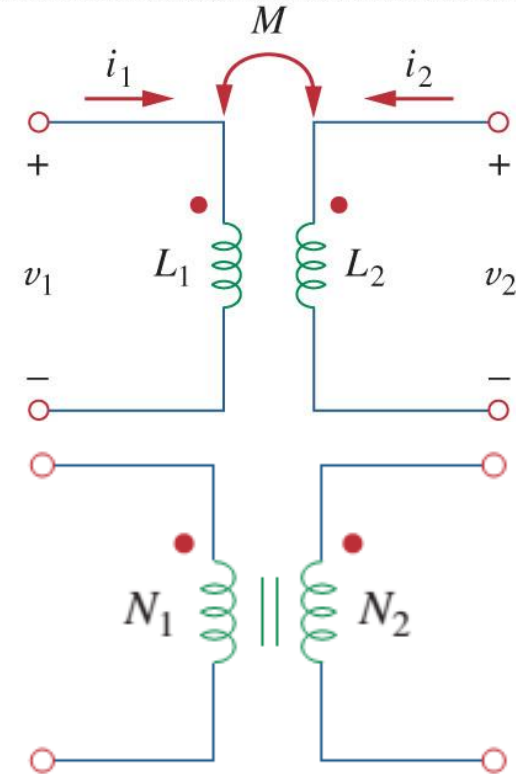
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$
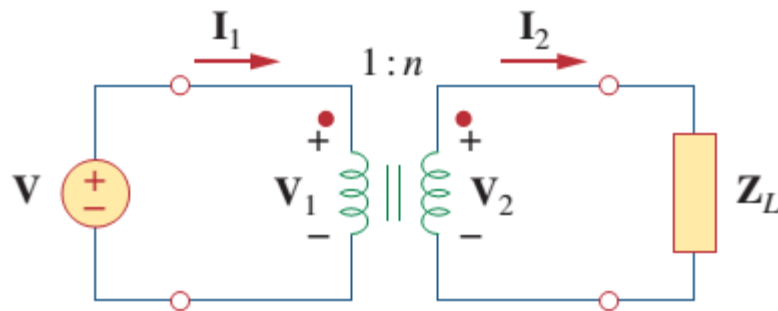
## Ideal Transformers II

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$




- The current is related as:
- Reflected impedance

$$Z_{in} = \frac{V_1}{I_1} =$$



# Example


Find  $V_o$  in the circuit of Fig. 13.40.

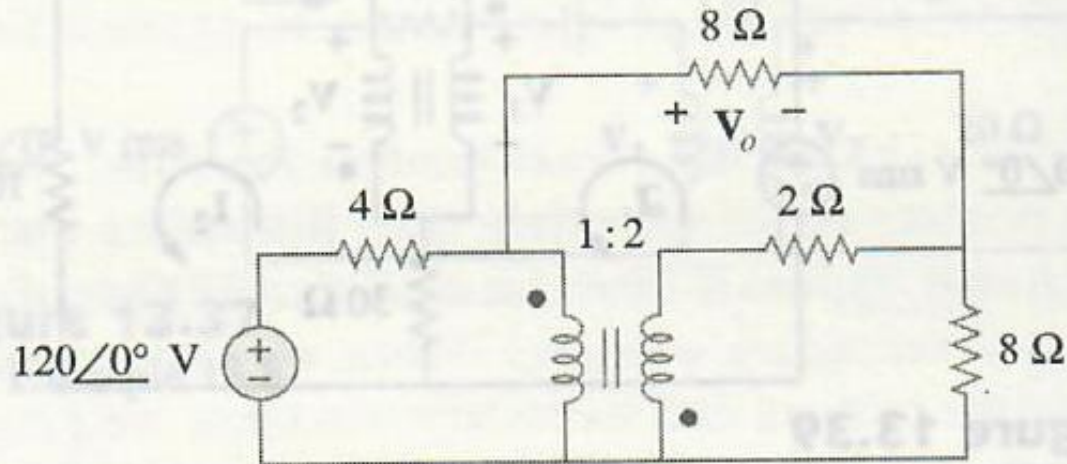

**Figure 13.40**  
For Practice Prob. 13.9.
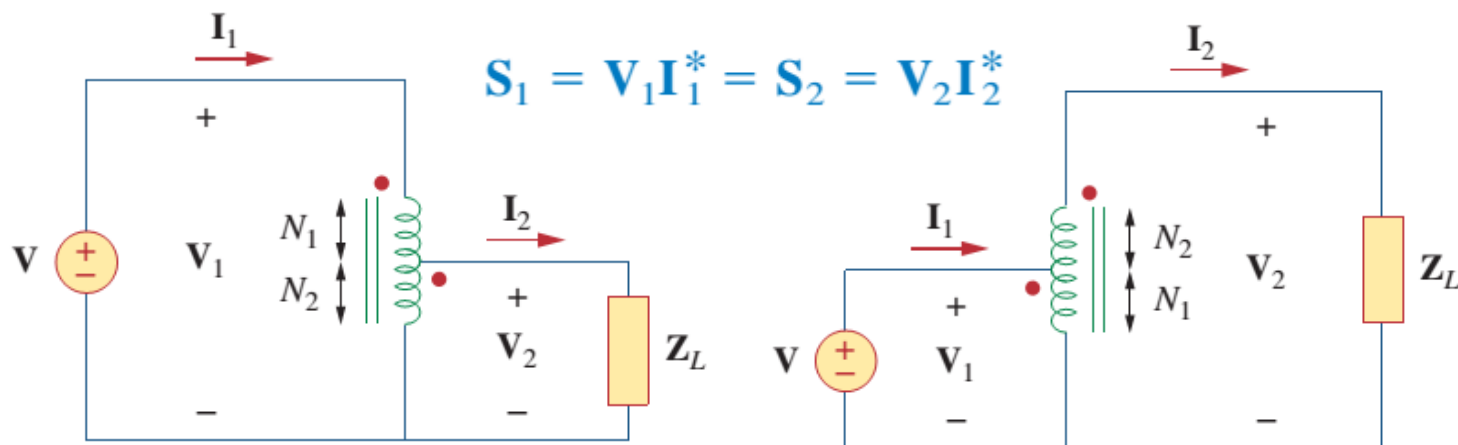
# Ideal Autotransformer

- Autotransformer uses one winding for primary & secondary
  - It does not offer isolation!



$$\frac{V_1}{V_2} = \frac{N_1 + N_2}{N_2} = 1 + \frac{N_1}{N_2}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1 + N_2}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_1 + N_2}$$

$$\frac{I_1}{I_2} = \frac{N_1 + N_2}{N_1} = 1 + \frac{N_2}{N_1}$$