

## Homework 8


Due date: 18:00, 23<sup>rd</sup>, Dec.

Turn in your homework to room 3-305, SIST


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

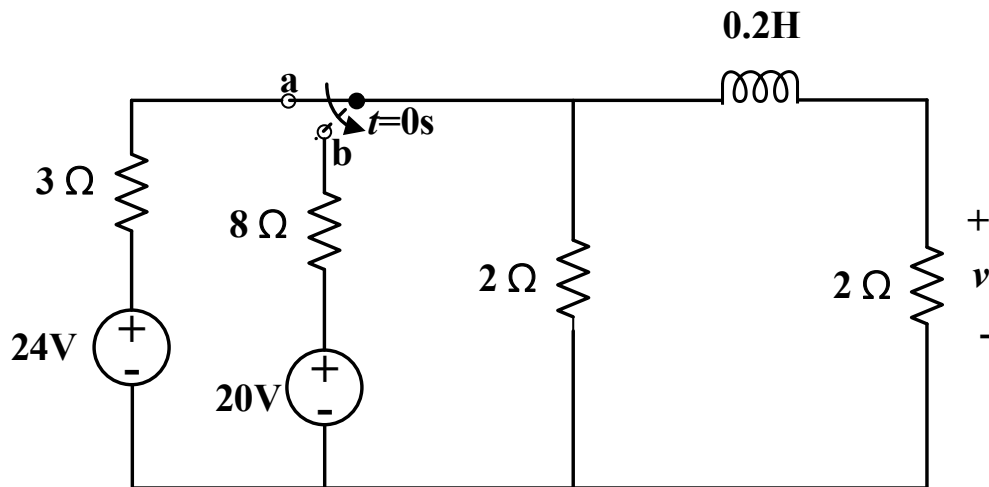1. For the following circuit, the switch had been at node **a** for a long time before  $t=0$ s. At  $t=0$ s, the switch was turned to node **b** immediately. Please find the voltage on the  $2\Omega$  resistor for  $t>0$ s by using **time domain method AND Laplace domain method, respectively.**



Q1: ① 初始条件:

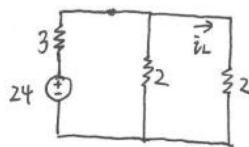


$$i_L(0-) = \frac{24}{3+2} \cdot \frac{1}{2} \text{ A} = 3 \text{ A}$$

time domain

略.

②  $t \geq 0$ s

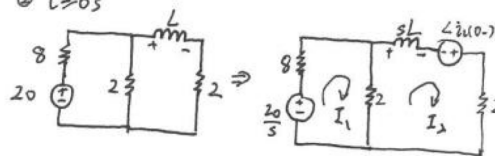

$$\begin{cases} 8I_1 + 2(I_1 - I_2) = \frac{20}{s} \quad \dots ① \\ 2(I_2 - I_1) + sLI_2 - L i_L(0-) + 2I_2 = 0 \quad \dots ② \end{cases}$$

$$\begin{cases} 10I_1 - 2I_2 = \frac{20}{s} \quad \dots ③ \\ -2I_1 + (4 + sL)I_2 = L i_L(0-) \quad \dots ④ \end{cases}$$

③ + ④ × 5

$$[5(4 + sL) - 2]I_2 = \frac{20}{s} + 4L i_L(0-)$$


$$(18 + 5sL)I_2 = \frac{20}{s} + 5L i_L(0-)$$

$$\begin{aligned} \Rightarrow I_2 &= \frac{20}{(18 + 5sL)s} + \frac{15L}{18 + 5sL} \quad (L = 0.2\text{H}) \\ &= \frac{20}{s(s + 18)} + \frac{34}{s + 18} \text{ A} \end{aligned}$$

$$i_2(t) = \frac{10}{9} + \frac{17}{9}e^{-18t} \text{ (A)}$$

$$V = 2i_2(t) = \frac{20}{9} + \frac{34}{9}e^{-18t} \text{ (V)}$$

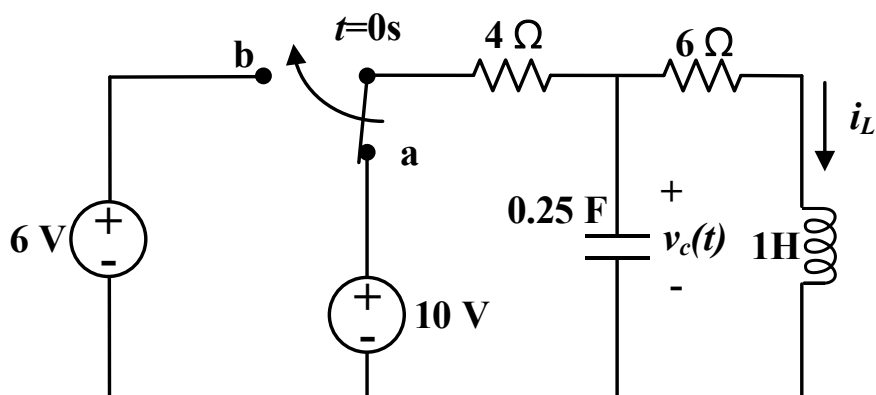2. For the following circuit, the switch had been at node **a** for a long time before  $t=0$ s. When  $t=0$ s, the switch was turned to node **b** immediately. Please use **Laplace domain method** to find  $i_L(t)$  for  $t>0$ s.




Solutions:

① Initial condition:

$$i_L(0^+) = i_L(0^-) = 1 \text{ A}$$

$$V_C(0^+) = V_C(0^-) = 6 \text{ V}$$

②  $t>0$


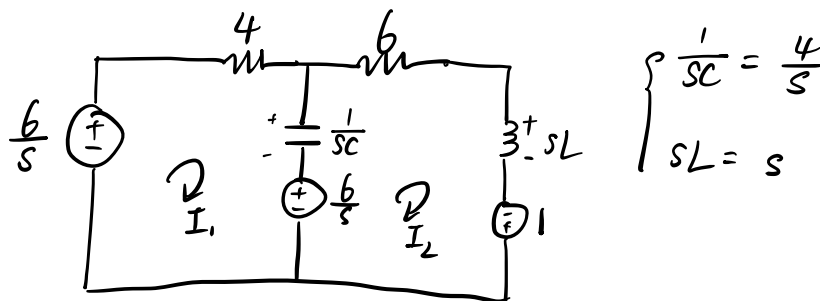


$$\begin{cases} 4I_1 + (I_1 - I_2)\frac{4}{s} + \frac{6}{s} = \frac{6}{s} & \text{mesh 1} \\ 6I_2 + sI_2 + (I_2 - I_1)\frac{4}{s} - 1 - \frac{6}{s} = 0 & \text{mesh 2} \\ i_L = I_2 \end{cases}$$

$$i_L = \frac{(s+6)(s+1)}{s(s+2)(s+5)} = \frac{3/5}{s} + \frac{2/3}{s+2} - \frac{4/15}{s+5} \quad \checkmark$$

$$i_L(t) = \frac{3}{5} + \frac{2}{3}e^{-2t} - \frac{4}{15}e^{-5t} \text{ A } (t \geq 0 \text{ s})$$

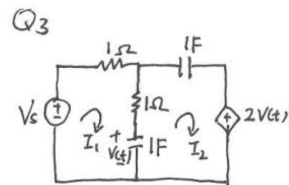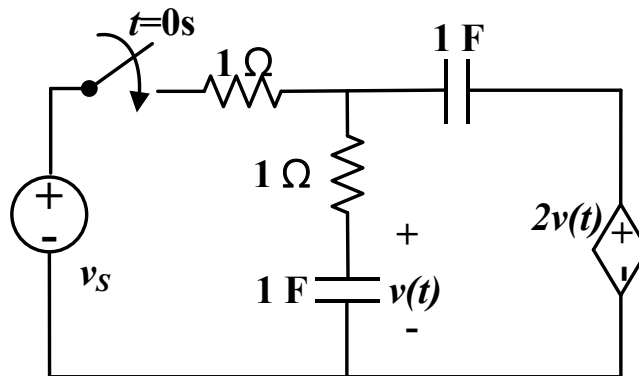3. For the circuit below, the switch closed immediately at  $t=0s$ , and  $v_S(t)=e^{-t}\sin(t)$  V. Please find the voltage  $v(t)$  shown in the circuit for  $t>0s$  by using **Laplace domain method**. Note that there is no energy stored in this circuit before  $t=0s$ .



$$v_S(t) = e^{-t} \sin t \text{ (V)}$$

$$\Rightarrow V_S(s) = \frac{1}{(s+1)^2 + 1} \text{ (V)}$$

Mesh  
KVL:

$$\begin{cases} I_1 + (I_1 - I_2) + \frac{1}{sC}(I_1 - I_2) = V_S(s) \quad \dots \textcircled{1} \\ (I_2 - I_1)\frac{1}{sC} + (I_2 - I_1) + \frac{1}{sC}I_2 + 2V(s) = 0 \quad \dots \textcircled{2} \end{cases}$$

$$\textcircled{1} \cdot C=1F \Rightarrow (1 + 1 + \frac{1}{s})I_1 - (1 + \frac{1}{s})I_2 = V_S(s) \quad \dots \textcircled{3}$$

$$-(1 + \frac{1}{s})I_1 + (1 + \frac{1}{s} + \frac{1}{s})I_2 = -2V(s) \quad \dots \textcircled{4}$$


$$\textcircled{3}, \textcircled{4} \Rightarrow V(s) = \frac{1}{s}(I_1 - I_2)$$

$$\begin{aligned} V(s) &= \frac{1}{s^2 + s + 1} V_S(s) \\ &= \frac{1}{s^2 + s + 1} \cdot \frac{1}{(s+1)^2 + 1} \text{ (V)} \end{aligned}$$


~~V(s) =~~

$$\begin{aligned} v(t) &= e^{-t} \cos t + \frac{\sqrt{2}}{3} e^{-\frac{t}{2}} \sin(\frac{\sqrt{2}}{2}t) - e^{-\frac{t}{2}} \cos(\frac{\sqrt{2}}{2}t) \text{ (V)} \\ &= e^{-t} \cos t + \frac{2\sqrt{2}}{3} e^{-\frac{t}{2}} \cos(\frac{\sqrt{2}}{2}t - 150^\circ) \text{ (V)} \end{aligned}$$

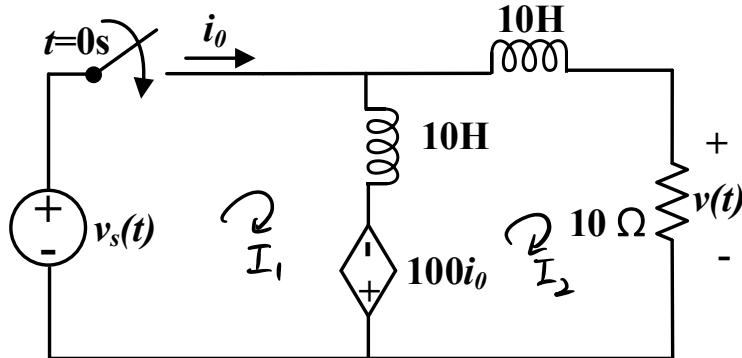4. For the following circuit,  $v_s(t) = 10\cos t$  V, and the switch closed immediately at  $t=0$ s. There is no energy stored in the circuit before  $t=0$ s. Please
- Use **phasor method** to find the **steady-state** for the voltage of  $v(t)$ .
  - Use **Laplace domain method** to find  $v(t)$  for  $t>0$ s and compare the results from (a).



Phasor

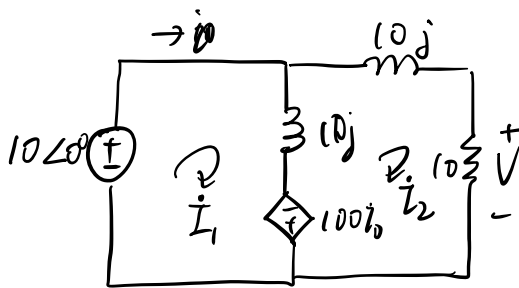

$$\begin{cases} (\dot{I}_1 - \dot{I}_2) 10j = 100\dot{I}_1 + 10\angle 0^\circ \\ 100\dot{I}_1 + (\dot{I}_2 - \dot{I}_1) 10j + 10j\dot{I}_2 + 10\dot{I}_2 = 0 \end{cases}$$

$$(10 + 10j) \dot{I}_2 = 10\angle 0^\circ$$

$$\begin{aligned} \dot{I}_2 &= \frac{10\angle 0^\circ}{10 + 10j} \\ &= \frac{\sqrt{2}}{2} \angle -45^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} V &= 10 \cdot \frac{\sqrt{2}}{2} \angle -45^\circ \text{ V} \\ &= 5\sqrt{2} \angle -45^\circ \text{ V} \\ &= 5\sqrt{2} \cos(t - 45^\circ) \text{ V} \end{aligned}$$

Laplace

$$V_s = 10 \cos t = \frac{10s}{s^2 + 1} \text{ V}$$

$$\textcircled{+} \begin{cases} 10s(I_1(s) - I_2(s)) = 100I_1(s) + V_s \\ 100I_1(s) + 10s[I_2(s) - I_1(s)] + 10sI_2(s) + 10I_2(s) = 0 \end{cases}$$

$$(10s + 10)I_2(s) = \frac{10s}{1 + s^2}$$

$$I_2(s) = \frac{10s}{(s^2 + 1)(10 + 10s)}$$

$$\text{transient: } -5e^{-t} \quad \checkmark$$

$$\text{steady-state: } 5\sqrt{2} \cos(t - 45^\circ) \text{ V} \quad \checkmark$$

$$i_2(t) = -\frac{1}{2}e^{-t} + \frac{\sqrt{2}}{2} \cos(t - 45^\circ) \text{ A}$$

$$V(t) = -5e^{-t} + 5\sqrt{2} \cos(t - 45^\circ) \text{ V } (t \geq 0)$$