





# Lecture 10

## - Three-Phase Circuits
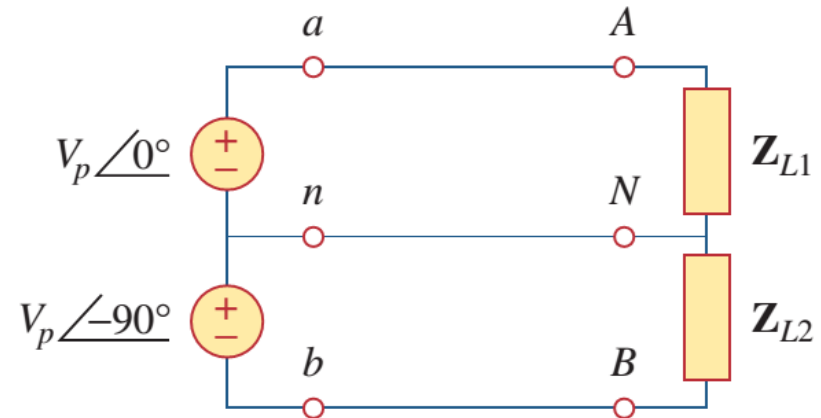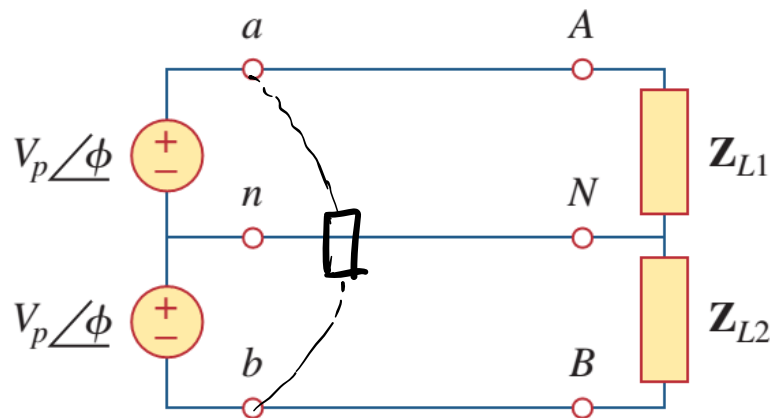
# Single phase vs. Polyphase

- Single-phase power supply
  - For example, two 120V sources with the same phase are connected in series.
  - This allows for appliances to use either 120 or 240V
- Circuits that operate with multiple sources, at the same frequency but *at different phases* are called polyphase.





# Outline--Three-Phase Circuits


- Balanced Three-Phase System
  - Balanced sources ←
  - Balanced loads ←
- Circuit analysis ←
  - Phase voltage/current
  - Line voltage/current



# Balanced Three-Phase Sources

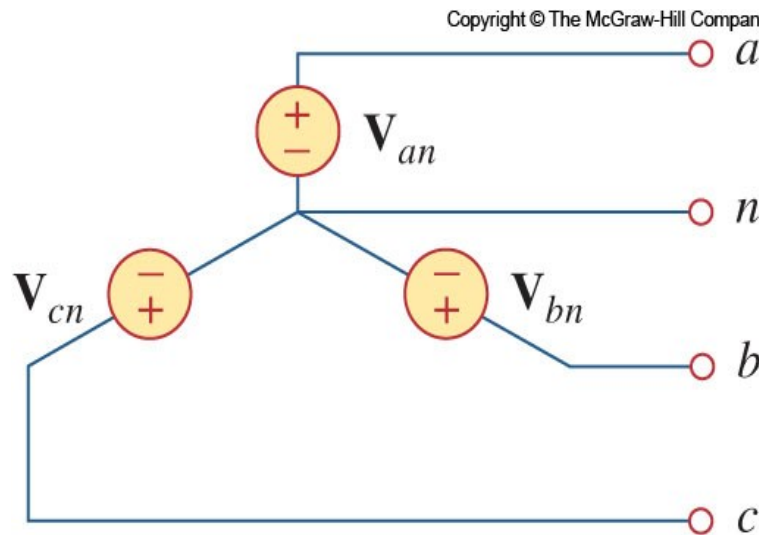
## Connecting the Sources

- Three phase voltage sources can be connected by either four or three wire configurations.
  - Four-wire system accomplished using a Y(Wye) connected source.
  - Three-wire configuration accomplished by Delta connected source.



(a)
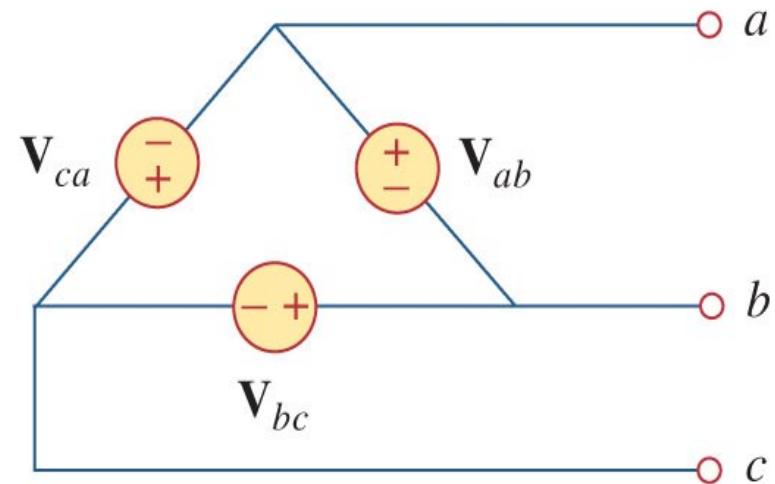
$$\begin{aligned}\dot{V}_{an} &= V_p \angle 0^\circ \\ \dot{V}_{bn} &= V_p \angle -120^\circ \\ \dot{V}_{cn} &= V_p \angle -240^\circ = V_p \angle +120^\circ\end{aligned}$$




(b)

$$\begin{aligned}\dot{V}_{ab} &= V_p \angle 0^\circ \\ \dot{V}_{bc} &= V_p \angle -120^\circ \\ \dot{V}_{ca} &= V_p \angle -240^\circ = V_p \angle +120^\circ\end{aligned}$$


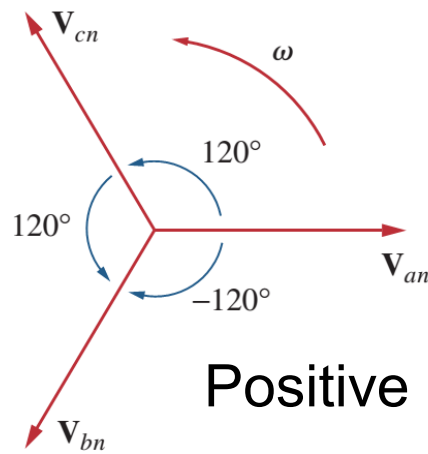
# Balanced Three-Phase Sources

- Balanced phase voltage are equal in magnitude and are out of phase with each other by 120deg
- It's easy to know  $\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn} = 0$
- Two sequences for the phases:



Positive

$$\vec{V}_{an} = V_p \angle 0^\circ$$

$$\vec{V}_{bn} = V_p \angle -120^\circ$$


$$\vec{V}_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$

$$V_p \angle 10^\circ$$

$$V_p \angle -110^\circ$$

$$V_p \angle 130^\circ$$

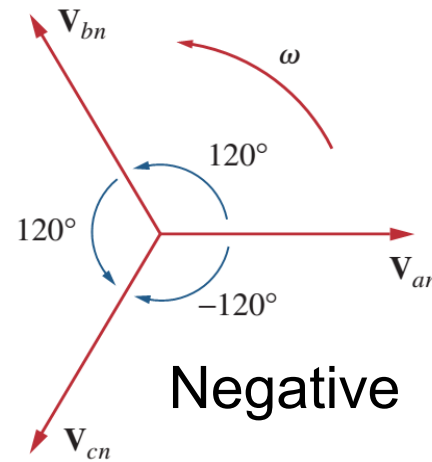$a \rightarrow b \rightarrow c \rightarrow a \rightarrow b \rightarrow c$



Negative

$$\vec{V}_{an} = V_p \angle 0^\circ$$



$$\vec{V}_{cn} = V_p \angle -120^\circ$$

$$\vec{V}_{bn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$

$a \rightarrow c \rightarrow b \rightarrow a \rightarrow c \rightarrow b$
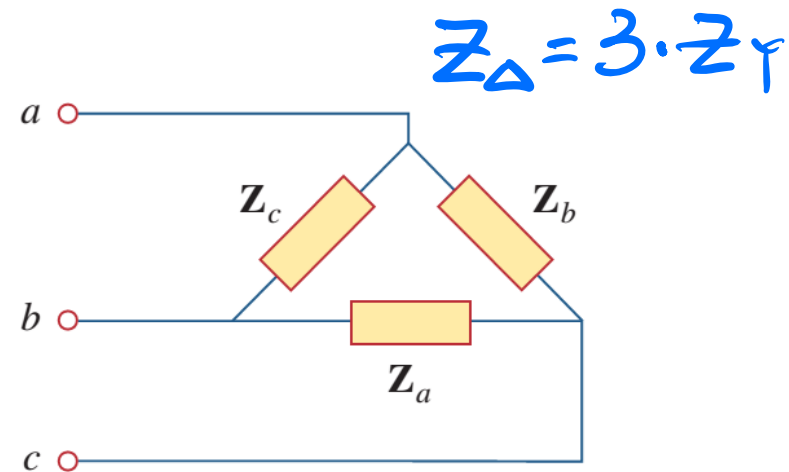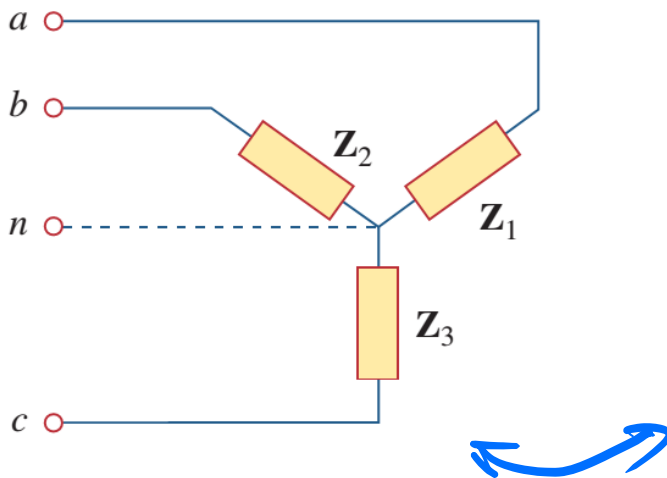
# Balanced Loads


- A balanced load means the same impedance for each load.  
*-- Impedance are equal in magnitude and in phase*
- They may also be connected in either Delta or wye
  - For a balanced wye connected load:  $Z_1 = Z_2 = Z_3 = Z_Y$
  - For a balanced delta connected load:  $Z_a = Z_b = Z_c = Z_\Delta$



- The load impedance per phase for the above configurations can be **interchanged**.



# Source-Load configurations

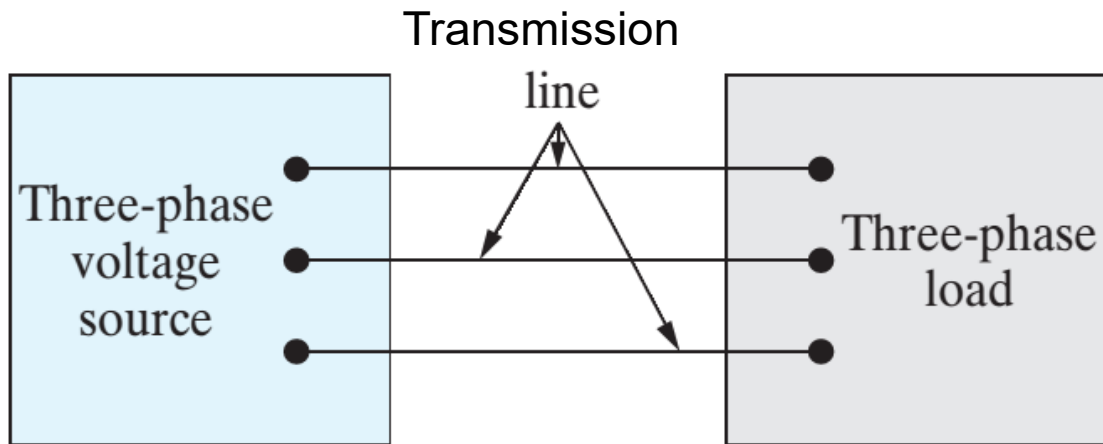


Source	Load
Y	Y
Y	$\Delta$
$\Delta$	Y
$\Delta$	$\Delta$



# Source-Load Configurations

Y-Y

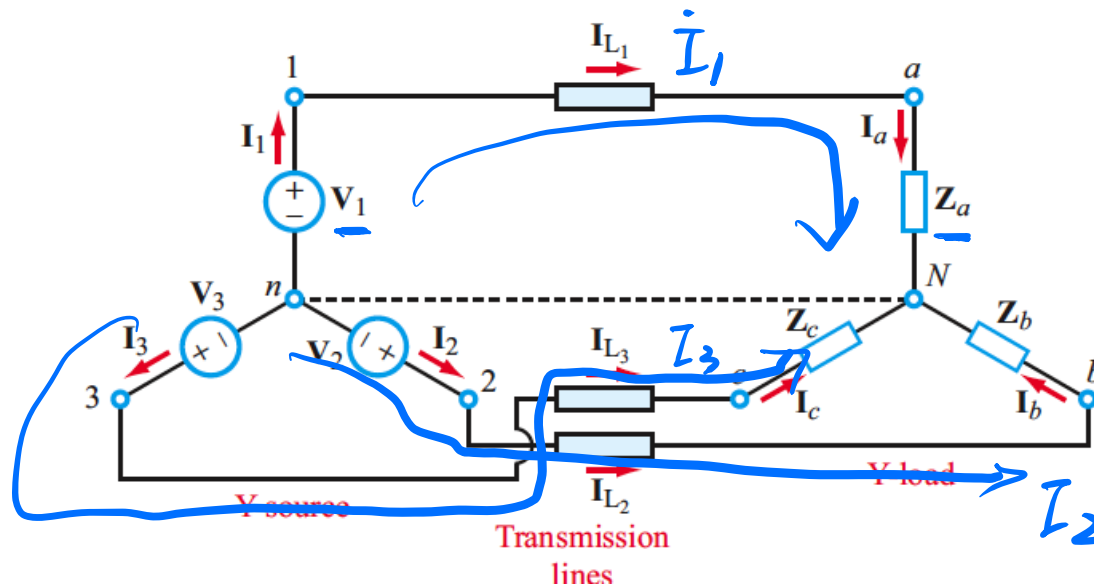


Load Phase Currents

$\underline{I_a}, \underline{I_b}, \underline{I_c}$   
(same as line currents  
 $\underline{I_{L1}}, \underline{I_{L2}}, \text{ and } \underline{I_{L3}}$ )

Load Phase Voltages

$\underline{V_{aN}}, \underline{V_{bN}}, \underline{V_{cN}}$

Y-Delta

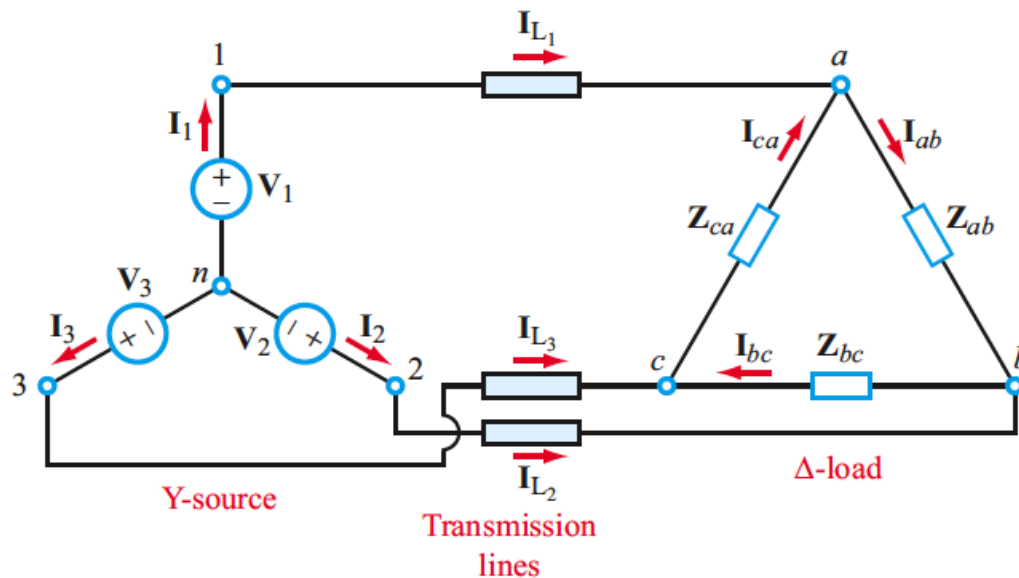

Load Phase Currents

$\underline{I_{ab}}, \underline{I_{bc}}, \underline{I_{ca}}$

Load Phase Voltages


$\underline{V_{ab}}, \underline{V_{bc}}, \underline{V_{ca}}$





# Source-Load Configurations (optional)

Delta-Y

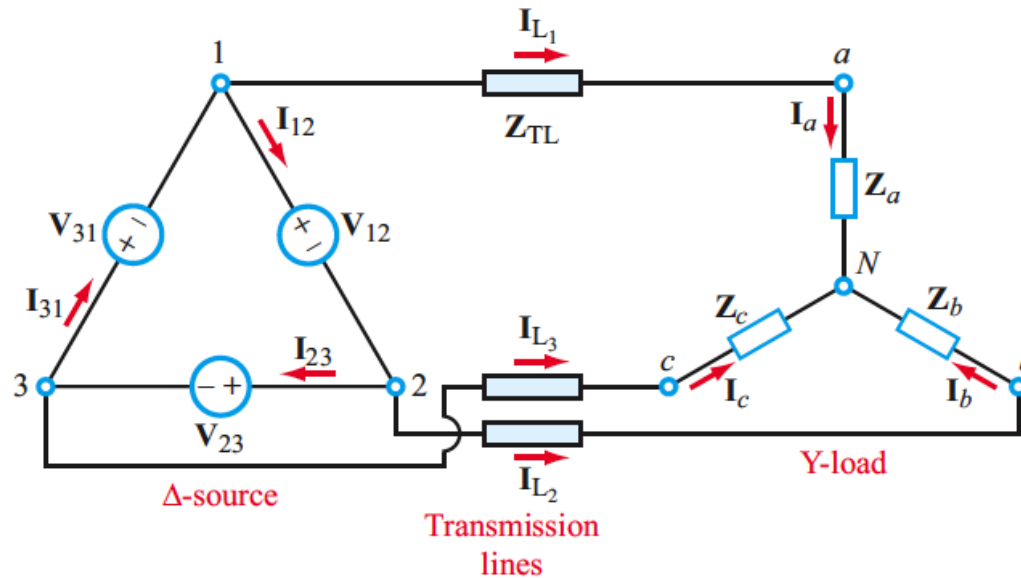


Load Phase Currents

$I_a, I_b, I_c$   
(same as line currents  
 $I_{L1}, I_{L2}, \text{ and } I_{L3}$ )

Load Phase Voltages

$V_{aN}, V_{bN}, V_{cN}$

Delta-Delta

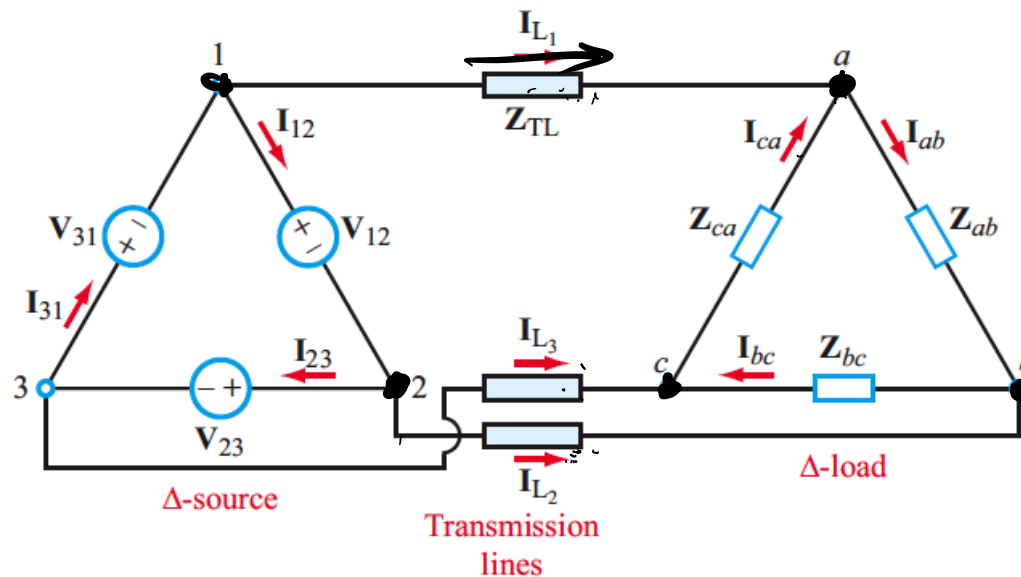

Load Phase Currents

$I_{ab}, I_{bc}, I_{ca}$

Load Phase Voltages


$V_{ab}, V_{bc}, V_{ca}$   
(same as source voltages  
if  $Z_{TL}$  is negligible)

# Balanced Y-Y connection


- The load impedances  $Z_Y$  will be assumed to be balanced.
  - This can be the source  $Z_s$ , line  $Z_l$  and load  $Z_L$  together.

$$Z_Y = Z_s + Z_\ell + Z_L$$

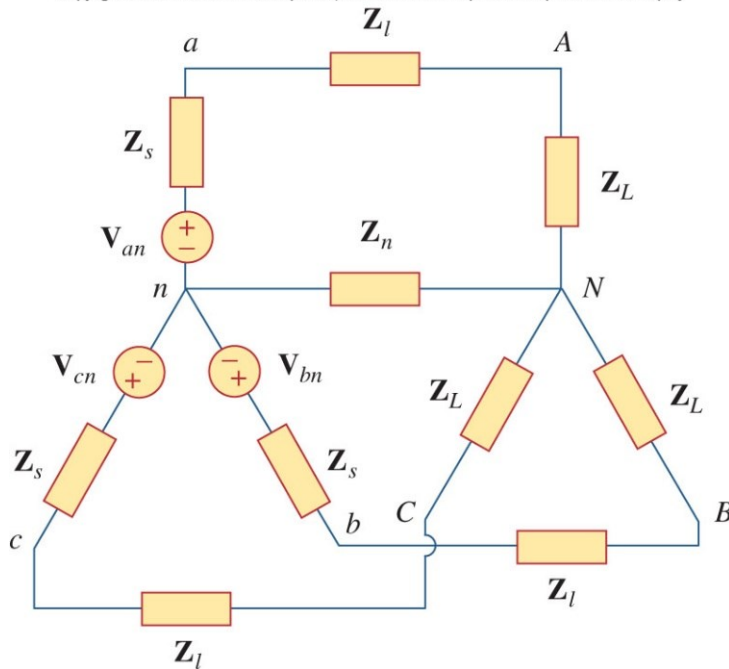Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



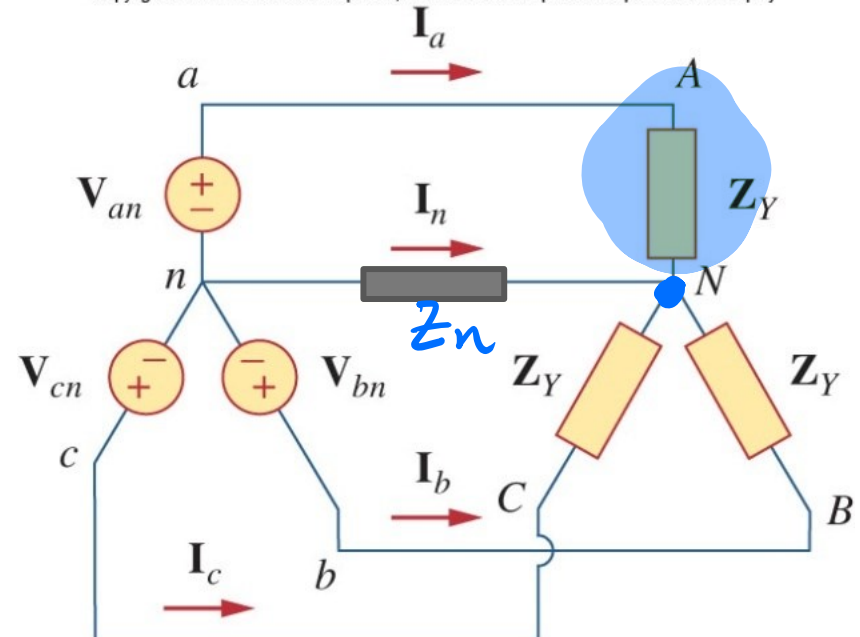Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Assume  $Z_n$  is minor value.

$$\dot{I}_a = \frac{\dot{V}_{an}}{Z_Y}$$

$$\dot{I}_b = \frac{\dot{V}_{bn}}{Z_Y}$$

$$\dot{I}_c = \frac{\dot{V}_{cn}}{Z_Y}$$

$$\dot{I}_a + \dot{I}_b + \dot{I}_c + \dot{I}_n = 0$$

$$0 + \underline{\dot{I}_n} = 0$$


# Phase Voltage & Line-to-Line Voltage

- Use the positive sequence:

Phase Voltage


$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

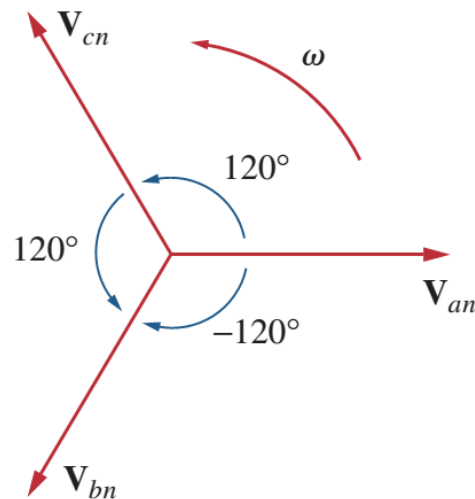


$$I_a = \frac{V_{an}}{Z_Y}$$

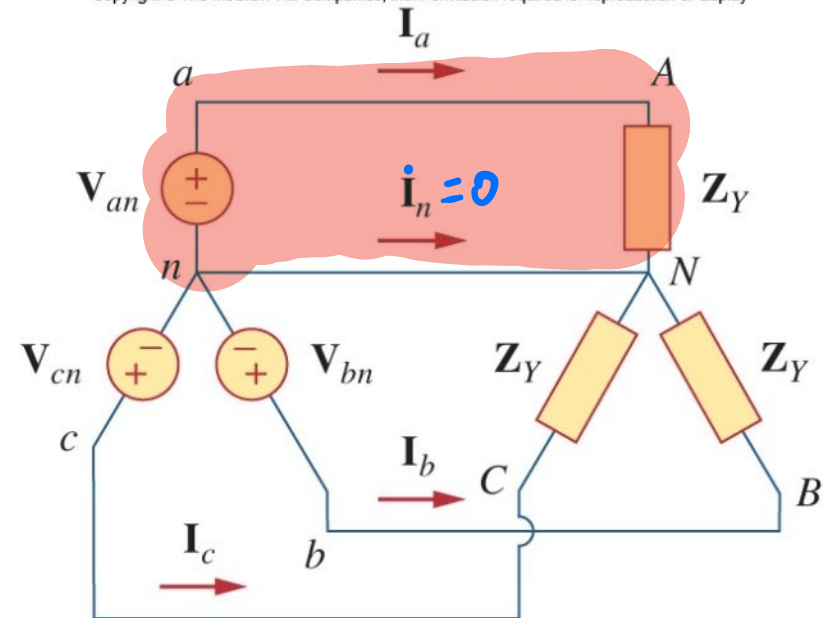Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



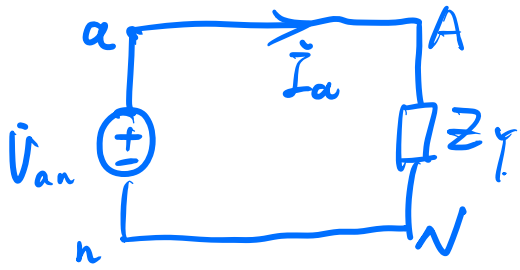- The line to line voltages (or just line voltages in short):**



$$\dot{I}_a = \frac{\dot{V}_{an}}{Z_Y}$$


$$\dot{I}_b = \dot{I}_a \cdot 1 \angle -120^\circ$$

$$\dot{I}_c = \dot{I}_b \cdot 1 \angle -120^\circ$$


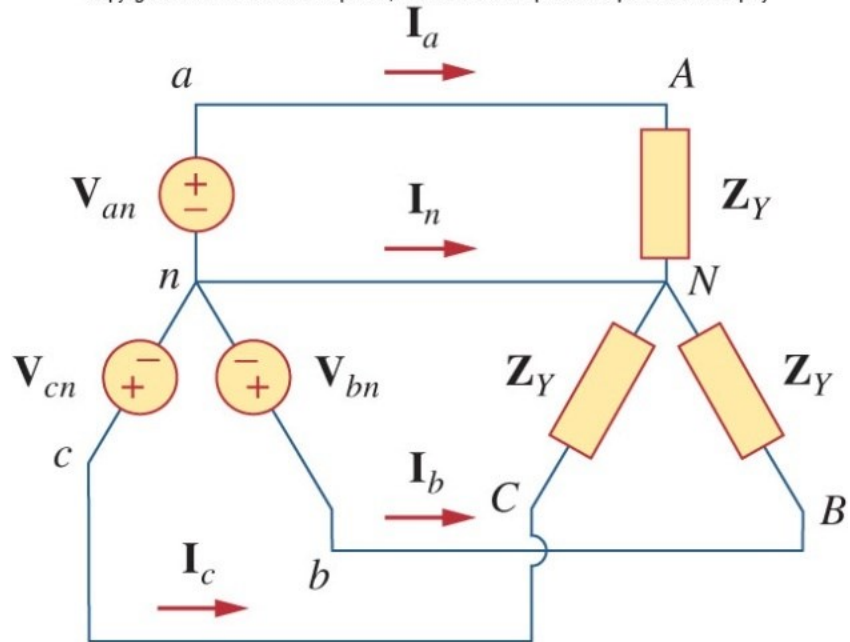
# Line Currents


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






## Example

- Calculate the line currents.


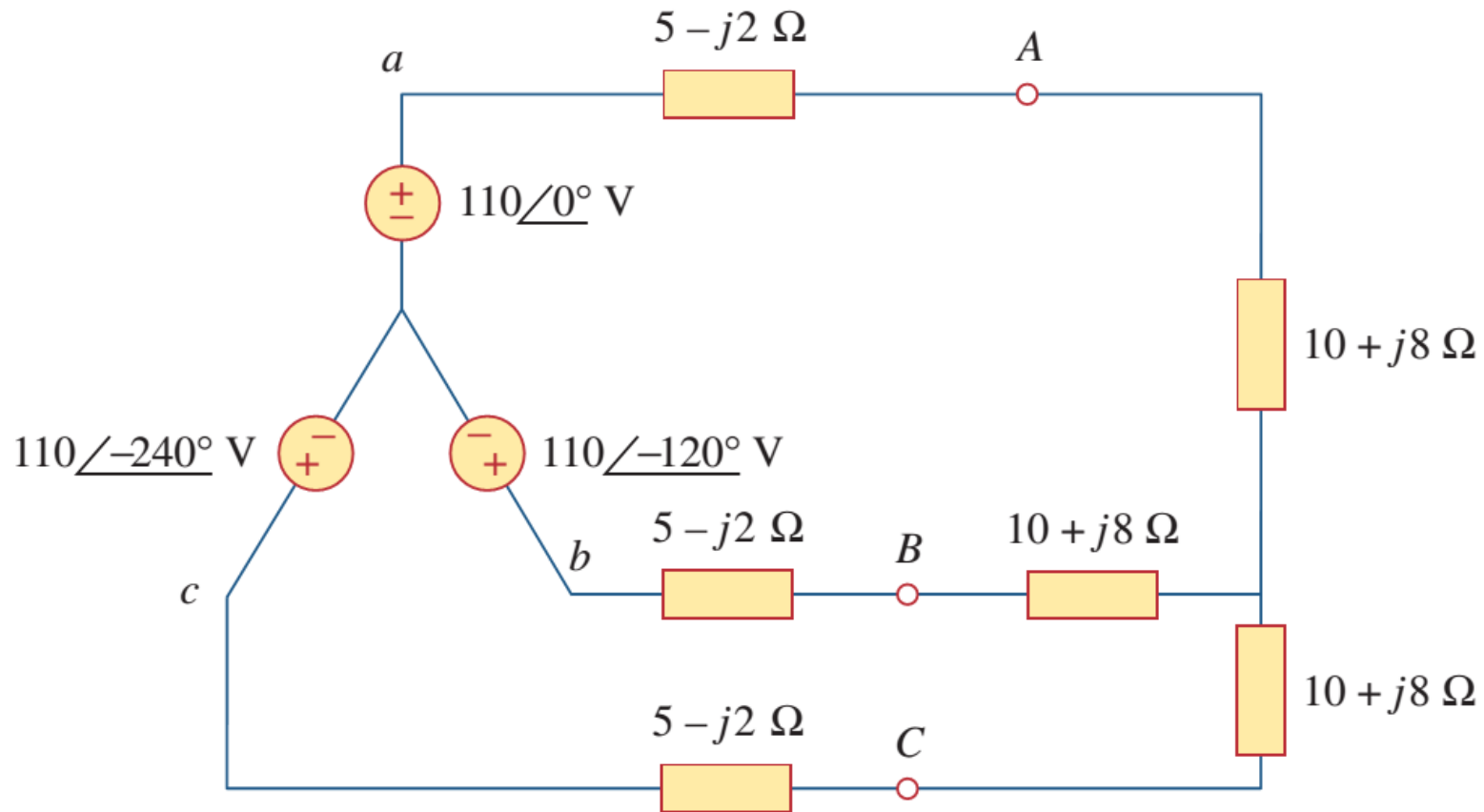






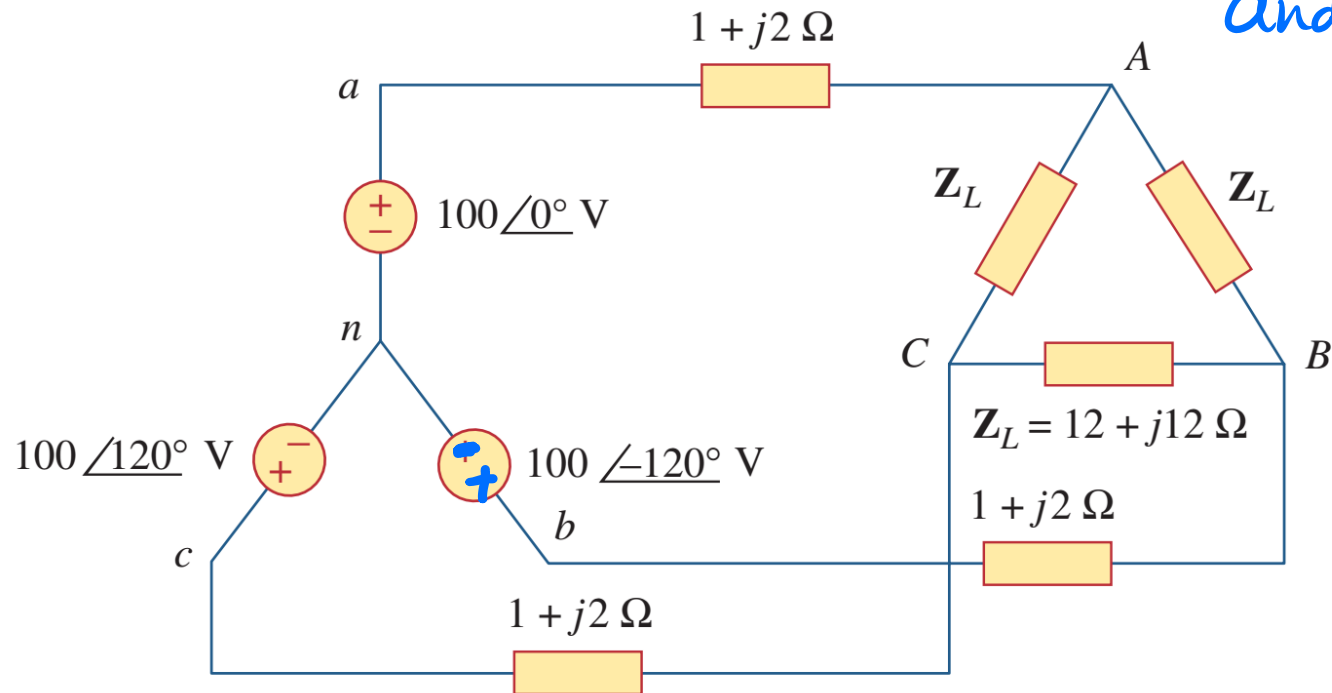**Wye- $\Delta$**  find complex power for each  $Z_L$ ?  
and complete Load.?





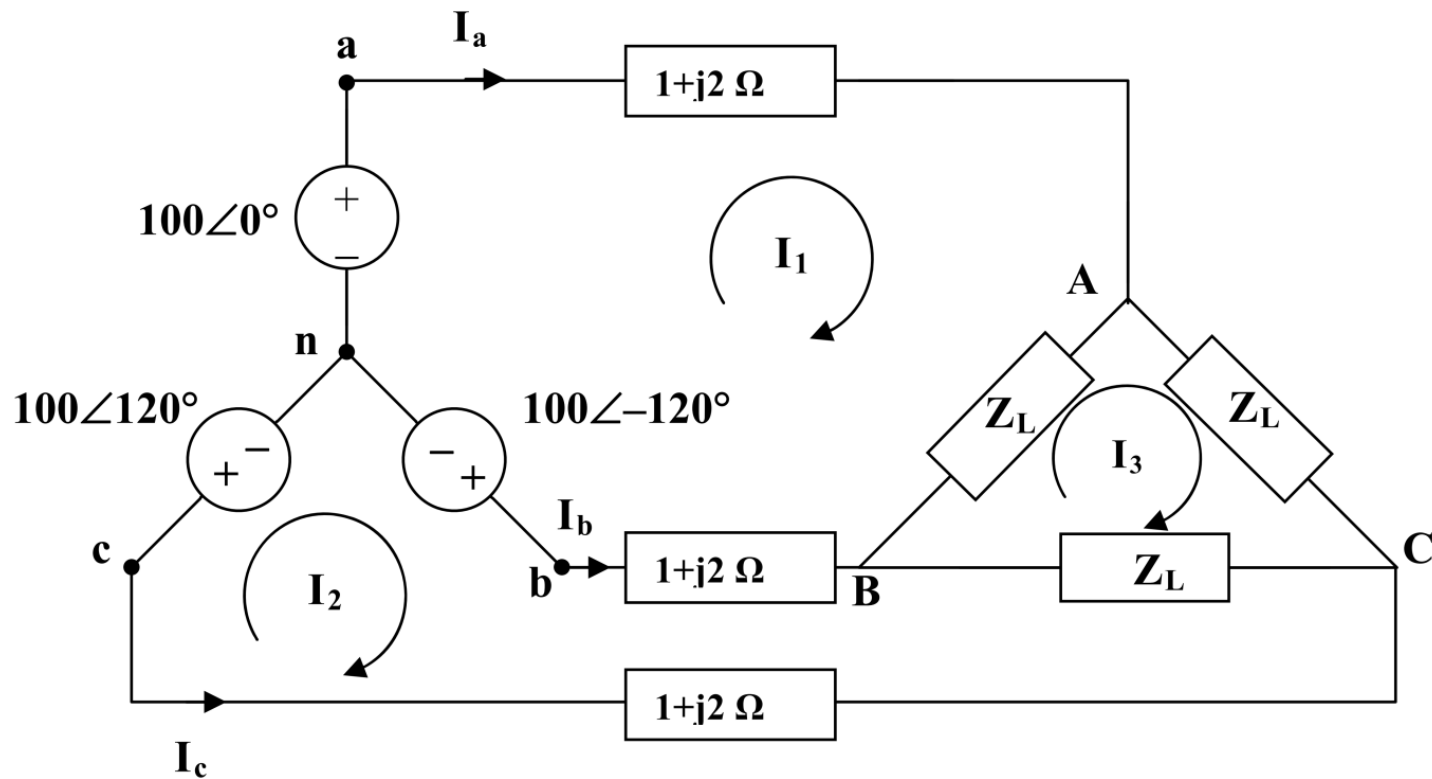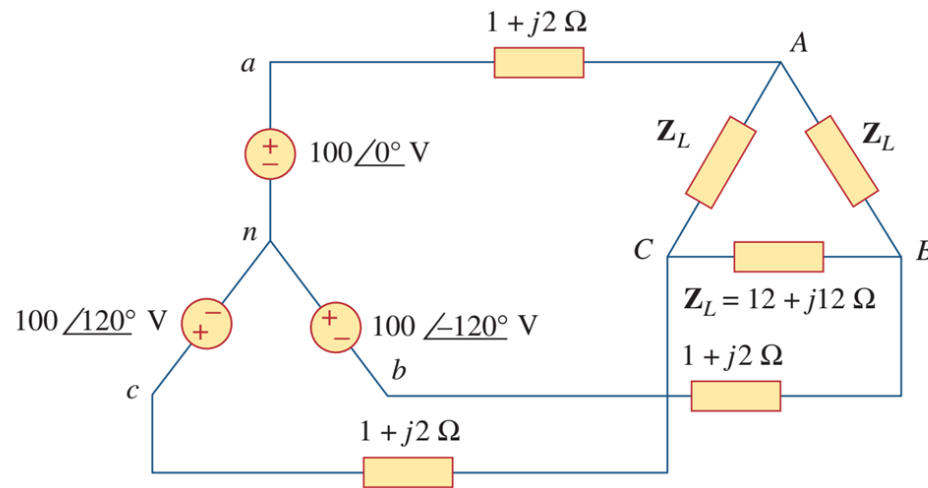

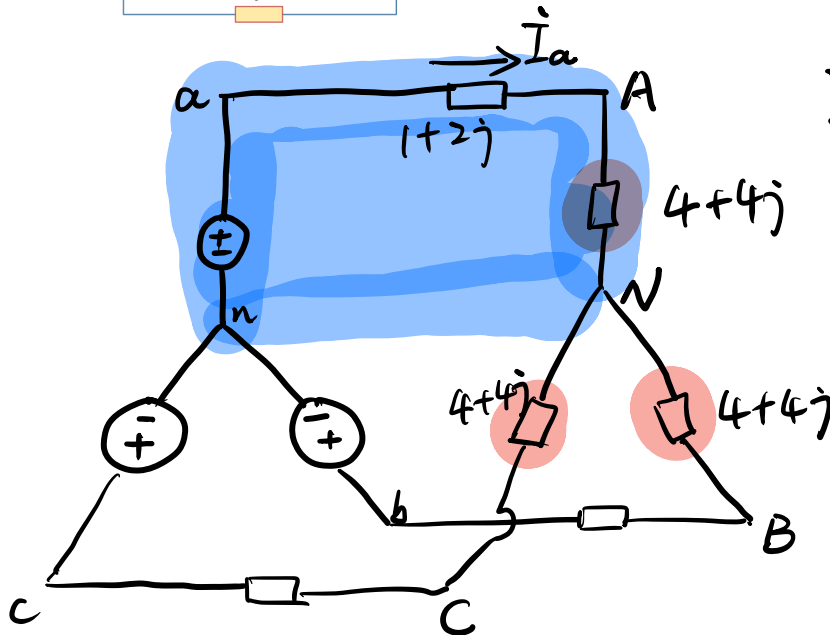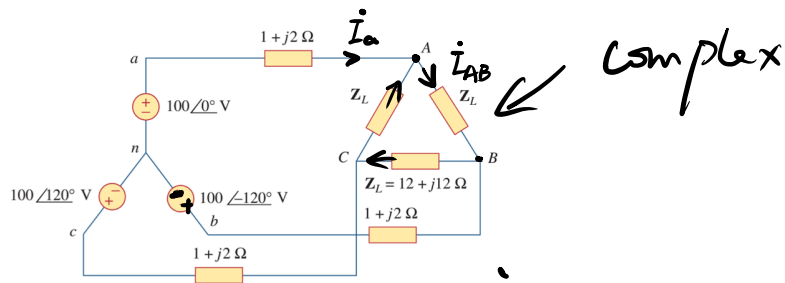

$$\dot{I}_a = \frac{\dot{V}_{an}}{Z_{total}^{IP}} = \frac{\dot{V}_{an}}{1 + j2 + 4 + 4j}$$

$$= \frac{100 \angle 0^\circ}{5 + 6j} = 12.8 \angle -50.19^\circ$$

$$\dot{I}_b = \dot{I}_a \cdot 1 \angle -120^\circ$$

$$= 12.8 \angle -170.19^\circ$$

$$\dot{I}_c = \dot{I}_b \cdot 1 \angle -120^\circ$$

$$= \dot{I}_a \cdot 1 \angle +120^\circ$$

$$= 12.8 \angle 69.81^\circ$$

A: KCL:

$$\dot{I}_a + \dot{I}_{CA} = \dot{I}_{AB} \quad (1)$$

$$\dot{I}_{AB} = \dot{I}_{BC} \cdot 1 \angle +120^\circ = \dot{I}_{CA} \cdot 1 \angle -120^\circ \quad (2)$$

$$\Rightarrow \dot{I}_{CA} = \frac{\dot{I}_a}{(1 \angle -120^\circ - 1)}$$

$$= 7.39 \angle 99.81^\circ$$

$$\tilde{S}_{1P} = \tilde{S}_{1P}^{CA} = |\dot{I}_{CA}|^2 \cdot Z_{CA}$$

$$= |\dot{I}_{CA}|^2 \cdot Z_L$$

$$= 7.39^2 \times (12 + 12j)$$

$$\tilde{S}_{3P} = 3 \times \tilde{S}_{1P} = \dots$$