

Homework 5

Due date: 17th, Nov.

Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

20pts

1. Given that the voltage and current of two-terminal elements adopt the passive sign convention, the instantaneous values are expressed as:

(1) $v(t) = 15\cos(400t + 30^\circ) \text{ V}$, $i(t) = 3\sin(400t + 30^\circ) \text{ A}$;

(2) $v(t) = 8\sin(500t + 50^\circ) \text{ V}$, $i(t) = 2\sin(500t + 140^\circ) \text{ A}$;

(3) $v(t) = 8\cos(250t + 60^\circ) \text{ V}$, $i(t) = 5\sin(250t + 150^\circ) \text{ A}$;

(a) Transform the three voltage & current pairs into phasors.

(b) Try to determine whether the element is a resistor, inductor or capacitor, and determine its value ($R=?$, $C=?$, $L=?$) for (1), (2), and (3), respectively.

Solutions:

(a) (1) $\dot{V} = 15\angle 30^\circ$; $\dot{I} = 3\angle -60^\circ$ at $\omega = 400 \text{ rad/s}$

(2) $\dot{V} = 8\angle -40^\circ$; $\dot{I} = 2\angle 50^\circ$ at $\omega = 500 \text{ rad/s}$

(3) $\dot{V} = 8\angle 60^\circ$; $\dot{I} = 5\angle 60^\circ$ at $\omega = 250 \text{ rad/s}$

(b) ① $Z_{(1)} = \frac{\dot{V}}{\dot{I}} = \frac{15\angle 30^\circ}{3\angle -60^\circ} = 5\angle 90^\circ$ (Inductor)

$$j\omega L = 5j \Rightarrow L = \frac{5}{400} \text{ H} = 0.0125 \text{ H}$$


② $Z_{(2)} = \frac{\dot{V}}{\dot{I}} = \frac{8\angle -40^\circ}{2\angle 50^\circ} = 4\angle -90^\circ$ (Capacitor)

$$-\frac{j}{\omega C} = -4j \Rightarrow C = \frac{1}{4 \times 500} = 0.5 \text{ mF}$$

③ $Z_{(3)} = \frac{\dot{V}}{\dot{I}} = \frac{8\angle 60^\circ}{5\angle 60^\circ} = \frac{8}{5} \Omega = 1.6 \Omega$ (Resistor)

20 pts

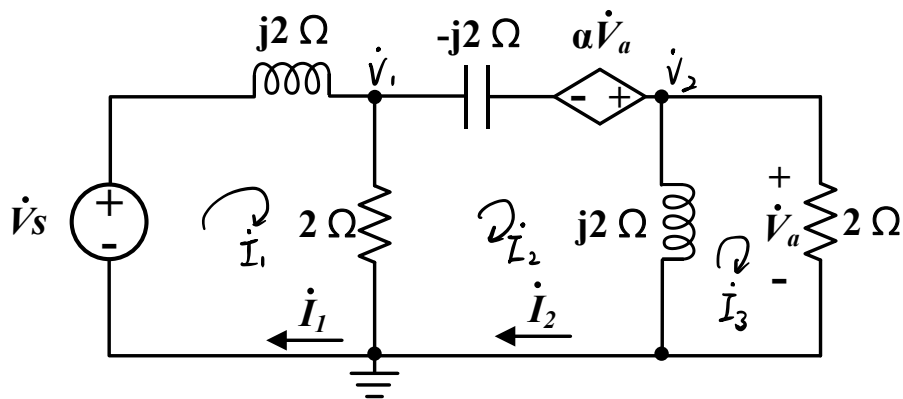2. Use nodal AND mesh analyze method to find \dot{V}_a , \dot{I}_1 and \dot{I}_2 for the circuit below, assuming that $\dot{V}_S = 10 \angle 0^\circ \text{ V}$, $\alpha = 0.5$.



Mesh:

$$\begin{cases} j2 \cdot \dot{I}_1 + (\dot{I}_1 - \dot{I}_2) \cdot 2 = \dot{V}_S & \dots \textcircled{1} \\ (\dot{I}_2 - \dot{I}_1) 2 - j2 \cdot \dot{I}_2 - \alpha \dot{V}_a + j2 \cdot (\dot{I}_2 - \dot{I}_3) = 0 & \dots \textcircled{2} \\ j2 \cdot (\dot{I}_3 - \dot{I}_2) + \dot{I}_3 \cdot 2 = 0 & \dots \textcircled{3} \\ \dot{V}_a = 2\dot{I}_3 & \dots \textcircled{4} \end{cases}$$

$$\begin{cases} (2+2j)\dot{I}_1 - 2\dot{I}_2 = 10 \angle 0^\circ \\ -2\dot{I}_1 + 2\dot{I}_2 - (1+2j)\dot{I}_3 = 0 \\ -2j\dot{I}_2 + (2+2j)\dot{I}_3 = 0 \end{cases} \Rightarrow \begin{aligned} \dot{I}_1 &= 6.52 \angle -57.53^\circ \text{ A} \\ \dot{I}_2 &= 4.47 \angle -26.57^\circ \text{ A} \\ \dot{I}_3 &= 3.16 \angle 18.43^\circ \text{ A} \end{aligned}$$

$$\dot{V}_a = 2\dot{I}_3 = 6.32 \angle 18.43^\circ \text{ V}$$


Nodal:

$$\begin{cases} \frac{\dot{V}_S - \dot{V}_1}{j2} + \frac{0 - \dot{V}_1}{2} + \frac{\dot{V}_2 - \alpha \dot{V}_a - \dot{V}_1}{-j2} = 0 \\ \frac{\dot{V}_2 - \alpha \dot{V}_a - \dot{V}_1}{-j2} + \frac{\dot{V}_2}{j2} + \frac{\dot{V}_2}{2} = 0 \\ \dot{V}_2 = \dot{V}_a \end{cases}$$

20pts

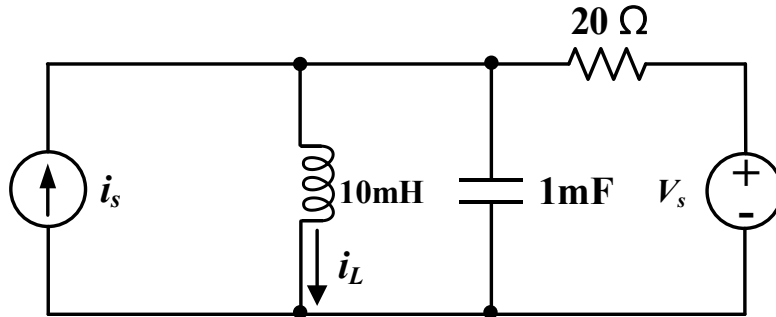
3. Using superposition method to find $i_L(t)$, assuming that $i_s(t) = 10\sqrt{2}\cos 100t$ A,

$$V_s(t) = 100\sqrt{2}\cos 1000t \text{ V}$$



Solution:

①

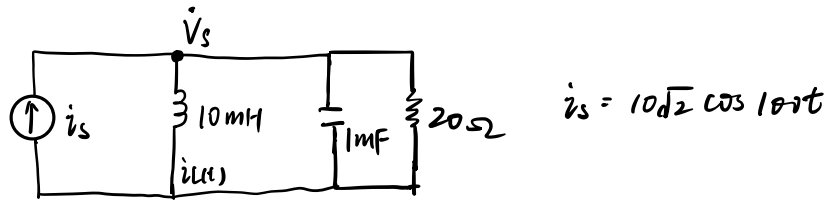

$$\dot{I}_s = 10\sqrt{2} \angle 0^\circ$$

$$Z_L = 20 \Omega \quad (\omega = 100)$$

$$Z_C = \frac{1}{j\omega C} = -\frac{1}{10^{-3} \times 100} j \Omega$$

$$= -10j \Omega$$


$$Z_L = j\omega L = j \cdot 100 \times 10 \times 10^{-3} \Omega = j \Omega$$

$$\begin{cases} \frac{\dot{V}_s}{20} + \frac{\dot{V}_s}{j} - \frac{\dot{V}_s}{10j} = \dot{I}_s \\ \dot{I}_{L1} = \dot{V}_s / j \text{ A} \end{cases}$$

$$\Rightarrow \dot{I}_{L1} = 15.69 \angle -3.18^\circ \text{ A}$$

$$i_{L1}(t) = 15.69 \cos(100t - 3.18^\circ) \text{ A}$$

②

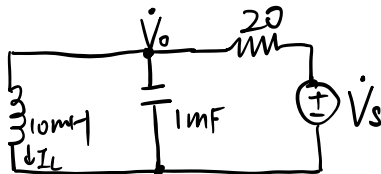

$$\dot{V}_s = 100\sqrt{2} \angle 0^\circ$$

$$Z_C = -\frac{j}{\omega C} = -j \Omega$$

$$Z_L = j\omega L = 10j \Omega$$


$$\frac{\dot{V}_s - \dot{V}_0}{20} = \frac{\dot{V}_0}{-j} + \frac{\dot{V}_0}{10j}$$

$$\dot{I}_{L2} = \frac{\dot{V}_0}{10j} \approx 0.78 \angle -176.82^\circ$$

$$i_{L2}(t) = 0.78 \cos(1000t - 176.82^\circ) \text{ A}$$


$$\Rightarrow i_L(t) = i_{L1}(t) + i_{L2}(t) = 15.69 \cos(100t - 3.18^\circ) + 0.78 \cos(1000t - 176.82^\circ) \text{ A}$$

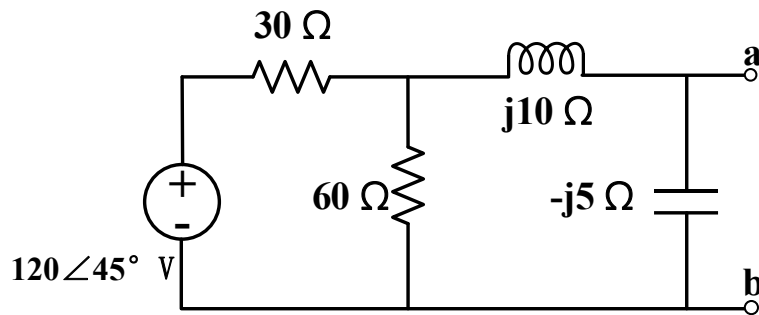4. For the circuit below, please find the Thevenin equivalent circuit with respect to node **a** and node **b**.




$$\begin{aligned}
 R_{Th} &= -j5\Omega \parallel (j10\Omega + 30\Omega \parallel 60\Omega) \\
 &= -j5\Omega \parallel (20 + 10j)\Omega \\
 &= 5.42 \angle -77.47^\circ \Omega \quad 1.17 - 5.29j\Omega
 \end{aligned}$$

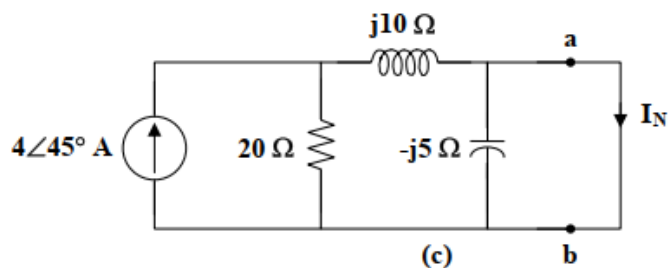To find V_{th} and I_N , we transform the voltage source and combine the 30Ω and 60Ω resistors. The result is shown in Fig. (c).




$$\begin{aligned}
 I_N &= \frac{20}{20 + j10} (4\angle 45^\circ) = \frac{2}{5} (2 - j)(4\angle 45^\circ) \\
 &= 3.578 \angle 18.43^\circ \text{ A}
 \end{aligned}$$
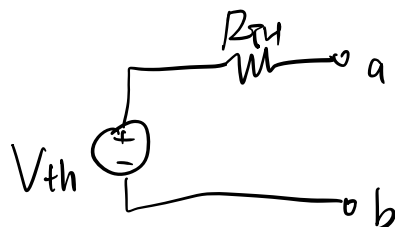
$$\begin{aligned}
 V_{th} &= Z_{th} I_N = (5.423 \angle -77.47^\circ) (3.578 \angle 18.43^\circ) \\
 &= 19.4 \angle -59^\circ \text{ V}
 \end{aligned}$$



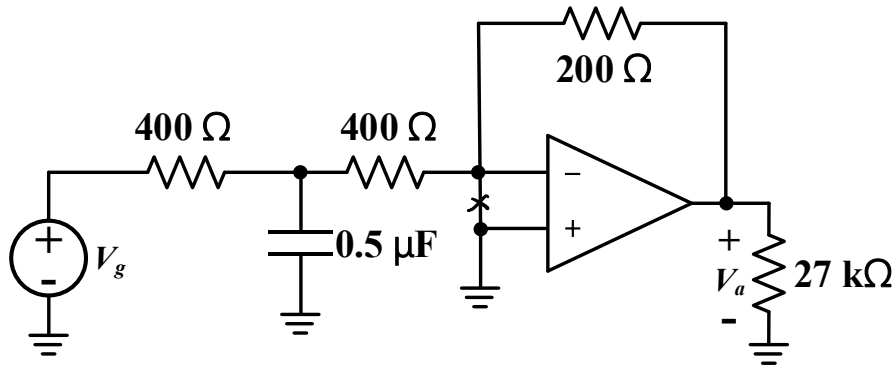5. As shown in the figure, $V_g = 20\cos(5000t)$ V. Please find the steady state expression for $V_a(t)$. The operational amplifier works in its linear region.



$$V_g = 20/\underline{0^\circ} \text{ V}; \quad \frac{1}{j\omega C} = -j400 \Omega$$

Let V_a = voltage across the capacitor, positive at upper terminal
Then:

$$\frac{V_a - 20/\underline{0^\circ}}{400} + \frac{V_a}{-j400} + \frac{V_a}{400} = 0; \quad \therefore V_a = (8 - j4) \text{ V}$$

$$\frac{0 - V_a}{400} + \frac{0 - V_o}{200} = 0; \quad V_o = -\frac{V_a}{2}$$

$$\therefore V_o = -4 + j2 = 4.47/\underline{153.43^\circ} \text{ V}$$

$$v_o = 4.47 \cos(5000t + 153.43^\circ) \text{ V}$$