

Homework 5

Due date: May.4th

Turn in your homework online before the class

Rules:

- Please work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1

[16 points]

- (a). The circuit is shown in **Fig 1:a**. Assume steady state of the circuit. Known that $u_S(t) = 1.5\sqrt{2}\cos(10^5 t + 60^\circ)$ V. Express $i_R(t)$, $i_L(t)$, $i_C(t)$, $i(t)$, in phasor domain.
- (b). The circuit is shown in **Fig 1:b**. Assume steady state of the circuit. Known that $i(t) = 1\cos(10^7 t + 90^\circ)$ A. Express $u_R(t)$, $u_L(t)$, $u_C(t)$, $u_S(t)$ in phasor domain..

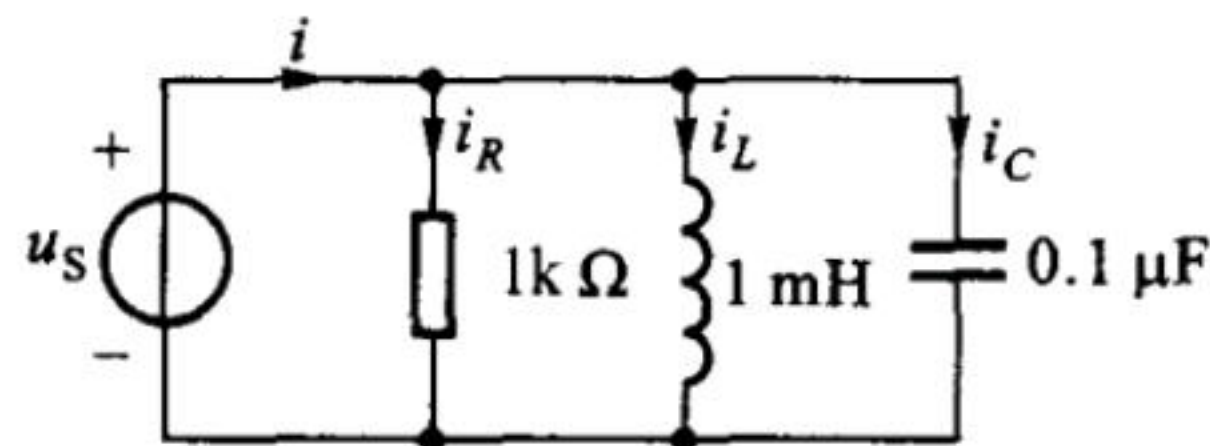


Figure 1: a

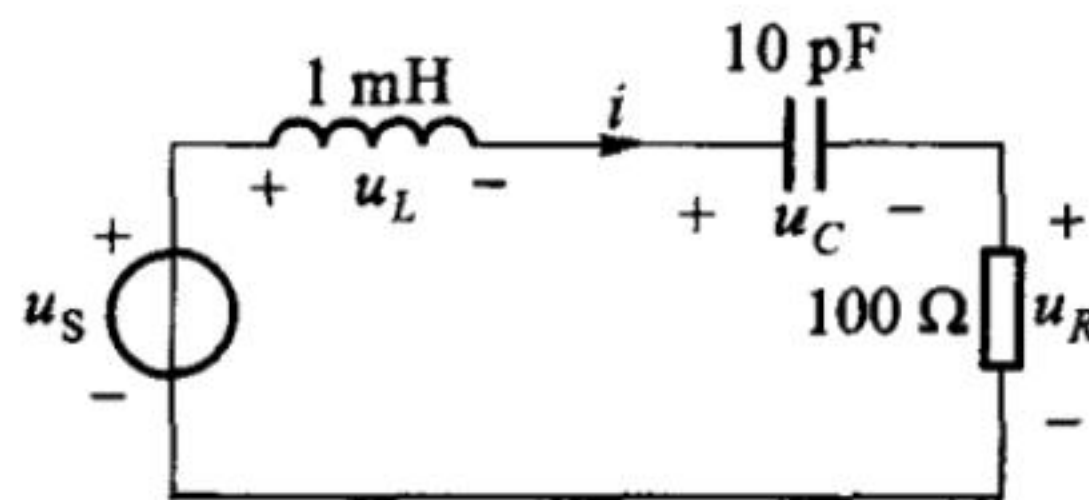


Figure 1: b

$$\begin{aligned}
 \text{(a)} \quad u_S(t) &\rightarrow \dot{U}_S = 1.5\sqrt{2} \angle 60^\circ \text{ V} \\
 \dot{I}_R &= \frac{\dot{U}_S}{R} = \frac{1.5 \angle 60^\circ}{1000} = 1.5 \times 10^{-3} \angle 60^\circ \text{ A} = 1.5\sqrt{2} \angle 60^\circ \text{ mA} = 2.12 \angle 60^\circ \text{ mA} \\
 \dot{I}_L &= \frac{\dot{U}_S}{j\omega L} = \frac{1.5 \angle 60^\circ}{j10^5 \times 10^{-3}} \text{ A} = 15 \times 10^{-3} \angle -30^\circ \text{ A} = 15\sqrt{2} \angle -30^\circ \text{ mA} = 21.21 \angle -30^\circ \text{ mA} \\
 \dot{I}_C &= j\omega C \dot{U}_S = j10^5 \times 10^{-7} \times 1.5 \angle 60^\circ \text{ A} = 15\sqrt{2} \angle 150^\circ \text{ mA} = 21.21 \angle 150^\circ \text{ mA} \\
 \dot{I} &= \dot{I}_R + \dot{I}_L + \dot{I}_C = 2.12 \angle 60^\circ \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b)} \quad i(t) &\rightarrow \dot{I} = 1 \angle 90^\circ \text{ A} = j1 \text{ A} \\
 \dot{U}_R &= R\dot{I} = j100 \text{ V} \\
 \dot{U}_L &= j\omega L \dot{I} = j10^7 \times 10^{-3} \times 1 \angle 90^\circ \text{ V} = 10^4 \angle 180^\circ \text{ V} \\
 \dot{U}_C &= \frac{1}{j\omega C} \dot{I} = 10^4 \angle 0^\circ \text{ V} \\
 \dot{U}_S &= \dot{U}_R + \dot{U}_L + \dot{U}_C = j100 \text{ V}
 \end{aligned}$$

2

[12 points] The circuit is shown in **Fig 2**. Use phasor approach to calculate the currents \dot{I}_R , \dot{I}_C , \dot{I}_L , and draw the phasor diagram of the above three currents.


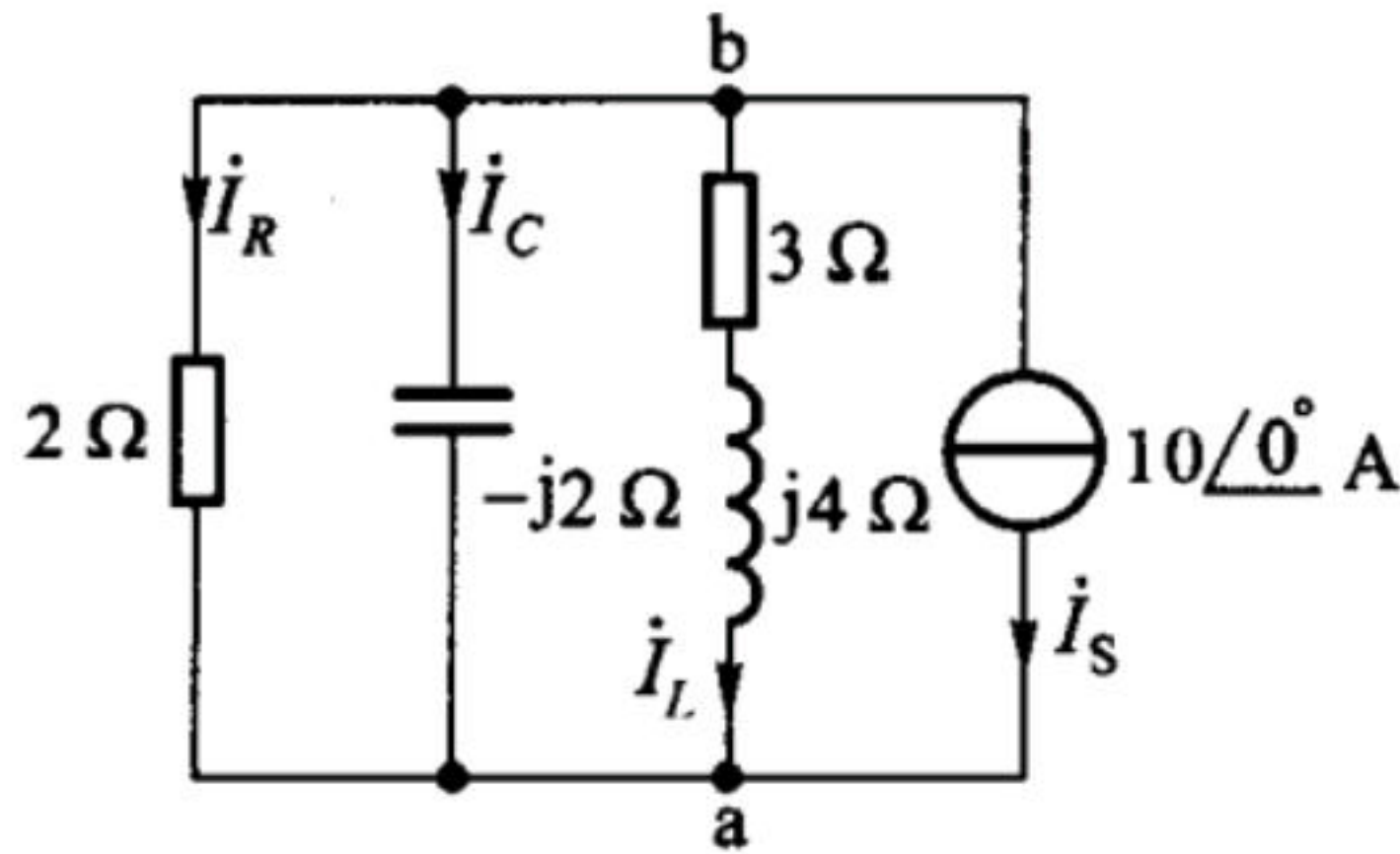


Figure 2

$$\dot{I}_R = \frac{0.5 \times (-10)}{0.5 + j0.5 + \frac{1}{3 + j4}} = \frac{-5}{0.62 + j0.34} = \frac{-5}{0.707 \angle 28.74^\circ} = 7.07 \angle 151.26^\circ \text{ A} \quad 2'$$

$$\dot{I}_C = \frac{j0.5 \times (-10)}{0.5 + j0.5 + \frac{1}{3 + j4}} = \frac{-j5}{0.707 \angle 28.74^\circ} = 7.07 \angle -118.74^\circ \text{ A} \quad 2'$$
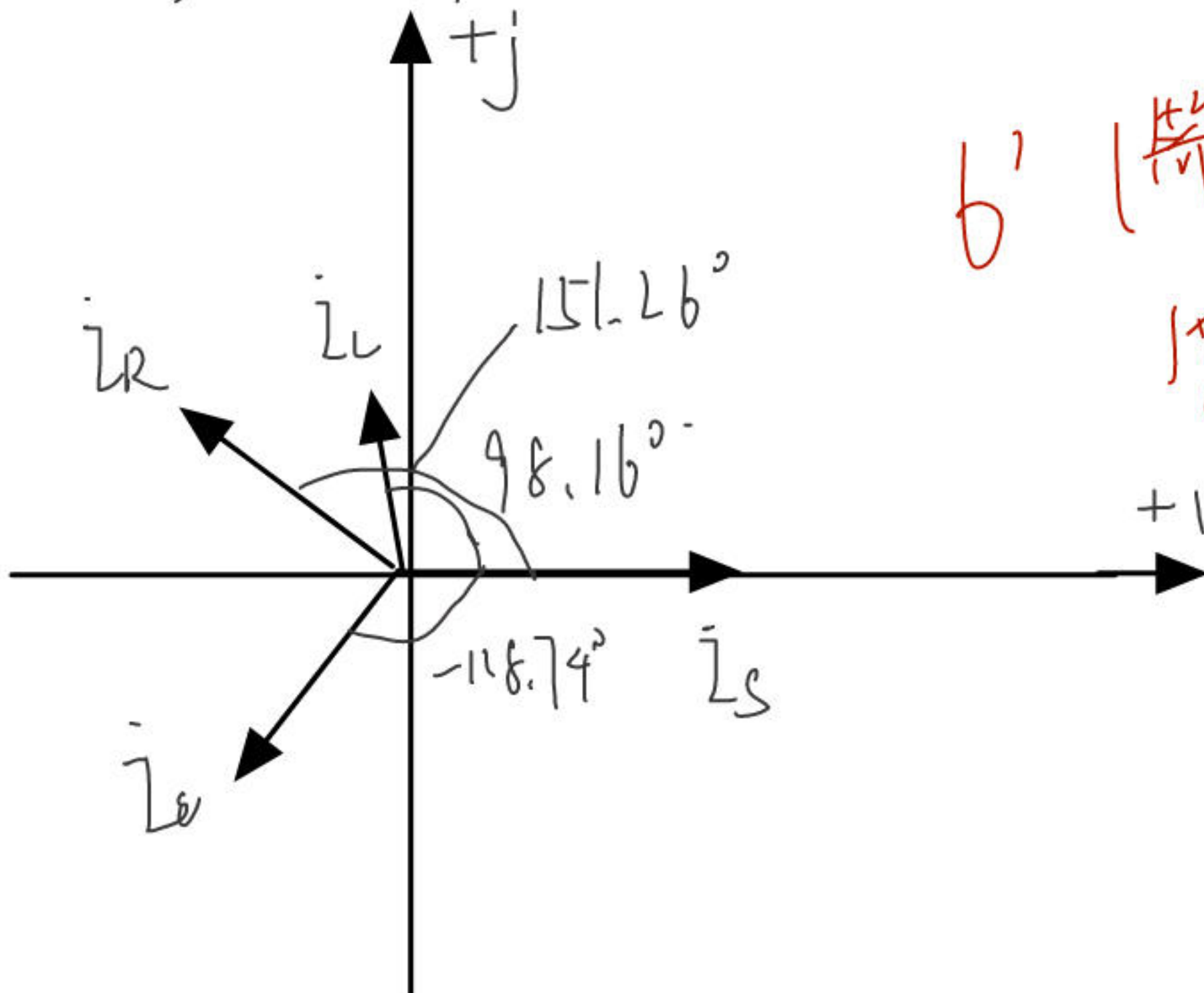
$$\dot{I}_L = \frac{\frac{1}{3 + j4} \times (-10)}{0.5 + j0.5 + \frac{1}{3 + j4}} = \frac{2 \angle 126.9^\circ}{0.707 \angle 28.74^\circ} = 2.82 \angle 98.16^\circ \text{ A} \quad 2'$$



6' (箭头长度、角度、相对位置
需调节即可得分)

3

[10 points] The circuit is shown in **Fig 3**. $\dot{U}_S = 24\angle 60^\circ \text{V}$, $\dot{I}_S = 6\angle 0^\circ \text{A}$. Use mesh analysis to calculate \dot{I}_1 and \dot{I}_2 .

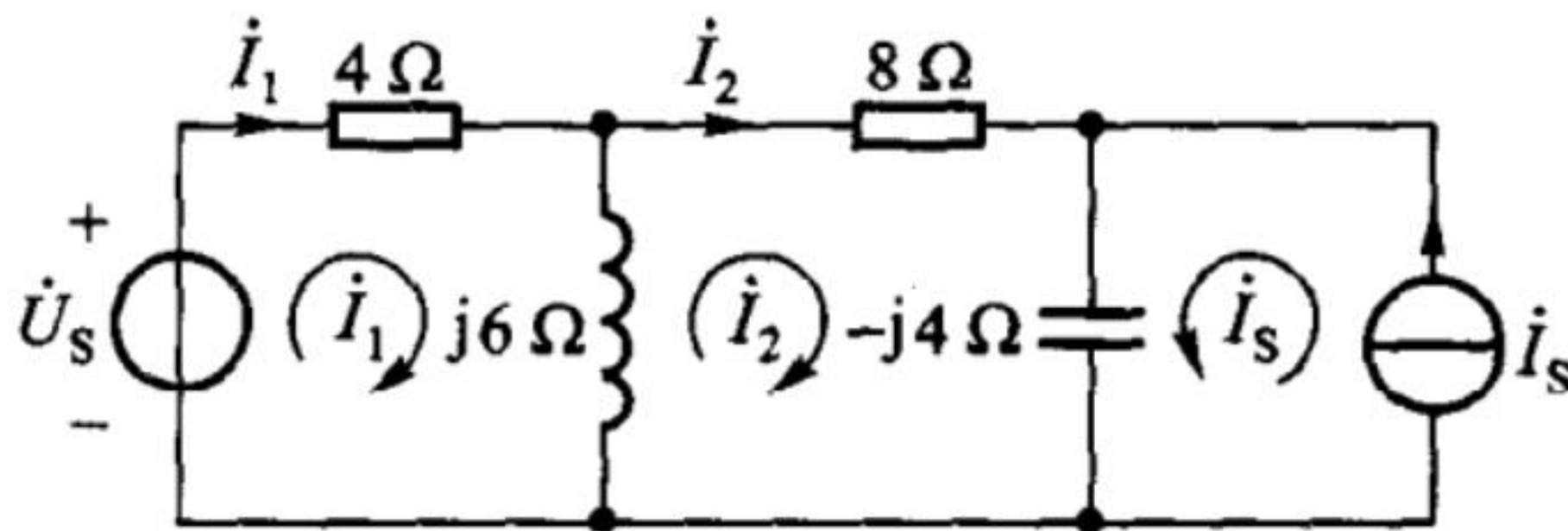


Figure 3

$$\begin{cases} (4+j6)\dot{I}_1 - j6\dot{I}_2 = 24\angle 60^\circ \\ -j6\dot{I}_1 + (8+j2)\dot{I}_2 - j4\dot{I}_S = 0 \\ \dot{I}_S = 6\angle 0^\circ \text{A} \end{cases} \Rightarrow \begin{cases} (4+j6)\dot{I}_1 - j6\dot{I}_2 = 12 + j20.8 \\ -j6\dot{I}_1 + (8+j2)\dot{I}_2 = j24 \end{cases}$$

4'

$$\dot{I}_1 = \frac{(12+j20.8)(8+j2) - 144}{(4+j6)(8+j2) + 36} \text{A}$$

$$= \frac{-89.6 + j190.4}{56 + j56} \text{A}$$

$$= \frac{210.4 \angle 115.2^\circ}{79.2 \angle 45^\circ} \text{A} = 2.66 \angle 70.2^\circ \text{A}$$

3'

$$\dot{I}_2 = \frac{j24 \times (4+j6) - (12+j20.8)(-j6)}{(4+j6)(8+j2) + 36} \text{A}$$

$$= \frac{317 \angle 48^\circ}{79.2 \angle 45^\circ} \text{A} = 4 \angle 3^\circ \text{A}$$

3'

4

[10 points] The circuit is shown in **Fig 4**. $\dot{U}_S = 10\angle 0^\circ \text{V}$, $\mu = 0.5$. Use nodal analysis to calculate \dot{U}_2 .

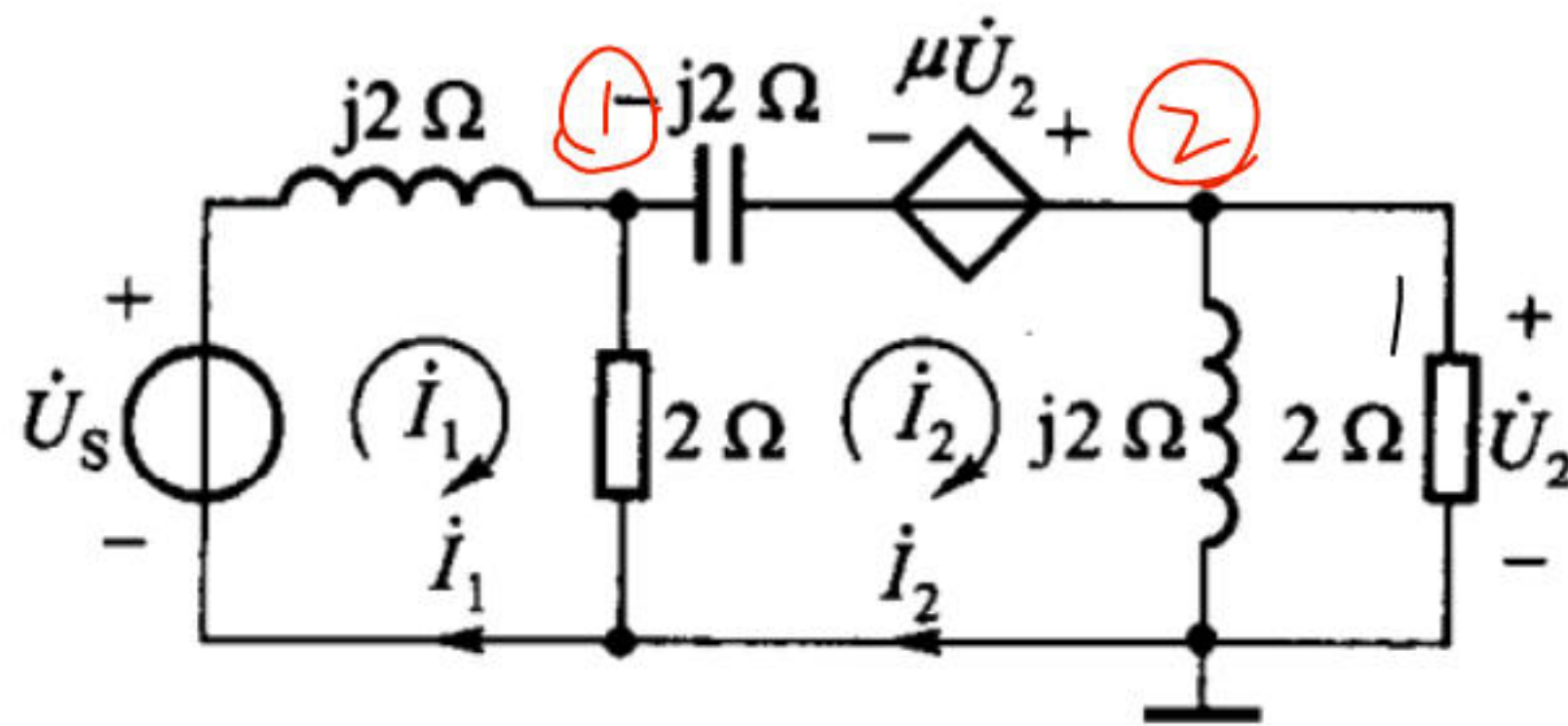


Figure 4

$$\begin{cases} (0.5 - j0.5 + j0.5)\dot{U}_1 - j0.5\dot{U}_2 = -j5 - j0.25\dot{U}_2 \\ -j0.5\dot{U}_1 + (0.5 + j0.5 - j0.5)\dot{U}_2 = j0.25\dot{U}_2 \end{cases}$$

4'

$$\Rightarrow \begin{cases} 2\dot{U}_1 - j1\dot{U}_2 = -j20 \\ -j2\dot{U}_1 + (2 - j1)\dot{U}_2 = 0 \end{cases}$$

$$\Rightarrow \dot{U}_1 = \frac{-j20 \times (2 - j1)}{2 \times (2 - j1) + 2} \text{V} = \frac{-20 - j40}{6 - j2} \text{V} = (-1 - j7) \text{V} = 7.07 \angle -98.1^\circ \text{V} \quad 3'$$

$$\Rightarrow \dot{U}_2 = \frac{-j20 \times j2}{2 \times (2 - j1) + 2} \text{V} = \frac{40}{6 - j2} \text{V} = 6 + j2 \text{V} = 6.32 \angle 18.43^\circ \text{V} \quad 3'$$

5

[12 points] The circuit is shown in **Fig 5**. The circuit is under sinusoidal steady state. Known that $i_S(t) = 30\sqrt{2}\cos 20t$ A. For the circuit excluding the 30Ω resistance, find the Thevenin equivalence (phasor domain) at the terminals a-b. Afterwards, use the Thevenin equivalence to calculate $u_k(t)$.


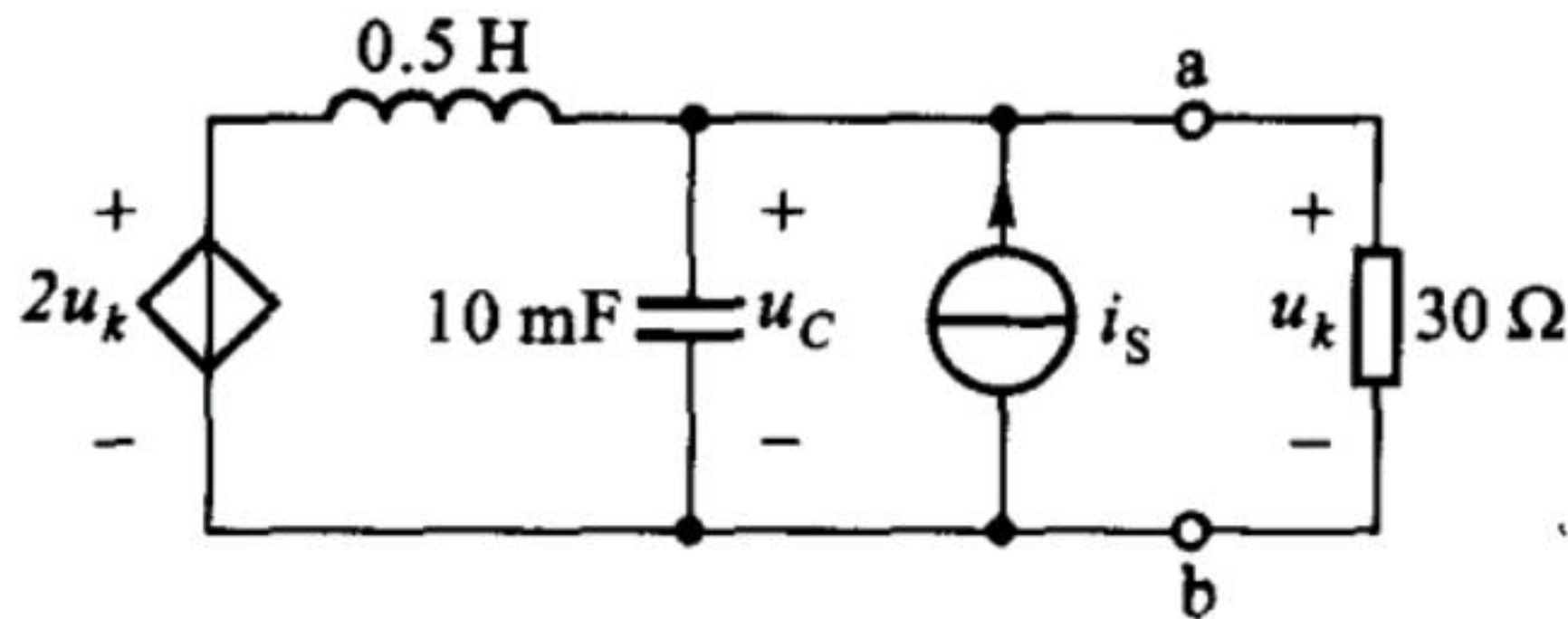


Figure 5

① find thevenin equivalence circuit:

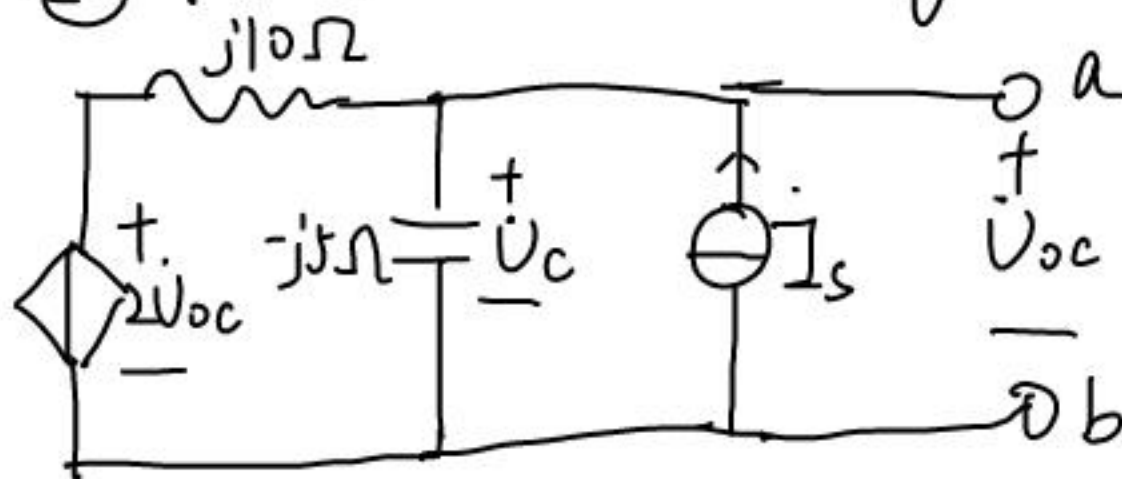

$$(-\frac{1}{j5} + \frac{1}{j10}) \dot{V}_{oc} = 30\sqrt{2} \angle 0^\circ - j0.2 \dot{V}_{oc} \Rightarrow \dot{V}_{oc} = 100\sqrt{2} \angle -90^\circ \text{ V}$$

$$\dot{I}_{sc} = \dot{I}_s = 30\sqrt{2} \angle 0^\circ \text{ A}$$

$$Z_{Th} = \frac{\dot{V}_{oc}}{\dot{I}_{sc}} = 3.33 \angle -90^\circ \Omega$$

② find $u_k(t)$

$$\dot{V}_k = \frac{30}{30 + Z_{Th}} \dot{V}_{oc} = \frac{30}{30 - j\frac{10}{3}} \times 100\sqrt{2} \angle -90^\circ = 140.56 \angle -83.66^\circ \text{ V}$$

$$u_k(t) = 140.56 \cos(20t - 83.66^\circ) \text{ (V)}$$

6

[14 points] The circuit is shown in **Fig 6**. The circuit is under sinusoidal steady state. Known that $i_S(t) = 10\sqrt{2}\cos 100t$ A, $u_S(t) = 100\sqrt{2}\cos 1000t$ V. Find $i_L(t)$. (Note: you should be careful about the operating frequency of the system when applying phasor domain equivalence)


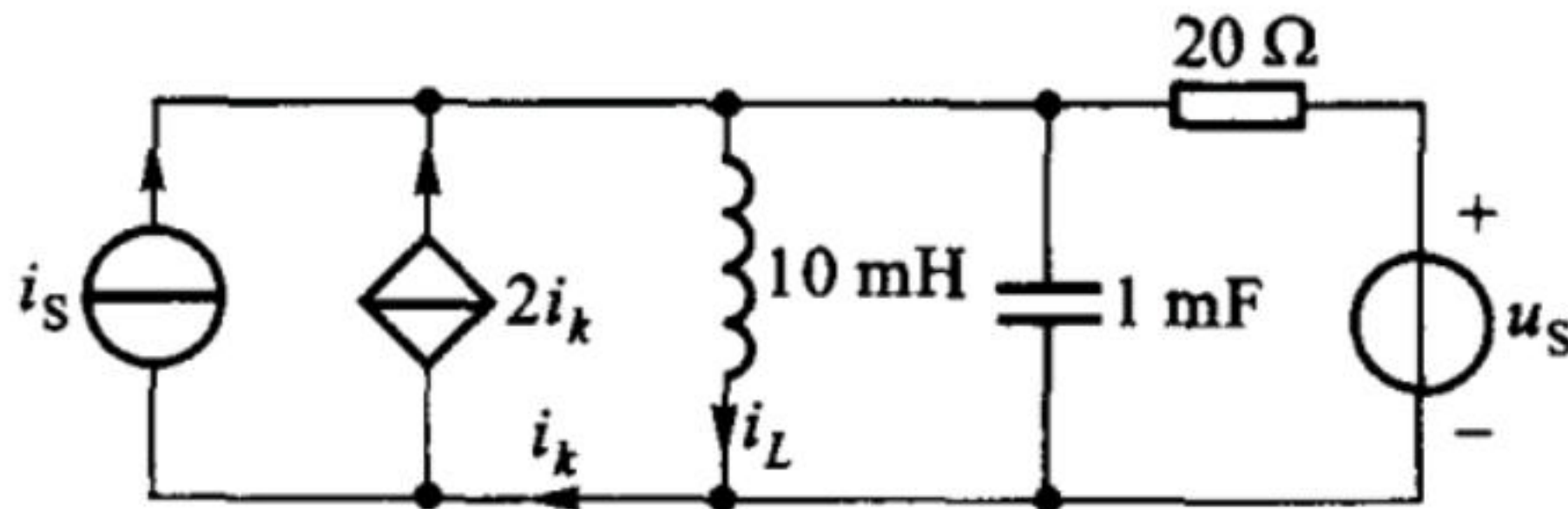


Figure 6

Let the two sources work separately.


① $\omega = 100$ rad/s.

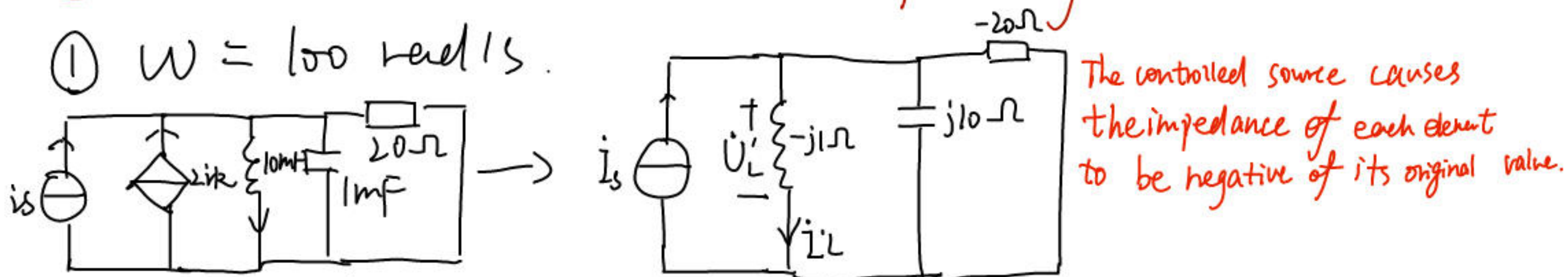

$$\dot{I}_L = \frac{10\sqrt{2} \angle 0^\circ \times \frac{1}{-j1}}{\frac{1}{-20} + \frac{1}{-j1} + \frac{1}{j10}} = \frac{10\sqrt{2} \angle 0^\circ \times \frac{1}{-j1}}{-0.05 + j0.9} = 15.69 \angle 176.82^\circ \text{ A} \quad \text{--- 2'}$$

$$i_L'(t) = 15.69 \cos(100t + 176.82^\circ) \text{ A} \quad \text{--- 2'}$$

② $\omega = 1000$ rad/s

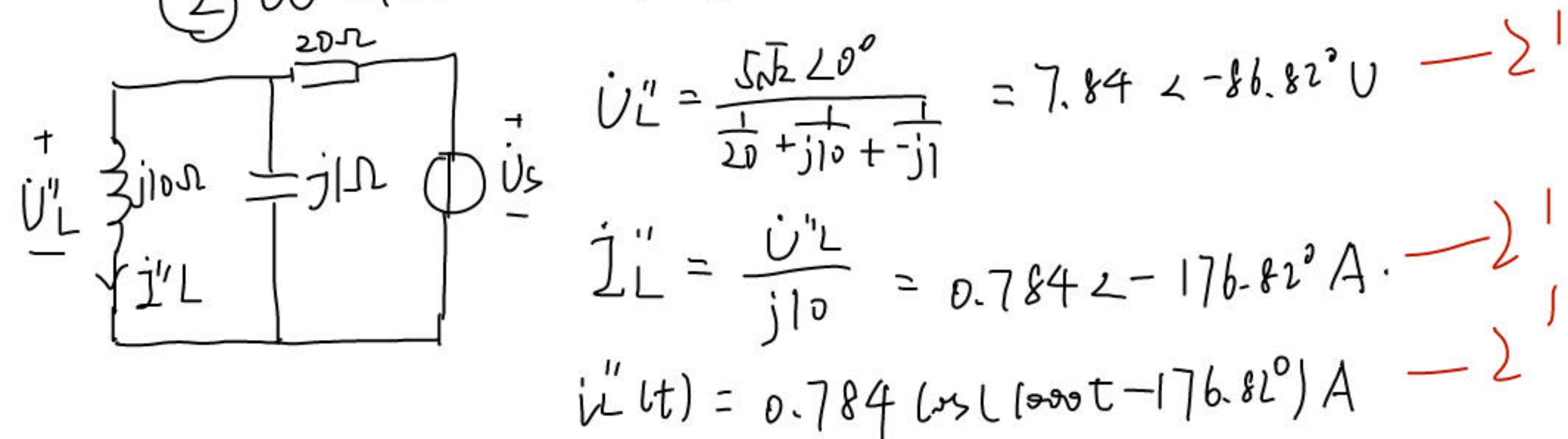

$$\dot{U}_L'' = \frac{5\sqrt{2} \angle 0^\circ}{\frac{1}{20} + \frac{1}{j10} + \frac{1}{-j1}} = 7.84 \angle -86.82^\circ \text{ V} \quad \text{--- 2'}$$

$$\dot{I}_L'' = \frac{\dot{U}_L''}{j10} = 0.784 \angle -176.82^\circ \text{ A} \quad \text{--- 2'}$$

$$i_L''(t) = 0.784 \cos(1000t - 176.82^\circ) \text{ A} \quad \text{--- 2'}$$

$$i_L(t) = 15.69 \cos(100t + 176.82^\circ) + 0.78 \cos(1000t - 176.82^\circ) \text{ A} \quad \text{--- 4'}$$

7

[12 points]

- (a). The circuit is shown in **Fig 7:a**. All of the elements are working in Sinusoidal Steady-state. Find out the relationship that the values of the elements satisfy to make the equivalent impedance (between a and b) pure resistive at any frequency. (Please make sure that you write down all of the conditions).
- (b). The circuit is shown in **Fig 7:b**. All of the elements are working in Sinusoidal Steady-state. Try to figure out what conditions the values of the elements and ω have to meet to make sure that $\frac{\dot{U}_1}{\dot{U}_2}$ has nothing to do with Z (Z is the value of the impedance of the element), and write down the ratio.

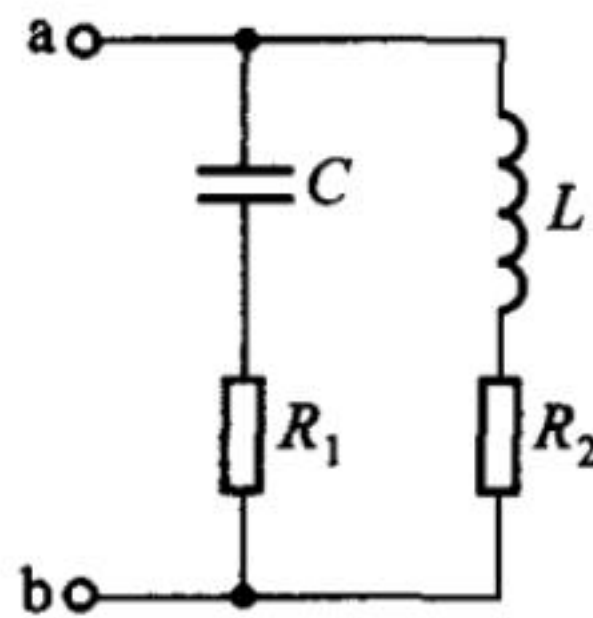


Figure 7: a

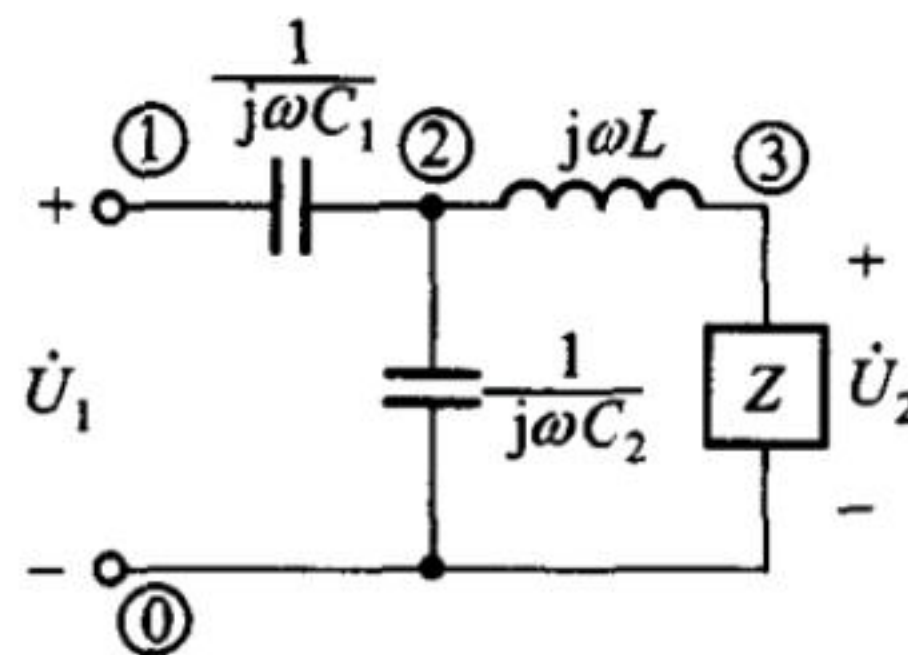


Figure 7: b

$$(a) Z_{ab} = \frac{(R_2 + j\omega L)(R_1 + \frac{1}{j\omega C})}{R_2 + j\omega L + R_1 + \frac{1}{j\omega C}} = R_2 \times \frac{1 + j\omega(\frac{L}{R_2} + R_1 C) - \frac{\omega^2 R_1 L C}{R_2}}{1 + j\omega C(R_1 + R_2) - \omega^2 L C}$$

$$\begin{cases} (R_1 + R_2)C = \frac{L}{R_2} + R_1 C \\ LC = \frac{R_1 L C}{R_2} \end{cases} \Rightarrow \begin{cases} R_1 = R_2 = R \\ L = R^2 C \end{cases} \text{ or } L = C = 0$$

$$(b) \frac{\dot{U}_1}{\dot{U}_2} = Z \cdot \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_2} + j\omega L + Z} \cdot \left(\frac{1}{j\omega C_1} + \frac{(j\omega L + Z) \frac{1}{j\omega C_2}}{\frac{1}{j\omega C_2} + j\omega L + Z} \right) = \frac{1 + j\omega C_2 Z - \omega^2 C_2 L}{j\omega C_1 Z} + \frac{(j\omega L + Z)(1 + j\omega C_2 Z - \omega^2 C_2 L)}{Z(1 - \omega^2 C_2 L + j\omega C_2 Z)}$$

$$= \frac{C_2}{C_1} + \frac{1 - \omega^2 C_2 L}{j\omega C_1 Z} + \frac{j\omega L}{Z} + 1$$

$$= \frac{C_1 + C_2}{C_1} + \frac{1 - \omega^2 (C_1 + C_2) L}{j\omega C_1 Z}$$

Then we can get that: $\omega^2 L(C_1 + C_2) = 1$

The ratio is $\frac{C_1 + C_2}{C_1}$

8

[14 points]

- (a). Known that the sinusoidal voltage has an amplitude of 100V. The instantaneous value of the voltage at $t=0$ is 10V, and the period is 1ms. Please write down the expression of the voltage as a cosine function.
- (b). $i_1(t) = 4\cos(\omega t - 80^\circ)A$, $i_2(t) = 10\cos(\omega t + 20^\circ)A$, $i_3(t) = 8\sin(\omega t - 20^\circ)A$. Please express these currents in phasor domain.

$$(a) \quad 100 \cos \phi_0 = 10 \Rightarrow \phi_0 = \arccos 0.1 = \pm 84.26^\circ \quad 2'$$

$$\omega = \frac{2\pi}{T} = 2\pi \times 10^3 \text{ rad/s} \quad 2'$$

$$u(t) = 100 \cos(2\pi \times 10^3 t \pm 84.26^\circ) \text{ V} \quad \checkmark$$

$$= 100 \cos(6.28 \times 10^3 t \pm 84.26^\circ) \text{ V} \quad \checkmark$$

$$= 100 \cos(3.14 \times 10^5 t \pm 84.26^\circ) \text{ V} \quad 4'$$

$$(b) \quad \dot{I}_1 = 4 \angle -80^\circ \text{ A} \quad 2'$$

$$\dot{I}_2 = 10 \angle 20^\circ \text{ A} \quad 2'$$

$$\dot{I}_3 = 8 \angle -110^\circ \text{ A} \quad 2'$$