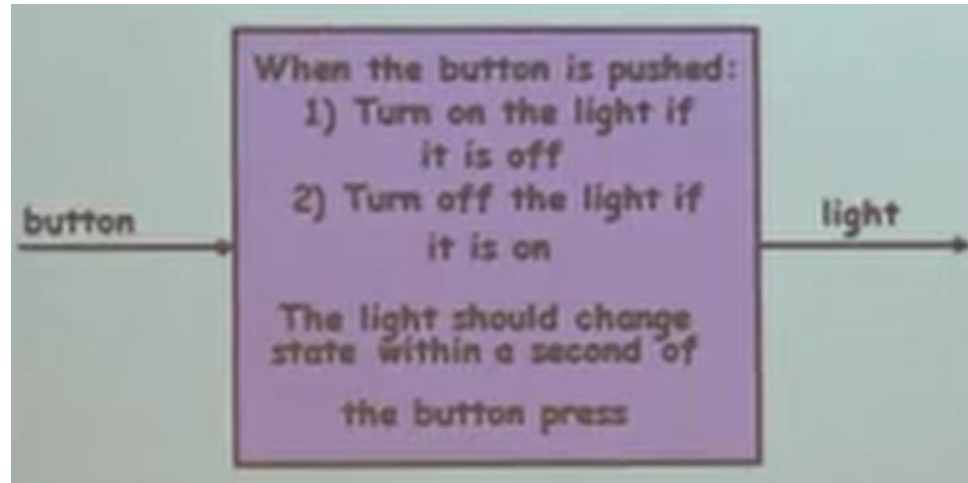


# Something We Cannot Build



按下 1	Input	original	Output	ON : 1
不按 0	button	State	Light	OFF : 0
	A	Q	Q	
	1	0	1	
	1	1	0	


Think about it:

- Can we build the circuit using the combinational logic?
- If not, what is missing here?


1. need storage  
2. need event rather than a fixed voltage
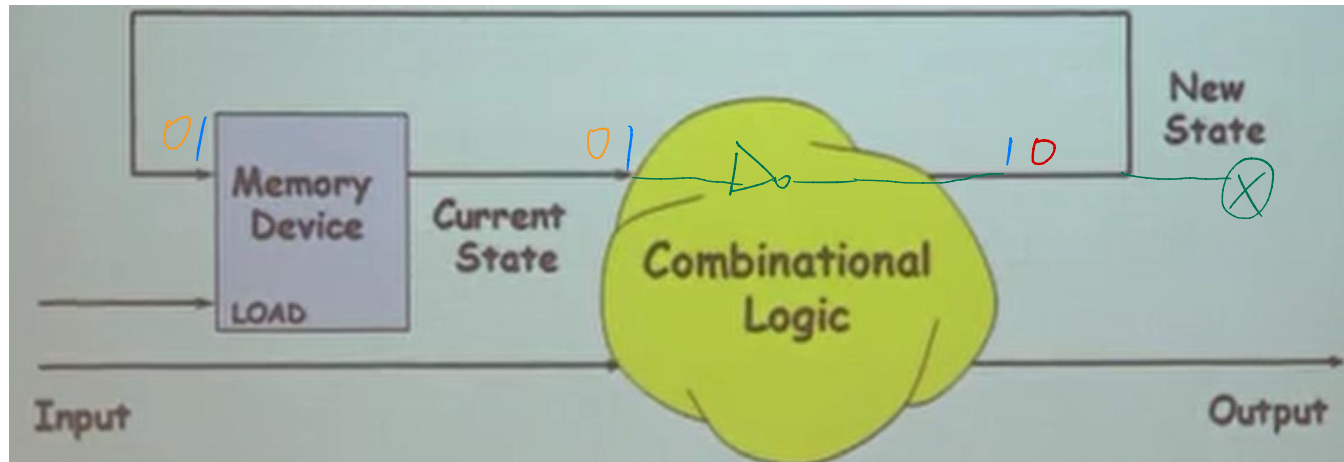
# Something We Cannot Build


- One needs the storage unit
- The output is triggered by an event instead of a value.



# Use feedback to store a bit

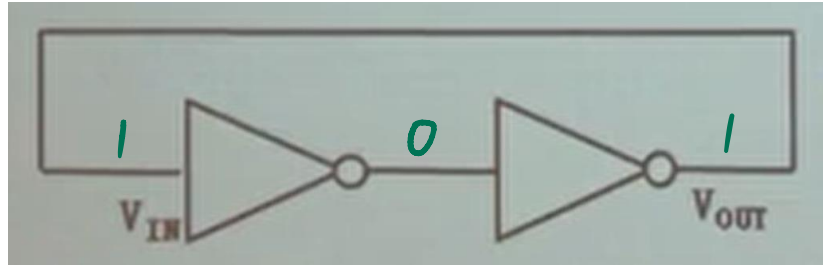


Add control terminals

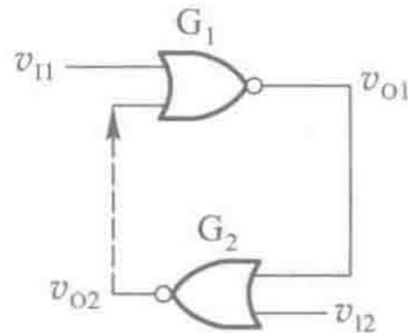

Question: if we want to maintain the state, what voltage should be applied to  $v_{11}$  and  $v_{12}$ ?

0


# S-R (SET-RESET) Latch

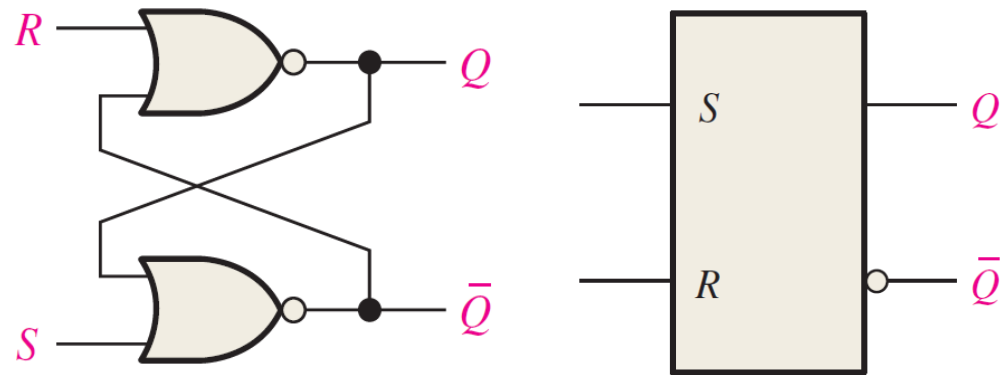

- The output of each gate is connected to an input of the opposite gate to provide a feedback.
- Even the input is removed, the output state is still maintained.
- This is the active high input SR latch

$S_D$	$R_D$	$Q$	$Q^*$
0	0	0	0
0	0	1	1
1	0	0	1
1	0	1	1
0	1	0	0
0	1	1	0
1	1	0	0 <sup>Ⓢ</sup>
1	1	1	0 <sup>Ⓢ</sup>

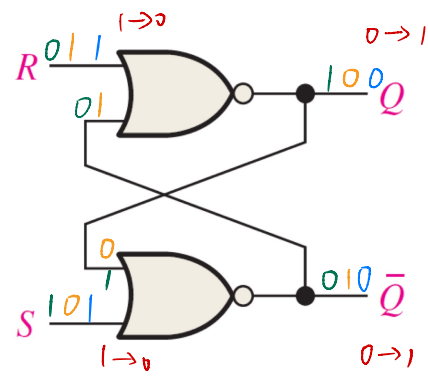
① The state is undetermined when  $S$  and  $R$  are removed simultaneously



R	S	Q	$Q^*$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	$0^0$
1	1	1	$0^0$




# S-R (SET-RESET) Latch

Active low input SR latch



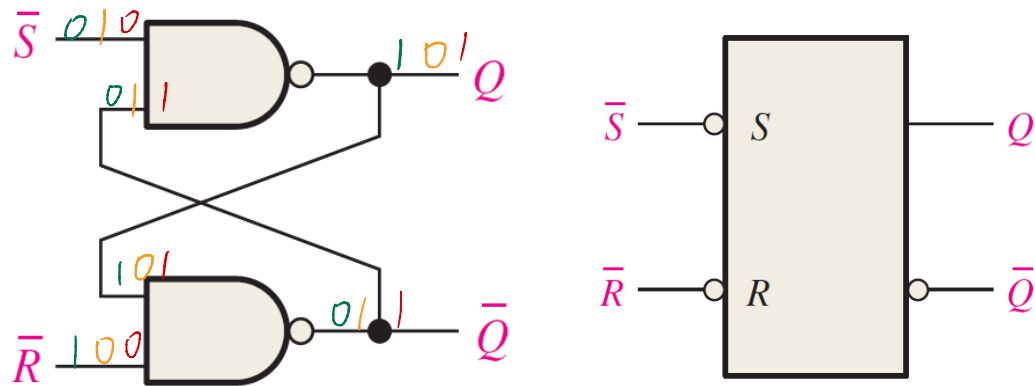


$S'_D$	$R'_D$	$Q$	$Q^*$
1	1	0	0
1	1	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
0	0	0	1 <sup>(1)</sup>
0	0	1	1 <sup>(1)</sup>

# S-R (SET-RESET) Latch

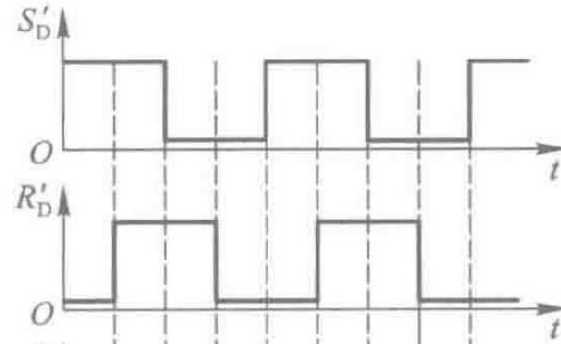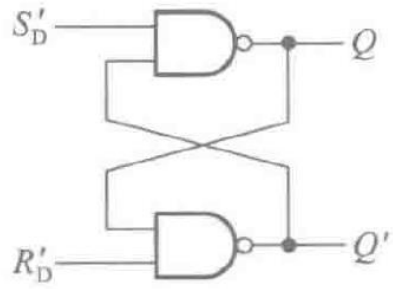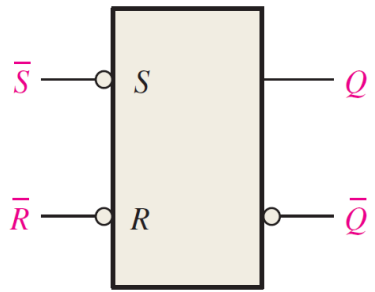


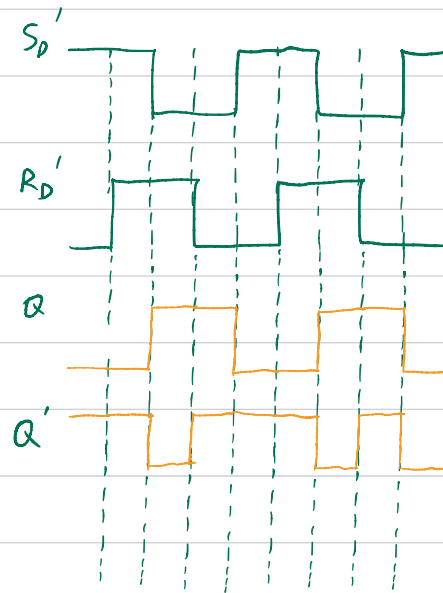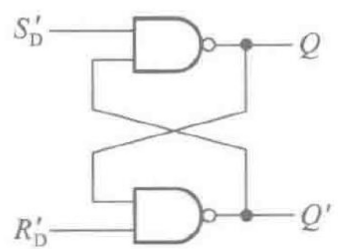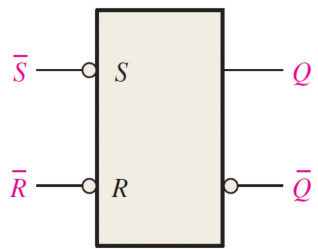Question: plot the waveform of  $Q$  and  $Q'$





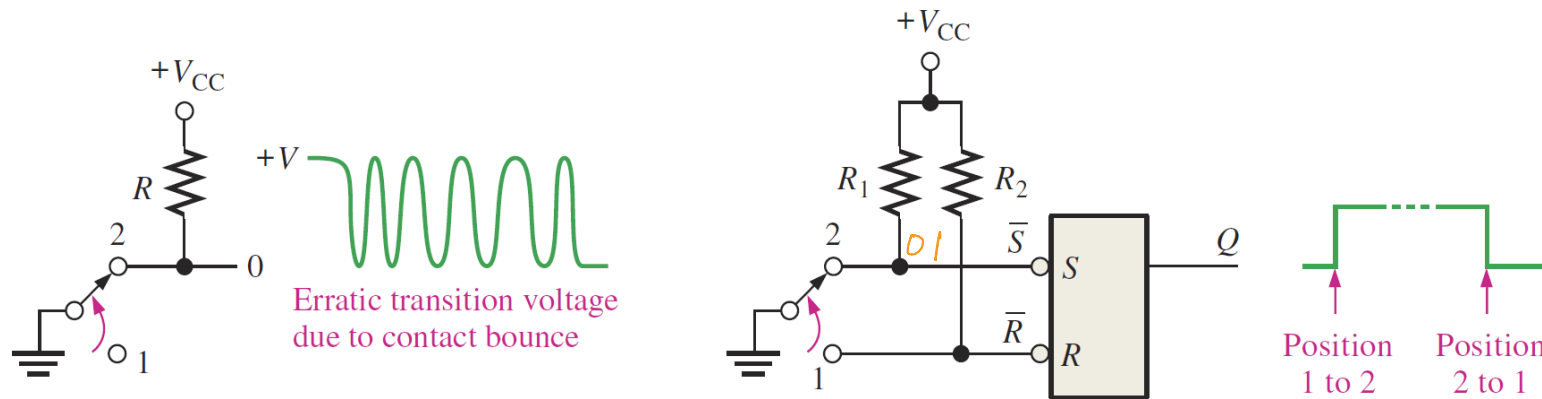
# S-R Latch as a Contact-Bounce Eliminator



- The closure of a mechanical switch is accompanied by the contact bounce
- An S-R latch can be used to eliminate the effects of switch bounce.
- The 1 to 2 transition sets the latch. Any further voltage spikes on the S input do not affect the latch.
- Similarly, a clean transition from HIGH to LOW is made for a 2 to 1 transition .



# The gated S-R Latch

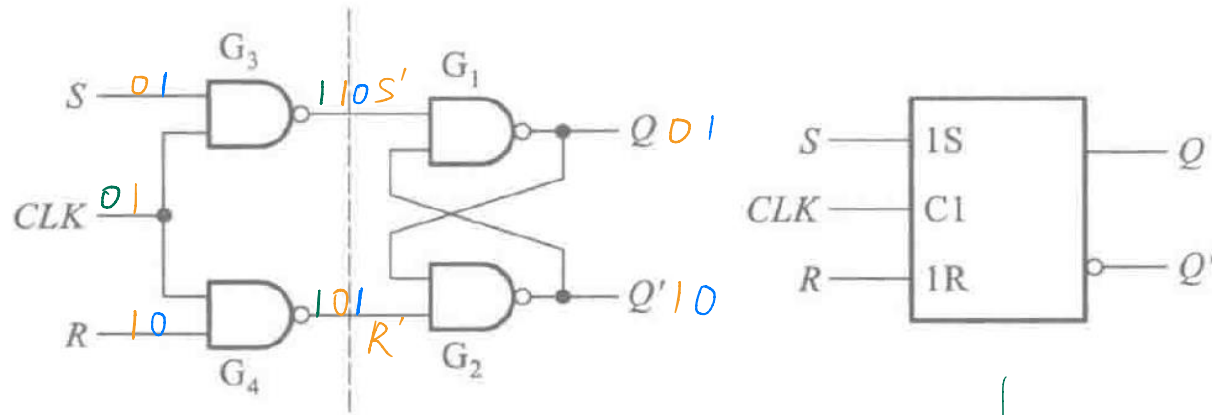



- C1 denotes that  $CLK$  is a control signal with the numbering 1
- 1S and 1R denotes that  $S$  and  $R$  are controlled by C1
- The gated latch is a level-sensitive device

$CLK$	$S$	$R$	$Q$	$Q'$
0	×	×	0	0
0	×	×	1	1
1	0	0	0	0
1	0	0	1	1
1	1	0	0	1
1	1	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	1	0	1 <sup>(1)</sup>
1	1	1	1	1 <sup>(1)</sup>

# The gated S-R Latch

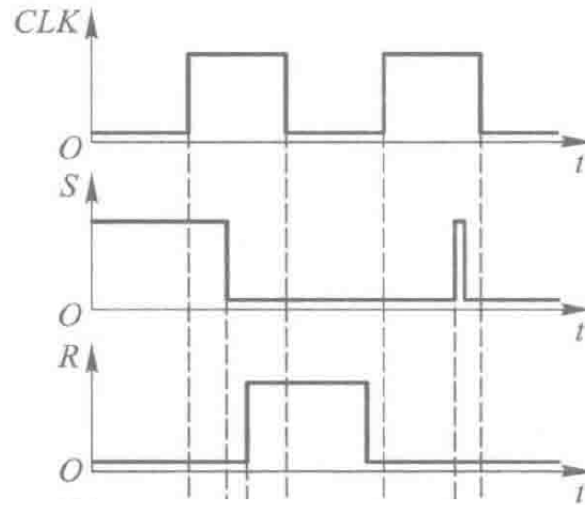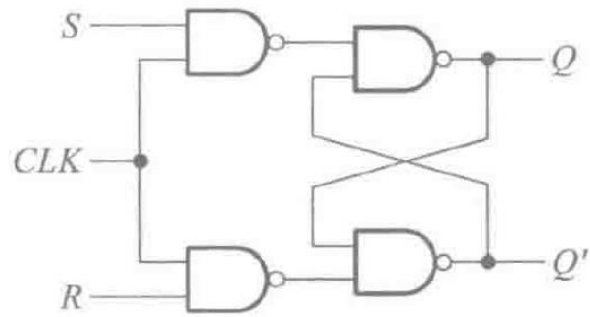


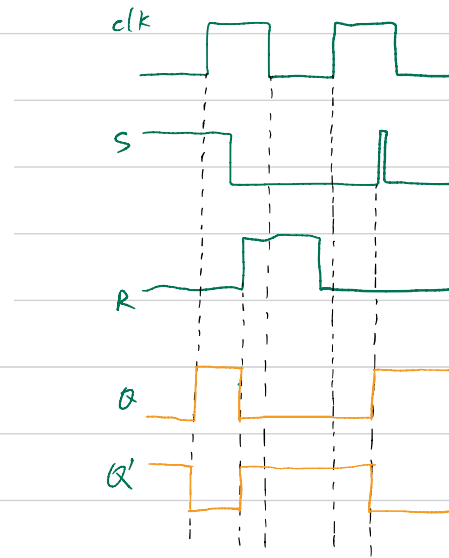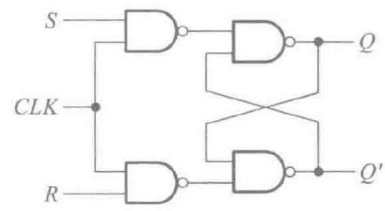Question: plot the waveform of  $Q$  and  $Q'$ ,  
assume the initial  $Q$  is 0




# The asynchronous gated S-R Latch

Synchronous : S, R

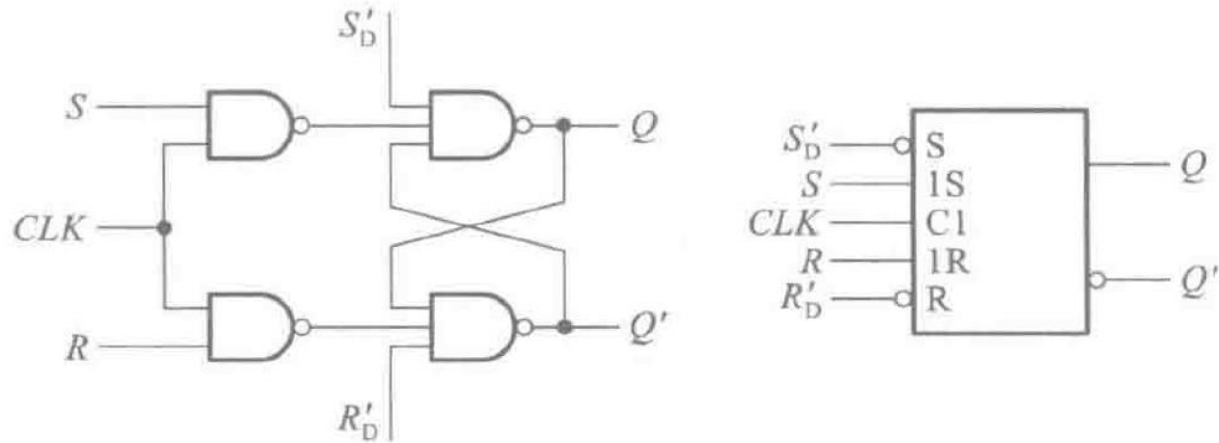

- When  $S'_D$  and  $R'_D$  are not used for asynchronous set and reset, one should set them to 1
- When they are used, CLK should be set to 0



# The gated D Latch

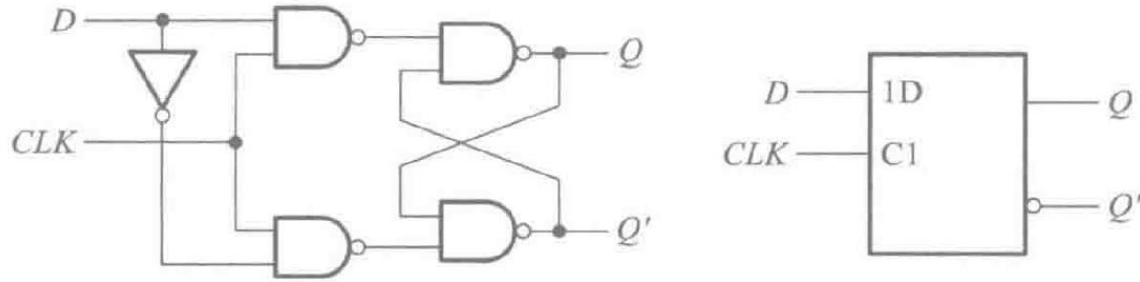


$CLK$	$D$	$Q$	$Q'$
0	$\times$	0	0
0	$\times$	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Compared to the S-R latch, it lost the keep function


# The gated D Latch

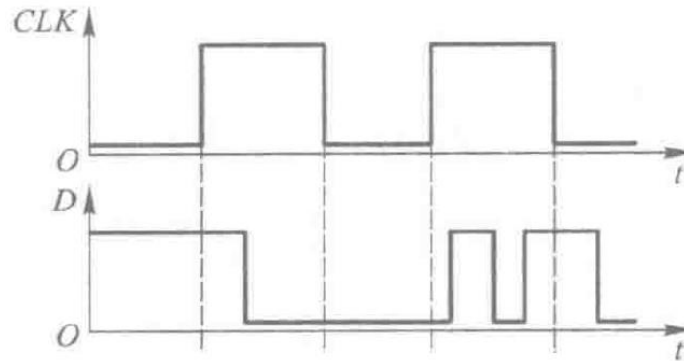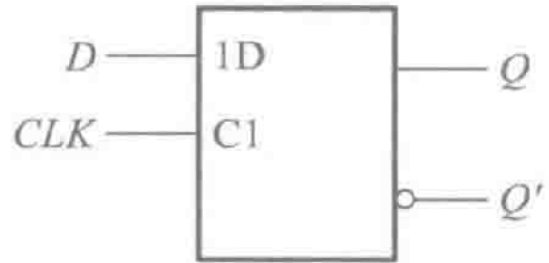

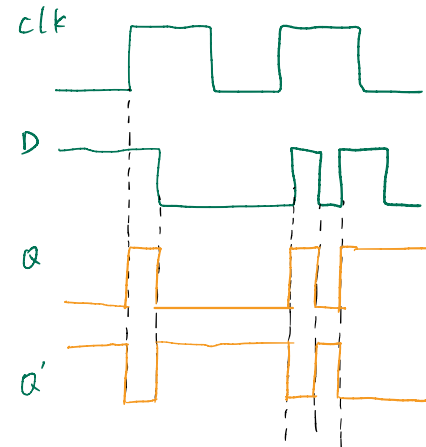
Question: plot the waveform of  $Q$  and  $Q'$ , assume the initial  $Q$  is 0



# The gated D Latch

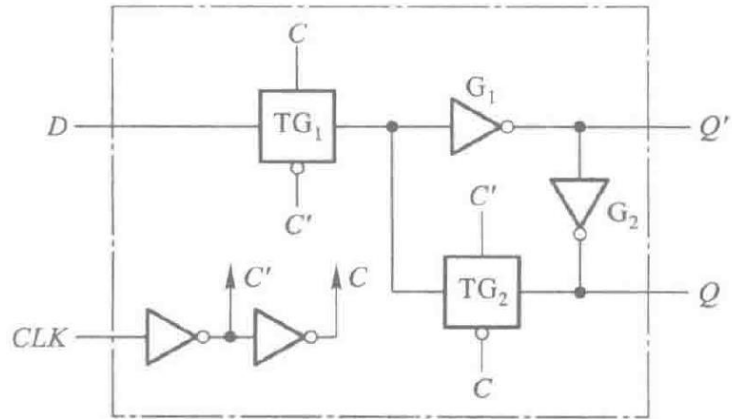

D latch using transmission gate

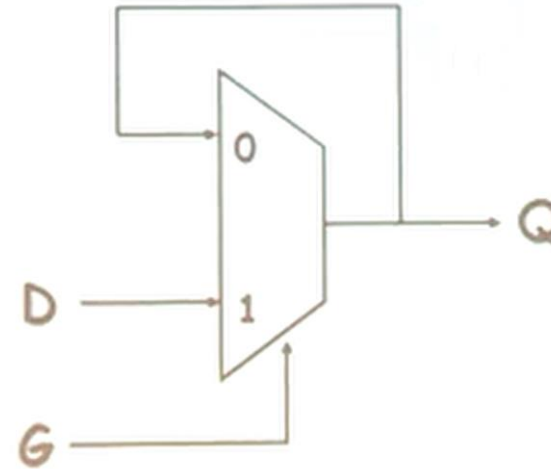

D latch using MUX