

Homework 6


Due date: 29th Nov.

Turn in your homework in class

Rules:


- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

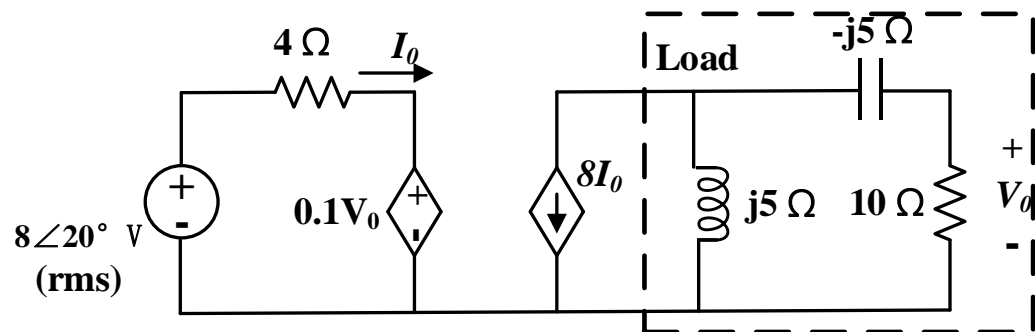1. For the circuit below, please find:
- (1) The average power absorbed by the load;
 - (2) The reactive power absorbed by the load;
 - (3) The complex power \mathbf{S} absorbed by the load;
 - (4) The power factor pf of the load.




2. For the three-load circuit shown below, L_1 absorbs 3 kW at unity power factor; L_2 absorbs 5 kVA at 0.8 leading; L_3 absorbs 5 kW and delivers 6 kvars.

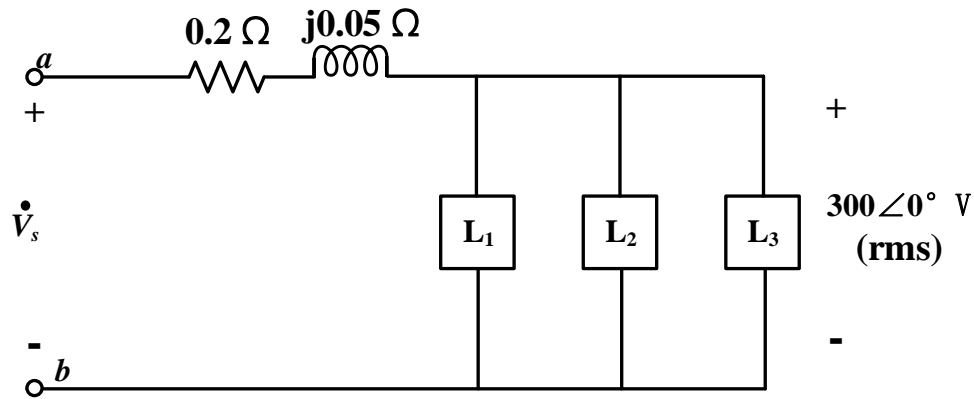- (1) Calculate the voltage \dot{V}_s .
- (2) Calculate the average power and reactive power associated with the line impedance ($0.2\Omega + j0.05\Omega$).
- (3) Calculate the average power and reactive power between port **a** and port **b**.




3. For the circuit below,

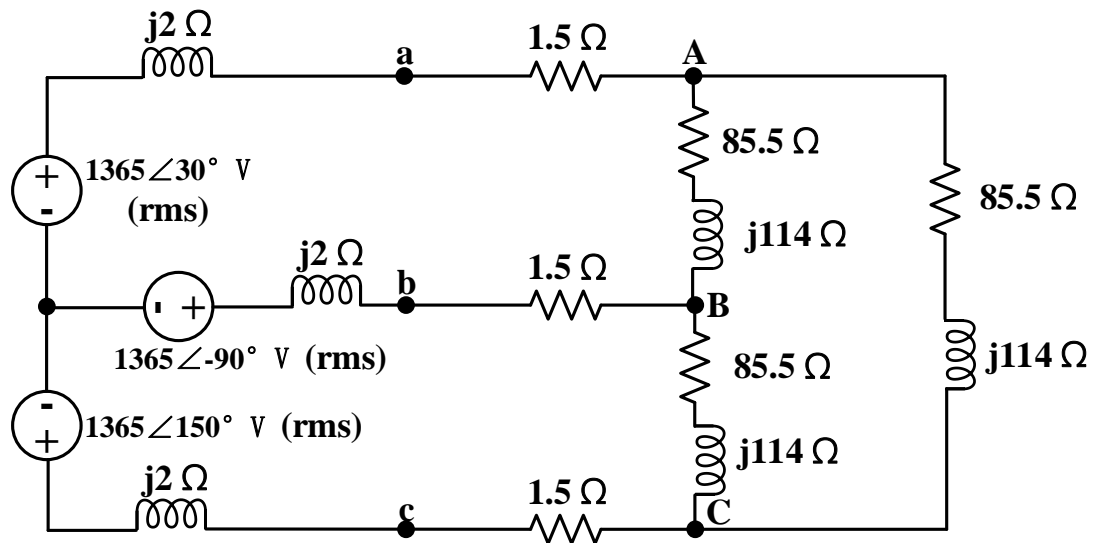- (1) Find \dot{I}_{AB} , \dot{I}_{BC} , \dot{I}_{CA} , and \dot{V}_{CA} in the circuit.
- (2) What percent of the average power delivered by the three-phase source is dissipated in the three-phase load?



4. For the circuit below, please find:

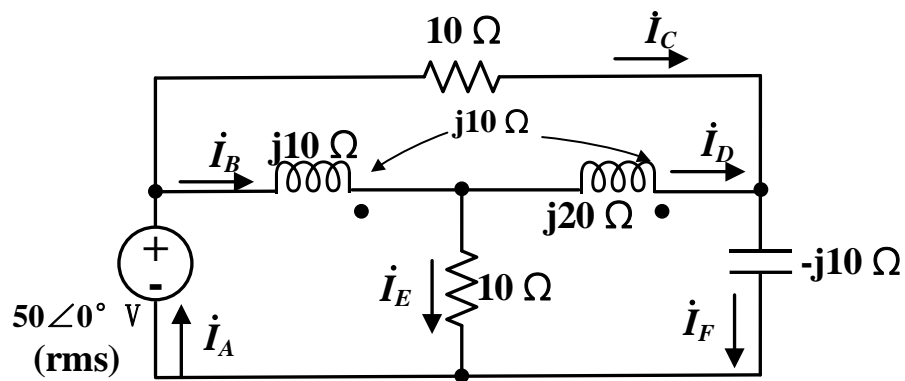- (1) Current \mathbf{i}_D , \mathbf{i}_E , and \mathbf{i}_F
- (2) The complex power on the capacitor, and the power factor pf of the capacitor.



5. For the circuit below:

- (a) Find the average power delivered to the 8Ω resistor.
- (b) Find the average power generated by the ideal sinusoidal source
- (c) Find the impedance of Z_{ab}

