



# **Lecture 14**

## **-- Laplace Transform in Circuit Analysis**



## V-I relations of R,L,C

• R  $U_R(s) = RI_R(s)$


• C 
$$V(s) = \frac{1}{sC}I(s) + \frac{V_0}{s}$$

$$I(s) = sCV(s) - CV_0$$

• L 
$$I(s) = \frac{1}{sL}V(s) + \frac{I_0}{s}$$

$$V(s) = sLI(s) - LI_0$$

• R  $U_R(s) = RI_R(s)$

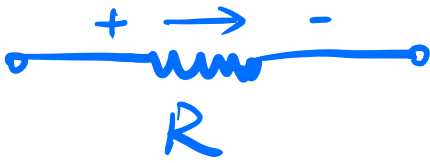


T.D. :  $v(t) = R \cdot i(t)$

S.D. :  $V(s) = R \cdot I(s)$

• C

$$V(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$

$$I(s) = sCV(s) - CV_0$$

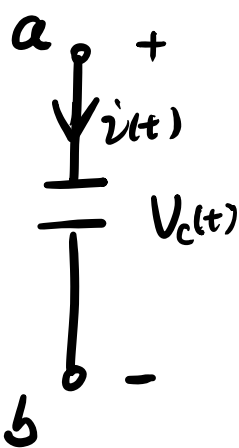

$$i(t) = C \cdot \frac{dV_c(t)}{dt}$$

$$I(s) = C \cdot [sV_c(s) - V_c(0)]$$

$$= C \cdot [sV(s) - V_0]$$

$$\Rightarrow V(s) = \frac{1}{sC} \cdot I(s) + \frac{V_0}{s}$$

①



②




$$V_c(t) = V_0 + \frac{1}{C} \int i(t) dt$$

$\downarrow \mathcal{L}$                        $\downarrow$                        $\downarrow$   
 $V(s) = \frac{V_0}{s} + \frac{1}{Cs} \cdot I(s)$

From


$$I(s) = C \cdot [sV(s) - V_0]$$

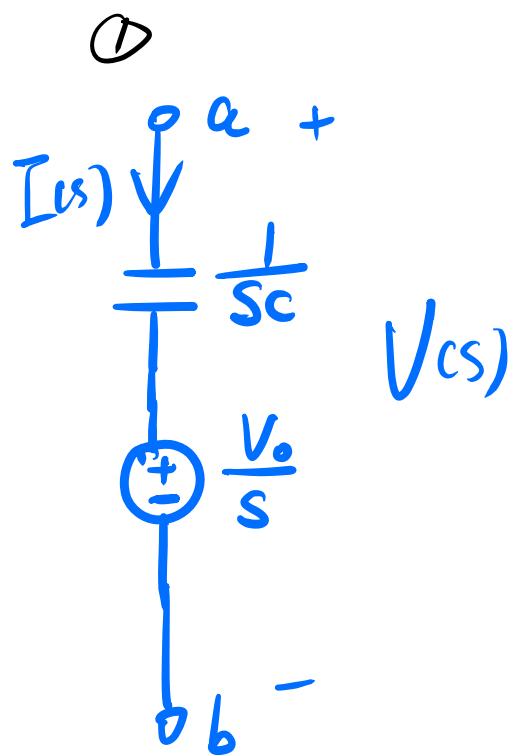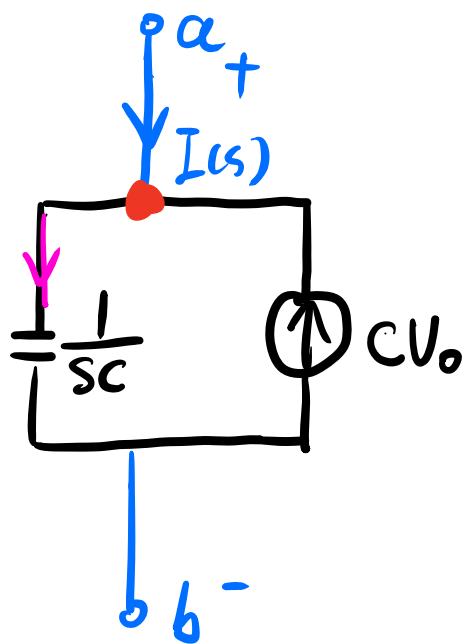

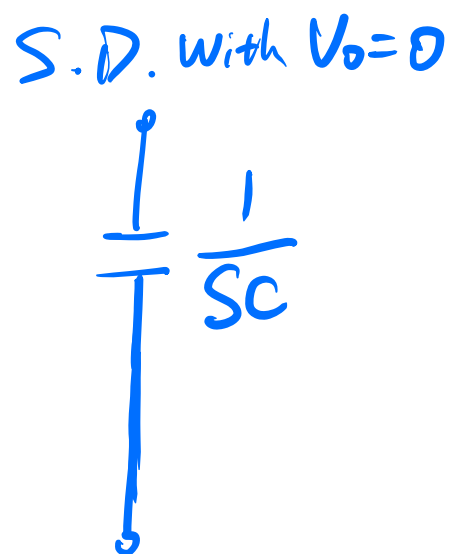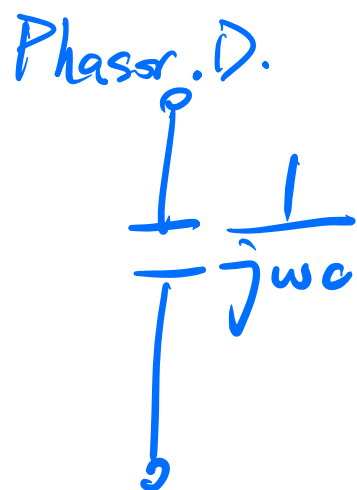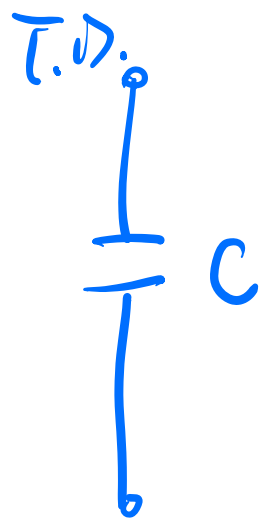

# S-domain circuit models for a capacitor


## s-Domain Circuit Models

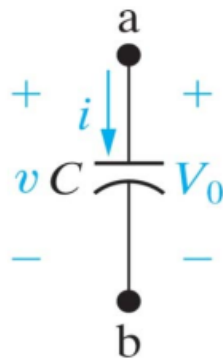


$$i(t) = C \frac{dv(t)}{dt}$$

For a capacitor  
(with initial conditions)

$$\Rightarrow I(s) = sCV(s) - CV_0$$

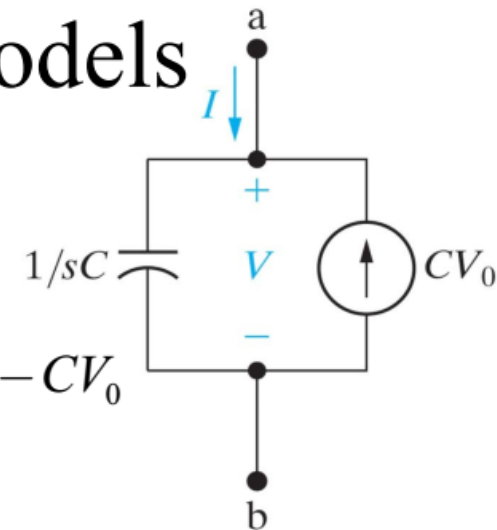

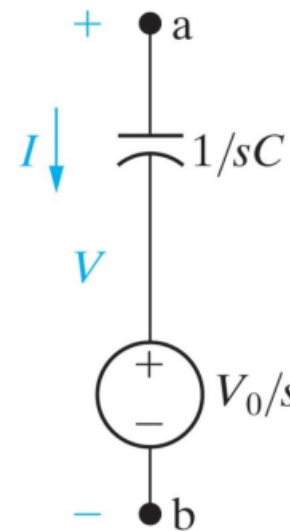
$$V(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$



I.D.

$$V(t) = L \cdot \frac{di(t)}{dt}$$

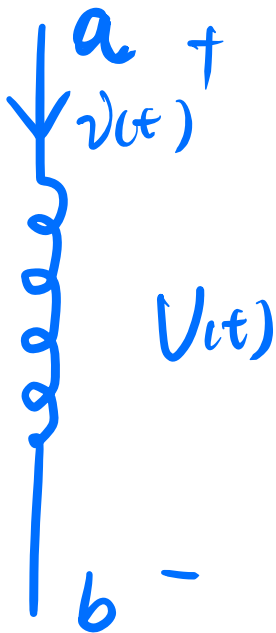

$L \rightarrow \varphi$

$$\underline{V(s)} = L [s \cdot \underline{I(s)} - i(0_-)]$$


$$= L \cdot s \cdot \underline{I(s)} - L \underline{I_0} \quad (1)$$

$$\underline{I(s)} = \frac{1}{sL} \cdot \underline{V(s)} + \frac{I_0}{s} \quad (2)$$

$$\underline{V(s)} = L \cdot s \cdot \underline{I(s)} - L \underline{I_0} \quad (1)$$



S.T.  $\Rightarrow$

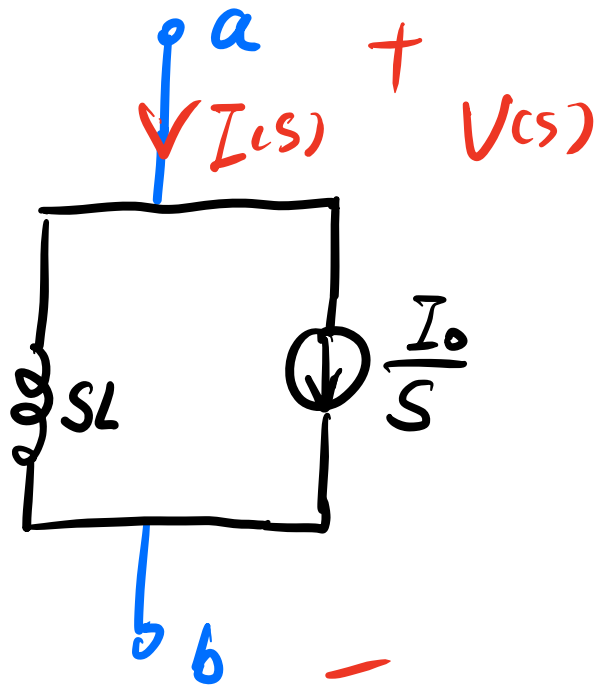

T.D.



Phasor D.



S.D. with  $I_0 = 0$








# S-domain circuit models for an inductor

## s-Domain Circuit Models

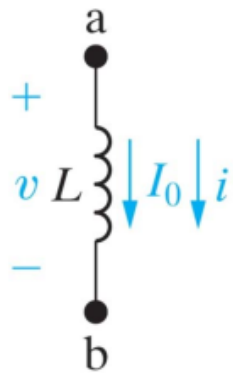


$$v(t) = L \frac{di(t)}{dt}$$


For an inductor  
(with initial conditions)



$$V(s) = sLI(s) - LI_0$$

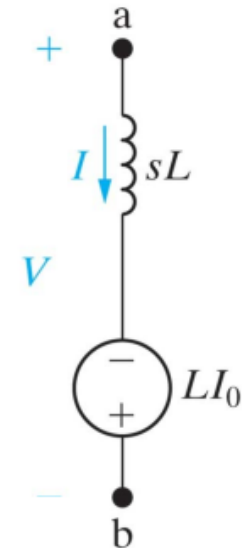








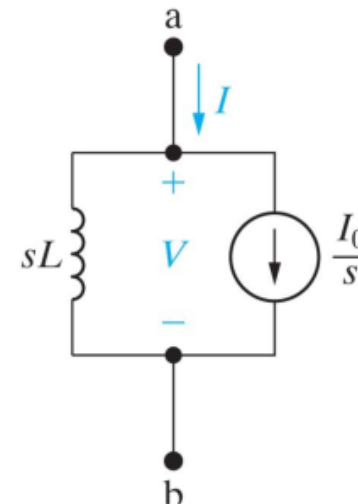
$$I(s) = \frac{1}{sL} V(s) + \frac{I_0}{s}$$






Time domain

s-domain

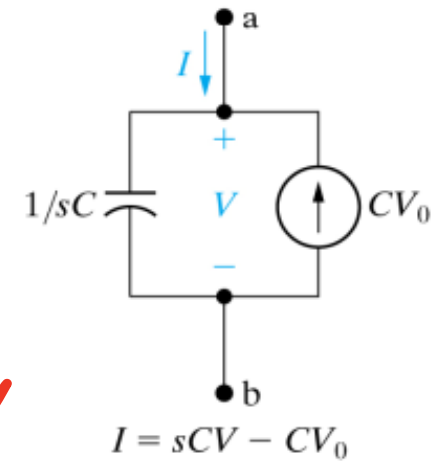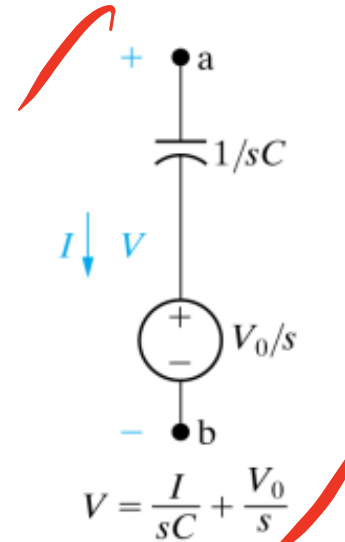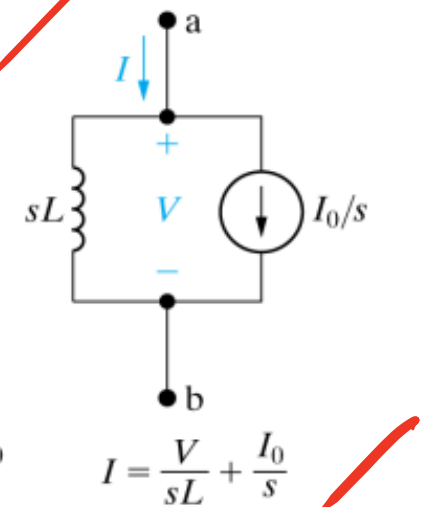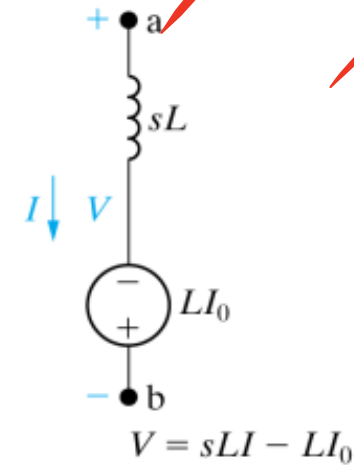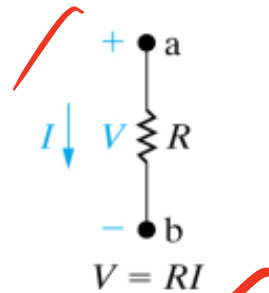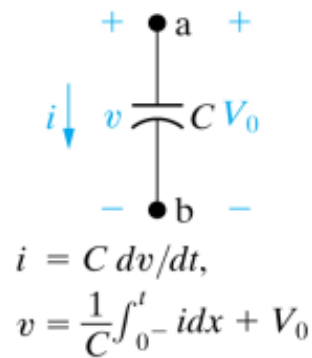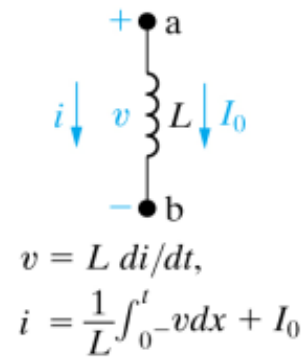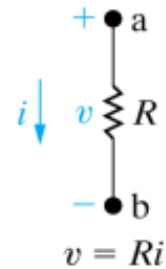




## D.C. sources and Dependent Sources

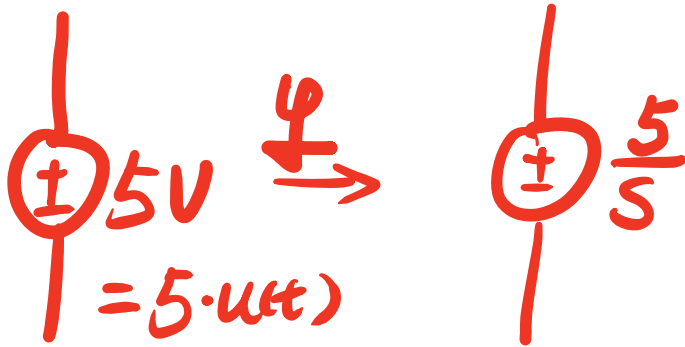

- The models for dependent sources are easy to develop, drawing from the simple fact that if the Laplace transform of  $f(t)$  is  $F(s)$ , then the Laplace transform of  $af(t)$  is  $aF(s)$  — the linearity property.


$$\mathcal{L}[av(t)] = aV(s)$$

$$\mathcal{L}[ai(t)] = aI(s)$$

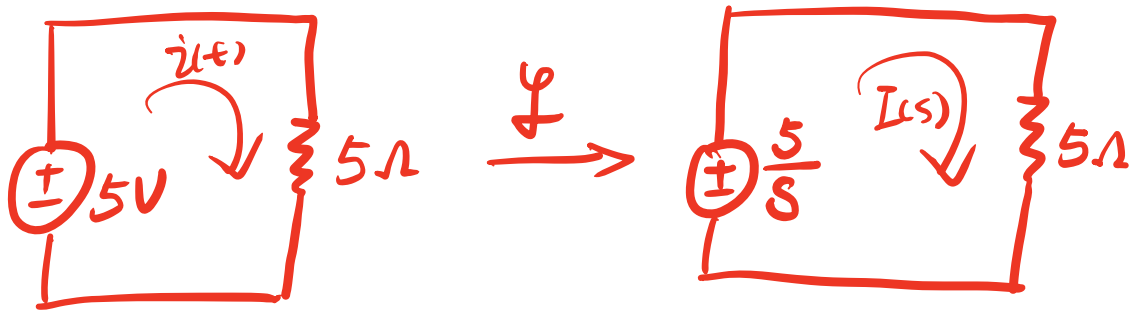

$$I(s) = \frac{\frac{5}{s}}{5} = \frac{1}{s}$$

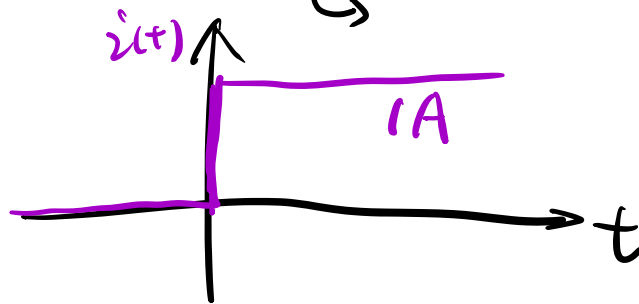$\phi^{-1} \rightarrow \underline{i(t) = u(t) = 1 \cdot u(t)} \quad t > 0$









# Steps in Applying the Laplace transform

- Transform the circuit from the time domain to the Laplace ( $s$ ) domain, including initial conditions.  
--The elegance of using the Laplace transform in circuit analysis lies in (1) transforming the differential equation into an *algebraic* equation; and (2) automatic inclusion of initial conditions in the transformation process, thus providing a complete (**transient and steady-state**) solution.
- Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.
- Take the inverse transform of the solution and thus obtain the solution in the time domain.
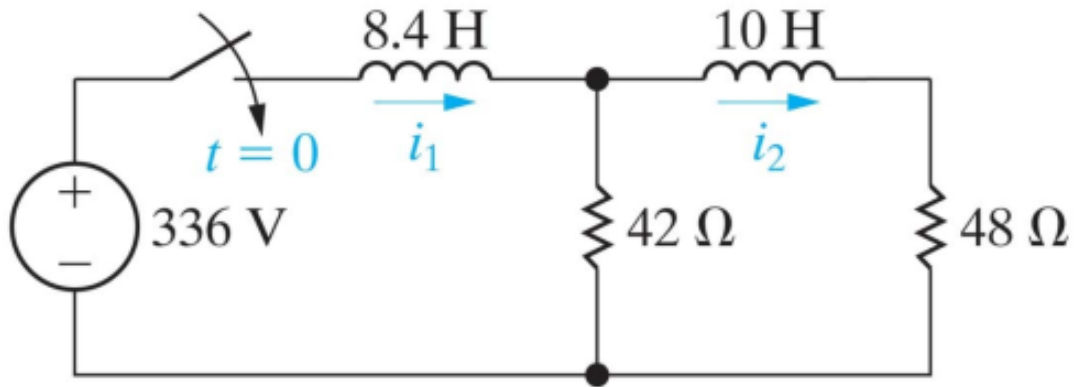
## Example 1

Assuming no initial energy storage, find  $i_1(t)$  and  $i_2(t)$  for  $t > 0$ .



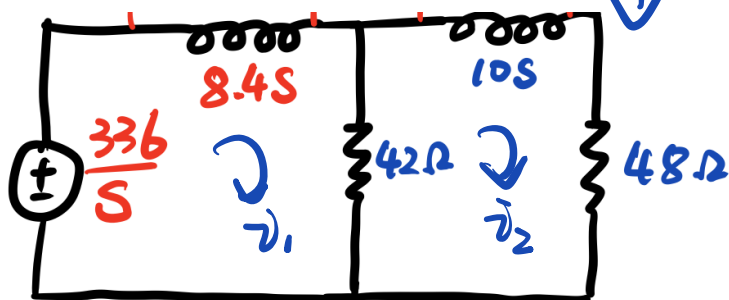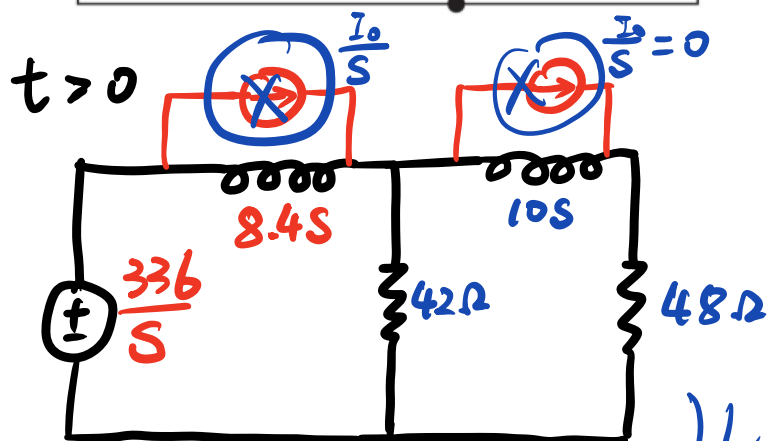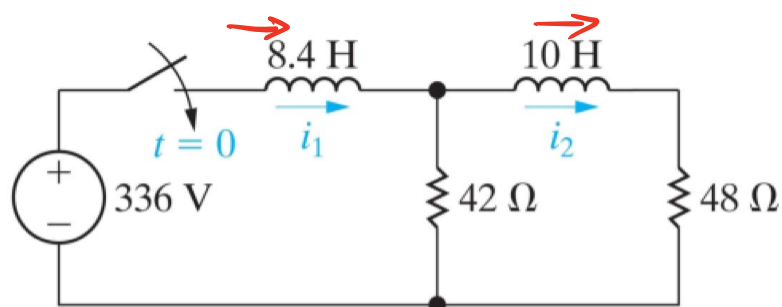

$$\begin{cases} \frac{336}{s} = 8.4 \dot{v}_1 + 42(\dot{v}_1 - \dot{v}_2) \quad (1) \end{cases}$$


$$\begin{cases} 42(\dot{v}_1 - \dot{v}_2) = 10s \cdot \dot{v}_2 + 48 \dot{v}_2 \quad (2) \end{cases}$$

$$\begin{aligned} \dot{v}_2 &= \frac{168}{s^3 + (4s^2 + 24s)} = \frac{168}{s(s+2)(s+12)} \\ &= \frac{k_1}{s} + \frac{k_2}{s+2} + \frac{k_3}{s+12} \end{aligned}$$

$k_1 = 7$        $k_2 = -8.4$        $k_3 = 1.4$

$$\Rightarrow i_2(t) = [7 - 8.4e^{-2t} + 1.4e^{-12t}] u(t)$$
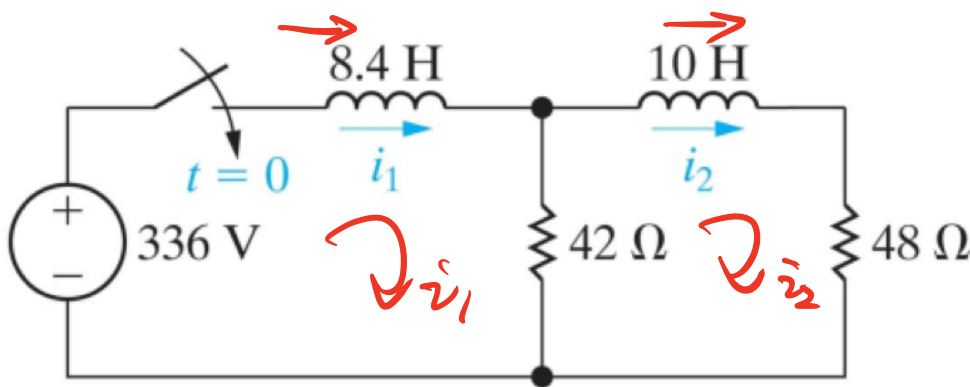
$$\tilde{v}_1(s) = \frac{80 + 10s}{42} \cdot \frac{168}{s^3 + 14s^2 + 24s}$$



$$336 = 8.4 \frac{di_1}{dt} + 42(v_1 - v_2)$$

$$42(v_1 - v_2) = 10 \cdot \frac{di_2}{dt} + 48v_2$$

$$\text{由 ②} \quad 42v_1 = 10 \frac{di_2}{dt} + 90v_2$$

$$v_2' + 14v_2' + 24v_2 = 168$$

$$s^2 + 14s + 24 = 0$$