

Homework 1

Due date: Sep. 27th, 2022, Tuesday


Turn in your hard-copy hand-writing homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.



(0)

1. (a) Find the resistance seen by the ideal voltage source V_s in the circuit.
 (b) If V_s equals 270V, how much power is dissipated in the 1S resistor?

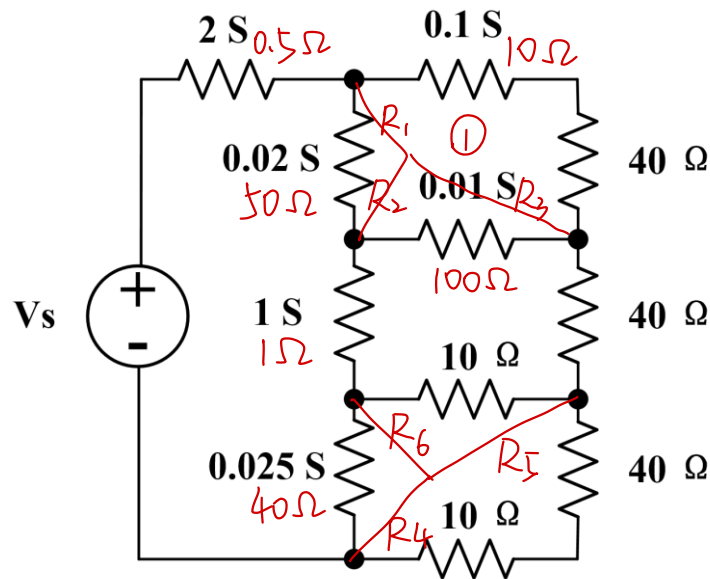S \rightarrow Ω |'

(a)

4'

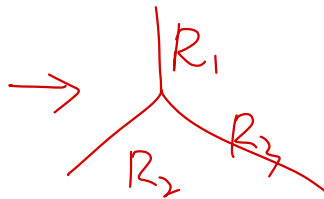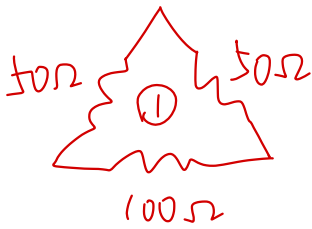

$$R_1 = \frac{50 \times 50}{50 + 50 + 100} = 12.5 \Omega$$


$$R_2 = \frac{50 \times 100}{200} = 25 \Omega$$

$$R_3 = \frac{50 \times 100}{200} = 25 \Omega$$


$$R_4 = \frac{40 \times 50}{10 + 40 + 50} = 20 \Omega$$

$$R_5 = \frac{50 \times 10}{100} = 5 \Omega$$
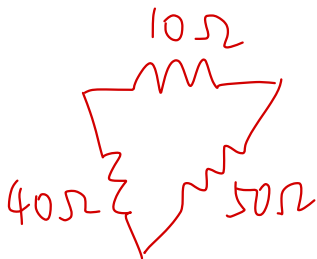
$$R_6 = \frac{40 \times 10}{100} = 4 \Omega$$



$$R_{eq} = 0.5 + 12.5 + 21 + 20 = 54 \Omega$$

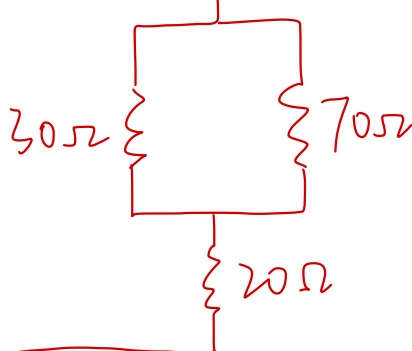 \Rightarrow  \Rightarrow

3' 2

$$(b) i_R = \frac{270}{54} \times \frac{70}{30+70} = 3.5 \text{ A}$$


$$P = i_R^2 R = 3.5^2 \times 1 = 12.25 \text{ W}$$

15'

2. Apply nodal analysis method to obtain:

(a) all the node voltages (V_1 , V_2 , and V_3) if assuming the bottomleft node as the reference node.(b) all the currents (i_1 to i_4) and the voltage on 20Ω resistor (V_0).

Umit 1'

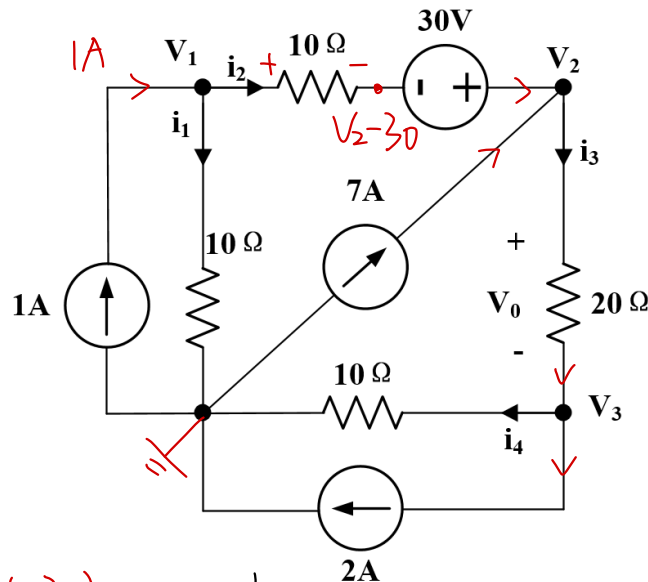

(a)

$$\begin{cases} 1 = \frac{V_1}{10} + \frac{V_1 - (V_2 - 30)}{10} \\ \frac{V_1 - (V_2 - 30)}{10} + 7 = \frac{V_2 - V_3}{20} \\ \frac{V_2 - V_3}{20} = \frac{V_3}{10} + 2 \end{cases}$$

6'

$$\begin{cases} V_1 = 40 \text{ V} \\ V_2 = 100 \text{ V} \\ V_3 = 20 \text{ V} \end{cases}$$

3'

$$(b) \quad i_1 = \frac{V_1}{10}$$

$$i_1 = 4 \text{ A}$$

$$i_2 = \frac{V_1 - (V_2 - 30)}{10}$$

$$i_2 = -3 \text{ A}$$

$$i_3 = \frac{V_2 - V_3}{20}$$

$$i_3 = 4 \text{ A}$$

$$i_4 = \frac{V_3}{10}$$


$$i_4 = 2 \text{ A}$$

$$V_0 = V_2 - V_3$$

$$V_0 = 80 \text{ V}$$

5'

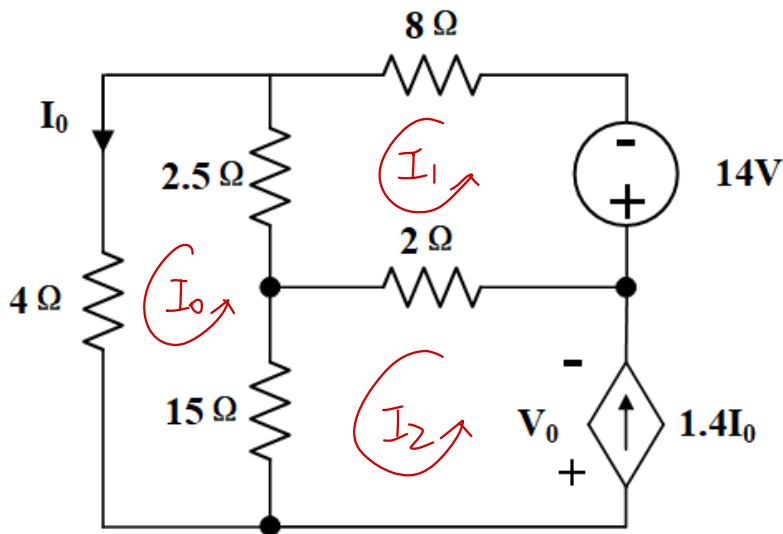3. Apply mesh analysis method to obtain I_0 and V_0 in the following circuit.



$$\begin{cases} 4I_0 + 15(I_0 - I_2) + 2.5(I_0 - I_1) = 0 \\ 2.5(I_1 - I_0) + 2(I_1 - I_2) + 8I_1 + 14 = 0 \\ I_2 = 1.4I_0 \end{cases}$$

$$\begin{cases} I_0 = 5A \\ I_1 = 1A \\ I_2 = 7A \end{cases}$$

6'

$$2(I_2 - I_1) + 15(I_2 - I_0) + V_0 = 0$$

$$V_0 = 2(I_1 - I_2) + 15(I_0 - I_2)$$

$$= 2 \times (-6) + 15 \times (-2)$$

$$= -42V$$


2'

15

4. For the circuit below,

(a) apply nodal analysis method to find V_a , V_b .(b) apply mesh analysis method to find V_a , V_b .

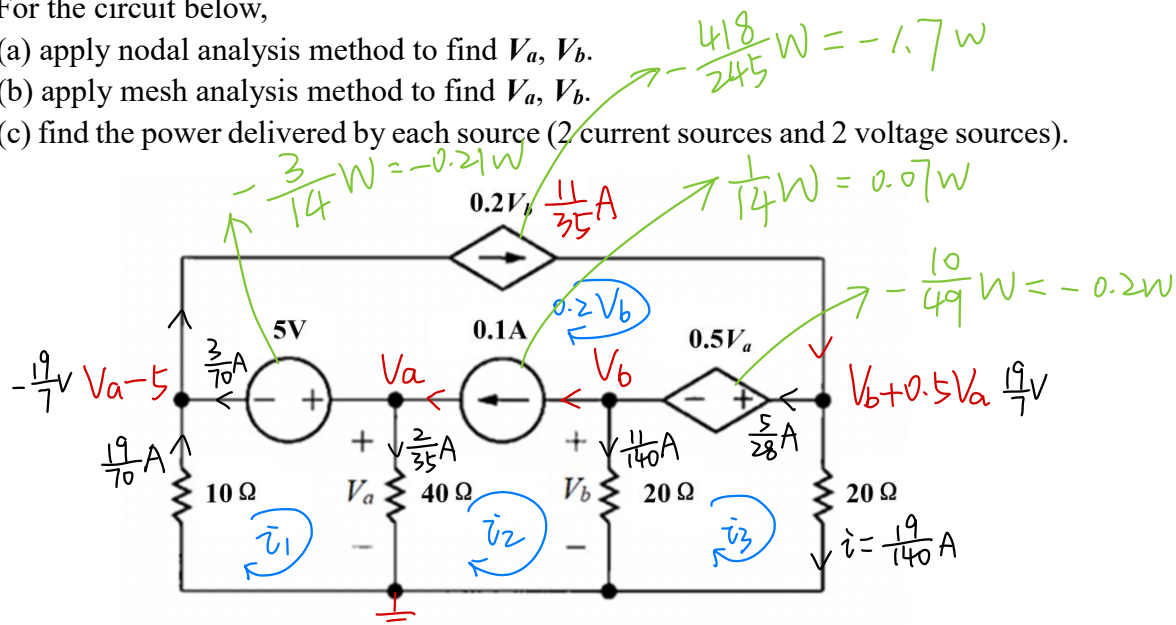(c) find the power delivered by each source (2 current sources and 2 voltage sources).



15 (a)
$$\begin{cases} \frac{V_a - 5}{10} + 0.2V_b + \frac{V_a}{40} = 0.1 \\ 0.1 + \frac{V_b}{20} + \frac{V_b + 0.5V_a}{20} = 0.2V_b \end{cases}$$

$$\begin{cases} V_a = \frac{16}{7} \text{ V} = 2.28 \text{ V} \\ V_b = \frac{11}{7} \text{ V} = 1.57 \text{ V} \end{cases}$$

15 (b)
$$\begin{cases} 10i_1 + 40(i_1 - i_2) = 5 \\ 40(i_2 - i_1) + 20(i_2 - i_3) = V_b - V_a \\ 20(i_3 - i_2) + 20i_3 + 0.5V_a = 0 \\ 0.2V_b - i_2 = 0.1 \\ V_b = 20(i_2 - i_3) \end{cases}$$


$$\begin{cases} V_a = \frac{16}{7} \text{ V} \\ V_b = \frac{11}{7} \text{ V} \end{cases}$$

15 (c)

5. For the circuit below, $R_1 = 1\Omega$, $R_2 = 2\Omega$,

(a) Apply nodal or mesh analysis method to find i_1

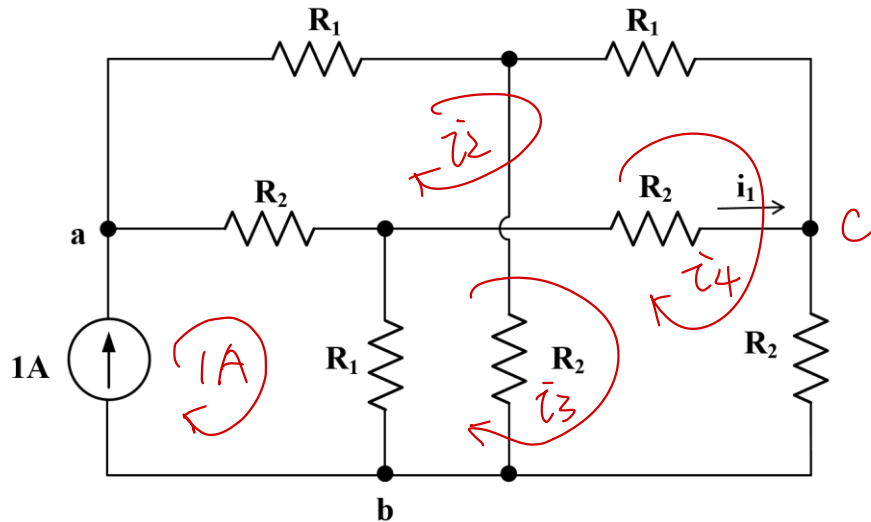
(b) If disconnect the current source from the circuit, try to find the equivalent resistance of the pure resistor network between node a and b.



$$\begin{cases} 2i_2 + i_4 + 2(i_2 - i_3) + 2(i_2 - 1) = 0 \\ i_2 + i_4 + 2(i_3 + i_4) + 2i_4 = 0 \\ i_3 - 1 + 2(i_3 - i_2) + 2(i_3 + i_4) = 0 \end{cases}$$

$$i_2 = \frac{18}{31} A \quad i_3 = \frac{53}{93} A \quad i_4 = -\frac{32}{93} A$$
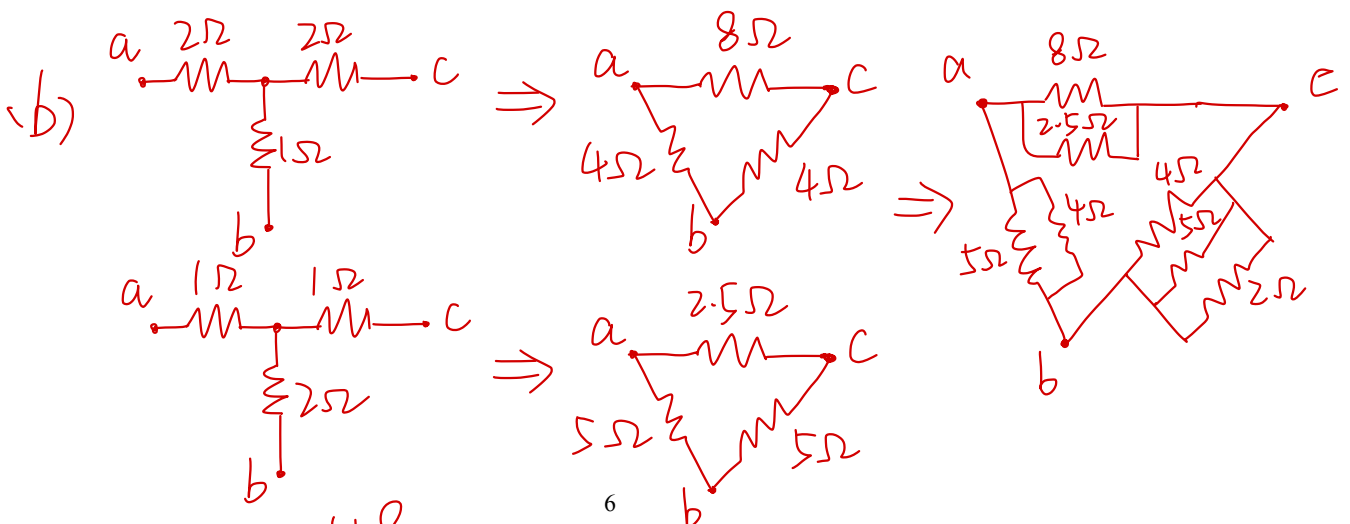
$$i_1 = i_3 - i_2 = -\frac{1}{93} A \approx -0.01075 A$$



$$R_{eq} = \frac{118}{93} \approx 1.2688 \Omega$$