

Homework 3


Due date: 25th, Oct.

Turn in your homework in class

Rules:


- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. (a). A capacitor with 10mF capacitance has the terminal voltage:

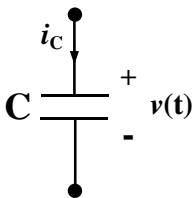
$$v(t) = \begin{cases} 15 \text{ V} & t \leq 0 \\ Ae^{-100t} + Be^{-500t} \text{ V} & t \geq 0 \end{cases}$$


Assuming that the initial current ($t=0$ s) on the capacitor is 5 A, please find: (1). constants A and B , (2). the capacitor current for $t > 0$, and (3). the energy of capacitor at $t=1$ ms.

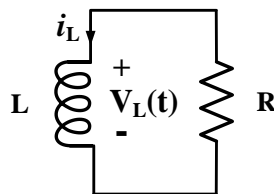
- (b). A 200-mH inductor is connected in parallel with a resistor. The current through the inductor is $i_L(t) = 10e^{-800t}$ mA. Please find the voltage $V_L(t)$ on the inductor with respect to time, as well as the energy of the inductor at $t = 1$ ms.



- (c). For the capacitance circuit below, $C_1 = 1 \mu\text{F}$, $C_2 = 0.125 \mu\text{F}$, $C_3 = C_4 = 0.25 \mu\text{F}$. Initially the switch is at “off state”, and the voltage on the capacitor C_1 is 10 V while other capacitors have the same voltage drop of 0 V. At $t=0$ s, the switch is closed. Please find the voltage V_2 after the circuit becomes stable. Note that no loss need to be considered.

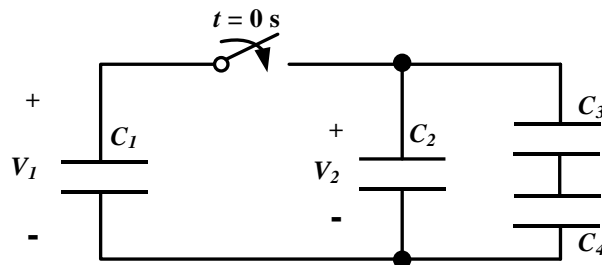


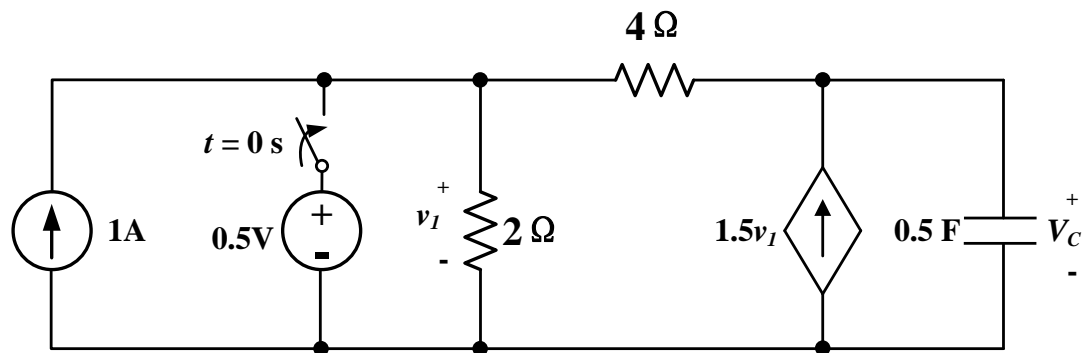2. In the following circuit, the switch is open for a long time for $t < 0$ s. At $t = 0$ s, the switch closes immediately. Please find out the voltage on 0.5 F capacitor ($V_C(t)$) when $t \geq 0$ s.




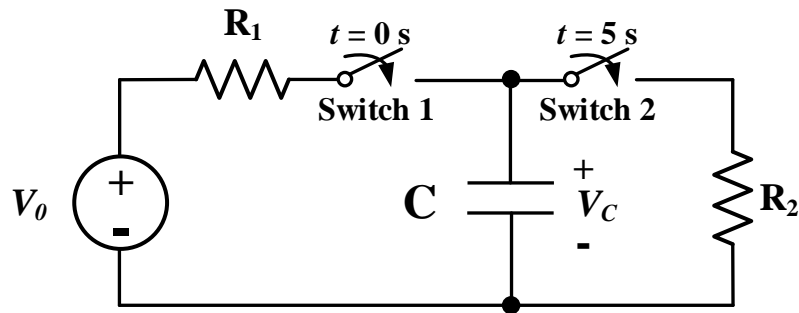3. The circuit contains two switches, both of which have been open for a long time before $t = 0$. **Switch 1** closes at $t = 0$ s, and **switch 2** closes at $t = 5$ s. Determine $V_C(t)$ for $t \geq 0$, given that $V_0=24$ V, $R_1=R_2=16$ k Ω , and $C=250$ μ F. Assume $V_C(0)=1$ V.

Also, please sketch $V_C(t)$, capacitor current $I_C(t)$, current on R_1 ($I_{R1}(t)$), and voltage on R_1 ($V_{R1}(t)$) for $t > 0$ s, respectively.



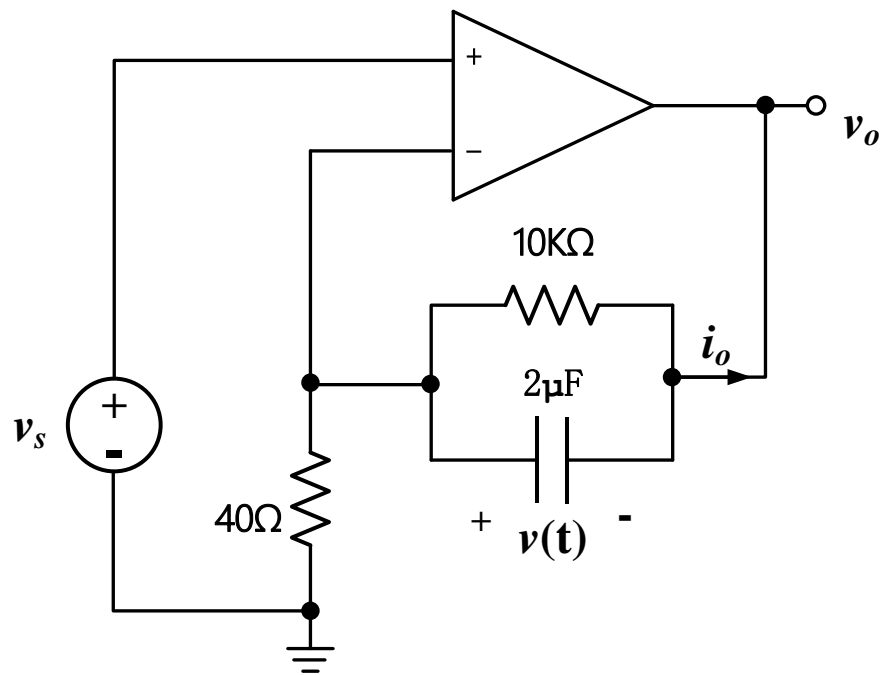
4. In the circuit below, find $v_o(t)$ and $i_o(t)$, given that $v_s = 4u(t)$ V and $v(0)=1$ V. (Note that $u(t)$ is step function.)



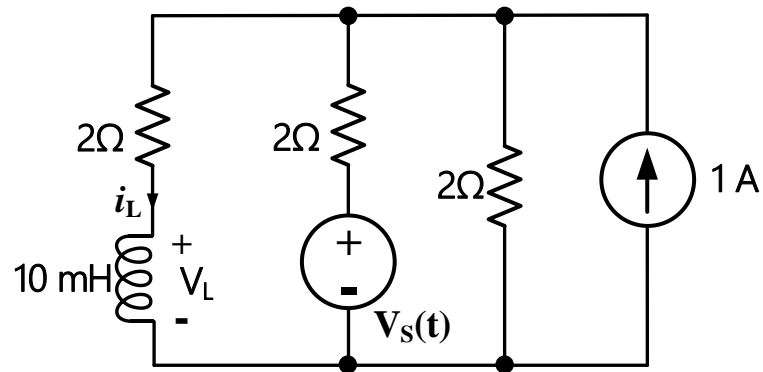5. For the circuit below, the independent voltage source has the voltage:

$$V_s(t) = \begin{cases} 0 \text{ V} & t < 0 \text{ s} \\ e^{-100t} \text{ V} & t \geq 0 \text{ s} \end{cases}$$

Please find the current on the inductor in terms of time ($i_L(t)$) for $t \geq 0$ s.



6. For the circuit below, assume the operational amplifier is always working in its linear mode, $V_C(0^-) = 5\text{V}$, $R_1 = 5\text{k}\Omega$, $R_2 = 500\Omega$, $C = 5\mu\text{F}$, and

$$V_S(t) = \begin{cases} 0, & t \leq 0 \\ e^{-200t}, & t > 0 \end{cases} \quad (\text{unit for } V_S(t) \text{ is V})$$

Find the output voltage of the operational amplifier $v_0(t)$ for $t > 0$.

