

ShanghaiTech University

EE 115B: Digital Circuits


Fall 2022

Lecture 15

Hengzhao Yang
November 22, 2022

Basic SR latch

- Characteristic table (alternate)

 



S	R	Q	\bar{Q}
0	0	Latched	
0	1	0	1
1	0	1	0
1	1	Metastable	

Source: https://en.wikibooks.org/wiki/Digital_Circuits/Latches

- S and R are **active high** signals.

Basic SR latch

- Characteristic table (alternate)

  


S_D	R_D	Q	Q^*
0	0	0	0
0	0	1	1
1	0	0	1
1	0	1	1
0	1	0	0
0	1	1	0
1	1	0	0 ^①
1	1	1	0 ^①

① S_D 、 R_D 的 1 状态同时消失后状态不定。


Basic SR latch

 - Timing diagram (assume no propagation delay)



Alternate basic SR latch

 - Implementation: NAND gates
- Set and reset are **active low** signals.
- Left to right: circuit, circuit symbol, and characteristic table



$\bar{S}\bar{R}$ latch operation		
\bar{S}	\bar{R}	Action
0	0	Not allowed
0	1	$Q = 1$
1	0	$Q = 0$
1	1	No change


Source: [https://en.wikipedia.org/wiki/Flip-flop_\(electronics\)](https://en.wikipedia.org/wiki/Flip-flop_(electronics))

Gated SR latch

- Gated SR latch
 - Add a signal to control the time when the set and reset signals change values
- Two implementations
 - NOR gates
 - NAND gates


Gated SR latch with NOR gates

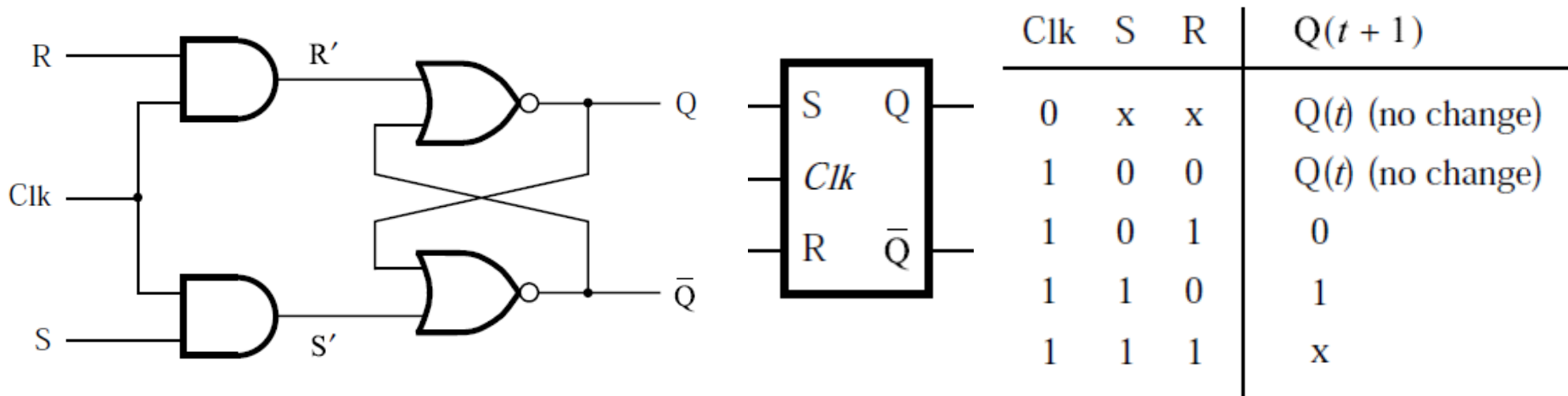- Control signal: Clk
 - Clk=0, disabled: latched
 - Clk=1, enabled: basic SR latch
 - Left to right: circuit, circuit symbol, and characteristic table




Gated SR latch with NOR gates

- Timing diagram

 

Gated SR latch with NAND gates

- Circuit

 



- Same circuit symbol and characteristic table

Clk	S	R	Q^+	Comments
0	\times	\times	Q	No change, typically stable states $Q = 0, \bar{Q} = 1$ or $Q = 1, \bar{Q} = 0$
1	0	0	Q	No change, typically stable states $Q = 0, \bar{Q} = 1$ or $Q = 1, \bar{Q} = 0$
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	\times	Avoid this setting

Source: <http://ecse.bd.psu.edu/cse271/memelem.pdf>


Summary: gated SR latch

  - Two implementations
 - NOR gates
 - **NAND gates**
 - Preferred (requires fewer transistors)




Gated D latch

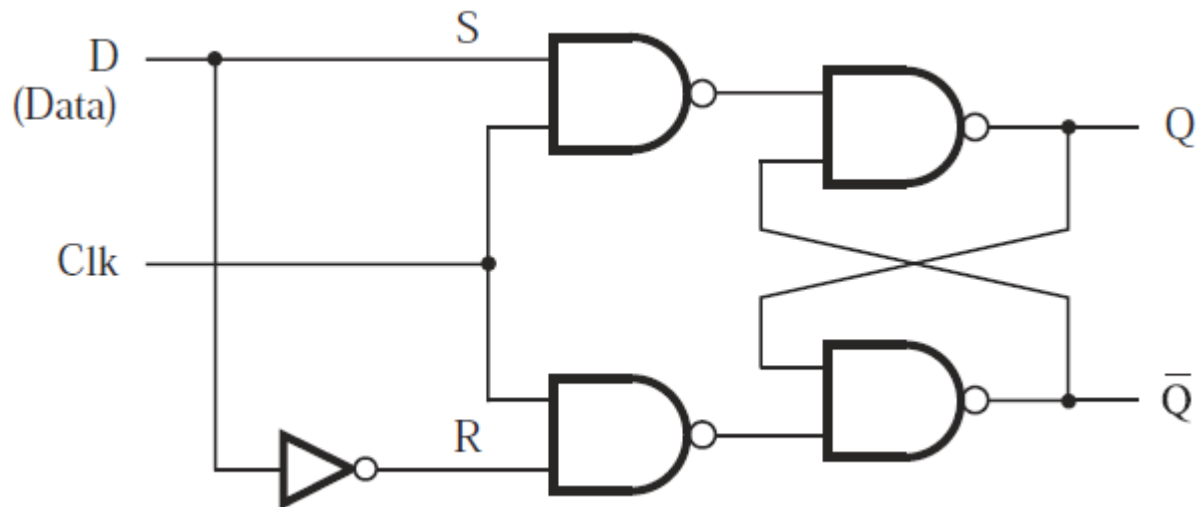- Only one input: D (data)
- Functionality
 - Clk=1: output (Q) follows input (D)
 - Clk=0: Q holds its previous value
- Circuit




Gated D latch

 - Circuit symbol and characteristic table



Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1


- Timing diagram

 

Level sensitive circuits

- Level sensitive circuits
 - Circuit output is controlled by **clock level**
 - Circuit output keeps changing according to inputs when **clock is active**
 - Circuit **output value may change multiple times** when clock is active
- Examples
 - Gated SR latch
 - Gated D latch
 - Clock is active high: $\text{Clk}=1$

VHDL code for gated D latch

 

Clk	D	$Q(t + 1)$
0	x	$Q(t)$
1	0	0
1	1	1

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT ( D, Clk : IN  STD_LOGIC ;
          Q       : OUT STD_LOGIC) ;
END latch ;
    
```

```

ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
    
```