

**Homework 8**Due data: Jun. 15<sup>th</sup>

Turn in your homework before 8:15 AM

Rules:

- Please work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

**1**

[8 points] Calculate the Laplace transform of the following functions. You can use definitions or properties of Laplace transform. Hint:  $\cosh(t) = \frac{e^t + e^{-t}}{2}$

(a).  $f(t) = ((1-t)e^{-t} - te^{-t} \sin t)u(t)$

(b).  $g(t) = 8e^{-3t} \cosh(t)u(t-2)$

**2**

[12 points] Calculate the inverse Laplace transform of the following functions.

(a).  $F(s) = \frac{s^2 - 2s + 1}{4(s-2)(s^2 + 2s + 4)}$

(b).  $G(s) = \frac{4(s-1)}{s^4 - 1} + \frac{7}{s(s+1)^3} + 1$

(c).  $P(s) = \frac{s e^{-\pi s}}{s^2 + 5}$

**3**

[18 points] The function  $f(t)$  is shown in **Fig. 3**.  $f(t) = 0$  for  $t \leq 0$ .

- (a). Calculate the Laplace transform of  $f(t)$ .
- (b). Verify the initial value theorem for  $f(t)$ .
- (c). Verify the final value theorem for  $f(t)$ .

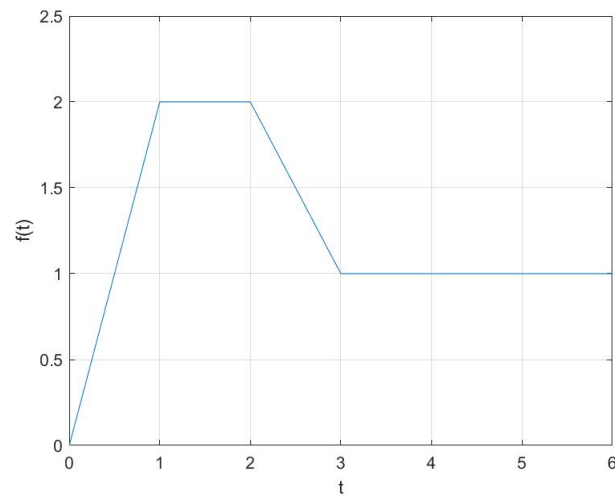


Figure 3:

## 4

[18 points] The circuit is shown in **Fig.4**. Assume the circuit has reached steady state before  $t = 0$ s. Given that  $C = \frac{1}{9}\text{F}$ ,  $R = 3\Omega$ ,  $L = 0.6\text{H}$ ,  $i(t) = te^{-t}u(t) + 5u(-t)$  A, determine  $U_1(t)$  for  $t > 0$ s using Laplace domain method.

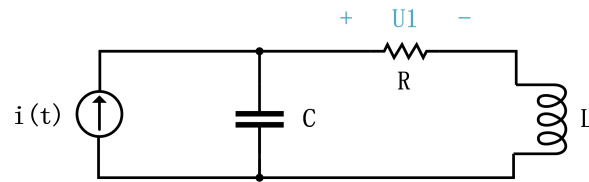


Figure 4:

## 5

[18 points] The circuit is shown in **Fig. 5**. The ideal operator amplifier is working at its linear region and  $v_1(0^-) = 3V$ ,  $v_2(0^-) = 2V$ . And a voltage source is applied to the circuit with  $v_s(t) = e^{-t}u(t)V$ . Determine the  $v_o(t)$  for  $t > 0$  s with Laplace transform.

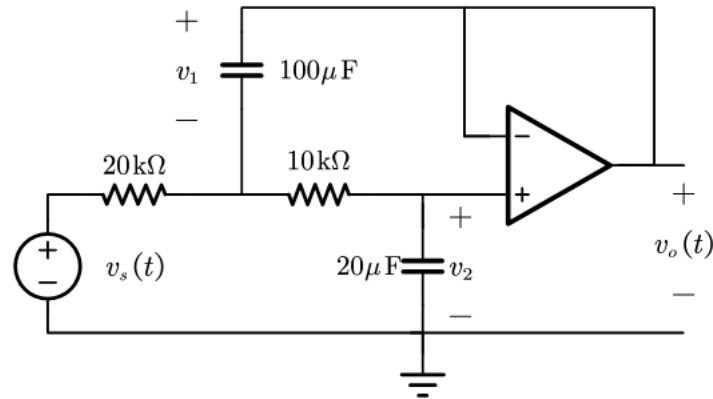


Figure 5:

## 6

[26 points] The circuit is shown in **Fig. 6**. Given that  $U_C(0^-)=1\text{V}$ ,  $i_C(0^-)=2\text{A}$ .

- Use the time domain method to determine  $i_L(t)$  for  $t > 0\text{s}$ .
- Use the Laplace transform to determine  $i_L(t)$  for  $t > 0\text{s}$ .
- Use the phasor domain method to determine  $i_L(t)$  if the circuit has reached the sinusoidal steady state.
- Determine the value of  $i_L(t)$  at  $t = 1\text{s}$  and  $t = 100\text{s}$  using the three expressions you obtained above respectively. Explain why the values are the same or different.

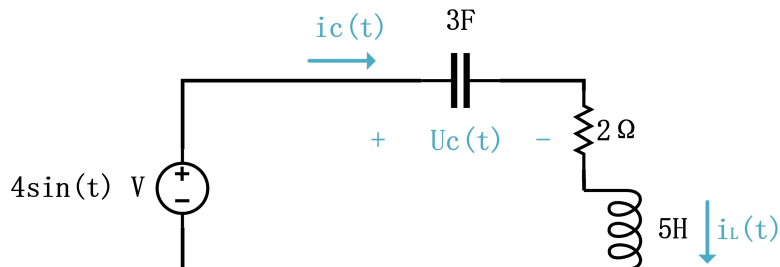


Figure 6: