





Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits
- Others

RC and RL Circuits

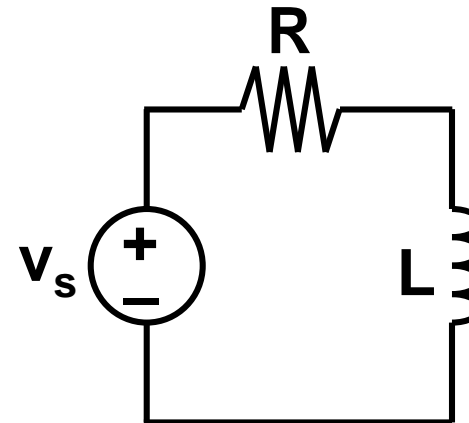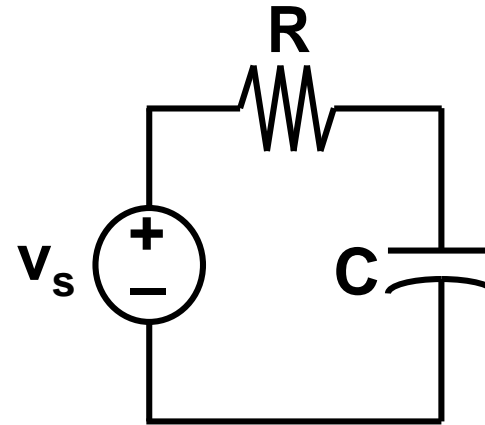- A circuit that contains only sources, resistors and a capacitor is called an **RC circuit**.
- A circuit that contains only sources, resistors and an inductor is called an **RL circuit**.





Natural Response


Behavior (*i.e.*, current and voltage) when stored energy in the inductor or capacitor is released to the resistive part of the network (containing no independent sources).

Natural Response of a Charged Capacitor

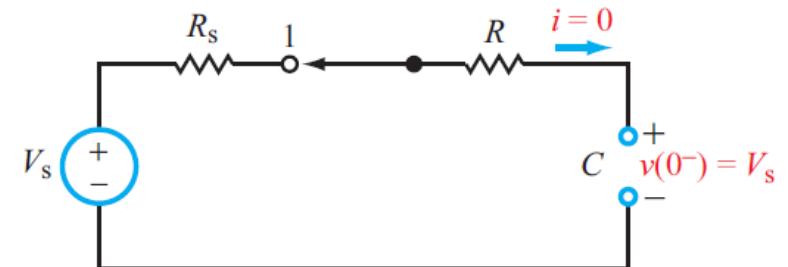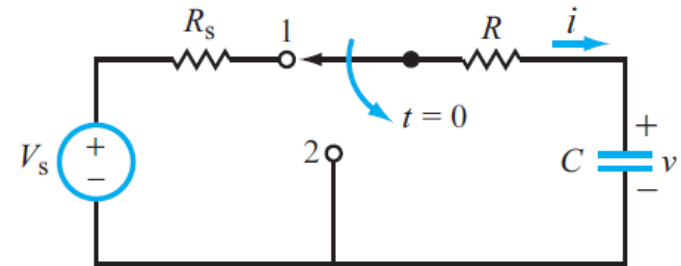(a) $t = 0^-$ is the instant just before the switch is moved from terminal 1 to terminal 2;




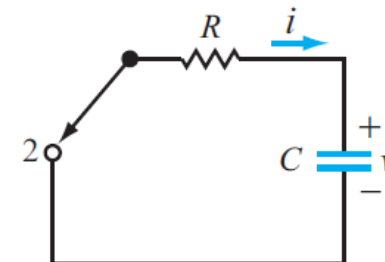(b) $t = 0$ is the instant just after it was moved, $t = 0$ is synonymous with $t = 0^+$.








Natural Response of a Charged Capacitor

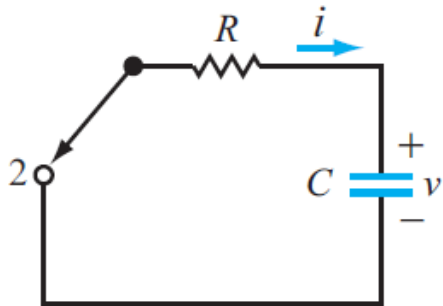




Natural Response of RC Circuit

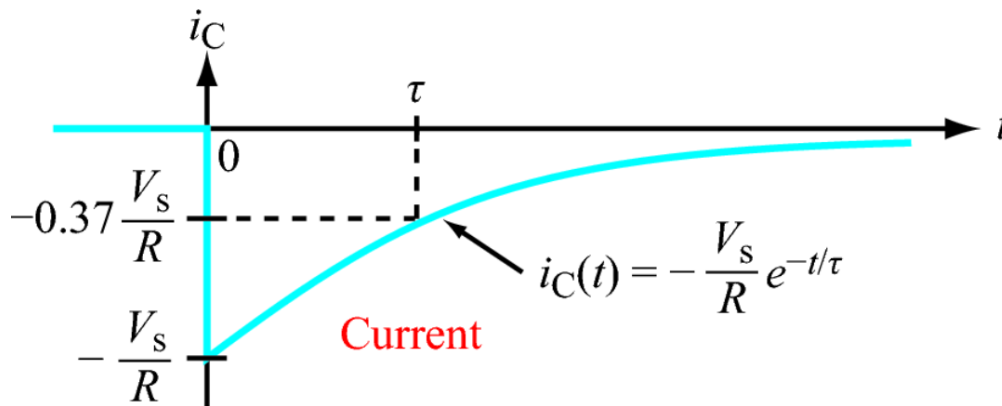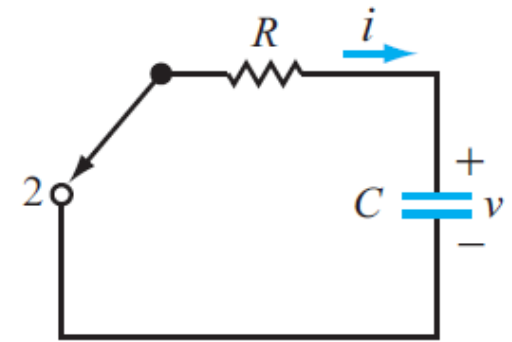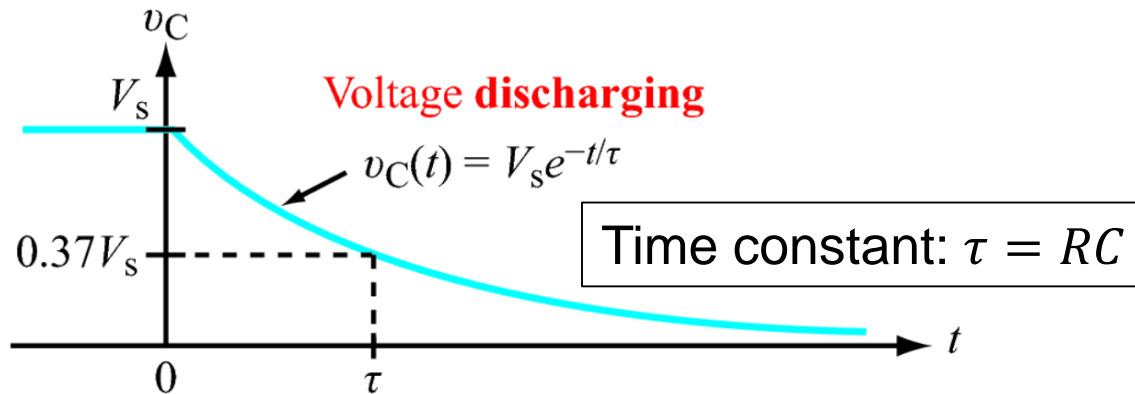




Time Constant $\tau (= RC)$

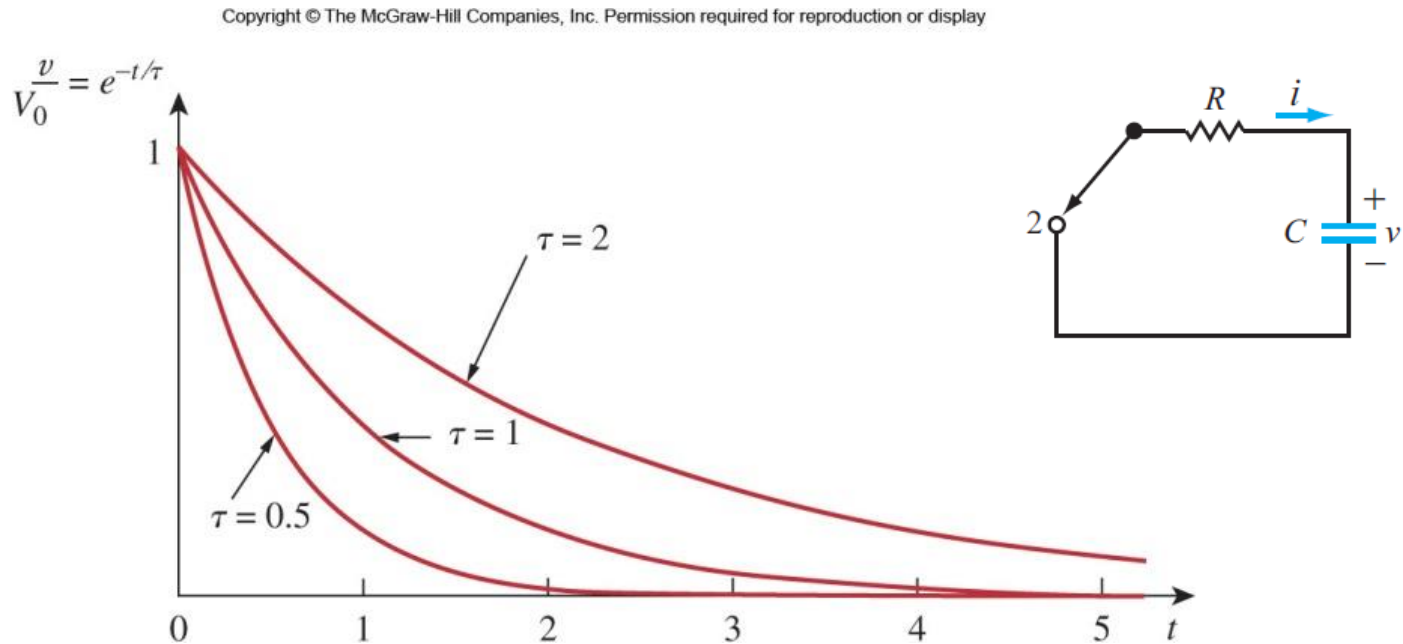- A circuit with a small time constant has a fast response and vice versa.






Natural Response of the RL Circuit

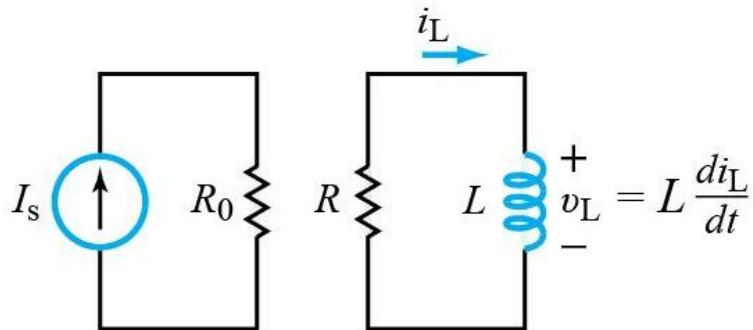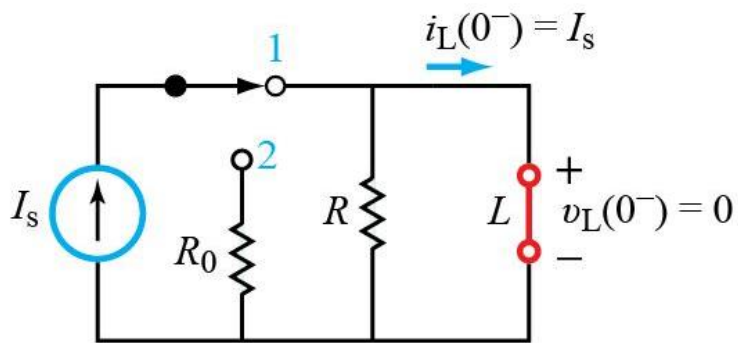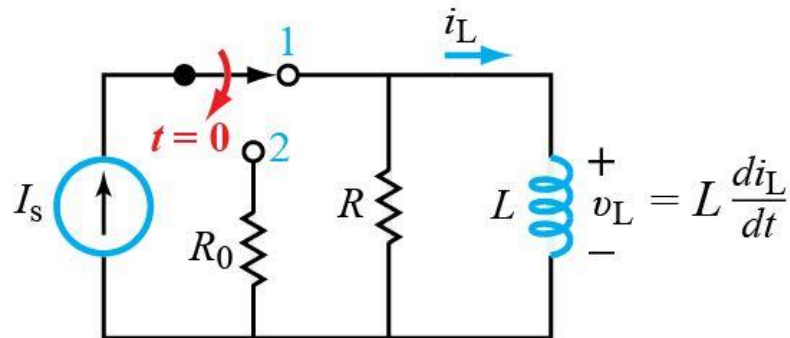




Natural Response of the RL Circuit

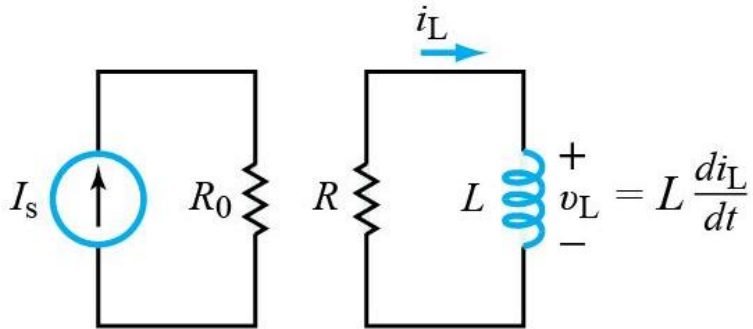




Natural Response of the RL Circuit

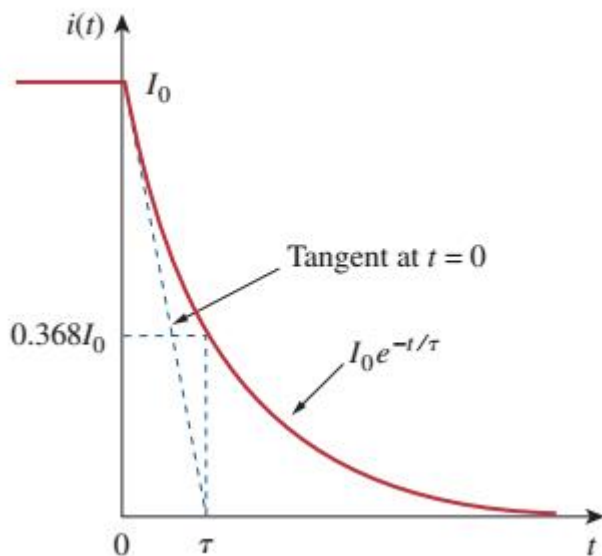

Natural Response Summary

RC Circuit

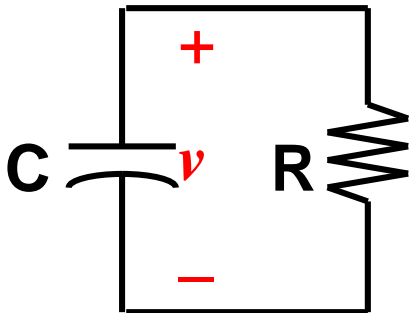


- **Capacitor voltage** cannot change instantaneously

$$v(0^-) = v(0^+)$$

$$v(t) = v(0)e^{-t/\tau}$$

- time constant $\tau = RC$

RL Circuit

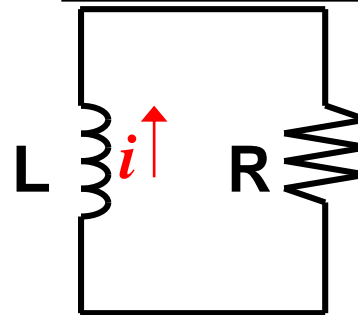

- **Inductor current** cannot change instantaneously

$$i(0^-) = i(0^+)$$

$$i(t) = i(0)e^{-t/\tau}$$


- time constant $\tau = \frac{L}{R}$



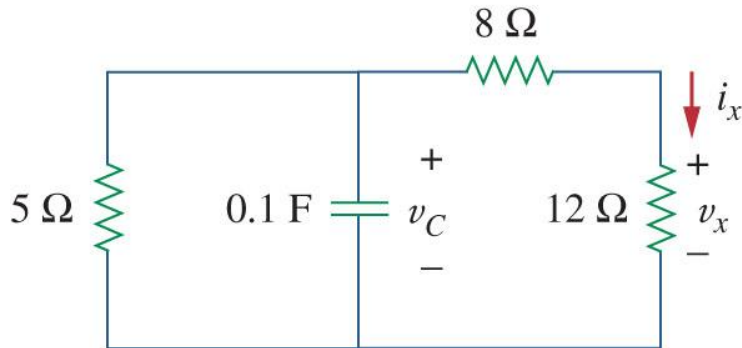Example

- In the circuit below, let $v_C(t = 0) = 15\text{V}$. Find v_C , v_x , and i_x for $t > 0$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






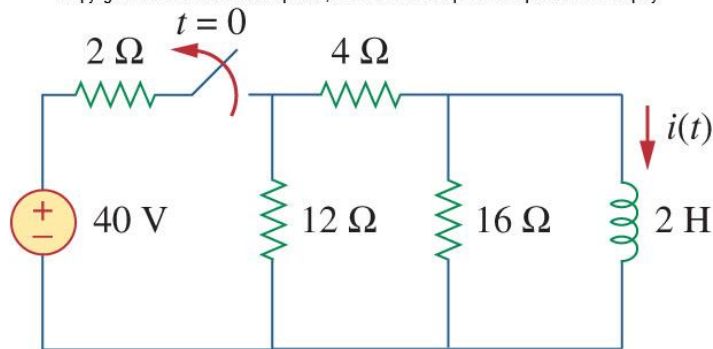
Example

- The switch in the circuit below has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



When $t < 0$

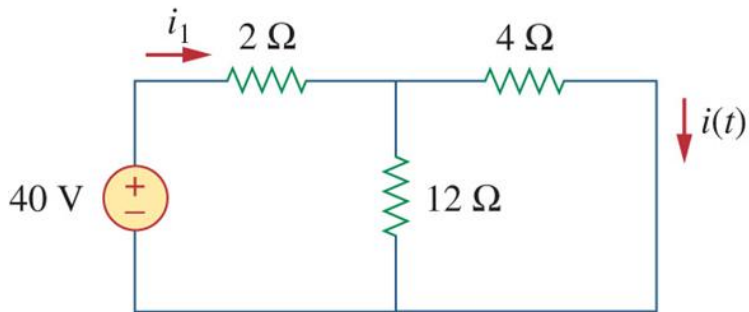

When $t > 0$

