



Lecture 9

- AC Power Calculation




Outline

- Instantaneous power
- Average power
- Apparent power
- Power factor
- Complex power



AC Power in Time Domain: Instantaneous

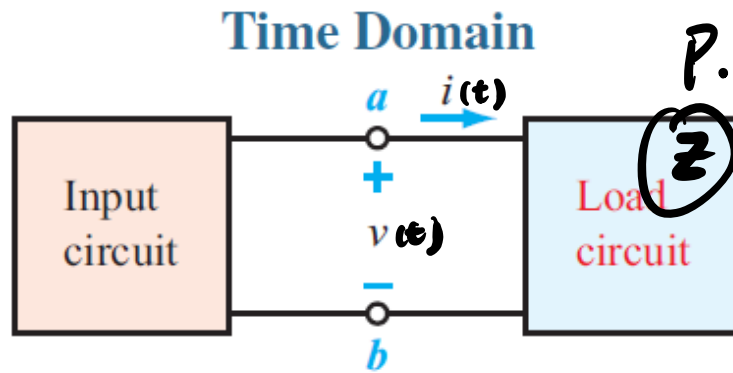

P.S.C.

$$v(t) \rightarrow \dot{V} = V_m \angle \theta_v$$

$$i(t) \rightarrow \dot{I} = I_m \angle \theta_i$$

$$Z = \frac{\dot{V}}{\dot{I}} = \frac{V_m}{I_m} \angle \theta_v - \theta_i = R + jX$$

$$v(t) = V_m \cos(\omega t + \theta_v) \quad i(t) = I_m \cos(\omega t + \theta_i)$$

Instantaneous power:
power at any instant of time.

$\Rightarrow |\theta_v - \theta_i| \leq 90^\circ$

Re


$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

abs.

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$




AC Power in Time Domain: Instantaneous

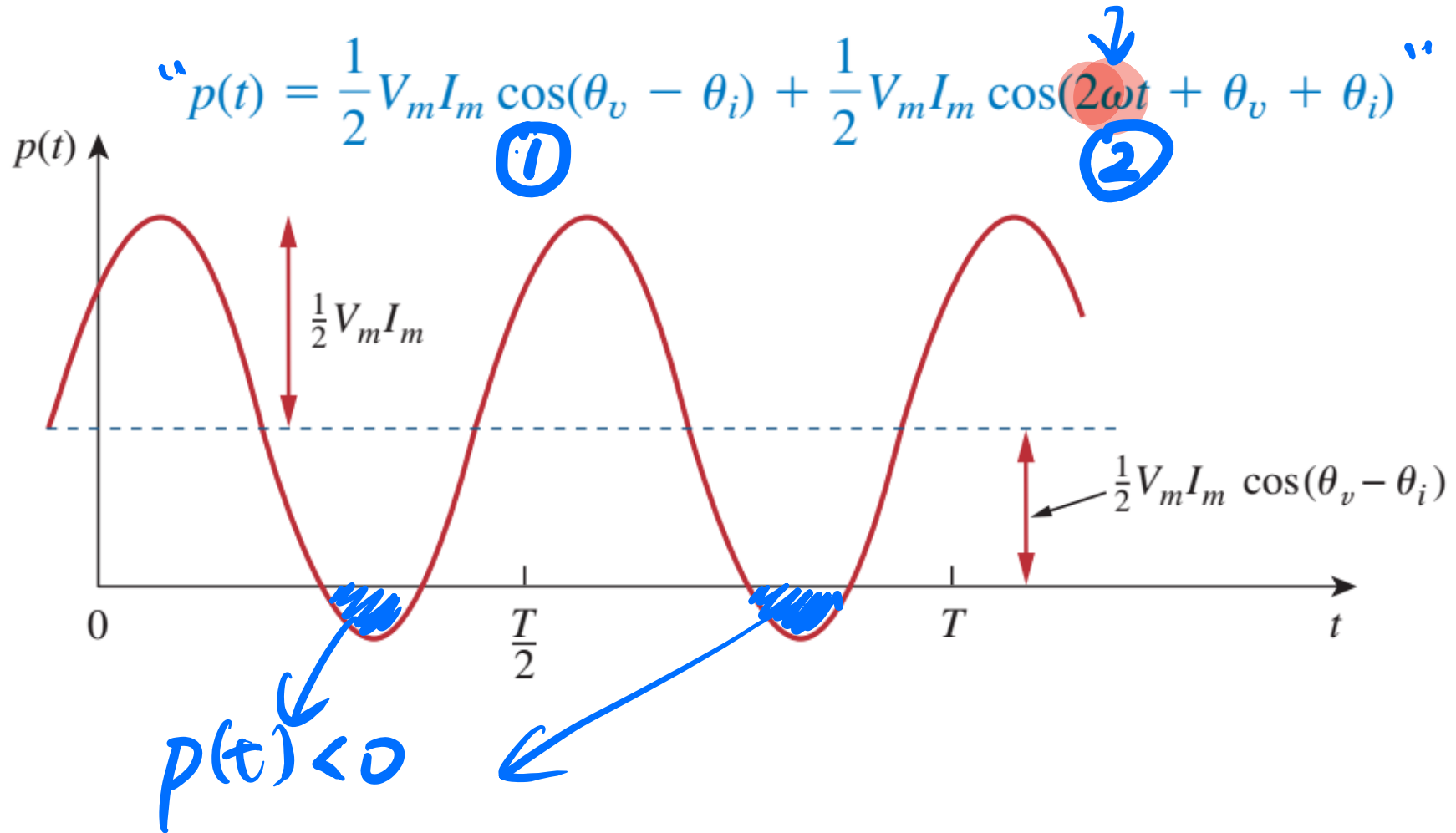

Average Power P (Capitalized)

$$v(t) = V_m \cos(\omega t + \theta_v) \quad i(t) = I_m \cos(\omega t + \theta_i)$$
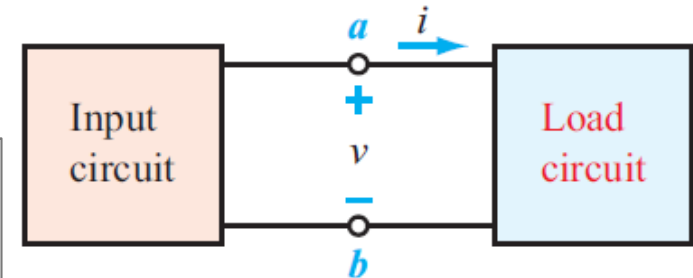
$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$



Average (or real) power (unit: watts) \mathcal{W}

The **average power**, in watts, is the average of the instantaneous power over one period.

$$P = \frac{1}{T} \int_0^T p(t) dt$$



Average Power P (time domain)

$$\begin{aligned} P &= \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt \\ &\quad + \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt \\ &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt \\ &\quad + \frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt \end{aligned}$$

ω

$$P = \frac{1}{2} \underline{V_m} \underline{I_m} \cos(\underline{\theta_v} - \underline{\theta_i})$$



Average Power P (phasor domain)

$$v(t) = V_m \cos(\omega t + \theta_v) \quad i(t) = I_m \cos(\omega t + \theta_i)$$

$$\dot{\mathbf{V}} = V_m \angle \theta_v \text{ and } \dot{\mathbf{I}} = I_m \angle \theta_i, \quad \dot{\mathbf{I}}^* = I_m \angle \underline{-\theta_i}$$

$$\begin{aligned} \underline{\frac{1}{2} \dot{\mathbf{V}} \dot{\mathbf{I}}^*} &= \frac{1}{2} V_m I_m \angle \theta_v - \theta_i \\ &= \frac{1}{2} V_m I_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)] \end{aligned}$$

$$P = \frac{1}{2} \text{Re}[\underline{\dot{\mathbf{V}} \dot{\mathbf{I}}^*}] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$



Two special cases for average power P

- For a purely resistive load R : $\dot{V} = V_m \angle \theta_v$, $\dot{I} = I_m \angle \theta_i$, $\theta_v - \theta_i = 0$

$$\dot{V} = R \cdot \dot{I}$$

$$\underline{P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{1}{2} |\dot{I}|^2 R} \quad \text{where } |\dot{I}|^2 = \dot{I} \times \dot{I}^* > 0$$

- For a purely reactive load:

$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

{

cap: $\theta_v - \theta_i = -90^\circ$

ind: $\theta_v - \theta_i = 90^\circ$


ave.

A resistive load (R) absorbs power ^{ave.} at all times, while a reactive load (L or C) absorbs zero average power.

Effective Value (RMS)

- For any periodic function $x(t)$ in general, its rms value is
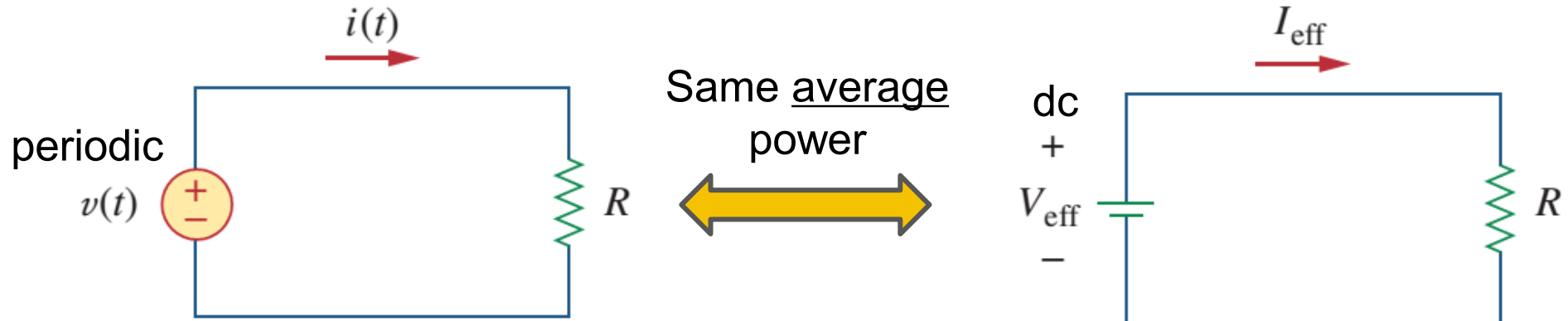
$$\frac{1}{T} \int_0^T \frac{v(t)}{R} \cdot v(t) dt \quad \underline{X_{\text{eff}}} = \underline{X_{\text{rms}}} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt} \quad \frac{1}{T} \int_0^T \frac{V_{\text{eff}}}{R} \cdot V_{\text{eff}} dt$$



$$\Rightarrow \underline{V_{\text{eff}}} = \sqrt{\frac{1}{T} \int_0^T \underline{v^2(t)} dt}$$


Similarly:

$$\underline{I_{\text{eff}}} = \sqrt{\frac{1}{T} \int_0^T \underline{i^2(t)} dt}$$

RMS of a sinusoidal signal

- The RMS value of $v(t) = V_m \cos(\omega t + \phi)$ is
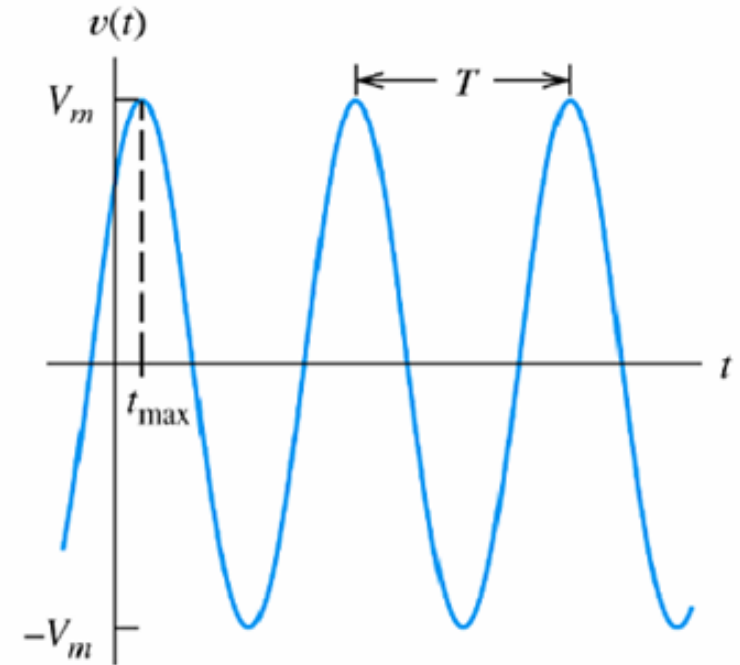
$$\begin{aligned}
 V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt} \\
 &= \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cdot \cos^2(\omega t + \phi) dt} \\
 &\quad \text{with the identity } \cos^2(x) = \frac{1 + \cos(2x)}{2} \\
 &= \frac{V_m}{\sqrt{2}}
 \end{aligned}$$



Average
Power

$$\begin{aligned}
 P &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\
 &= \underline{V_{\text{rms}} \cdot I_{\text{rms}}} \quad = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)
 \end{aligned}$$

$$V_s: \quad \underline{v(t) = V_m \cos(\omega t + \phi)} \quad 5 \cos(2t + 30^\circ)$$

$$\left. \begin{array}{l} \text{Mag:} \end{array} \right\} \quad \underline{\dot{V}_m = V_m \angle \phi} \rightarrow \dot{V}_m = 5 \angle 30^\circ$$

$$\left. \begin{array}{l} \text{RMS:} \end{array} \right\} \quad \underline{\dot{V}_{rms} = V_{rms} \angle \phi} \quad \dot{V}_{rms} = \frac{5}{\sqrt{2}} \angle 30^\circ$$

$$\quad \quad \quad = \frac{V_m}{\sqrt{2}} \angle \phi$$



Outline

- Instantaneous power
- Average power
- Apparent power
- Power factor
- Complex power



Apparent Power

$$\begin{aligned} \downarrow P &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\ &= \dot{V}_{rms} \cdot \dot{I}_{rms}^* = \boxed{V_{rms} I_{rms}} \cos(\theta_v - \theta_i) \end{aligned}$$

$$\boxed{S \text{ or } S_a = V_{rms} I_{rms}} \quad \text{Unit: volt-amp (VA)}$$

It seems apparent that the power should be the voltage-current product, *by analogy with dc resistive circuits*.



Power Factor


$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\ = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

- The power factor

$$\text{pf} = \frac{P}{S_a} = \cos(\theta_v - \theta_i)$$

- $(\theta_v - \theta_i)$ is called power factor angle.
 - >0 means a *lagging* pf (current lags voltage)
 - <0 means a *leading* pf (current leads voltage)
- pf ranges from 0 to 1.

Power Factor-2

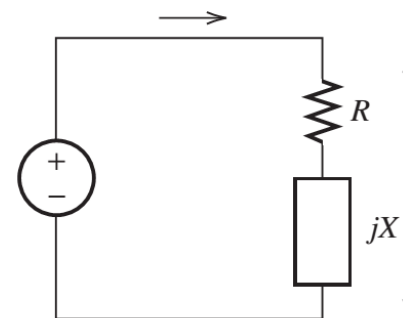

Power factor leading and lagging relationships for a load $\mathbf{Z} = R + jX$.

Load Type	$\phi_z = (\theta_v - \theta_i)$	I-V Relationship	pf
Purely Resistive ($X = 0$)	$\phi_z = 0$	\mathbf{I} in-phase with \mathbf{V}	1
Inductive ($X > 0$)	$0 < \phi_z \leq 90^\circ$	\mathbf{I} lags \mathbf{V}	lagging
Purely Inductive ($X > 0$ and $R = 0$)	$\phi_z = 90^\circ$	\mathbf{I} lags \mathbf{V} by 90°	lagging
Capacitive ($X < 0$)	$-90^\circ \leq \phi_z < 0$	\mathbf{I} leads \mathbf{V}	leading
Purely Capacitive ($X < 0$ and $R = 0$)	$\phi_z = -90^\circ$	\mathbf{I} leads \mathbf{V} by 90°	leading



Power Factor-3

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\ = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

- The power factor

$$\text{pf} = \frac{P}{S_a} = \cos(\theta_v - \theta_i)$$

- $(\theta_v - \theta_i)$ is called power factor angle.
- $(\theta_v - \theta_i)$ is equal to the angle of the load impedance

$$\mathbf{Z} = \frac{\dot{\mathbf{V}}}{\dot{\mathbf{I}}} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i} = \frac{V_m}{I_m} \angle \theta_v - \theta_i$$

Also

$$\mathbf{Z} = \frac{\dot{\mathbf{V}}}{\dot{\mathbf{I}}} = \frac{\dot{\mathbf{V}}_{\text{rms}}}{\dot{\mathbf{I}}_{\text{rms}}} = \frac{V_{\text{rms}}}{I_{\text{rms}}} \angle \theta_v - \theta_i$$



Outline

- Instantaneous power
- Average power
- Apparent power
- Power factor
- **Complex power**



Complex Power

$$v(t) = V_m \cos(\omega t + \theta_v) \Rightarrow \mathbf{V} = V_m \angle \theta_v$$

$$i(t) = I_m \cos(\omega t + \theta_i) \Rightarrow \mathbf{I} = I_m \angle \theta_i$$

We observe that:

$$\begin{aligned} \frac{1}{2} \mathbf{V} \mathbf{I}^* &= \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i) \\ &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + j \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \end{aligned}$$

- Define a **single power metric**


$$\tilde{\mathbf{S}} = \frac{1}{2} \dot{\mathbf{V}} \dot{\mathbf{I}}^* = \dot{\mathbf{V}}_{\text{rms}} \dot{\mathbf{I}}_{\text{rms}}^* = V_{\text{rms}} I_{\text{rms}} \angle (\theta_v - \theta_i) = P + jQ$$

Unit: volt-amp (VA)


Complex power is important in power analysis because it contains *all* the information pertaining to the power absorbed by a given load.

$$\tilde{S} = \frac{1}{2} \dot{V} \dot{I}^* = \dot{V}_{rms} \dot{I}_{rms}^* = V_{rms} I_{rms} \angle(\theta_v - \theta_i) = P + jQ$$

Unit: volt-amp (VA)

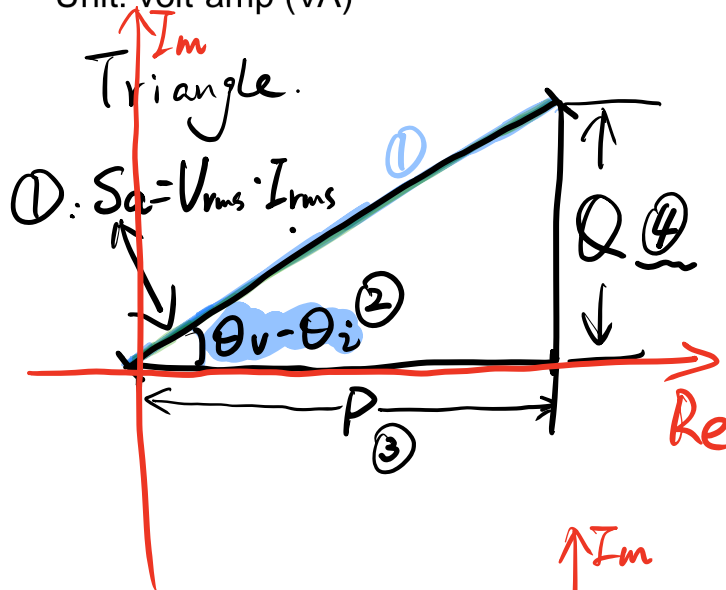

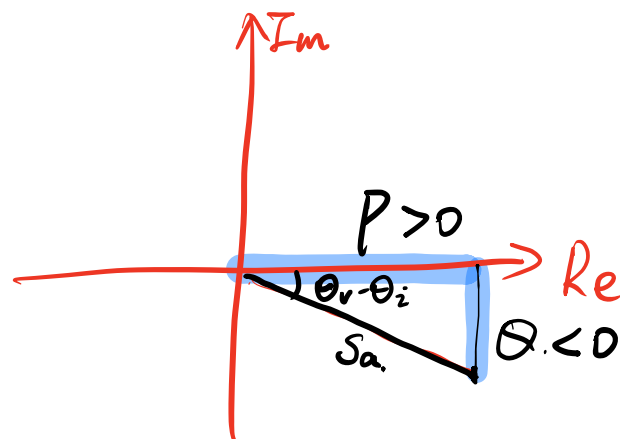
$$\begin{array}{l} P \geq 0 \checkmark \\ \leq 0 \\ \hline \text{Both} \\ Q \geq 0 \\ \leq 0 \\ \hline \text{Both} \checkmark \end{array}$$





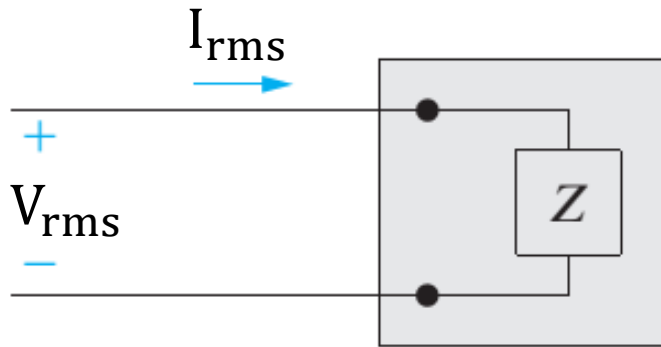Another Way to Calculate Complex Power using impedance



$$\dot{\mathbf{V}}_{\text{rms}} = \dot{\mathbf{I}}_{\text{rms}} \mathbf{Z}$$

$$\tilde{\mathbf{S}} = \dot{\mathbf{V}}_{\text{rms}} \dot{\mathbf{I}}_{\text{rms}}^*$$

$$= \dot{\mathbf{V}}_{\text{rms}} \left(\frac{\dot{\mathbf{V}}_{\text{rms}}}{\mathbf{Z}} \right)^*$$

$$= \frac{|\dot{\mathbf{V}}_{\text{rms}}|^2}{\mathbf{Z}^*}$$

$$\tilde{\mathbf{S}} = \dot{\mathbf{V}}_{\text{rms}} \dot{\mathbf{I}}_{\text{rms}}^*$$

$$= \dot{\mathbf{I}}_{\text{rms}} \mathbf{Z} \dot{\mathbf{I}}_{\text{rms}}^*$$

$$= |\dot{\mathbf{I}}_{\text{rms}}|^2 \mathbf{Z}$$

$$= |\mathbf{I}_{\text{rms}}|^2 (R + jX)$$

$$= |\mathbf{I}_{\text{rms}}|^2 R + j |\mathbf{I}_{\text{rms}}|^2 X$$

$$= I_{\text{rms}}^2 R + j I_{\text{rms}}^2 X$$



$$\tilde{\mathbf{S}} = I_{\text{rms}}^2 \mathbf{Z} = \frac{V_{\text{rms}}^2}{\mathbf{Z}^*} = \dot{\mathbf{V}}_{\text{rms}} \dot{\mathbf{I}}_{\text{rms}}^*$$

$$P = \text{Re}(\mathbf{S}) = I_{\text{rms}}^2 R$$


$$Q = \text{Im}(\mathbf{S}) = I_{\text{rms}}^2 X$$

Power Triangle

$$P = \text{Re}(S) = I_{\text{rms}}^2 R$$


$$Q = \text{Im}(S) = I_{\text{rms}}^2 X$$

$$\tilde{S} = P + jQ$$

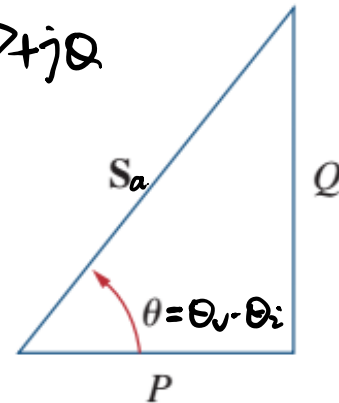

(a)

$$\tilde{Z} = R + jX$$

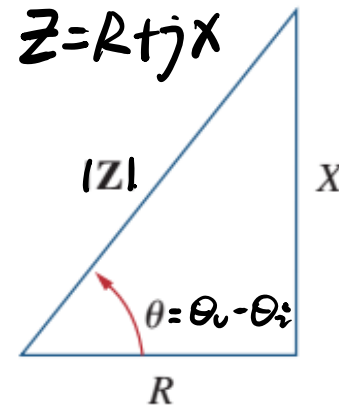

(b)

Figure 11.21

(a) Power triangle, (b) impedance triangle.

Quantity	Units
\tilde{S} Complex power	volt-amps (VA)
P Average power	watts (W)
Q Reactive power	var $\hat{=}$



$$\mathbf{S} = \frac{1}{2} \mathbf{V} \mathbf{I}^* = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = V_{\text{rms}} I_{\text{rms}} \angle(\theta_v - \theta_i) = P + jQ$$

$$P = \text{Re}(\mathbf{S}) = I_{\text{rms}}^2 R$$

$$Q = \text{Im}(\mathbf{S}) = I_{\text{rms}}^2 X$$

- Average (or real) power

$$P = \text{Re}\left[\frac{1}{2} \mathbf{V} \mathbf{I}^*\right]$$

Unit: W

- Reactive power

$$Q = \text{Im}\left[\frac{1}{2} \mathbf{V} \mathbf{I}^*\right]$$

Unit: Volt Amperes Reactive (VAR)

- Apparent power

$$S_a = |\mathbf{S}| = \frac{1}{2} V_m I_m = V_{\text{rms}} I_{\text{rms}}$$

Unit: volt-amp (VA)

$$= \sqrt{P^2 + Q^2}$$



$$\begin{aligned}\text{Complex Power} = \tilde{\mathbf{S}} &= P + jQ = \mathbf{V}_{\text{rms}}(\mathbf{I}_{\text{rms}})^* \\ &= |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| \angle \theta_v - \theta_i\end{aligned}$$

$$\text{Apparent Power} = S_a = |\tilde{\mathbf{S}}| = |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| = \sqrt{P^2 + Q^2}$$

$$\text{Real Power} = P = \text{Re}(\tilde{\mathbf{S}}) = S_a \cos(\theta_v - \theta_i)$$

$$\text{Reactive Power} = Q = \text{Im}(\tilde{\mathbf{S}}) = S_a \sin(\theta_v - \theta_i)$$

$$\text{Power Factor} = \frac{P}{S_a} = \cos(\theta_v - \theta_i)$$



Reactive Power Q

$$\begin{cases} v(t) = V_m \cos(\omega t) \\ i(t) = I_m \cos(\omega t - \phi) \end{cases}$$

$$\theta_v - \theta_i = \phi$$

Let us look at Instantaneous power again

$$\begin{aligned} p(t) &= v(t)i(t) \\ p(t) &= p_R(t) + p_X(t) \\ p_R(t) &= \\ p_X(t) &= \end{aligned}$$


$$P(t) = V(t) \cdot i(t) = \frac{V_m I_m}{2} [\cos \phi + \cos(2\omega t - \phi)] \quad (1)$$

$$\begin{aligned} P(t) &= V \cdot i \\ &= (V_R + V_X) \cdot i \\ &= V_R \cdot i + V_X \cdot i \\ &= P_R(t) + P_X(t) \end{aligned}$$

$$P_R(t) = i^2(t) \cdot R = I_m^2 \cos^2(\omega t - \phi) \cdot R$$

$$R + jX = \frac{\dot{V}_m}{\dot{I}_m} = \frac{V_m \angle 0^\circ}{I_m \angle -\phi} = \frac{V_m}{I_m} \angle \phi$$
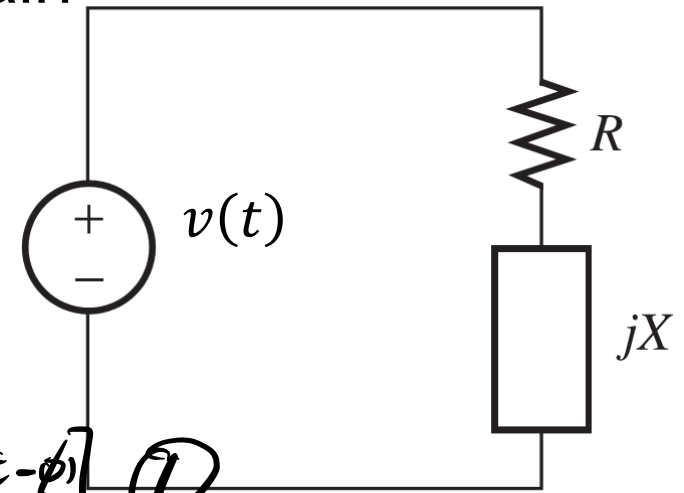
$$\therefore R = \frac{V_m}{I_m} \cdot \cos \phi$$



$$P_R(t) = I_m^2 \cos^2(\omega t - \phi) \cdot \frac{V_m}{I_m} \cdot \cos \phi$$

$$= \frac{V_m I_m}{2} \cos \phi [1 + \cos(2\omega t - 2\phi)] \quad (2)$$


$$P_x(t) = (1) - (2)$$

$$= \frac{V_m I_m}{2} \sin \phi \cos(2\omega t - 2\phi + 90^\circ) \quad (3)$$

$$\frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

Reactive Power Q : Peak Exchanged Power

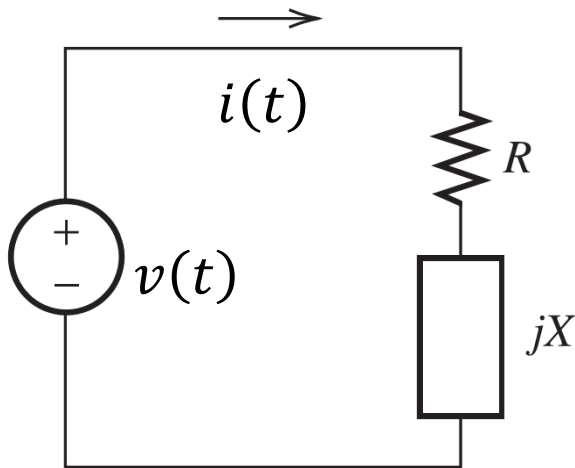- Definition: The peak instantaneous power associated with the energy storage elements contained in a general load.




$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

$$Q = \begin{cases} 0 & \text{for resistive } (\theta_v - \theta_i = 0^\circ) \\ \frac{1}{2} V_m I_m & \text{for inductive } (\theta_v - \theta_i = 90^\circ) \\ -\frac{1}{2} V_m I_m & \text{for capacitive } (\theta_v - \theta_i = -90^\circ) \end{cases}$$

- Reactive power is still of concern to power-system engineers
 - Transmission lines/transformers/fuses et al. must be capable of withstanding the current associated with reactive power.

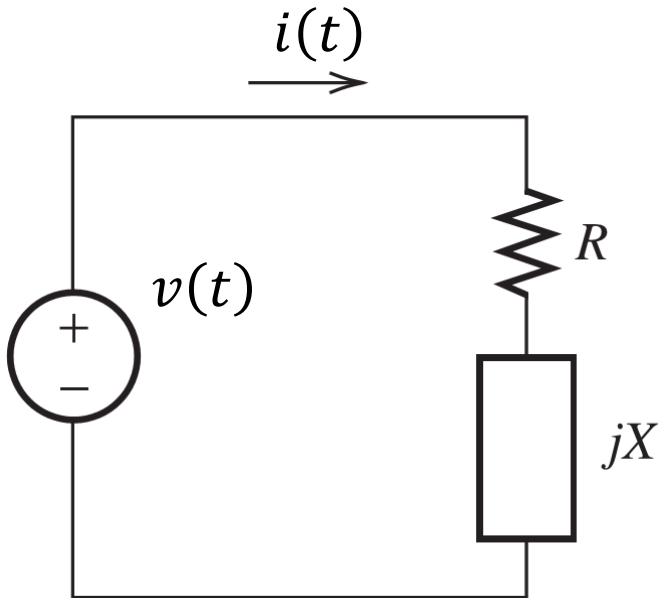
Example

- Find the average power and reactive power absorbed by an impedance $Z = 30 - j70\Omega$, when a voltage $\dot{V}_m = 120\angle 0^\circ$ is applied across it.



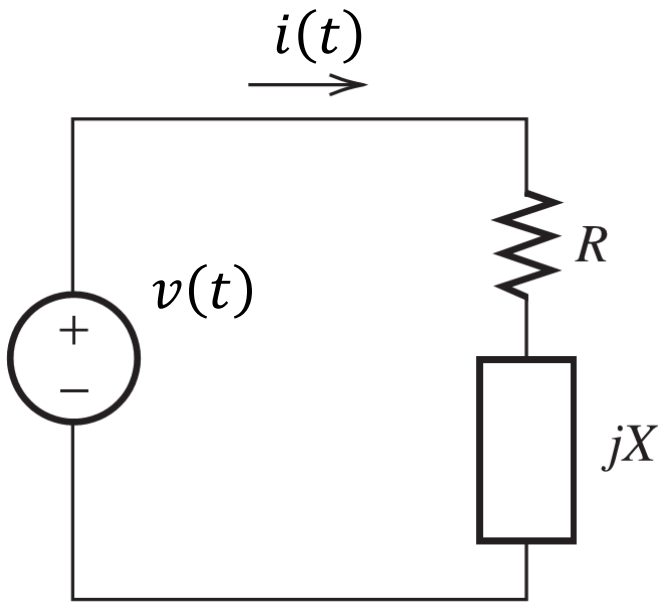Example

- Find the average power and reactive power absorbed by an impedance $Z = 30 - j70\Omega$, when a voltage $V_m = 120\angle 0^\circ$ is applied across it.



$$\begin{aligned} \mathbf{I}_m &= \frac{\mathbf{V}_m}{Z} = \frac{120\angle 0^\circ}{30 - j70} = \frac{120\angle 0^\circ}{76.16\angle -66.8^\circ} \\ &= 1.576\angle 66.8^\circ \text{ A} \end{aligned}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = 37.24 \text{ W}$$

$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = -86.91 \text{ VAR}$$



Exercise

- The voltage across a load is $v(t) = 60\cos(\omega t - 10^\circ)\text{V}$, and the current through the load is $i(t) = 1.5\cos(\omega t + 50^\circ)$. Find
 - The complex and apparent powers.
 - The real and reactive powers.
 - The power factor and the load impedance.



Exercise


- The voltage across a load is $v(t) = 60\cos(\omega t - 10^\circ)\text{V}$, and the current through the load is $i(t) = 1.5\cos(\omega t + 50^\circ)$. Find
 - The complex and apparent powers.
 - The real and reactive powers.
 - The power factor and the load impedance.

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = 45 \angle -60^\circ \text{ VA}$$

$$\text{pf} = 0.5 \text{ (leading)}$$


$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = 40 \angle -60^\circ \Omega$$

Example

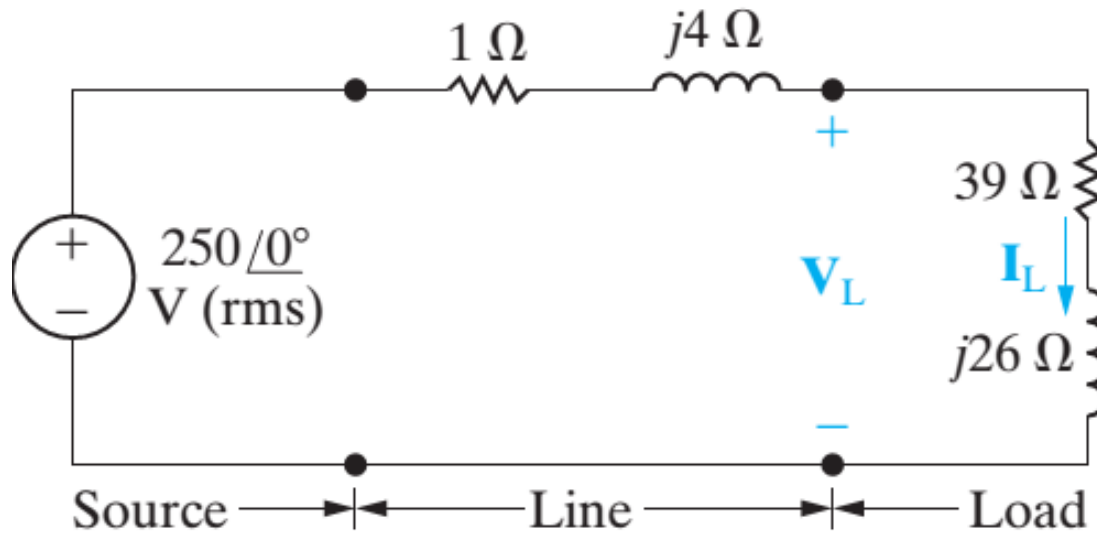

- Find V_L and I_L .
- Find the average and reactive power
 - Delivered to the load
 - Delivered to the line
 - Supplied by the source

Example

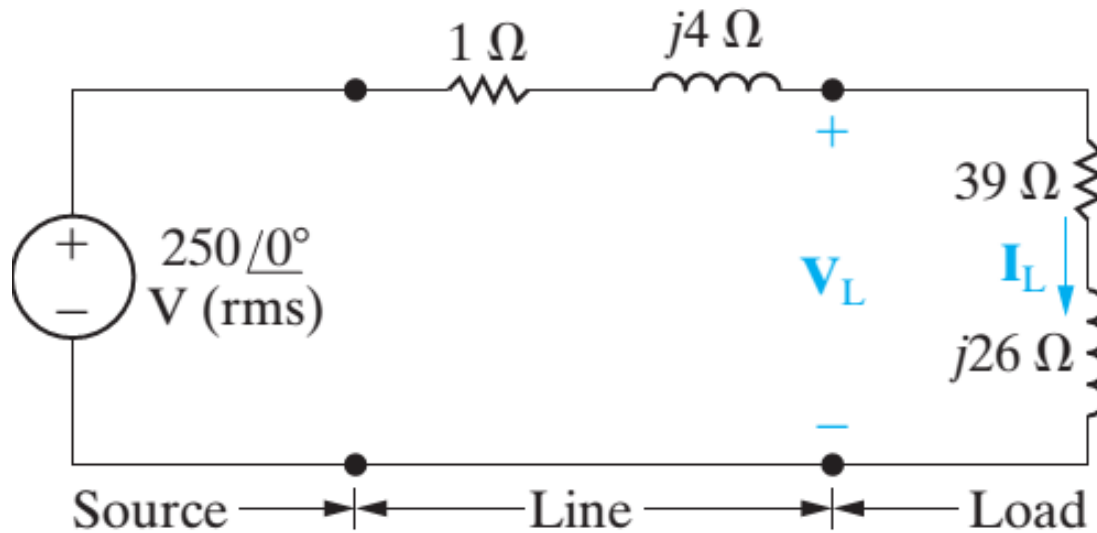

- Find V_L and I_L .
- Find the average and reactive power
 - Delivered to the load
 - Delivered to the line
 - Supplied by the source

$$\begin{aligned} I_L &= \frac{250\angle 0^\circ}{40 + j30} = 4 - j3 \\ &= 5\angle -36.87^\circ \text{ (rms)} \end{aligned}$$

$$\begin{aligned} V_L &= I_L(39 + j26) \\ &= 234 - j13 \\ &= 234.36\angle -3.18^\circ \end{aligned}$$

Load:

$$V_L I_L^* = 975 + j650 \text{ VA}$$

Line:

$$P = (5)^2(1) = 25 \text{ W}$$

$$Q = (5)^2(4) = 100 \text{ VAR}$$


Source:

$$250\angle 0^\circ I_L^* = 1000 + j750 \text{ VA}$$




Complex Power

Time Domain

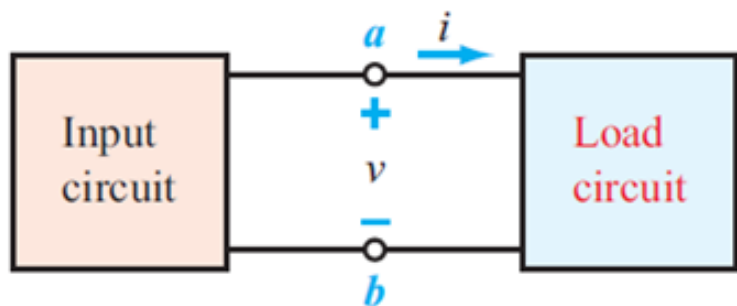

$$\begin{aligned} v(t) &= V_m \cos(\omega t + \phi_v) \\ i(t) &= I_m \cos(\omega t + \phi_i) \\ V_{\text{rms}} &= V_m / \sqrt{2} \\ I_{\text{rms}} &= I_m / \sqrt{2} \end{aligned}$$

Phasor Domain

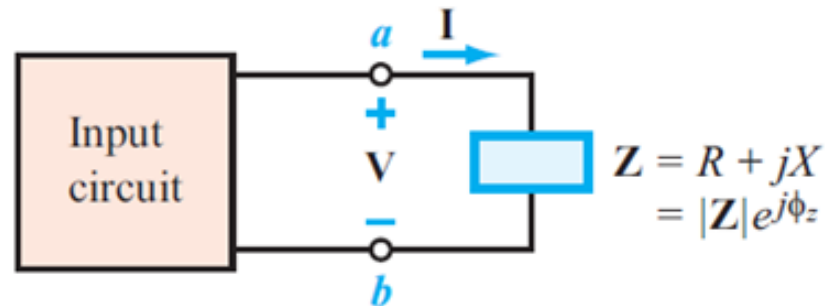

$$\begin{aligned} V &= V_m e^{j\phi_v} \\ I &= I_m e^{j\phi_i} \\ V_{\text{rms}} &= V_{\text{rms}} e^{j\phi_v} \\ I_{\text{rms}} &= I_{\text{rms}} e^{j\phi_i} \end{aligned}$$

Complex Power

$$S = \frac{1}{2} \mathbf{V} \mathbf{I}^* = V_{\text{rms}} \mathbf{I}_{\text{rms}}^* = P + jQ$$

Real Average Power

$$\begin{aligned} P &= \Re [S] \\ &= V_{\text{rms}} I_{\text{rms}} \cos(\phi_v - \phi_i) \\ &= I_{\text{rms}}^2 R \end{aligned}$$

Apparent Power

$$\begin{aligned} S &= |S| = \sqrt{P^2 + Q^2} \\ &= V_{\text{rms}} I_{\text{rms}} \\ &= I_{\text{rms}}^2 |Z| \end{aligned}$$

Reactive Power

$$\begin{aligned} Q &= \Im [S] \\ &= V_{\text{rms}} I_{\text{rms}} \sin(\phi_v - \phi_i) \\ &= I_{\text{rms}}^2 X \end{aligned}$$

Power Factor

$$\begin{aligned} pf &= \frac{P}{S} \\ &= \cos(\phi_v - \phi_i) \\ &= \cos \phi_z \end{aligned}$$

$$\begin{aligned} S &= S e^{j\phi_s} \\ \phi_s &= \phi_v - \phi_i = \phi_z \end{aligned}$$



- Maximum average power transfer (不做要求)

