

Homework 2

Due date: 11th Oct, 2022

Turn in your homework in class

Rules:


- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1. For the circuit below,


(a) Use superposition theorem to find the voltage drop between a and b , namely V_{ab}

(b) Use source transformation (at least twice) to find V_{ab}

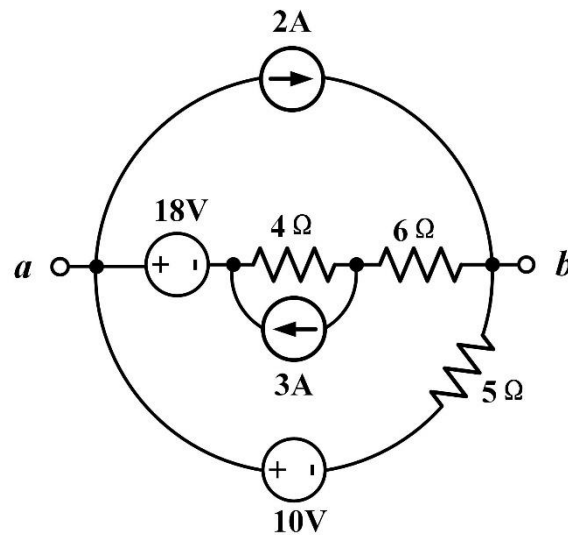
(c) Find the Norton equivalent circuit at terminals a and b



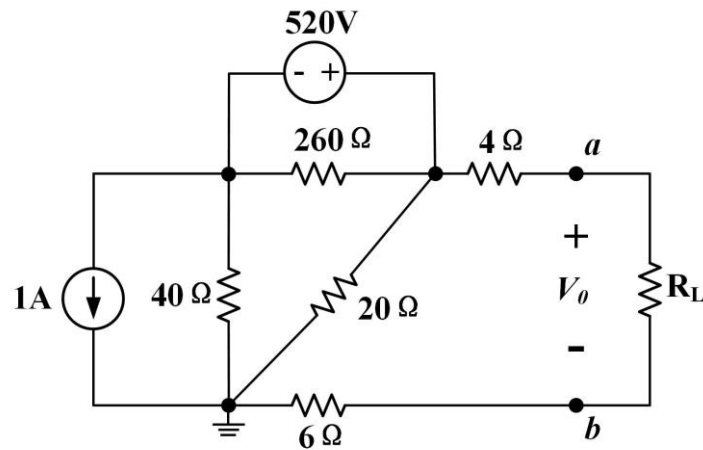
2. (a) Apply superposition to find V_o in the circuit below when $R_L=250\Omega$.
(b) Find the Thevenin equivalent circuit for the left hand side circuit of node a and node b .
(c) Determine the value of R_L when maximum power could be transferred to it.
(d) for the situation in (c), find the power absorbed by the 520V voltage source and the 1A current source, **respectively**.



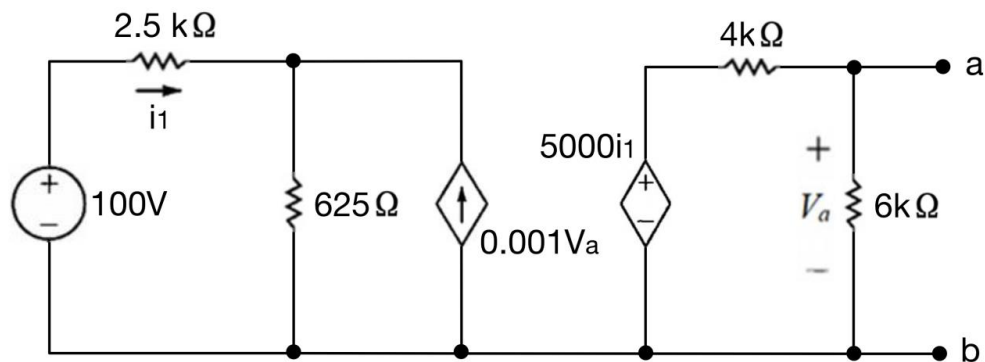3. (a) Find the Thevenin equivalent circuit at the terminals **a** and **b**.
(b) If a load resistor $\mathbf{R_L}$ is connected at terminals **a** and **b**, what is the maximum power that could be transferred to it by this circuit, and what is the value of $\mathbf{R_L}$ in this situation? Also, find the power absorbed by the three sources, **respectively**.



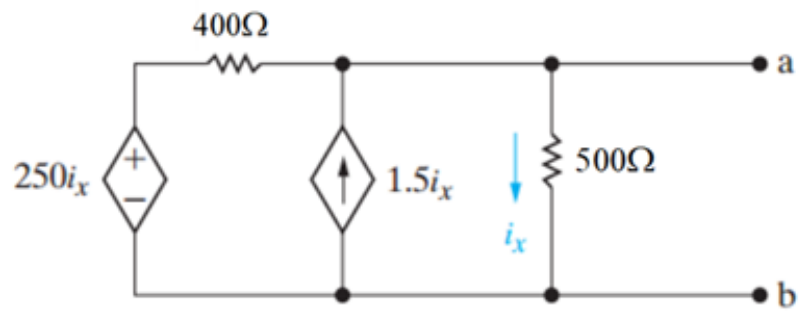
4. For the circuit below, find the Norton equivalent with respect to the terminals **a**, **b**.




5. The values of V_S , R_1 , R_2 , R_3 , R_4 are known positive constants.

Use them to find:

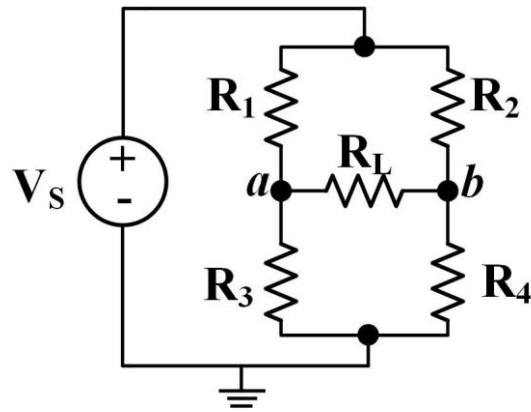- (a) The Thevenin equivalent circuit between node a and b .
- (b) The resistance of R_L that absorbs the maximum power, and the maximum power P_{\max} absorbed by the load R_L .



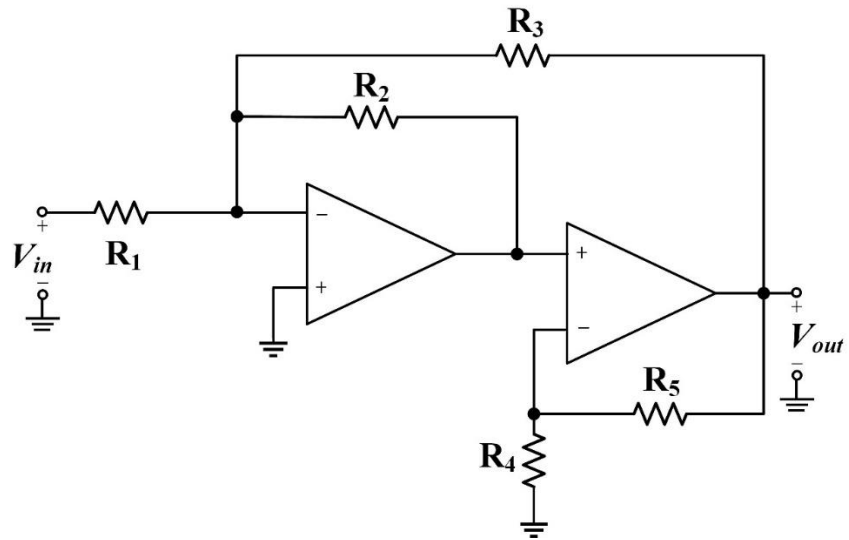6. Find the voltage gain V_{out}/V_{in} of the following circuit, if $R_1=1\text{k}\Omega$, $R_2=R_3=2\text{k}\Omega$, $R_4=R_5=4\text{k}\Omega$.



7. For the following circuit, find the output voltage V_{out} in terms of V_1 to V_4 . Note that all the resistors in the circuit have the same resistance of $1\text{k}\Omega$. (Also, please pay attention to the given reference direction of the independent voltage sources)

