

ShanghaiTech University

EE 115B: Digital Circuits


Fall 2022

Lecture 21

Hengzhao Yang
December 20, 2022

VHDL code for Moore FSMs

 - Design input: state diagram
- Example: “11” sequence detector



Moore type: code 1

- **TYPE** keyword
 - User-defined signal type
 - Name: State_type
 - Values: A, B, C
- Signal **y**
 - Type: State_type
 - Describes FSM state
 - Takes values (A, B, C)
- Initial state A by Resetn
- CASE statement
 - State transitions

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;

3  ENTITY simple IS
4      PORT ( Clock, Resetn, w      : IN    STD_LOGIC ;
5              z                      : OUT  STD_LOGIC ) ;
6  END simple ;

7  ARCHITECTURE Behavior OF simple IS
8      TYPE State_type IS (A, B, C) ;
9      SIGNAL y : State_type ;
10 BEGIN
11     PROCESS ( Resetn, Clock )
12     BEGIN
13         IF Resetn = '0' THEN
14             y <= A ;
15         ELSIF (Clock'EVENT AND Clock = '1') THEN
16             CASE y IS
17                 WHEN A =>
18                     IF w = '0' THEN
19                         y <= A ;
20                     ELSE
21                         y <= B ;
22                     END IF ;
```


Moore type: code 1 (continued)

- WHEN statement
 - Output expression
- Summary
 - One signal (y) for state
 - One PROCESS block

```
23      WHEN B =>
24          IF w = '0' THEN
25              y <= A ;
26          ELSE
27              y <= C ;
28          END IF ;
29      WHEN C =>
30          IF w = '0' THEN
31              y <= A ;
32          ELSE
33              y <= C ;
34          END IF ;
35      END CASE ;
36  END IF ;
37  END PROCESS ;
38  z <= '1' WHEN y = C ELSE '0' ;
39  END Behavior ;
```

Moore type: code 1, simulation results

- Signal y: state

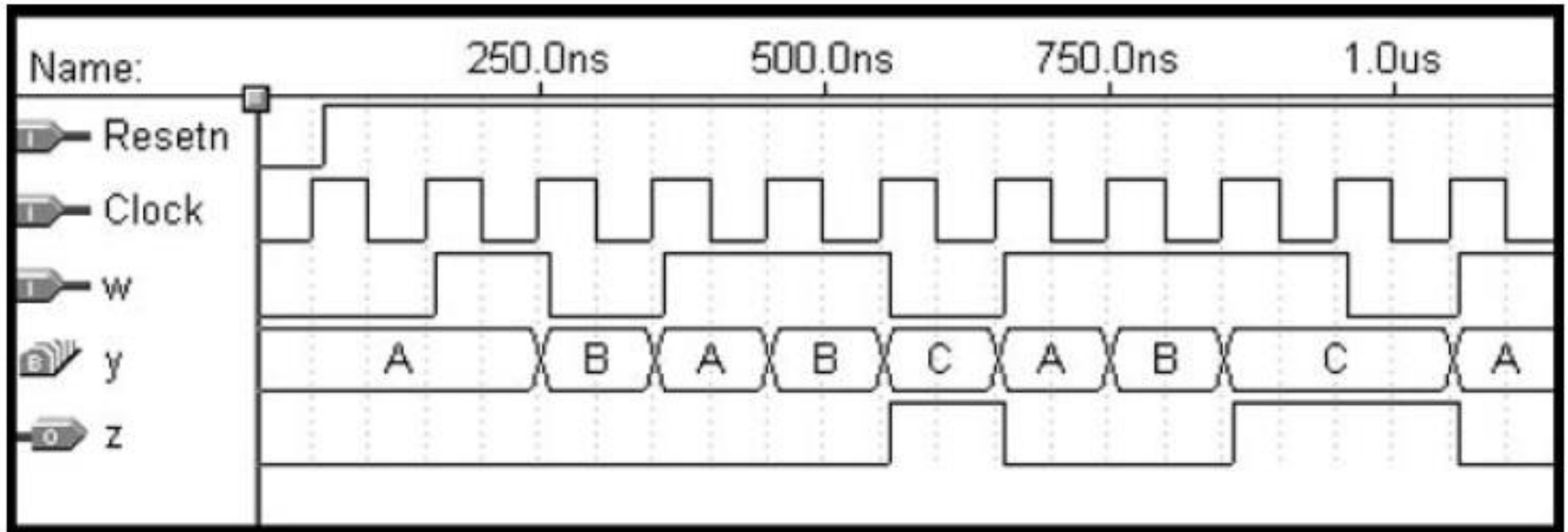

Moore type: code 2

- Same ENTITY


```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;

3  ENTITY simple IS
4      PORT ( Clock, Resetn, w      : IN  STD_LOGIC ;
5              z                      : OUT STD_LOGIC ) ;
6  END simple ;
```
- Two signals for state
 - Present state: `y_present`
 - Next state: `y_next`
 - Same type: `State_type`
 - Same values: A, B, C
- Two PROCESS blocks

```
ARCHITECTURE Behavior OF simple IS
    TYPE State_type IS (A, B, C) ;
    SIGNAL y_present, y_next : State_type ;
```

Moore type: code 2 (continued)

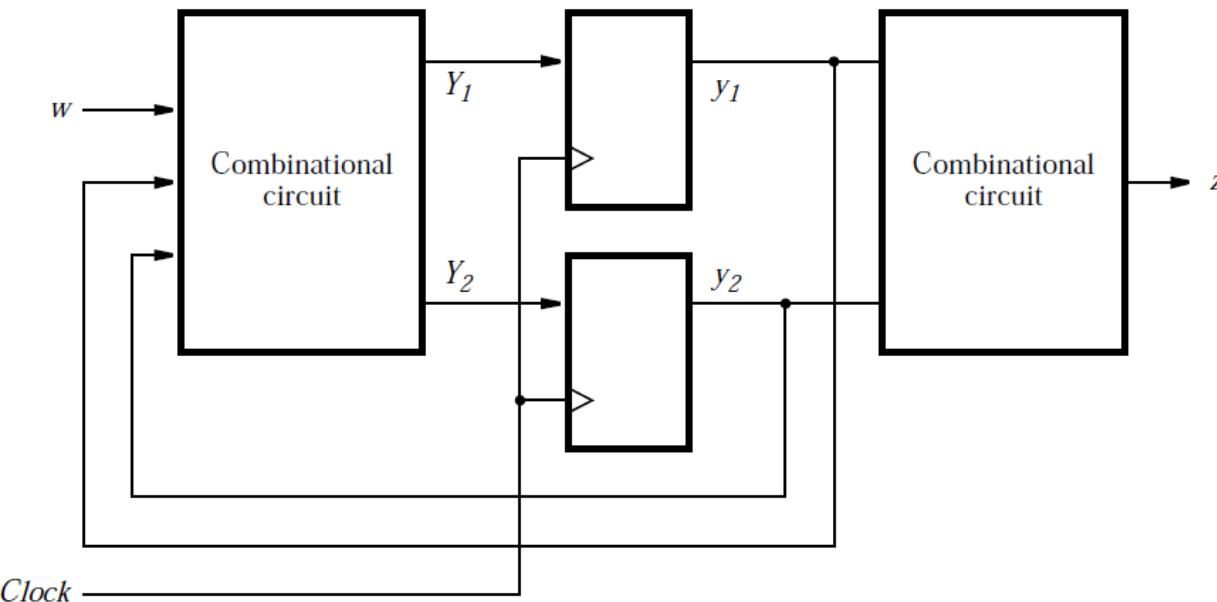- PROCESS 1
 - Next-state expressions
 - Left combinational circuit



```
BEGIN
  PROCESS ( w, y_present )
  BEGIN
    CASE y_present IS
      WHEN A =>
        IF w = '0' THEN
          y_next <= A ;
        ELSE
          y_next <= B ;
        END IF ;
      WHEN B =>
        IF w = '0' THEN
          y_next <= A ;
        ELSE
          y_next <= C ;
        END IF ;
      WHEN C =>
        IF w = '0' THEN
          y_next <= A ;
        ELSE
          y_next <= C ;
        END IF ;
    END CASE ;
  END PROCESS ;
```

Moore type: code 2 (continued)

- PROCESS 2
 - State update
 - Sequential circuit

```
PROCESS (Clock, Resetn)
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;
```

- WHEN statement
 - Output expression
 - Right combinational circuit

```
z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;
```


Moore type: code 3

- Code 1 and 2
 - Automatic state assignment
 - Type of state signals (y, y_present, y_next): user-defined (State_type)
- Code 3
 - Manual (explicit) state assignment
 - Type of state signals: standard (std_logic_vector)

Moore type: code 3 (continued)

- State assignment

- A: 00, B: 01, C: 11

- State signals

- y_present, y_next: 2-bit vector

- States and values: A="00", B="01", C="11"

- State is defined as **CONSTANT**

- Operator for **CONSTANT** value assignment: **“:=”**

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS
```

```
    PORT ( Clock, Resetn, w : IN  STD_LOGIC ;  
          z                   : OUT STD_LOGIC ) ;
```

```
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);
```

```
    CONSTANT A : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00" ;
```

```
    CONSTANT B : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01" ;
```

```
    CONSTANT C : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11" ;
```

Moore type: code 3 (continued)

- PROCESS 1 (right)
 - WHEN OTHERS
 - Covers unused values
- PROCESS 2 (left)
- Output (left)

```
PROCESS ( Clock, Resetn )
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;
z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;
```

```
BEGIN
    PROCESS ( w, y_present )
    BEGIN
        CASE y_present IS
            WHEN A =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= B ;
                END IF ;
            WHEN B =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= C ;
                END IF ;
            WHEN C =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= C ;
                END IF ;
            WHEN OTHERS =>
                y_next <= A ;
        END CASE ;
    END PROCESS ;
```

Mealy FSM

- Sequence detector
 - Circuit has one input (w) and one output (z)
 - All changes occur at positive clock edges
 - Operation: $z=1$ in the same clock cycle when the second occurrence of $w=1$ is detected; $z=0$, otherwise

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0


Comparison: Moore FSM

- Design specifications (problem statement)
 - Circuit has one input (w) and one output (z)
 - All changes occur on positive clock edges
 - Operation: $z=1$ if $w=1$ during two immediately preceding clock cycles; $z=0$, otherwise

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0


State diagram

 - States
 - State A (starting state): when a reset signal is applied or $w=0$, circuit enters this state
 - State B: $w=1$ for one clock cycle



Comparison: Moore FSM

 - State diagram
 - Nodes: states
 - Directed arcs: state transitions



State table and state-assigned table

- Two states: A and B

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

- One state variable: y

– A: 0, B: 1

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

Comparison: Moore FSM

- Convert state diagram to state table
 - First state is starting state (state A)
 - Present state, next state, and state transitions
 - Output is specified with respect to present state

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Output and next-state expressions

- Expressions

$$Y = D = w$$

$$z = wy$$

A
B

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
0	0	1	0	0
1	0	1	0	1

- Truth table: output and next-state

y	w	z
0	0	0
0	1	0
1	0	0
1	1	1


y	w	Y
0	0	0
0	1	1
1	0	0
1	1	1

Circuit


- Expressions

$$Y = D = w$$

$$z = wy$$

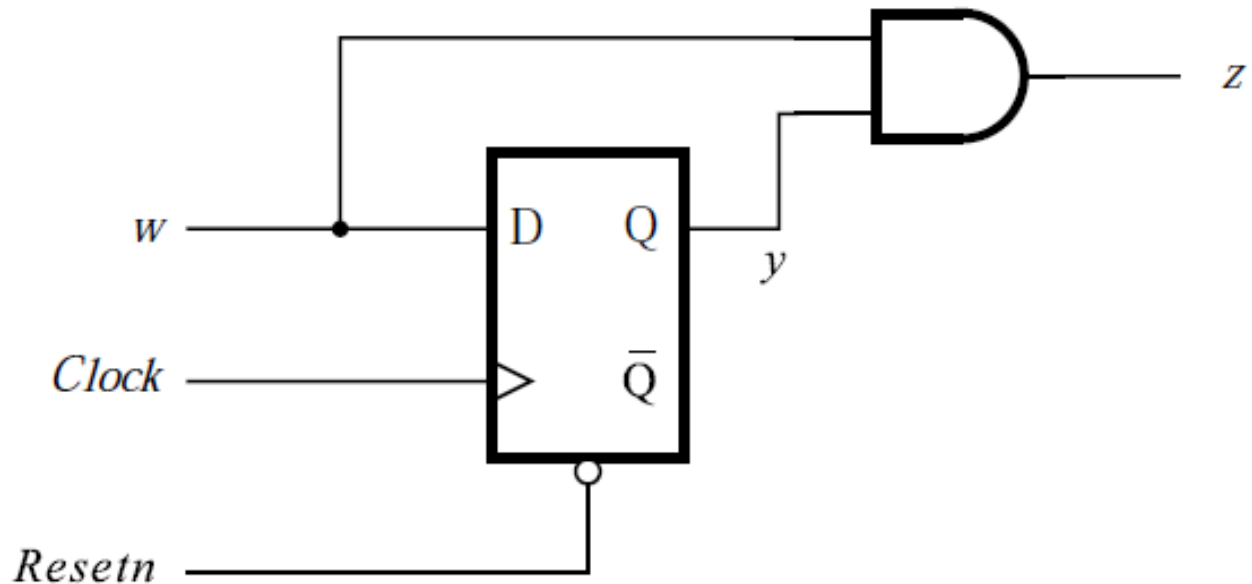


Timing diagram

 

VHDL code for Mealy FSMs

 - Design input: state diagram
- Example: “11” sequence detector




Mealy type code

- Similar to Moore type code 1
- Two states: A, B
- User-defined state signal type: State_type

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY mealy IS  
    PORT ( Clock, Resetn, w : IN    STD_LOGIC ;  
          z                  : OUT  STD_LOGIC ) ;  
END mealy ;  
  
ARCHITECTURE Behavior OF mealy IS  
    TYPE State_type IS (A, B) ;  
    SIGNAL y : State_type ;
```

Mealy type code (continued)

- PROCESS 1
 - State transitions

 


```
BEGIN
PROCESS ( Resetn, Clock )
BEGIN
    IF Resetn = '0' THEN
        y <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        CASE y IS
            WHEN A =>
                IF w = '0' THEN y <= A ;
                ELSE y <= B ;
                END IF ;
            WHEN B =>
                IF w = '0' THEN y <= A ;
                ELSE y <= B ;
                END IF ;
        END CASE ;
    END IF ;
END PROCESS ;
```

Mealy type code (continued)

- PROCESS 2

- Output depends on y and w

 

```
PROCESS ( y, w )
BEGIN
    CASE y IS
        WHEN A =>
            z <= '0' ;
        WHEN B =>
            z <= w ;
    END CASE ;
END PROCESS ;
END Behavior ;
```


Review

- Chapter 1: Introduction
 - Basic concepts

Chapter 2: Numbers and codes

- Numbers
 - Decimal
 - Binary
 - Hexadecimal
 - Octal
- Codes
 - BCD, Gray, and ASCII
 - Parity check

Chapter 3: Logic gates

- Circuit symbol, operation, truth table, and logic expression
 - NOT
 - AND
 - OR
 - NAND
 - NOR
 - XOR
 - XNOR

Chapter 4: Boolean algebra and logic simplification

- Basic Boolean algebra relationships
- DeMorgan's theorem
- SOP and POS expressions: standard and minimum, explicit and concise
- Karnaugh map: minimum SOP and POS expressions, with and without don't cares
- Quine-McCluskey method

Chapter 5: Combinational logic analysis

- Logic forms: AND-OR, AND-OR-Invert (AOI), NAND, and NOR
- Combinational logic design flow

Chapter 6: Combinational logic blocks

- Adder
- Encoder
- Decoder
- Comparator
- MUX
- DEMUX

VHDL

- Basic structures: entity and architecture
- Behavioral and structural coding
- Combinational and sequential logic

Chapter 7: Basic sequential circuits

- Blocks: circuit symbol, operation, and characteristic table
 - Latches
 - Flip-flops
- Modules
 - Registers
 - Counters

Chapter 8: Synchronous sequential circuits

- Design flow
 - Moore FSMs
 - Mealy FSMs