
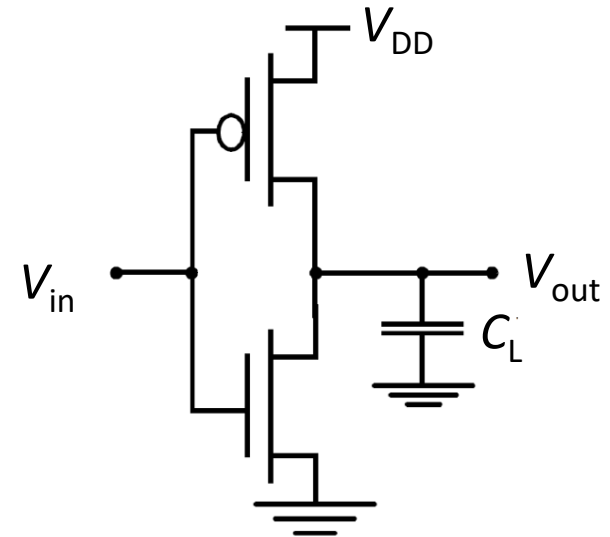


NOT function (Inverter)


- Boolean expression $X = \bar{A}$
- Truth table

Input	Output
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)

- Logic circuit

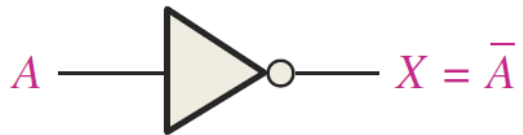

Circuit implementation

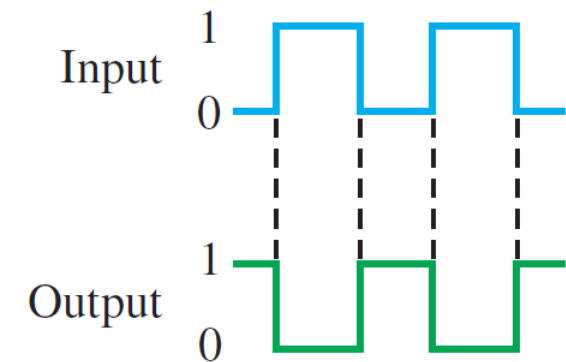

Waveform


AND operation

- Boolean expression $X = AB$


- Truth table

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	0
1	0	0
1	1	1

- Logic circuit

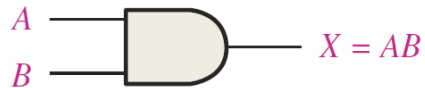


Inputs			Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

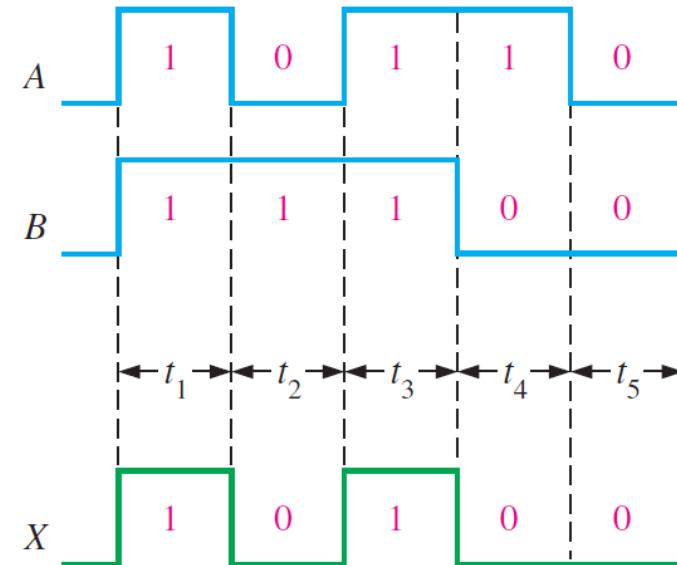

Application of AND gate

Seat Belt Alarm System

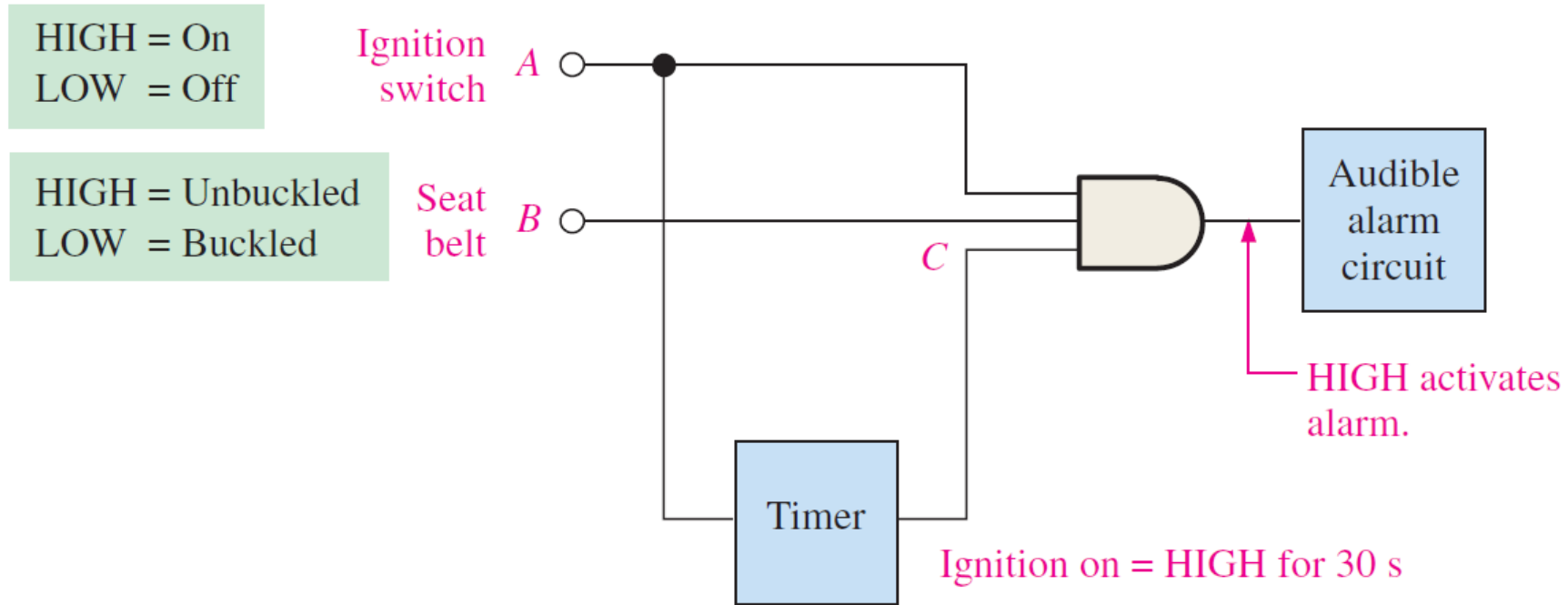

If the ignition is on and the seat belt is unbuckled and the timer is running, the output is HIGH.



OR operation

- Boolean expression $X = A + B$

- Truth table


A	B	$A + B = X$
0	0	$0 + 0 = 0$
0	1	$0 + 1 = 1$
1	0	$1 + 0 = 1$
1	1	$1 + 1 = 1$

- Logic circuit

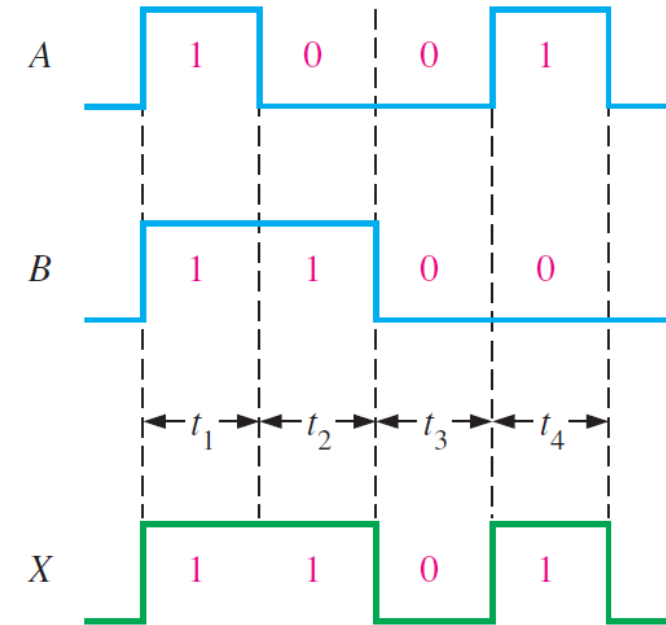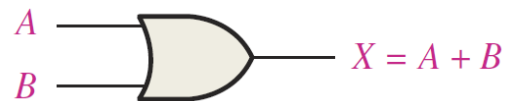

Question: draw the truth table for 3-input OR gate

Application of OR gate

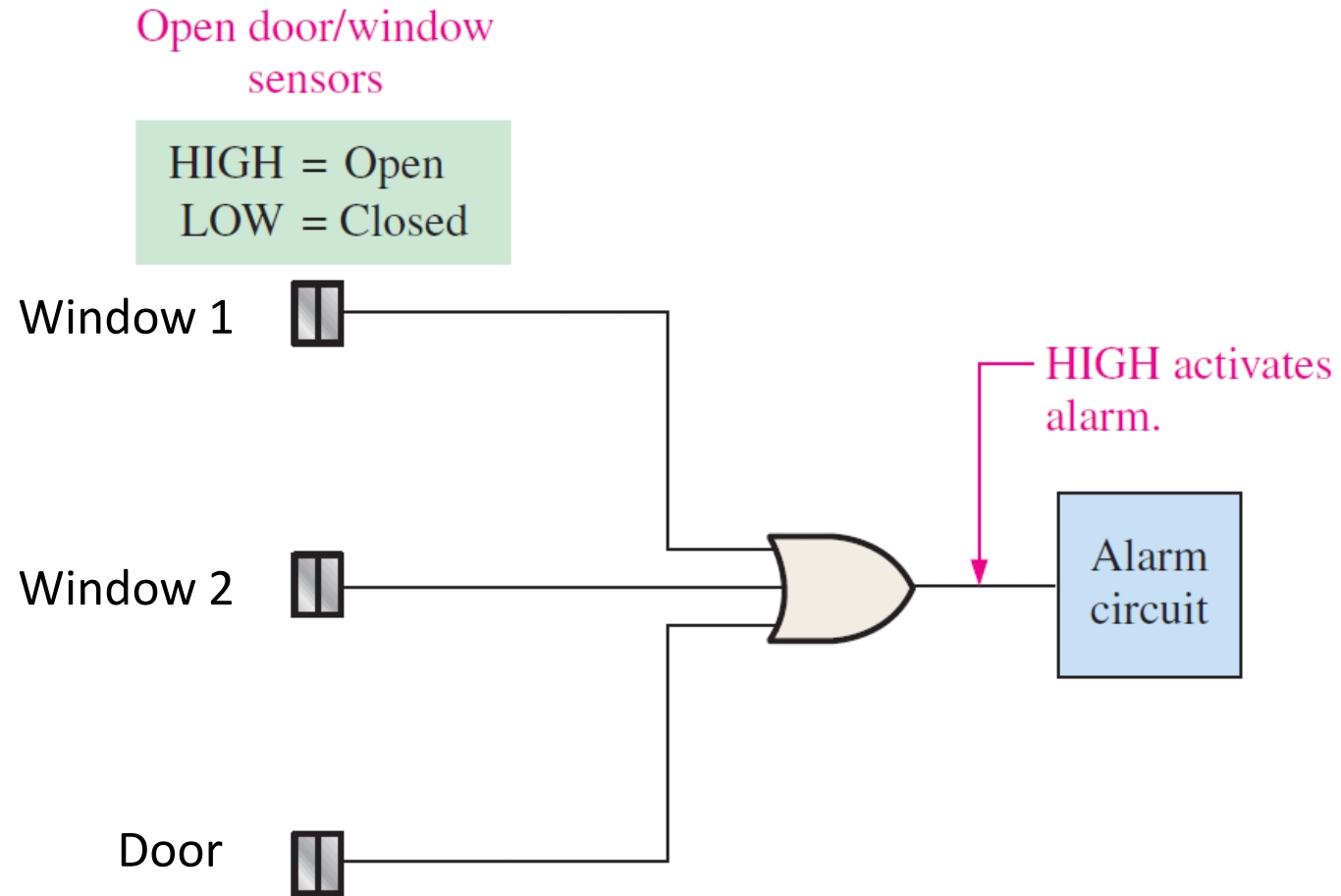


When one of the windows or the door is opened, the gate output goes HIGH.

NAND gate

- Boolean expression

$$X = \overline{AB}$$


- Logic circuit

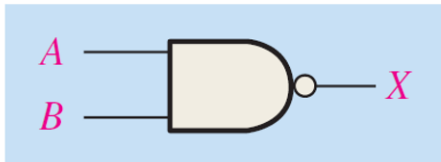

- Truth table


Inputs		Output
A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

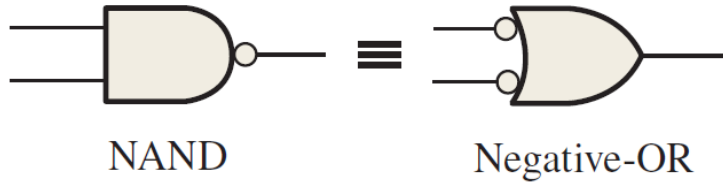- Inherent in a NAND gate's operation is the fact that one or more LOW inputs produce a HIGH output



$$\overline{AB} = \overline{A} + \overline{B}$$

Verify this using truth table

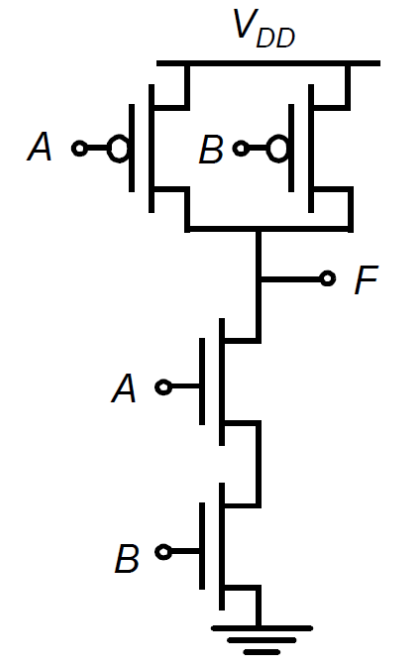

Circuit


Question: draw the truth table for 3-input NAND gate

NOR gate

- Boolean expression

$$X = \overline{A + B}$$


- Logic circuit

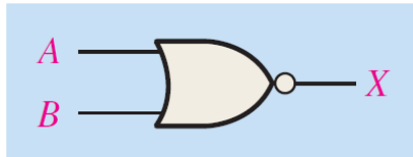

- Truth table


Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

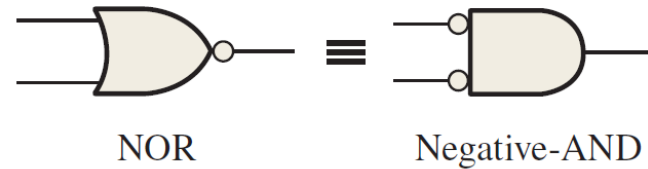- A HIGH is produced on the gate output only when all of the inputs are LOW



$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

Verify this using truth table

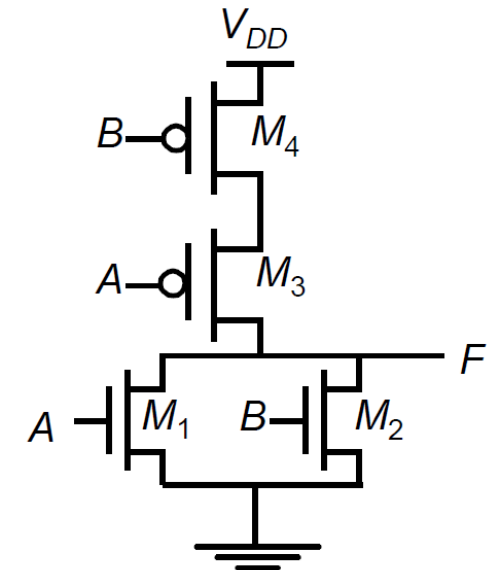

Circuit



Question: draw the truth table for 3-input NOR gate

Exclusive-OR (XOR) gate

- The output of XOR is HIGH only when the two inputs are at opposite logic levels.
- Truth table

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0

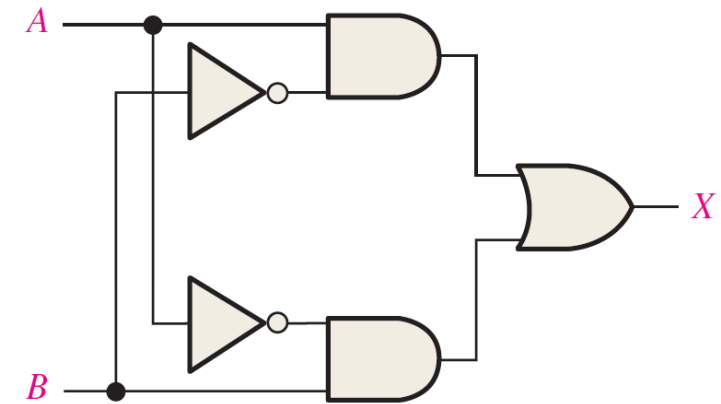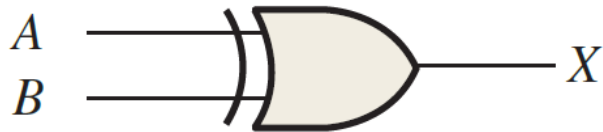- Boolean expression $X = A\bar{B} + \bar{A}B$ or $X = A \oplus B$
- Logic circuit





Question: draw the truth table for 3-input XOR gate

Exclusive-NOR (XNOR) gate

- The output of XNOR is LOW only when the two inputs are at opposite logic levels.
- Truth table

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	1

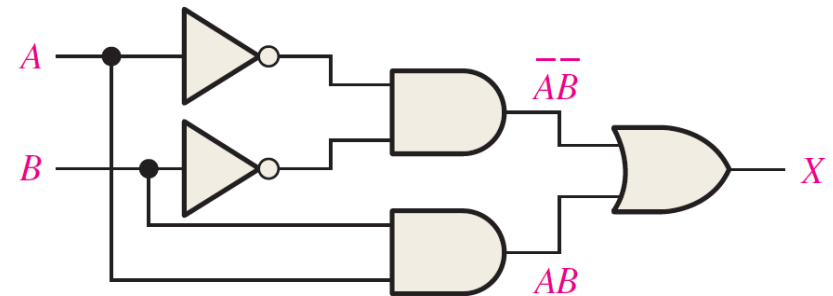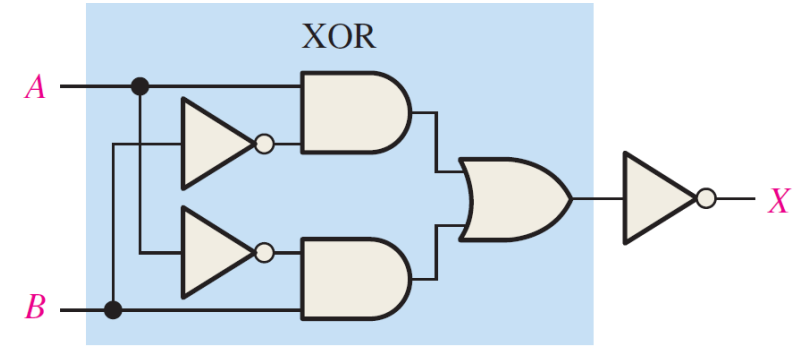- Boolean expression $X = \overline{A}\overline{B} + AB$
- Logic circuit



Think about it:

- In the truth table with two inputs, how many lines? How many columns?

Truth Table & Boolean Expression

Even or odd 1s

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0





$$y = A'BC + AB'C + ABC'$$




Boolean Expression & Logic Circuit

$$A(B + CD)$$

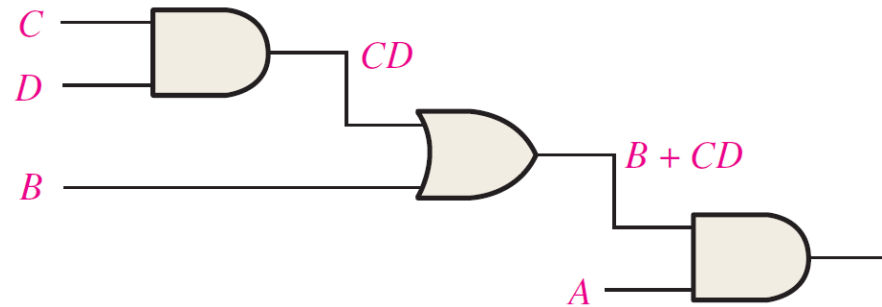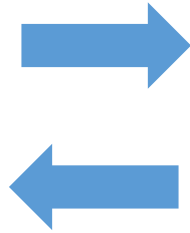

Truth Table & Logic Circuit

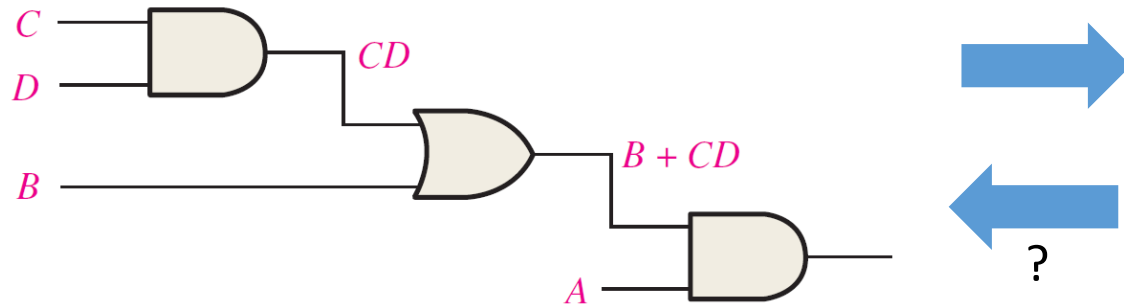

Inputs				Output
A	B	C	D	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Reading materials

- Chapter 3 of Floyd book