

Homework 4


Due date: 8th, NOV.

Turn in your homework in class


Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

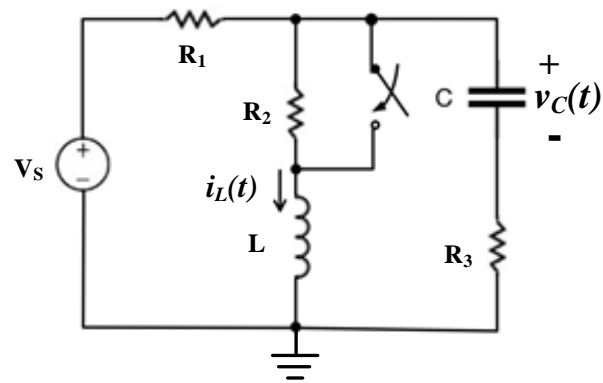
1. For the circuit below, the switch has been open for a long time. The switch is closed at $t = 0$ s immediately. Given $V_s = 10\text{V}$, $R_1 = 2\Omega$, $R_2 = 3\Omega$, $R_3 = 1\Omega$, $L = 4\text{H}$, $C = 2\text{F}$, please find $v_C(0^+)$, $dv_C(0^+)/dt$, $i_L(0^+)$, $di_L(0^+)/dt$. (Hint: remember to assign units for your answers)



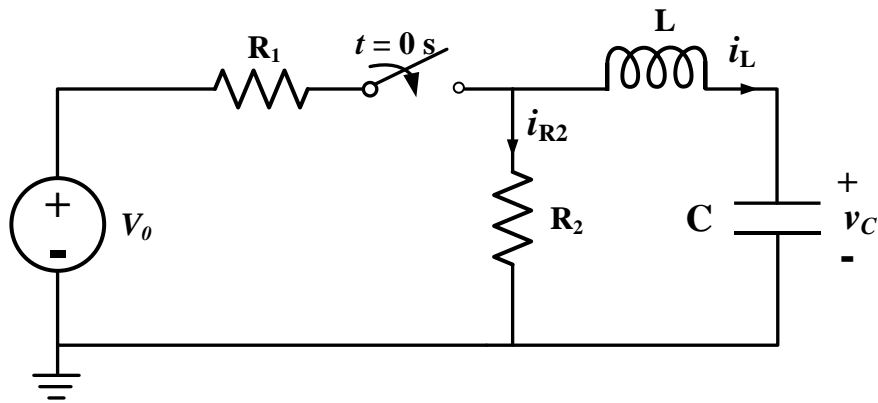2. Determine $v_C(t)$, $i_L(t)$, and $i_{R2}(t)$ in the circuit for $t \geq 0$, given that $V_0 = 12V$, $R_1 = 2\ \Omega$, $R_2 = 2\ \Omega$, $L = 0.25\text{ H}$ and $C = 0.5\text{ F}$. Note that the switch has been open for a long time before $t = 0\text{ s}$




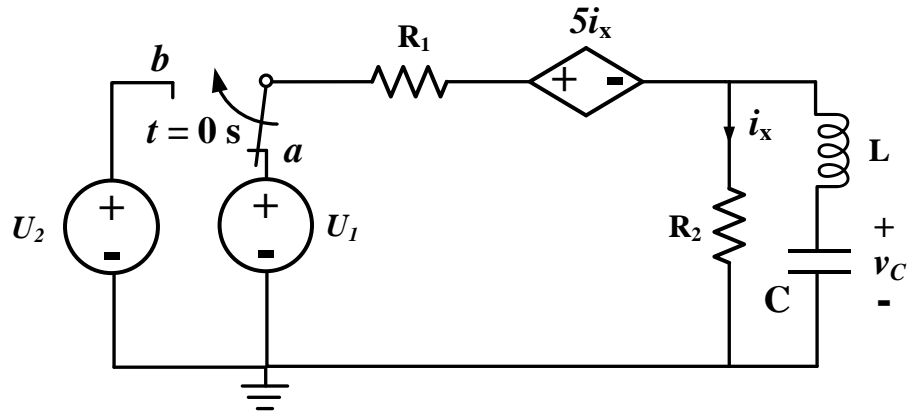3. In the circuit below, $R_1 = 10\Omega$, $R_2 = 5\Omega$, $L = 4\text{mH}$, $C = 10\text{mF}$, $U_1 = 5\text{V}$, and $U_2 = 12\text{V}$. When $t = 0\text{s}$, the switch changes from node a to node b immediately. Assume that the circuit reaches steady state before $t = 0$. Determine the expression for $v_C(t)$ and $i_x(t)$ when $t \geq 0\text{s}$.



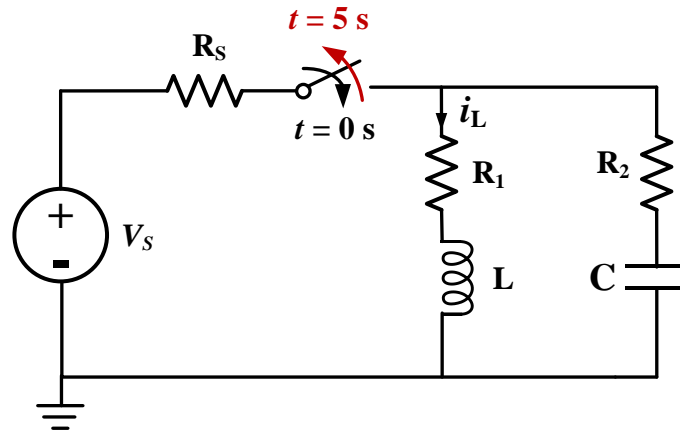4. In the following circuit, the switch was closed at $t = 0$ s and re-opened at $t = 0.5$ s. Determine the response $i_L(t)$ for $t \geq 0$, and there's no energy stored in the inductor and capacitor before $t = 0$ s.

Assume that $V_S = 18\text{V}$, $R_S = 1\Omega$, $R_1 = 5\Omega$, $R_2 = 2\Omega$, $L = 2\text{H}$ and $C = \frac{1}{17}\text{F}$.



5. For the following circuit, $R_1 = 1\Omega$, $R_2 = 2\Omega$, $C_1 = 3\text{F}$, $C_2 = 2\text{F}$, $V_0 = 20\text{V}$, and the coefficient $\alpha = 1$. The switch closes at $t = 0\text{s}$ immediately. Please find the voltage on the capacitors $v_{C1}(t)$ and $v_{C2}(t)$ for $t > 0\text{s}$, respectively. Note that the switch has been open for a long time before $t = 0\text{s}$.

