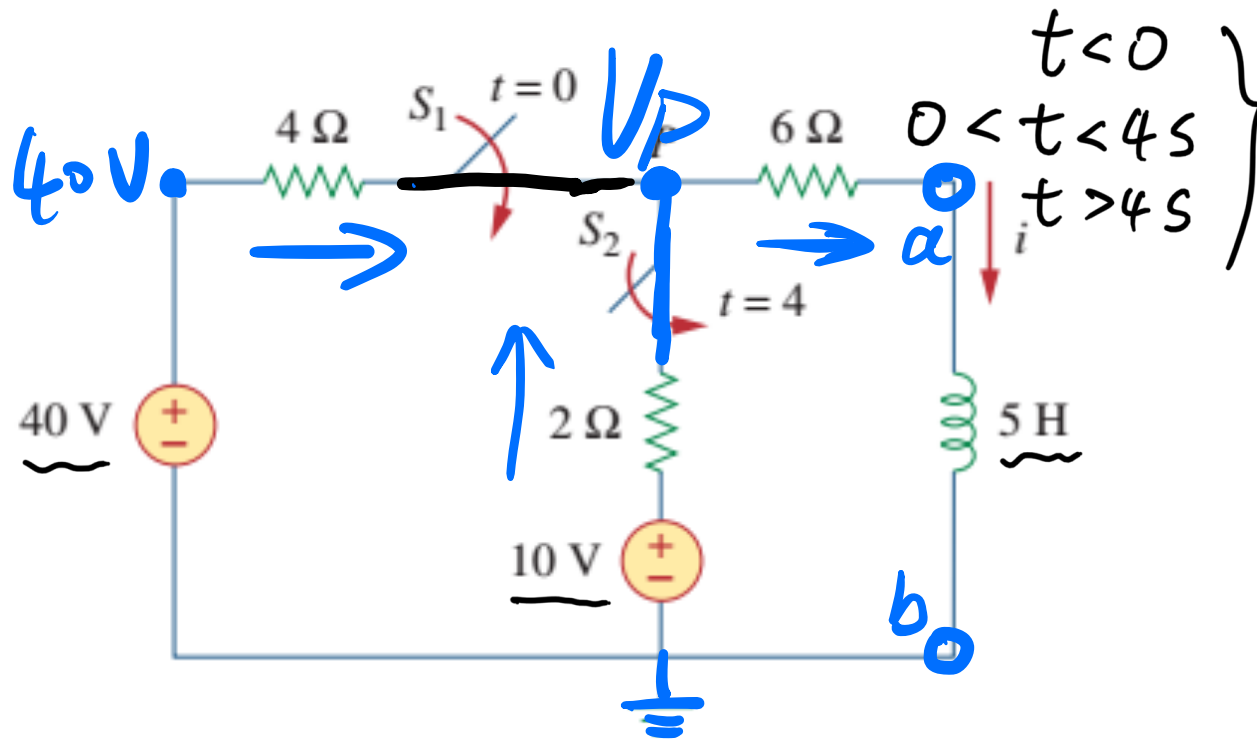




## Sequential switch

At  $t = 0$ , switch 1 in Fig. 7.53 is closed, and switch 2 is closed 4 s later. Find  $i(t)$  for  $t > 0$ . Calculate  $i$  for  $t = 2$  s and  $t = 5$  s.



We need to consider the three time intervals  $t \leq 0$ ,  $0 \leq t \leq 4$ , and  $t \geq 4$  separately. For  $t < 0$ , switches  $S_1$  and  $S_2$  are open so that  $i = 0$ . Since the inductor current cannot change instantly,

$$\underline{i(0^-) = i(0) = i(0^+) = 0}$$

$$i(\infty): \frac{40 - V_p}{4} + \frac{10 - V_p}{2} = \frac{V_p - 0}{6}$$

$$\Rightarrow V_p = \frac{180}{11} \text{ V}, \quad \underline{i(\infty) = \frac{V_p}{6} = \frac{30}{11} \text{ A}}$$

$$R_{TH} = (4 \parallel 2) + 6 = \frac{22}{3} \Omega$$

$$t < 0: i_L(0^+) = i_L(0^-) = 0$$

$$0 < t < 4s:$$

$$i_L(t) = \underbrace{i(\infty)}_{\substack{\downarrow \\ \text{from } t < 0}} + [\underbrace{i(0)}_{\substack{\downarrow \\ \text{from } t < 0}} - i(\infty)] e^{-t/\tau}$$

$$i(\infty) = \frac{40}{4+6} = 4A, \quad \tau = \frac{L}{R} = \frac{1}{2}s$$

$$\underline{i_L(t)}|_{0 < t < 4s} = \underline{4 + (-4)e^{-2t}} A.$$

$$\underline{t > 4s:}$$

$$\underline{i_L(t)}|_{t > 4} = \underline{i(\infty) + [i(4s) - i(\infty)] \cdot e^{-(t-4)/\tau}}$$

$$i(4s^+) = i(4s^-) = 4 + (-4) \cdot e^{-8} \approx \underline{4A}$$

$$i(\infty) = \frac{30}{11} A.$$

$$\tau = L/R_{TH} = \frac{5}{22} = \underline{\underline{\frac{15}{22} s}}$$

$t > 4s$


$$\hat{v}_L(t) = \underline{2.73} + \underline{1.27} e^{-\underline{1.47}(t-4)}, \quad t \geq 4$$

---


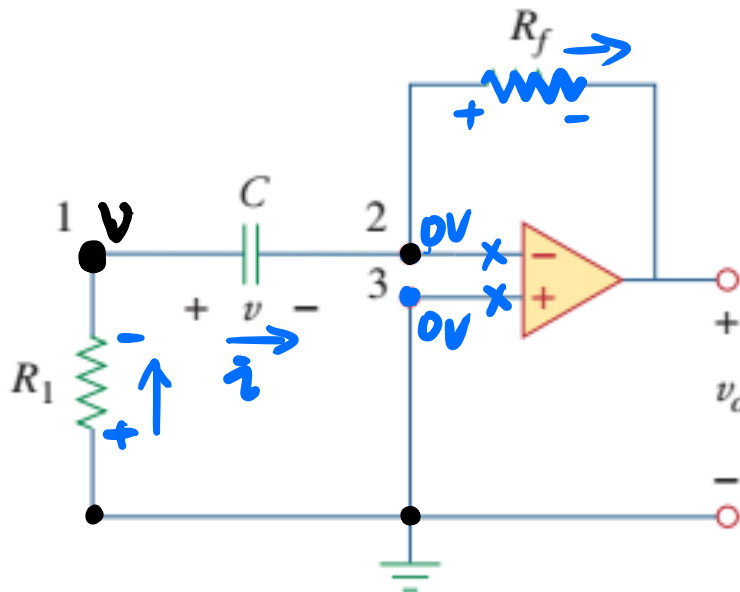
# First order op-amp circuit

For the op amp circuit in Fig. 7.55(a), find  $v_o$  for  $t > 0$ , given that  $v(0) = 3 \text{ V}$ . Let  $R_f = 80 \text{ k}\Omega$ ,  $R_1 = 20 \text{ k}\Omega$ , and  $C = 5 \mu\text{F}$ .



NI:

$$\frac{0 - v}{R_1} = C \cdot \frac{dv}{dt} \Rightarrow \frac{dv}{dt} + \frac{1}{R_1 C} \cdot v = 0$$

$V(0) = 3 \text{ V}$

$$V(t) = A \cdot e^{-\frac{1}{R_1 C} \cdot t} \quad \checkmark$$

$$\therefore A = 3 \quad \therefore \underline{V(t) = 3 \cdot e^{-t/R_1 C}}$$

$$N_2: C \cdot \frac{dV}{dt} = \frac{0 - V_0}{R_f}$$

$$\therefore \underline{V_0 = -R_f \cdot C \cdot \frac{dV}{dt}} \quad \checkmark$$


$$= -R_f \cdot C \cdot 3 \cdot -\frac{1}{R_1 C} \cdot e^{-t/R_1 C}$$

$$= \frac{R_f}{R_1} \cdot 3 \cdot e^{-t/R_1 C}$$

$$= 12 \cdot e^{-10t} \quad (V), t > 0$$



find  $V(t)$  and  $V_o(t)$

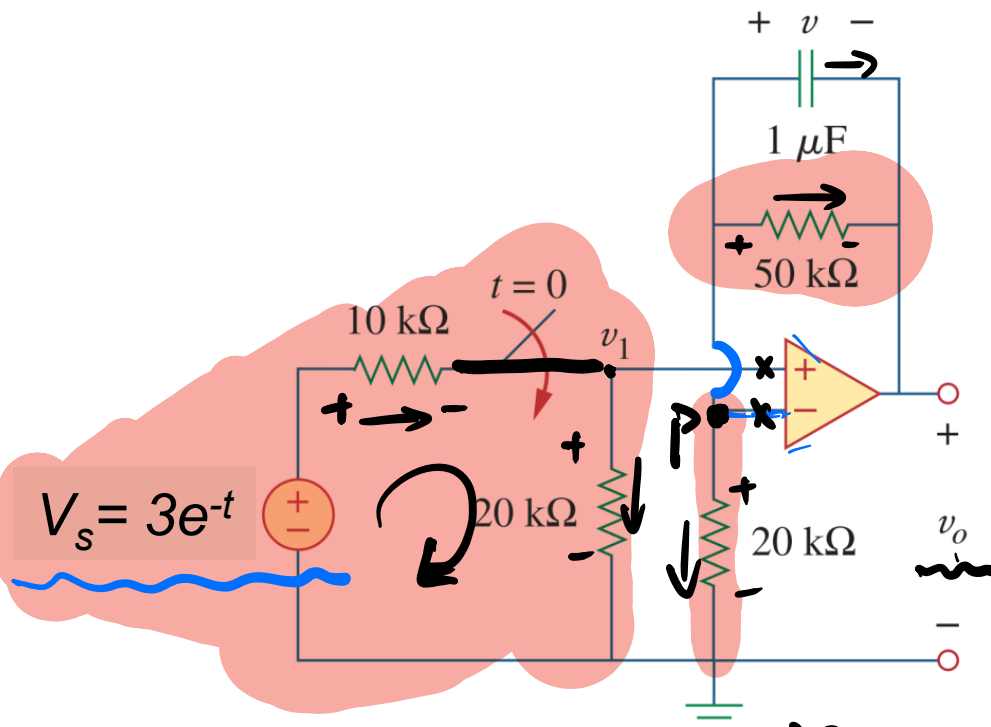

$t < 0$   
 $V_{(0^+)} = V_{(0^-)} = 0\text{ V}$

$V_o = V_p - V$

Node P  $\rightarrow$   $t = 0, V_1 = 2\text{ V}$   $V_p = V_1 = 2\text{ V}$

KCL:  $C \cdot \frac{dV}{dt} + \frac{V}{50\text{ k}} + \frac{2}{20\text{ k}} = 0$

$\frac{20}{10+20} \times 3$

$$\underline{t > 0} \quad V_s = 3 \cdot e^{-t}, \quad V_i = \frac{20}{10+20} \cdot 3 \cdot e^{-t} = 2 \cdot e^{-t}$$

$$V_p = V_i = \underline{2 \cdot e^{-t}}$$

$$P \rightarrow KCL: \quad C \cdot \frac{dV}{dt} + \frac{V}{50k} + \frac{2 \cdot e^{-t}}{20k} = 0$$

$$\frac{dV}{dt} + \frac{V}{C \cdot 50k} = - \frac{2 \cdot e^{-t}}{C \cdot 20k}$$

$$\frac{1}{C \cdot 50k} = 20$$

$$G.S. \quad \underline{V' = A \cdot e^{-20t}}$$

$$P.S. \quad \underline{V'' = B \cdot e^{-t}}$$

$$-B \cdot e^{-t} + \frac{B \cdot e^{-t}}{C \cdot 50k} = - \frac{2 \cdot e^{-t}}{C \cdot 20k}$$

$$2. \quad B = - \frac{100}{19}$$

①




$$\therefore V'' = -\frac{100}{19} \cdot e^{-t}$$


---

$$\begin{aligned} \underline{V(t)} &= V' + V'' \\ &= A \cdot e^{-20t} - \frac{100}{19} e^{-t} \end{aligned}$$


---

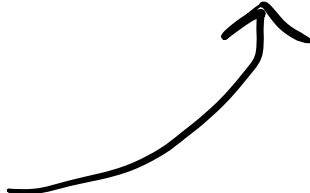
$$V(0^+) = V(0^-)$$


$$A: A = \frac{100}{19}$$

$$V(t) = \frac{100}{19} \cdot e^{-20t} - \frac{100}{19} e^{-t} \quad (2)$$

$$\underline{V_o(t)} = V_p - V(t) = 2 \cdot e^{-t}$$



---

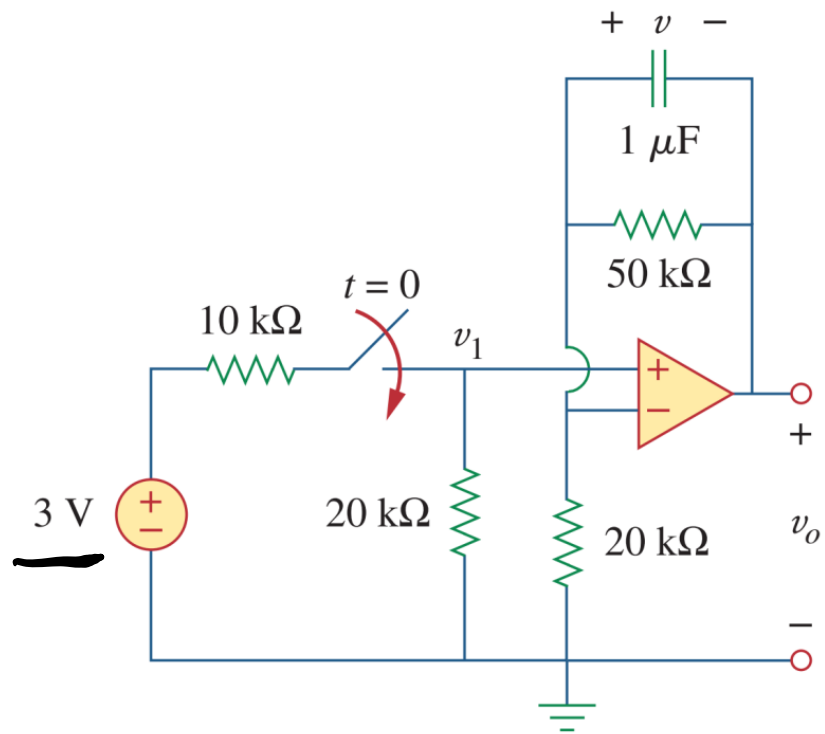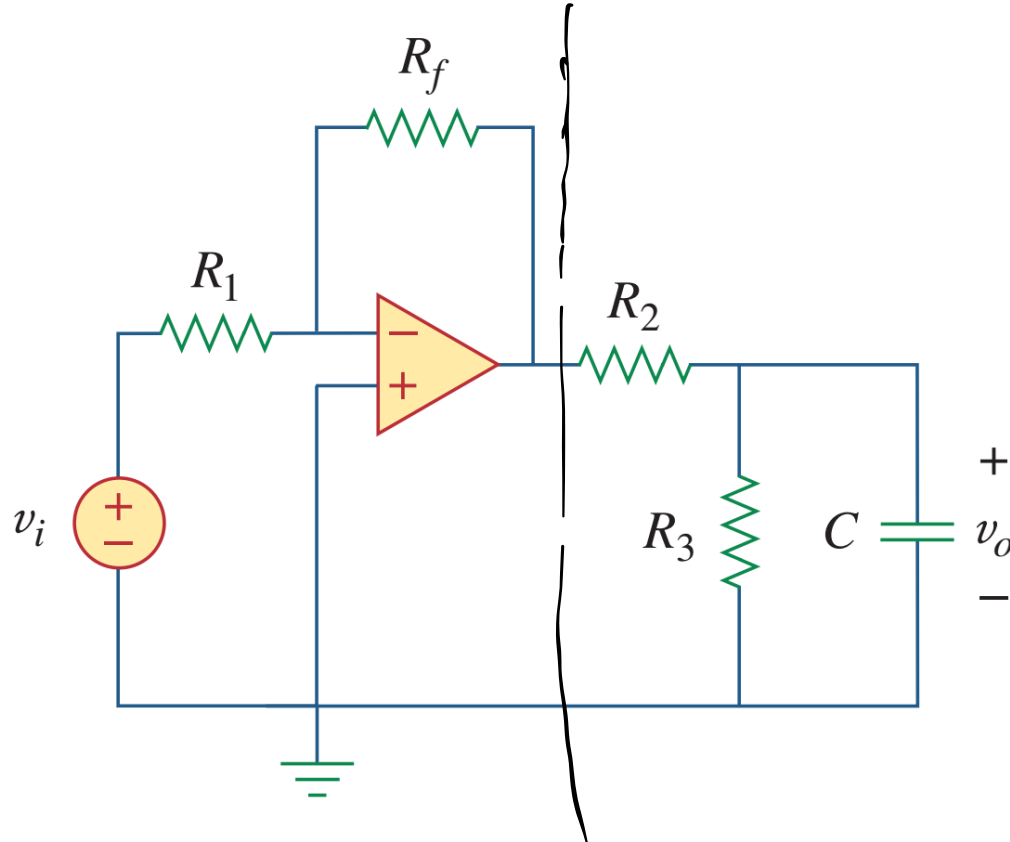





Find the step response  $v_o(t)$  for  $t > 0$  in the op amp circuit of Fig. 7.59. Let  $v_i = 2u(t)$  V,  $R_1 = 20 \text{ k}\Omega$ ,  $R_f = 50 \text{ k}\Omega$ ,  $R_2 = R_3 = 10 \text{ k}\Omega$ ,  $C = 2 \text{ }\mu\text{F}$ .





# Practice

