

ShanghaiTech University

EE 115B: Digital Circuits


Fall 2022

Lecture 18

Hengzhao Yang
December 6, 2022


Registers

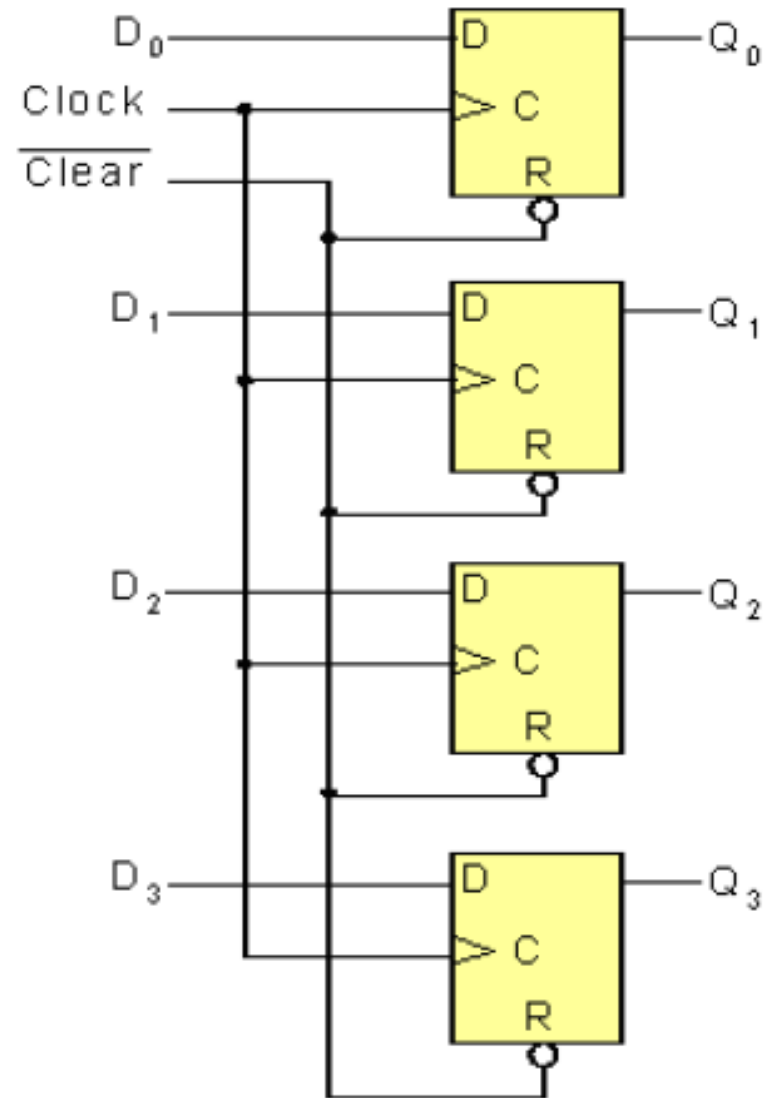- An N-bit register is a set of N flip-flops used to store N bits of information.
- Example: 4-bit register
 - One D flip-flop for each bit
 - Same Clock and Clear signals for all 4 D flip-flops
 - Input: D_0 - D_3
 - Output: Q_0 - Q_3




Shift registers

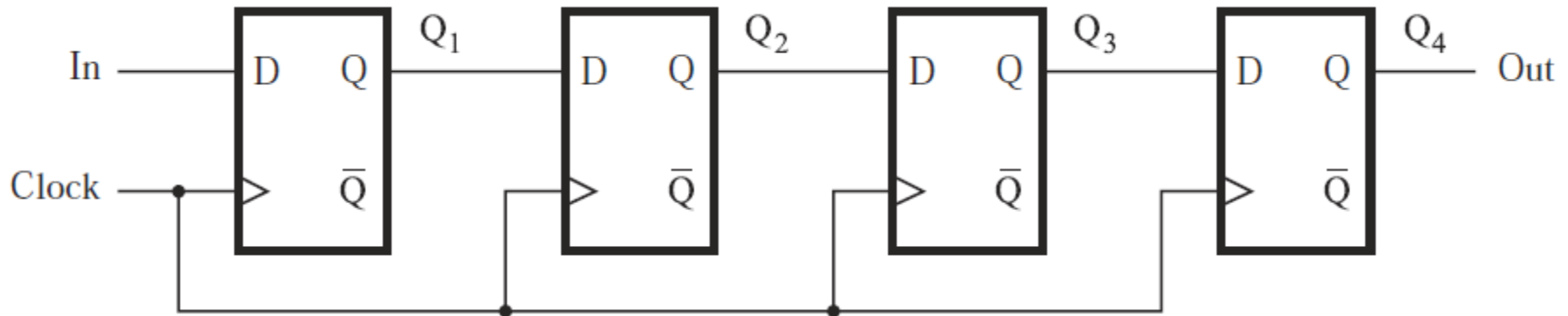- Shift register: a register with the ability to shift its contents
- Example: 4-bit shift register




4-bit shift register

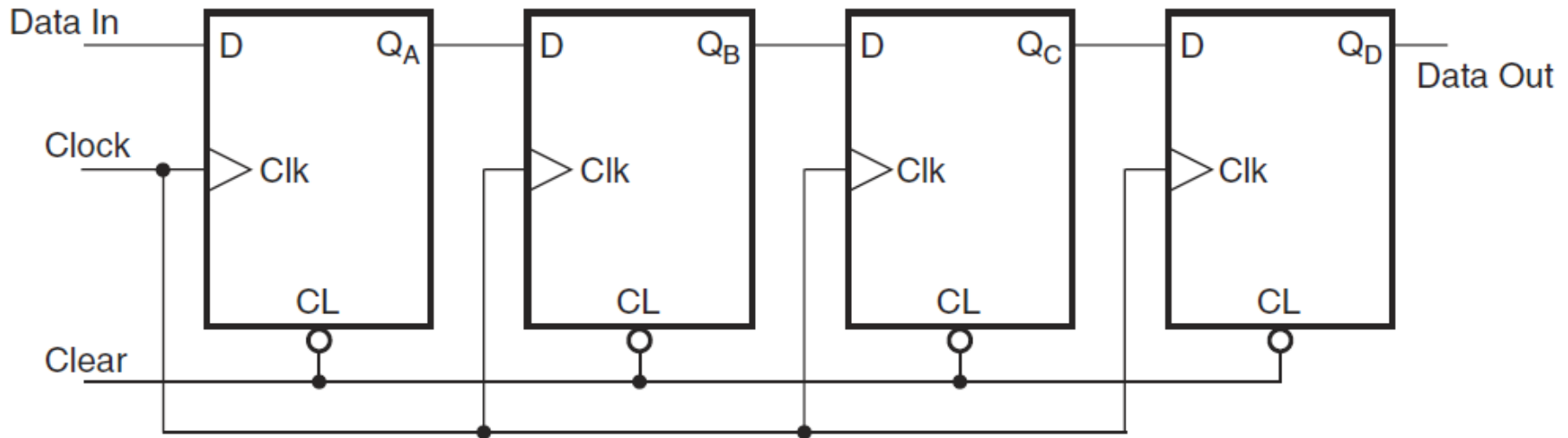- Circuit diagram (with asynchronous clear)



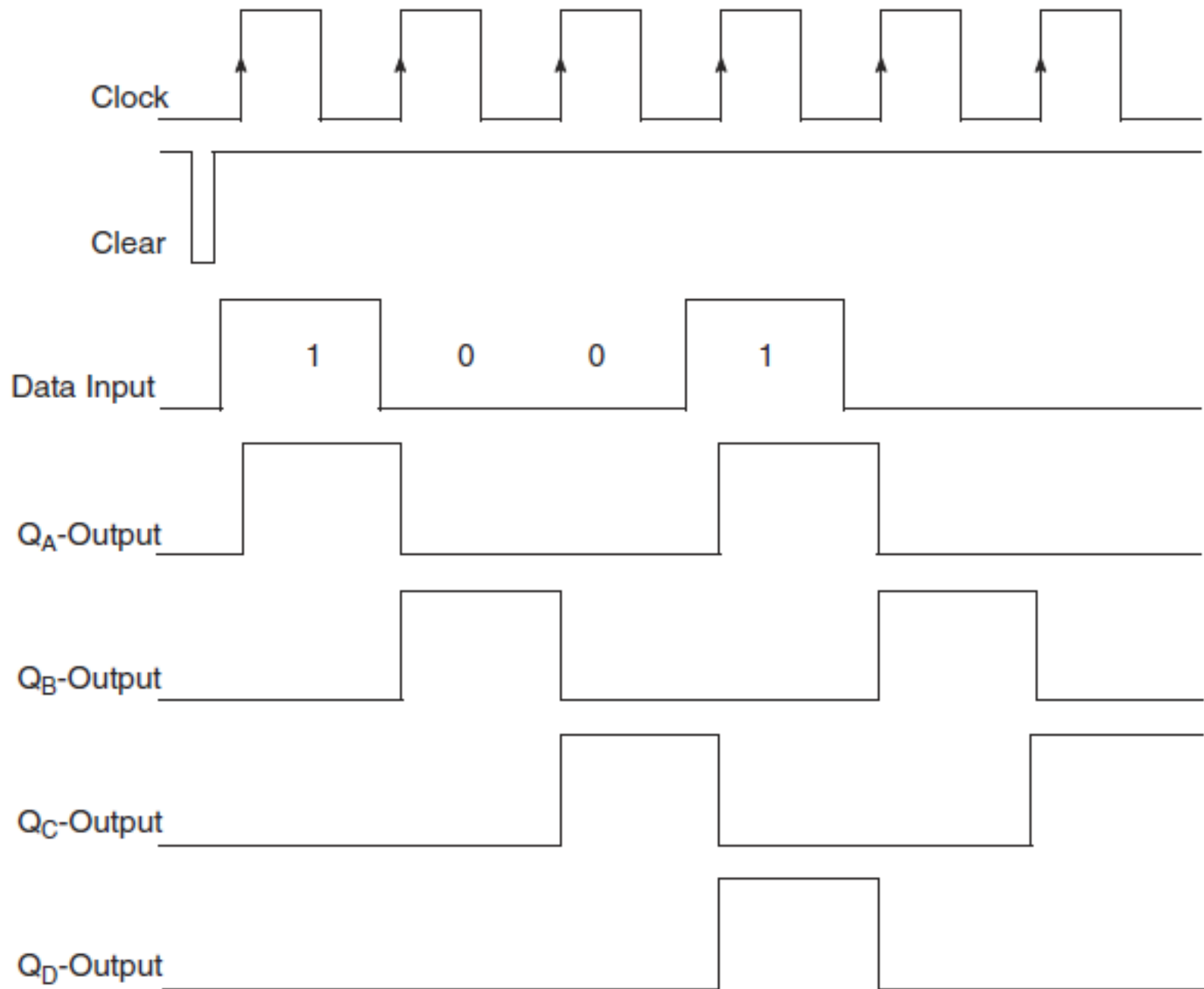- Timing diagram (next page)
 - Input: 1 (first bit), 0, 0, 1 (last bit)




4-bit shift register

- Contents of flip-flops
 - Input is **shifted to the right** by one bit during each clock cycle
 - An input bit propagates to output after 4 clock cycles
 - 4 clock cycles to load input, another 4 cycles to read output


Clock	Q_A	Q_B	Q_C	Q_D
Initial contents	0	0	0	0
After first clock transition	1	0	0	0
After second clock transition	0	1	0	0
After third clock transition	0	0	1	0
After fourth clock transition	1	0	0	1
After fifth clock transition	0	1	0	0
After sixth clock transition	0	0	1	0
After seventh clock transition	0	0	0	1
After eighth clock transition	0	0	0	0

4-bit registers: shift-right and shift-left

- Shift-right

 





- Shift-left

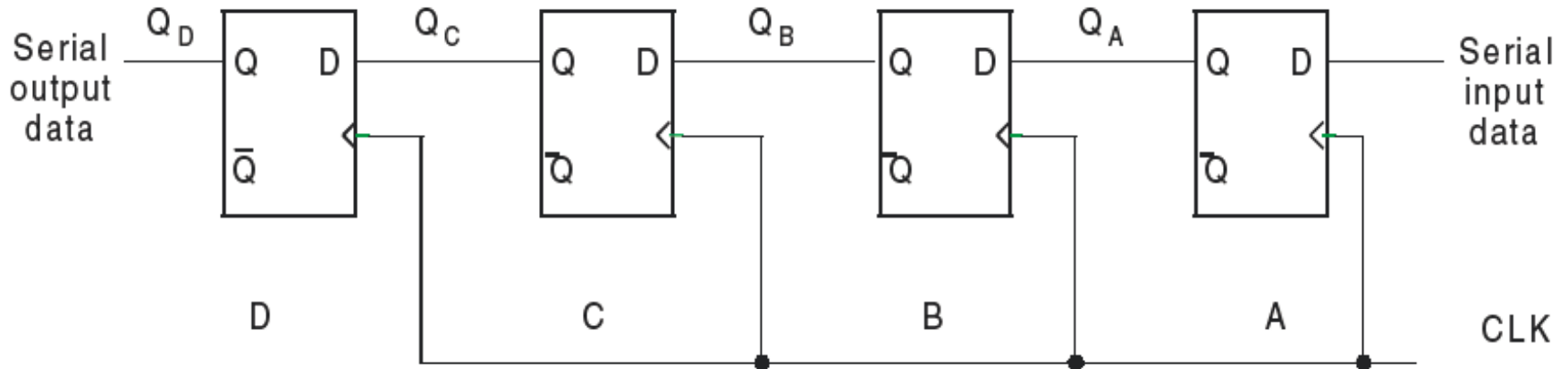

Shift register types


- 4 types depending on the method to load and read data
 - Serial-in serial-out (SISO)
 - Serial-in parallel-out (SIPO)
 - Parallel-in serial-out (PISO)
 - Parallel-in parallel-out (PIPO)

Shift register types

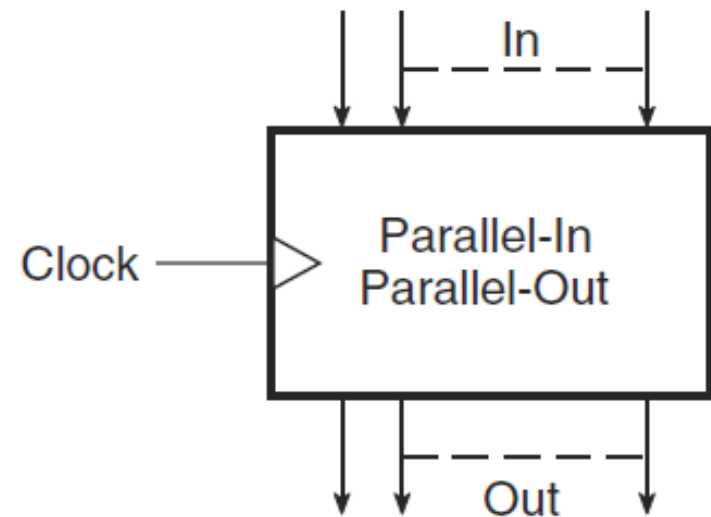  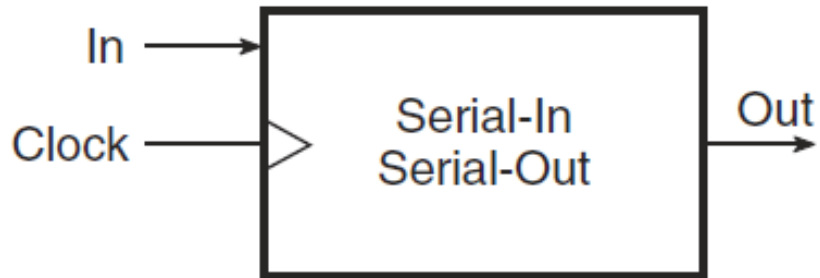

Parallel-access (parallel-loading) shift register

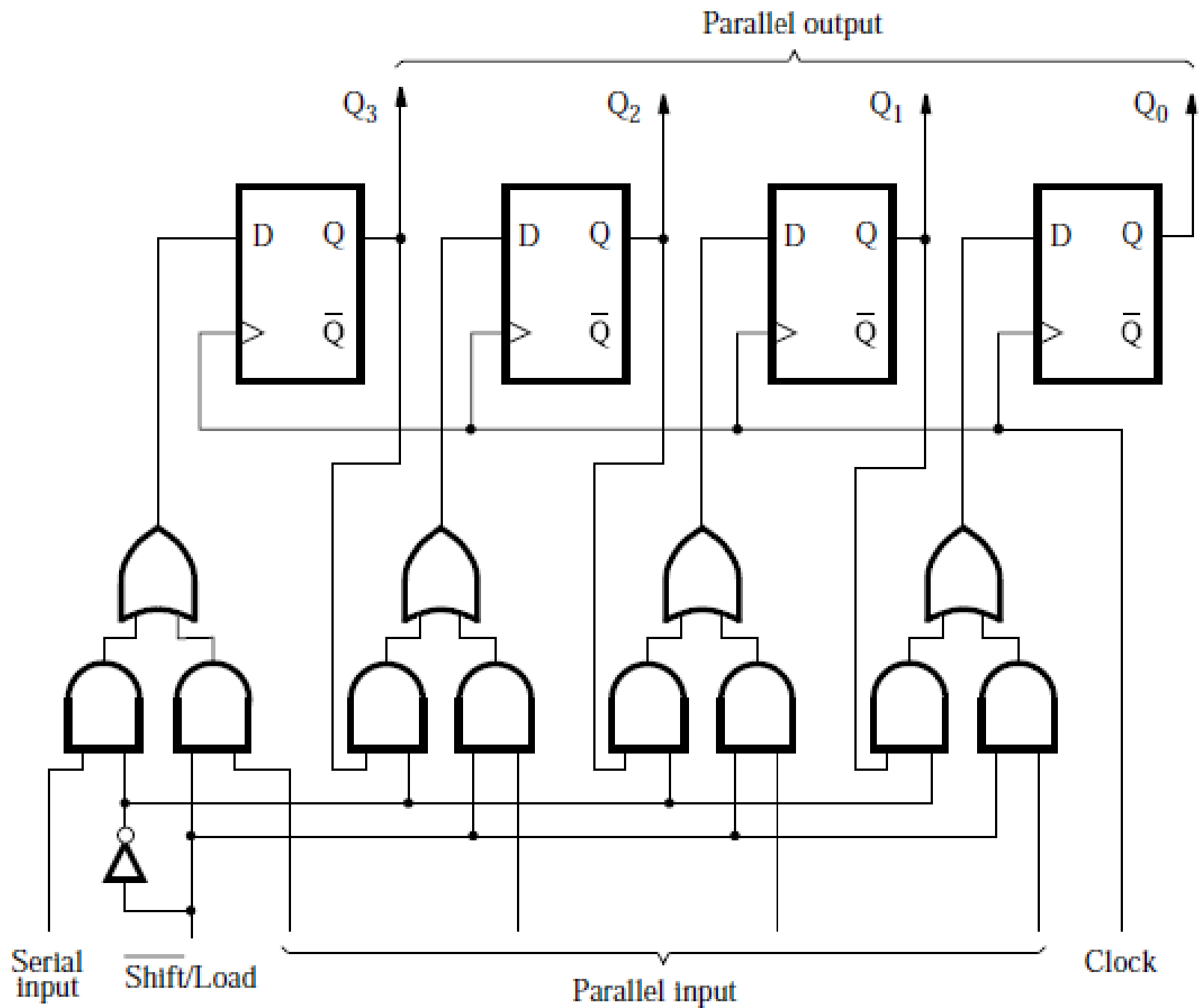- Circuit structure
 - Top (D flip-flops): register
 - Bottom (2 AND + 1 OR gates): 2-to-1 mux
- Mode selection signal: *Shift/Load*
 - Value 0: shift register
 - Serial input is selected: serial input to D_3 (D input of leftmost flip-flop), Q_3 to D_2 , Q_2 to D_1 , Q_1 to D_0
 - Shift-right register
 - Value 1: parallel loading
 - Parallel input is selected



Code for 8-bit register with asynchronous clear

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY reg8 IS  
    PORT ( D          : IN   STD_LOGIC_VECTOR(7 DOWNT0 0) ;  
          Resetn, Clock : IN   STD_LOGIC ;  
          Q           : OUT  STD_LOGIC_VECTOR(7 DOWNT0 0) ) ;  
END reg8 ;
```

```
ARCHITECTURE Behavior OF reg8 IS
```

```
BEGIN
```

```
    PROCESS ( Resetn, Clock )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```

```
            Q <= "00000000" ;
```


```
        ELSIF Clock'EVENT AND Clock = '1' THEN
```

```
            Q <= D ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

 


Comparison: Code for D flip-flop with asynchronous reset (clear)

- Asynchronous reset (clear): active low

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN  STD_LOGIC ;
          Q : OUT STD_LOGIC) ;
END flipflop ;

 ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



Code for N-bit register with asynchronous clear

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY regn IS
    GENERIC ( N : INTEGER := 16 ) ;
    PORT ( D          : IN  STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
          Resetn, Clock : IN  STD_LOGIC ;
          Q           : OUT STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
END regn ;


ARCHITECTURE Behavior OF regn IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= (OTHERS => '0') ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Code for N-bit register with asynchronous clear

- **GENERIC (N: INTEGER := 16)**
 - Define a parameter (N), its type (INTEGER), and its value (16)
 - Assignment operator: “:=”
- **Q <= (OTHERS => '0')**
 - Reset all bits of Q to 0 regardless of the bit length of Q
 - For N=16, this statement is equivalent to Q<=“0000000000000000”

Structural code for 4-bit parallel-access shift register

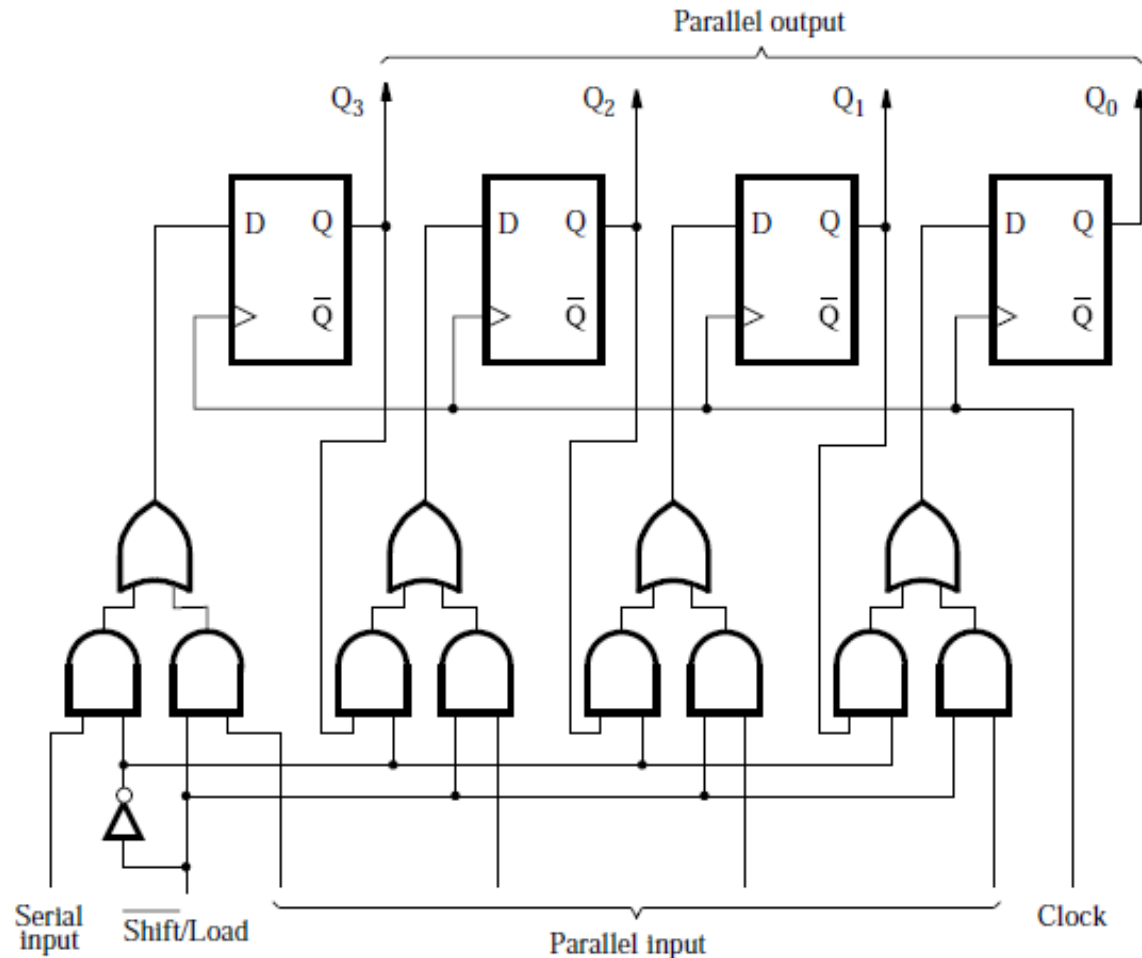
- Component: a D flip-flop with a 2-to-1 MUX on D input



Structural code for 4-bit parallel-access shift register: component

- Sel: mode selection

 - Sel=0: D=D0 (left-hand AND is active, left signal is selected: serial input or preceding Q)
- Sel=1, D=D1 (right-hand AND is active, right signal is selected: parallel input)



```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY muxdff IS
    PORT ( D0, D1, Sel, Clock : IN  STD_LOGIC ;
          Q                   : OUT STD_LOGIC ) ;
END muxdff ;

ARCHITECTURE Behavior OF muxdff IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Sel = '0' THEN
            Q <= D0 ;
        ELSE
            Q <= D1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Structural code for 4-bit parallel-access shift register: entire circuit

- R: parallel input, L: mode selection, w: serial input

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY shift4 IS
    PORT ( R          : IN          STD_LOGIC_VECTOR(3 DOWNTO 0) ;
           L, w, Clock : IN          STD_LOGIC ;
           Q          : BUFFER STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END shift4 ;

ARCHITECTURE Structure OF shift4 IS
    COMPONENT muxdff
        PORT ( D0, D1, Sel, Clock : IN    STD_LOGIC ;
              Q                  : OUT STD_LOGIC ) ;
    END COMPONENT ;
BEGIN
    Stage3: muxdff PORT MAP ( w, R(3), L, Clock, Q(3) ) ;
    Stage2: muxdff PORT MAP ( Q(3), R(2), L, Clock, Q(2) ) ;
    Stage1: muxdff PORT MAP ( Q(2), R(1), L, Clock, Q(1) ) ;
    Stage0: muxdff PORT MAP ( Q(1), R(0), L, Clock, Q(0) ) ;
END Structure ;
```

Behavioral code for 4-bit parallel-access shift register

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;
3  ENTITY shift4 IS
4      PORT ( R      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
5             Clock   : IN      STD_LOGIC ;
6             L, w    : IN      STD_LOGIC ;
7             Q       : BUFFER STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
8  END shift4 ;

9  ARCHITECTURE Behavior OF shift4 IS
10 BEGIN
11     PROCESS
12     BEGIN
13         WAIT UNTIL Clock'EVENT AND Clock = '1' ;
14         IF L = '1' THEN
15             Q <= R ;
16         ELSE
17             Q(0) <= Q(1) ;
18             Q(1) <= Q(2) ;
19             Q(2) <= Q(3) ;
20             Q(3) <= w ;
21         END IF ;
22     END PROCESS ;
23 END Behavior ;
```

Behavioral code for N-bit parallel-access shift register

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;
3  ENTITY shiftn IS
4      GENERIC ( N : INTEGER := 8 ) ;
5      PORT ( R      : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
6            Clock   : IN      STD_LOGIC ;
7            L, w    : IN      STD_LOGIC ;
8            Q       : BUFFER STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
9  END shiftn ;
10 ARCHITECTURE Behavior OF shiftn IS
11 BEGIN
12     PROCESS
13     BEGIN
14         WAIT UNTIL Clock'EVENT AND Clock = '1' ;
15         IF L = '1' THEN
16             Q <= R ;
17         ELSE
18             Genbits: FOR i IN 0 TO N-2 LOOP
19                 Q(i) <= Q(i + 1) ;
20             END LOOP ;
21             Q(N-1) <= w ;
22         END IF ;
23     END PROCESS ;
24 END Behavior ;
```

FOR LOOP: generate
a set of sequential
statements

Counters

- Asynchronous (serial or ripple): different stages are driven by different clocks
 - Up-counters
 - Down-counters
- Synchronous (parallel): different stages are driven by the same clock
 - Up-counters
 - Down-counters

Asynchronous up-counter with T flip-flops

- A 3-bit up-counter
 - It counts the number of clock cycles
 - Stage 1 is driven by Clock, stages 2 and 3 are driven by preceding output complement
 - Counter output: $Q_2Q_1Q_0$ (MSB to LSB)
 - Counter modulus (MOD number): number of different logic states represented by counter
 - Modulo-8 or MOD-8: states 0-7
 - Asynchronous (serial or ripple): three stages respond after different delays

Asynchronous up-counter with T flip-flops

