
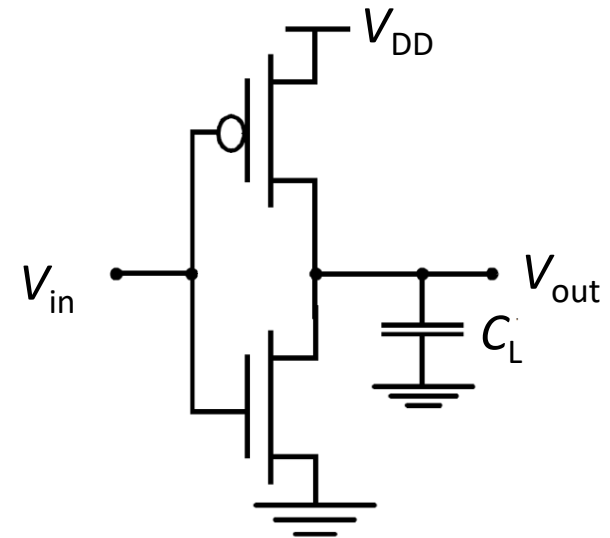


NOT function (Inverter)


- Boolean expression $X = \bar{A}$
- Truth table

Input	Output
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)

- Logic circuit

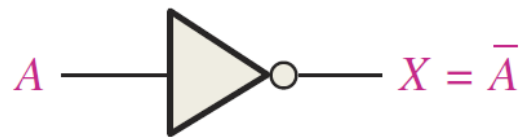

Circuit implementation

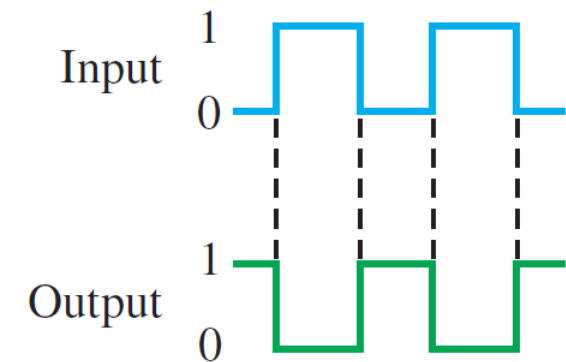

Waveform


AND operation

- Boolean expression $X = AB$


- Truth table

Inputs		Output
A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

- Logic circuit

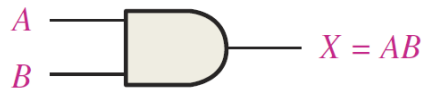


Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

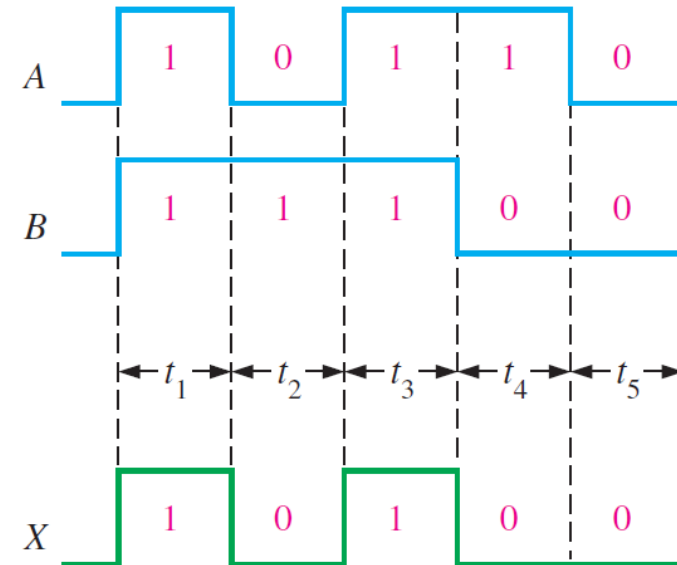

Application of AND gate

Seat Belt Alarm System

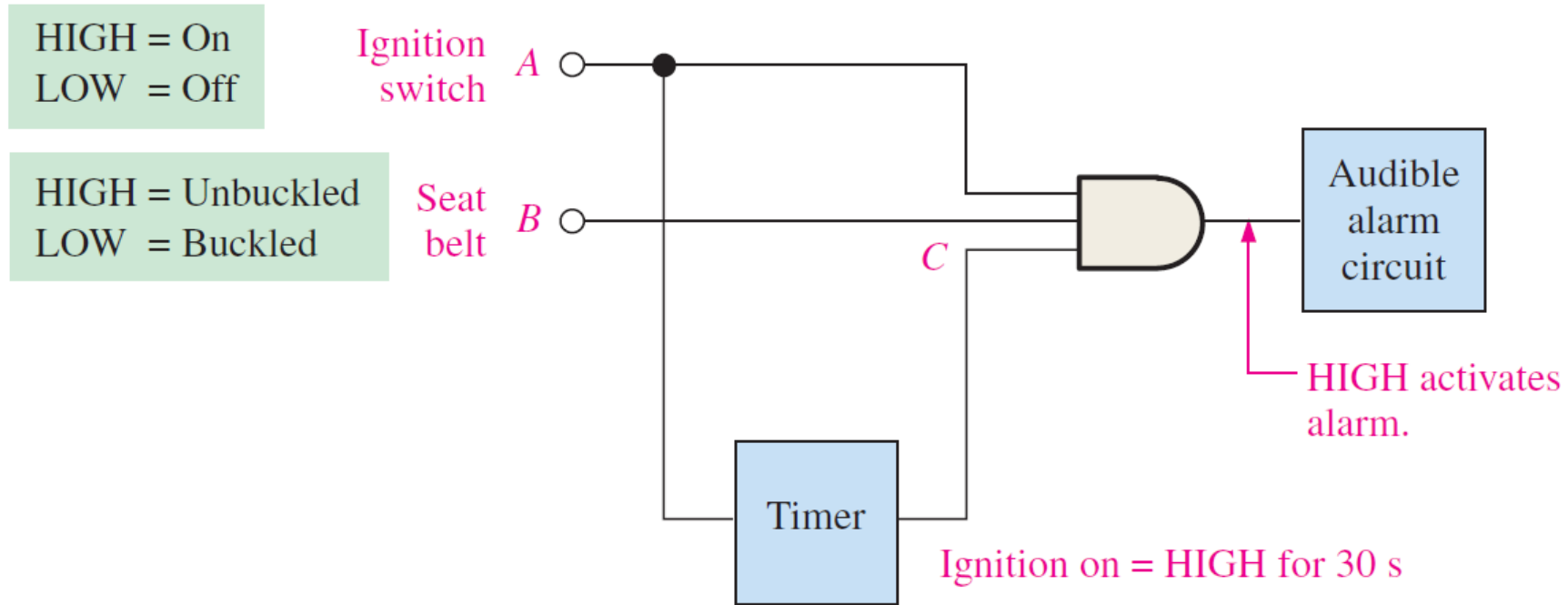

If the ignition is on and the seat belt is unbuckled and the timer is running, the output is HIGH.


OR operation

- Boolean expression $X = A + B$
- Truth table


A	B	$A + B = X$
0	0	$0 + 0 = 0$
0	1	$0 + 1 = 1$
1	0	$1 + 0 = 1$
1	1	$1 + 1 = 1$

$A \quad B \quad C$

$X = A + B + C$

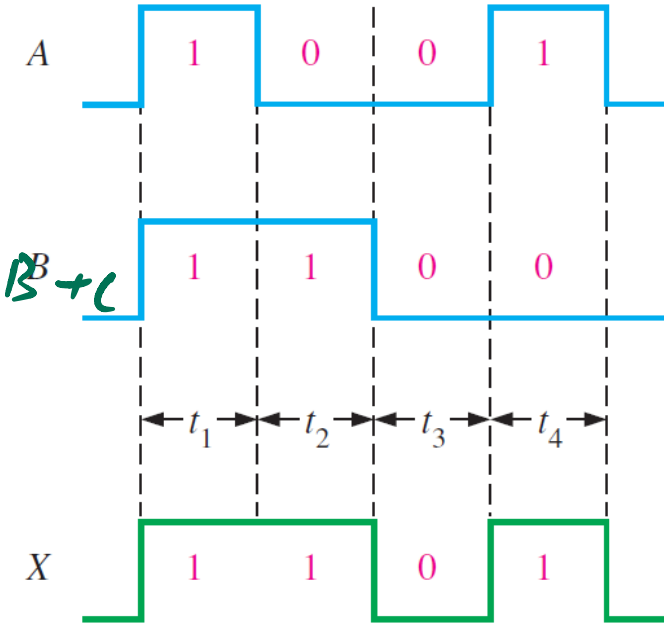


- Logic circuit

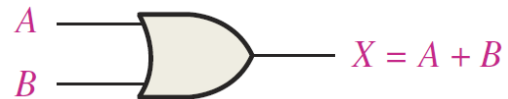

Question: draw the truth table for 3-input OR gate

Application of OR gate

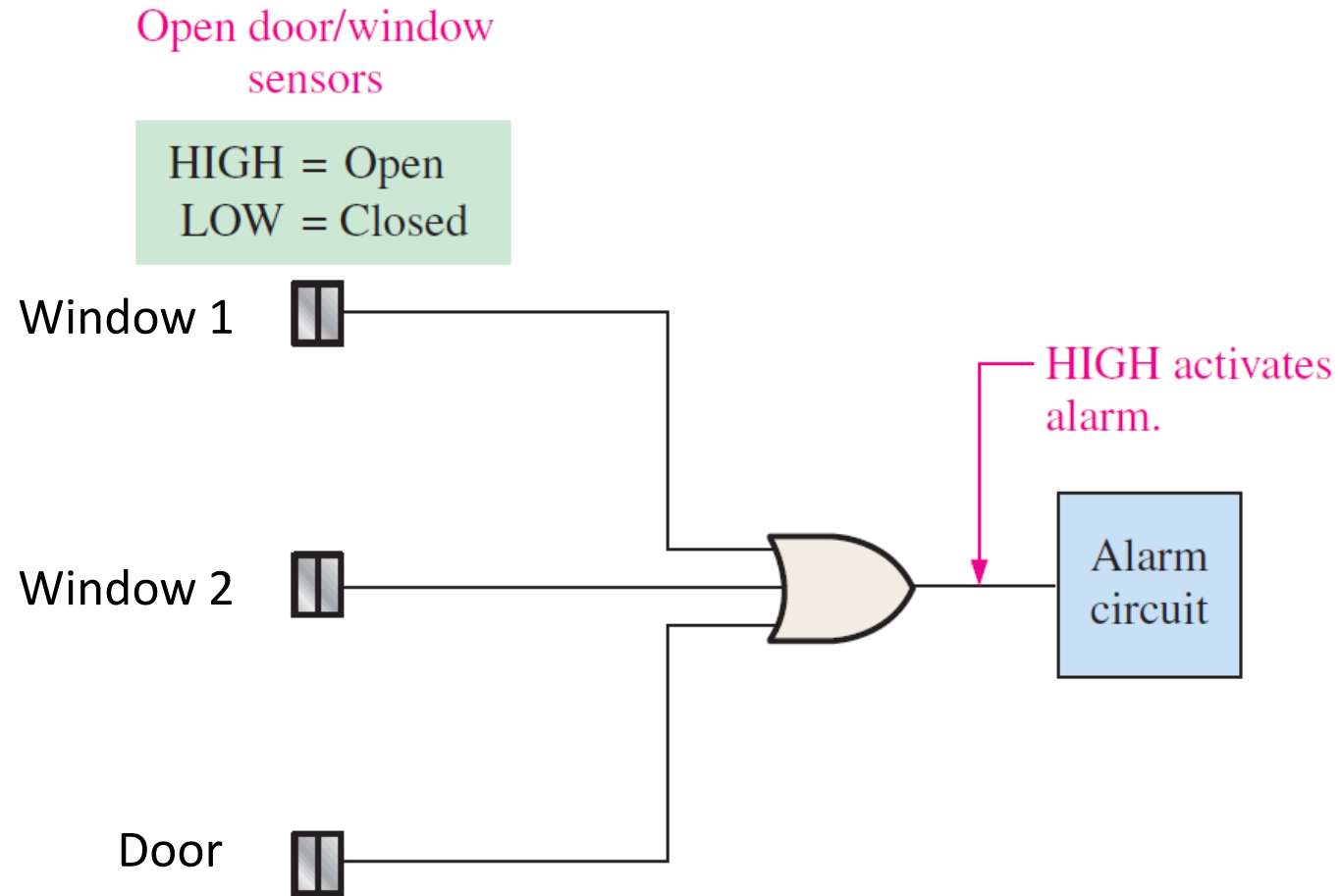


When one of the windows or the door is opened, the gate output goes HIGH.

NAND gate

- Boolean expression

$$X = \overline{AB}$$


- Logic circuit

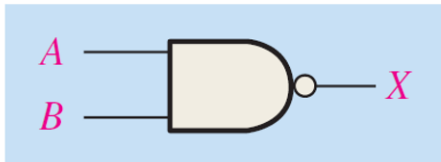

- Truth table

Inputs		Output
A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

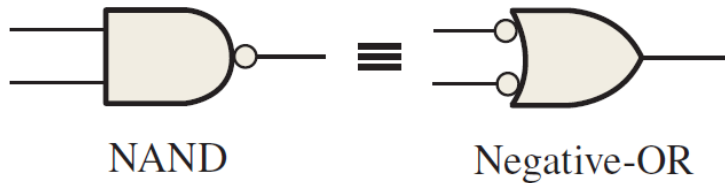
- Inherent in a NAND gate's operation is the fact that one or more LOW inputs produce a HIGH output



$$\overline{AB} = \overline{A} + \overline{B}$$

Verify this using truth table

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

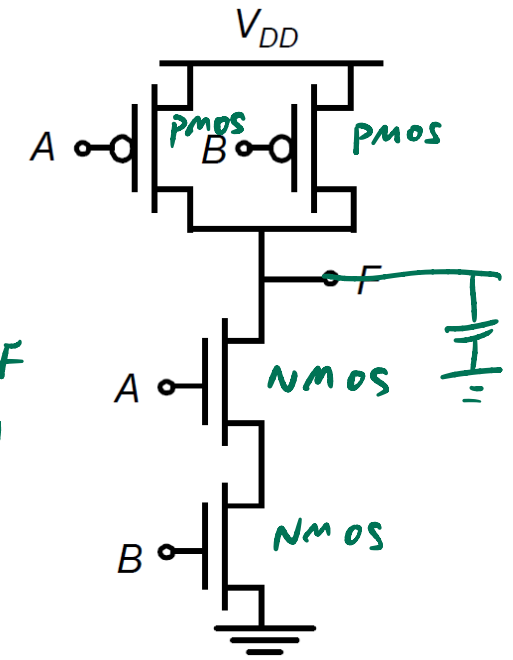

Circuit


Question: draw the truth table for 3-input NAND gate

NOR gate

- Boolean expression

$$X = \overline{A + B}$$


- Logic circuit

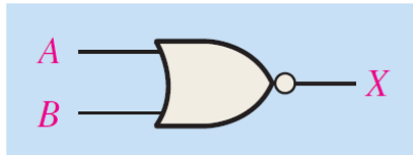

- Truth table

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

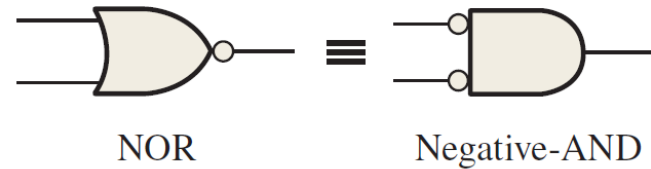
- A HIGH is produced on the gate output only when all of the inputs are LOW



$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

Verify this using truth table

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

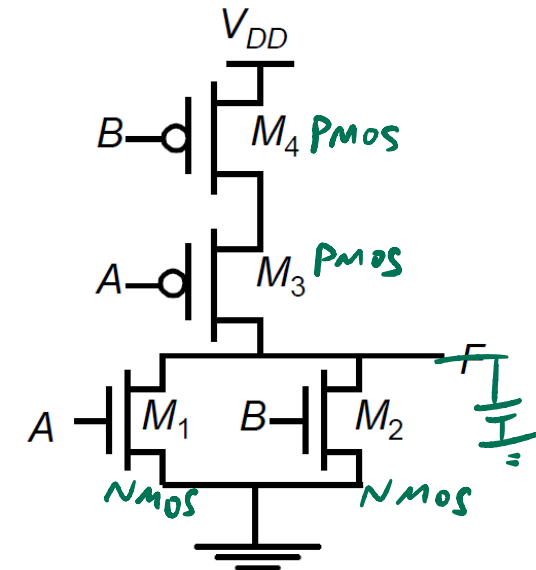


Circuit

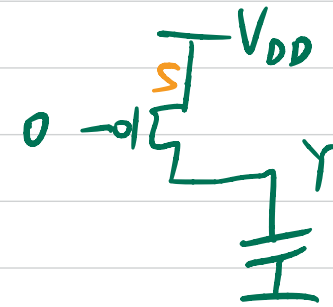Question: draw the truth table for 3-input NOR gate

pull up $\Rightarrow V_Y = V_{DD} \Rightarrow \text{pmos}$

pull down $\Rightarrow V_Y = 0 \Rightarrow \text{nmos}$




$$V_{GS} = -V_{DD} < V_{TP}$$

$$V_{Y,max} = V_{DD}$$

Nmos is not good pull up
Pmos is not good pull down
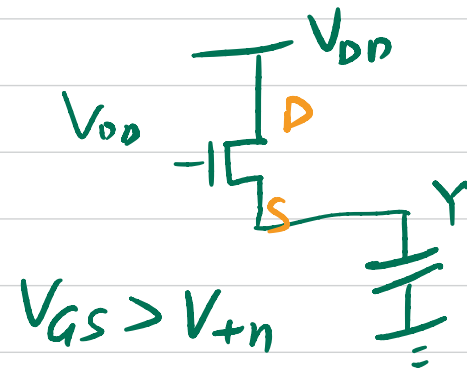
$$\begin{aligned} V_Y &= V_{DD} - V_+ \\ \Rightarrow V_{GS} &= V_{DD} - (V_{DD} - V_+) \\ &= V_+ \end{aligned}$$



$$V_{GS} > V_{TN}$$



$$V_{Y,max} = V_{DD} - V_{TN}$$

Exclusive-OR (XOR) gate

- The output of XOR is HIGH only when the two inputs are at opposite logic levels.
- Truth table

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0

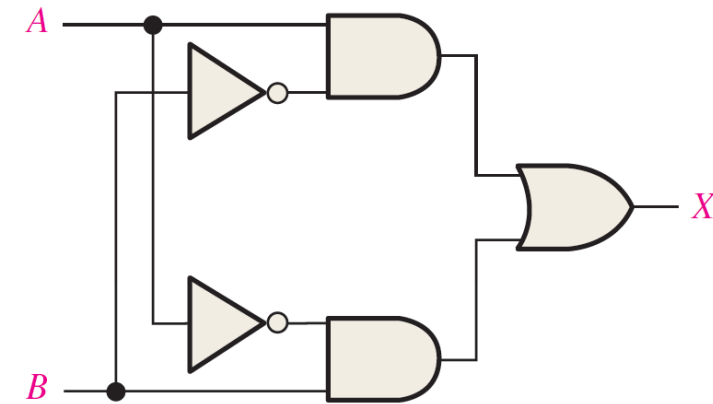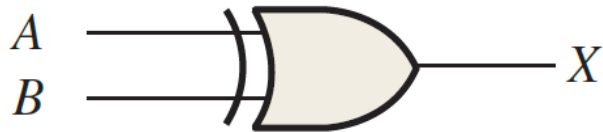- Boolean expression $X = A\bar{B} + \bar{A}B$ or $X = A \oplus B$
- Logic circuit



Question: draw the truth table for 3-input XOR gate

$$(A+B)' = A'B'$$

$$(AB)' = A' + B'$$

$$A \oplus B = A'B + AB'$$

$$A \oplus B \oplus C = (A'B + AB') \oplus C$$

$$= (A'B + AB')'C + (A'B + AB')C'$$

$$= (A'B)'(AB')'C + \dots$$

$$= (A+B')(A'+B)C + \dots$$

$$= \cancel{AA'}C + ABC + A'B'C + \cancel{BB'}C + A'BC' + AB'C'$$

$$= ABC + A'B'C + A'BC' + AB'C'$$



A	B	C	$A \oplus B$	$A \oplus B \oplus C$	X
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	1	1
0	1	1	1	0	0
1	0	0	1	1	1
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1

Exclusive-NOR (XNOR) gate

- The output of XNOR is LOW only when the two inputs are at opposite logic levels.
- Truth table

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	1

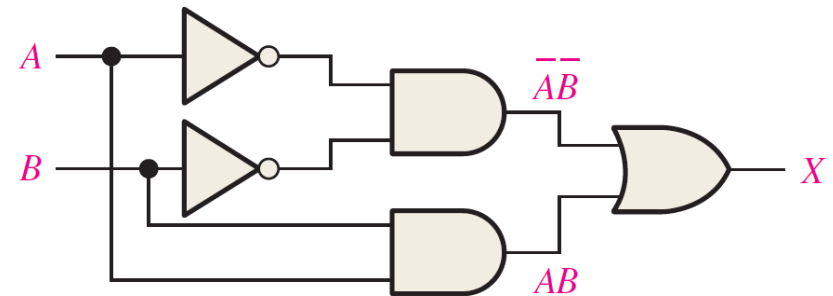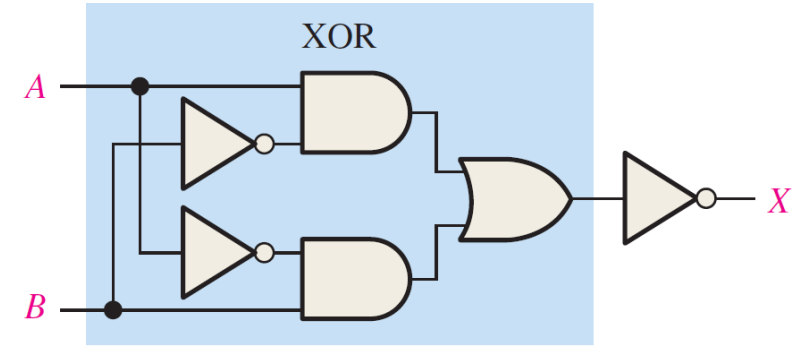- Boolean expression $X = \overline{A}\overline{B} + AB$
- Logic circuit



Think about it:

- In the truth table with two inputs, how many lines? How many columns?

Truth Table & Boolean Expression

Even or odd 1s

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

1
0
1
0
1
0
1
0

Y =






$$y = A'BC + AB'C + ABC'$$

Boolean Expression & Logic Circuit


$B[(AB)' + C(DE + A)'] \Rightarrow \text{circuit?}$

$A(B + CD)$

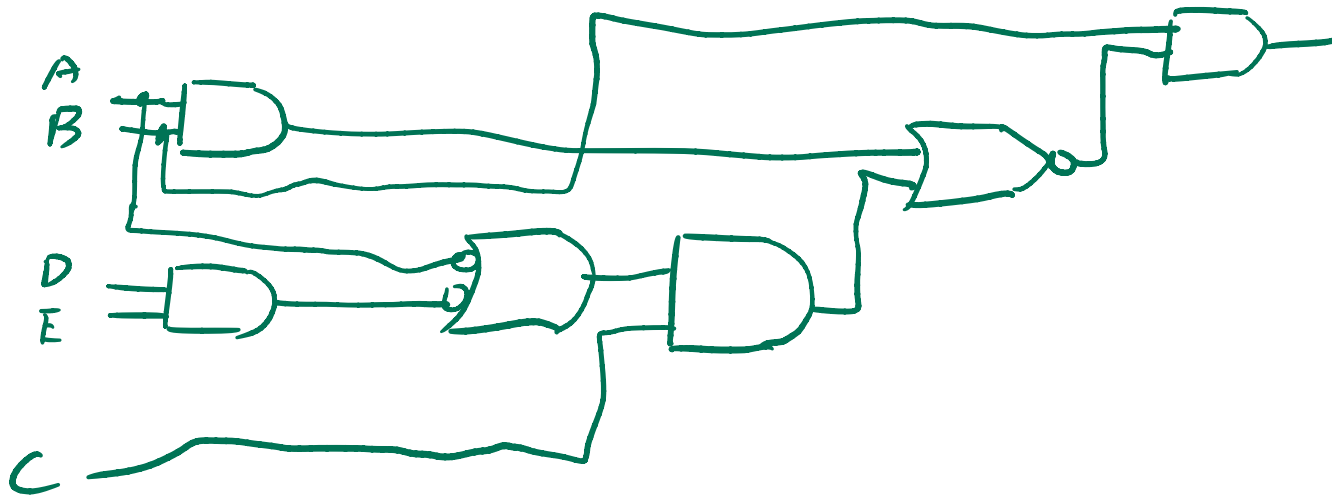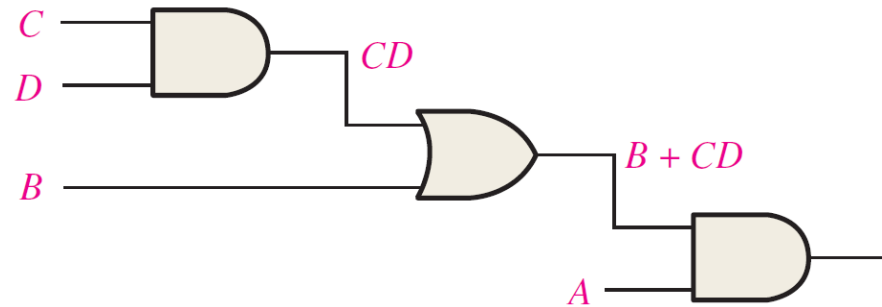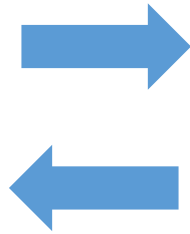

$\Rightarrow \text{Boolean expression?}$

Truth Table & Logic Circuit

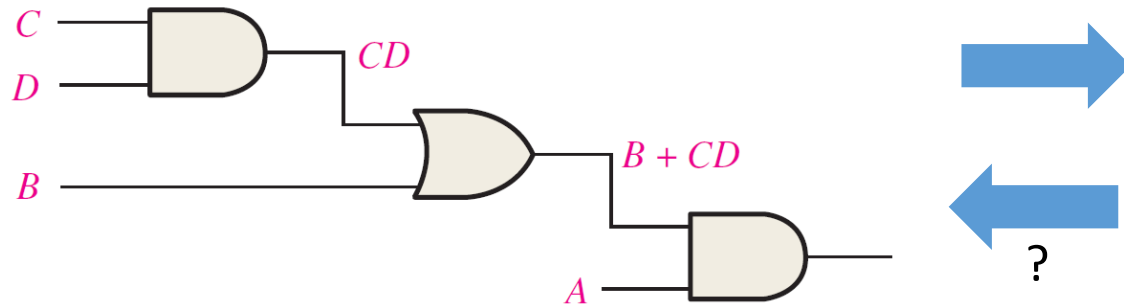

Inputs				Output
A	B	C	D	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Reading materials

- Chapter 3 of Floyd book