



# **Lecture 14**


## **-- Laplace Transform in Circuit Analysis**

## Example 2

Find (1) the voltage across the capacitor

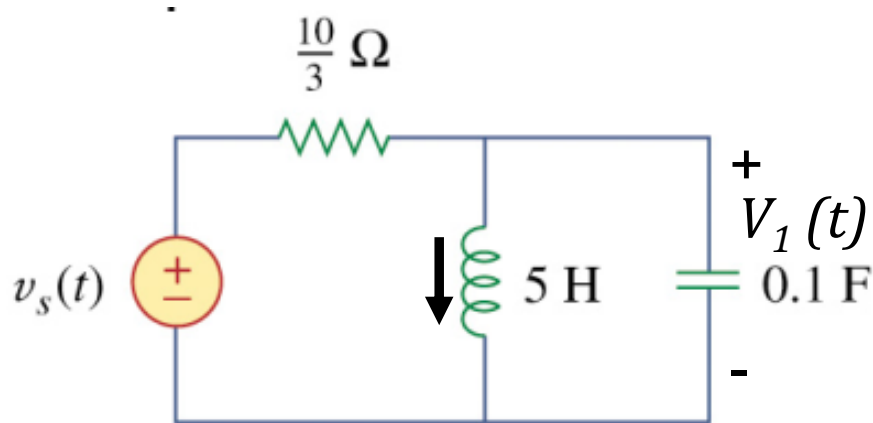(2) current through the inductor


assuming that  $v_s(t) = 10u(t)$  V, and assume that at  $t = 0$ ,  $-1$  A flows through the inductor and  $+5$  V is across the capacitor.


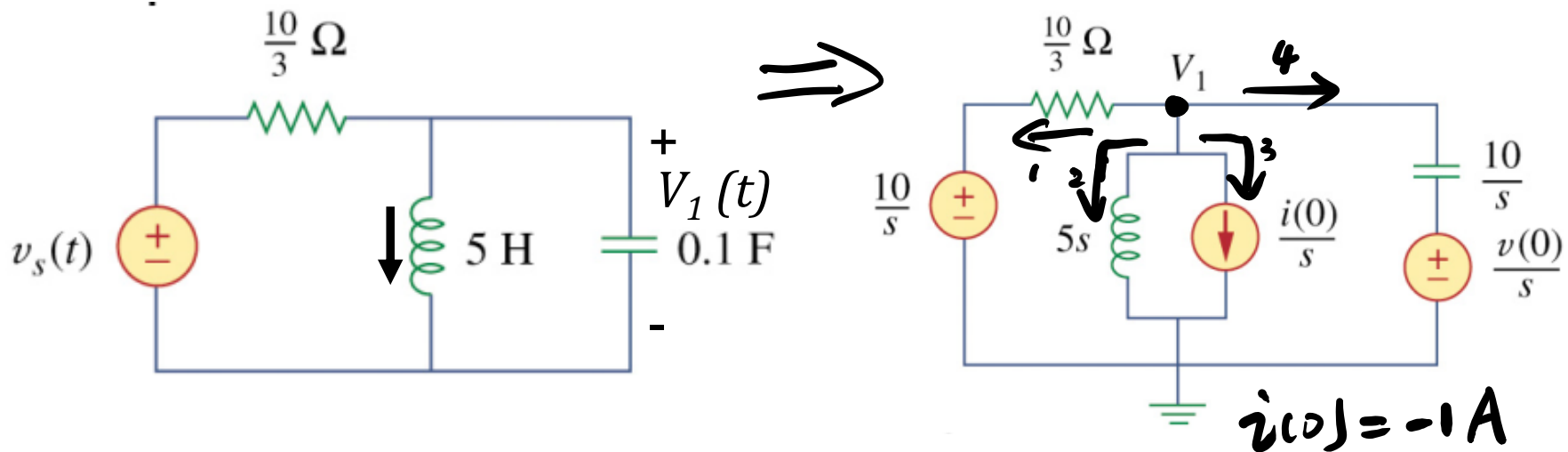
## Example 2

Find (1) the voltage across the capacitor  
(2) current through the inductor

assuming that  $v_s(t) = 10u(t)$  V, and assume that at  $t = 0$ ,  $-1$  A flows through the inductor and  $+5$  V is across the capacitor.




Nodal  $V_1$  :

$$\frac{V_1 - \frac{10}{s}}{\frac{10}{3}} + \frac{V_1 - 0}{5s} + \frac{-1}{s} + \frac{V_1 - \frac{5}{s}}{\frac{10}{s}} = 0$$

$$\Rightarrow V_1(s) = \frac{40 + 5s}{(s+1)(s+2)} = \frac{k_1^{35}}{s+1} + \frac{k_2^{-30}}{s+2}$$

$$V_1(s) = \frac{35}{s+1} - \frac{30}{s+2}$$
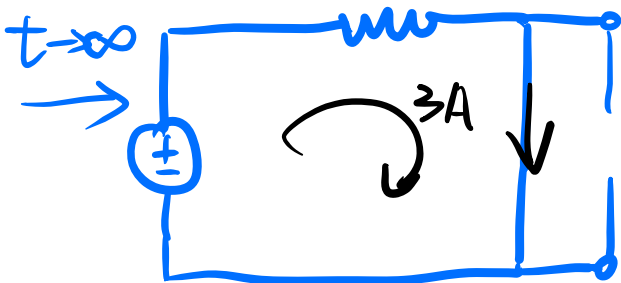
$$\xrightarrow{\mathcal{L}^{-1}} : V_1(t) = [35e^{-t} - 30e^{-2t}]u(t) \quad t > 0$$



For  $I(s)$

$$I(s) = \frac{V_1 - 0}{5s} + \frac{1}{s}$$

$$\& V_1(s) = \frac{40 + 5s}{(s+1)(s+2)}$$

$$\Rightarrow I(s) = \frac{40 + 5s}{5s(s+1)(s+2)} - \frac{1}{s}$$

$$= \frac{-s^2 - 2s + 6}{s(s+1)(s+2)}$$

$$= \frac{k_1' \textcircled{3}}{s} + \frac{k_2' \textcircled{-7}}{s+1} + \frac{k_3' \textcircled{3}}{s+2}$$


$$\Rightarrow \mathcal{L}^{-1} \quad i(t) = (3 - 7e^{-t} + 3e^{-2t}) u(t), t > 0 \quad A$$

In T. 1).

$$i_L(t) = i_0 + \frac{1}{L} \int_0^t v_L(t) dt \quad \leftarrow$$

$$v_L(t) = v_1(t) = [35 \cdot e^{-t} - 30e^{-2t}] u(t) \quad t > 0$$
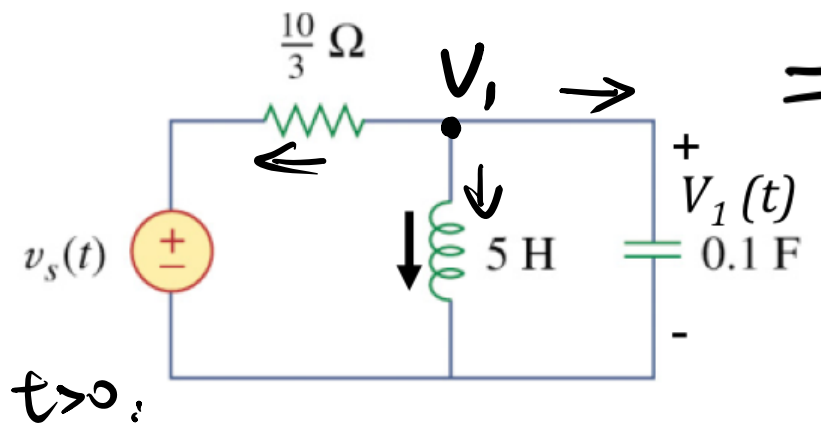
$$i_L(t) = (3 - 7e^{-t} + 3e^{-2t}) u(t) \quad A, t > 0$$



$$\frac{V_1 - 10}{\frac{10}{3}} + \dot{i}_L + C \cdot \frac{dV_1}{dt} = 0 \quad (1)$$

$$\dot{i}_L = \dot{i}_0 + \frac{1}{L} \int V_1 dt \quad (2)$$


$$V_1'' + 3V_1' + 2V_1 = 0$$

$$s^2 + 3s + 2 = 0$$

$$(s+1)(s+2) = 0$$

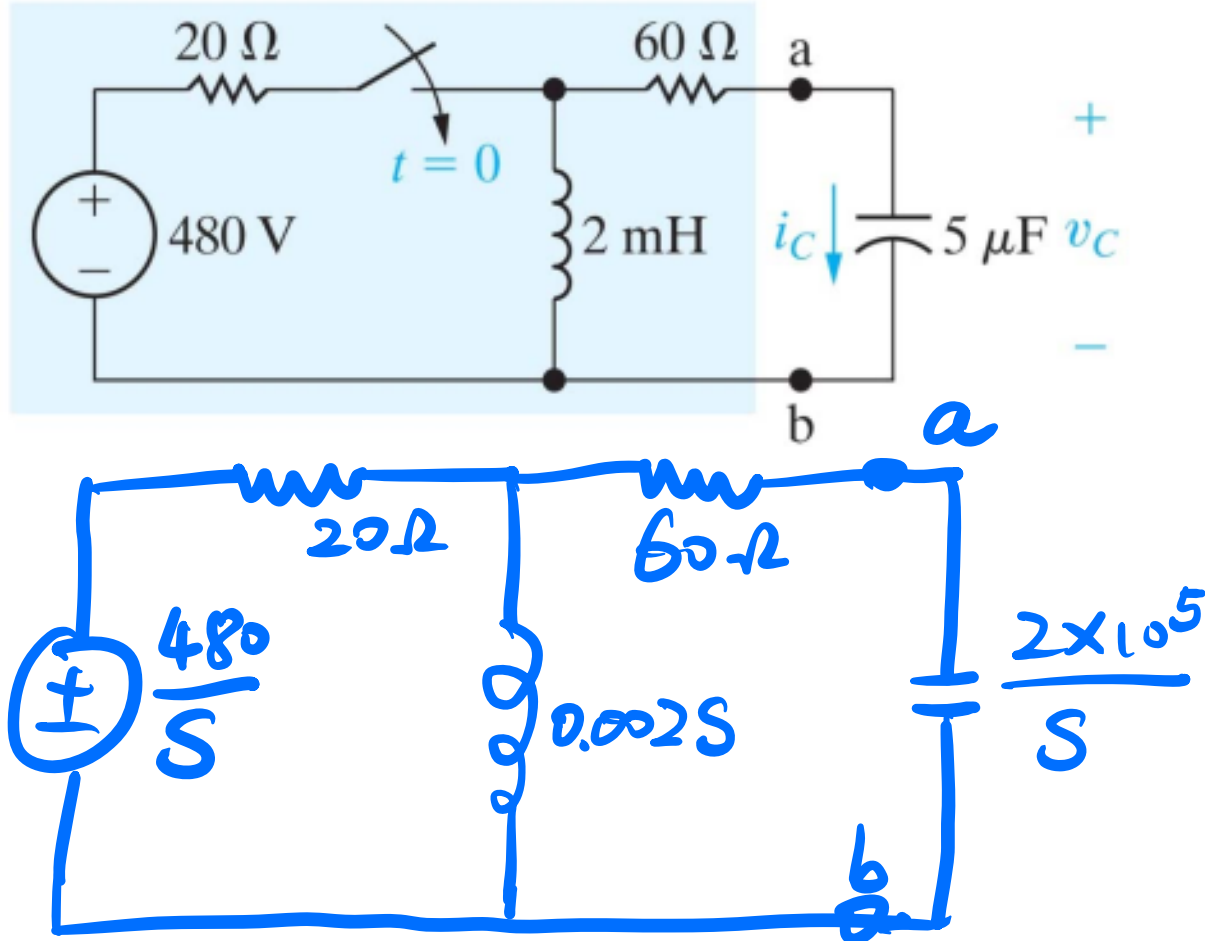
## Example 3

- Use Thevenin's equivalent circuit w.r.t. terminals  $a$ - $b$  to find current  $i_C(t)$  for  $t > 0$ .



$$V_{TH} = V_{oc} = \frac{0,002S}{20 + 0,002S} \cdot \frac{480}{S} = \frac{480}{S + 10^4}$$
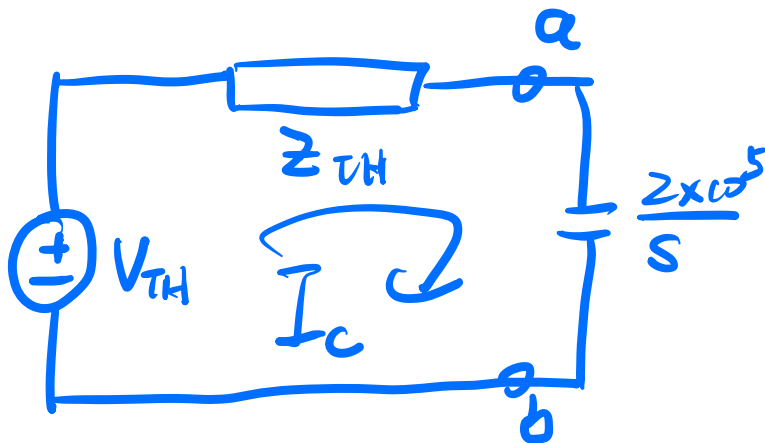
$$Z_{TH} = 60 + (0,002S \parallel 20) = \frac{80(S + 7500)}{S + 10^4}$$



$$I_c(s) = \frac{V_{TH}}{Z_{TH} + Z_C}$$

$$= \frac{6S}{(S + 5000)^2}$$

$$= \frac{A}{S + 5000} + \frac{B}{(S + 5000)^2}$$

$$B = 6S \big|_{S = -5000} = -30000$$



$$A = (6s)' = 6$$

$$I_c(s) = \frac{6}{s+5000} + \frac{-30000}{(s+5000)^2}$$

$\xrightarrow{\mathcal{L}^{-1}}$

$$i_c(t) = \left( 6 \cdot e^{-5000t} - 30000t \cdot e^{-5000t} \right) u(t) \quad A$$

$t > 0$


## Example 4

- Find  $v_o(t)$  for  $t > 0$



initial condition

$$V_C(0) = 0$$
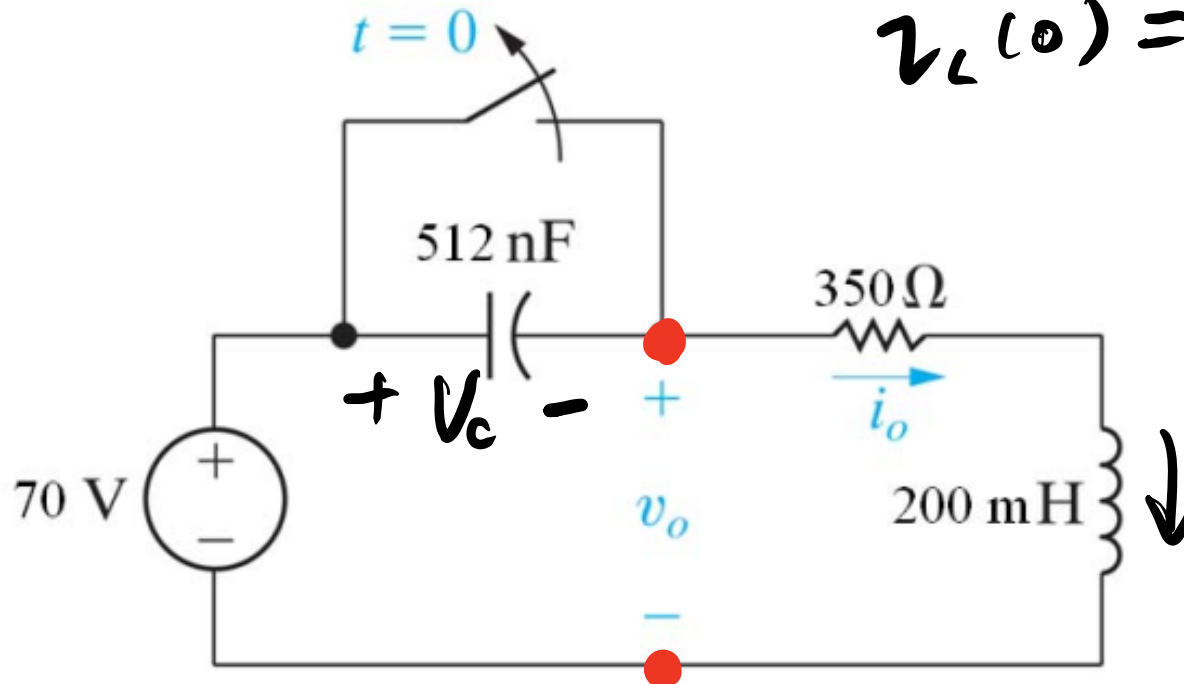
$$i_L(0) = \frac{70}{350} = 0.2 \text{ A}$$



$t > 0$ . S.D.  $\downarrow$

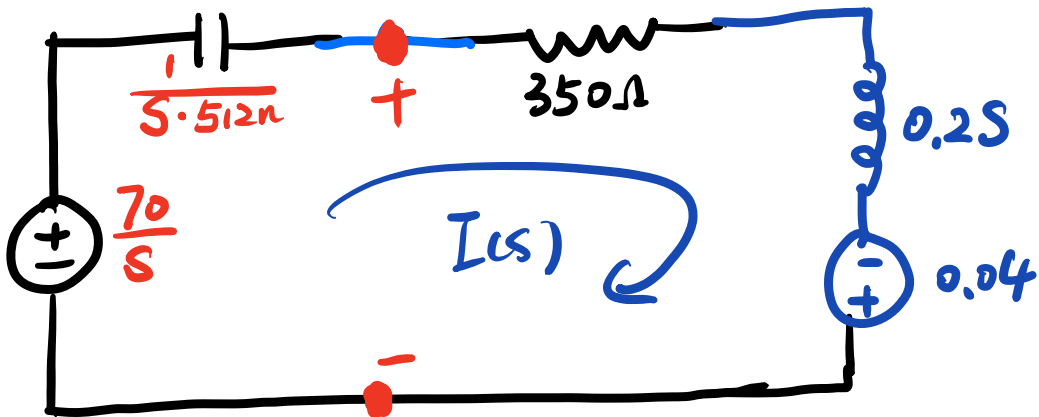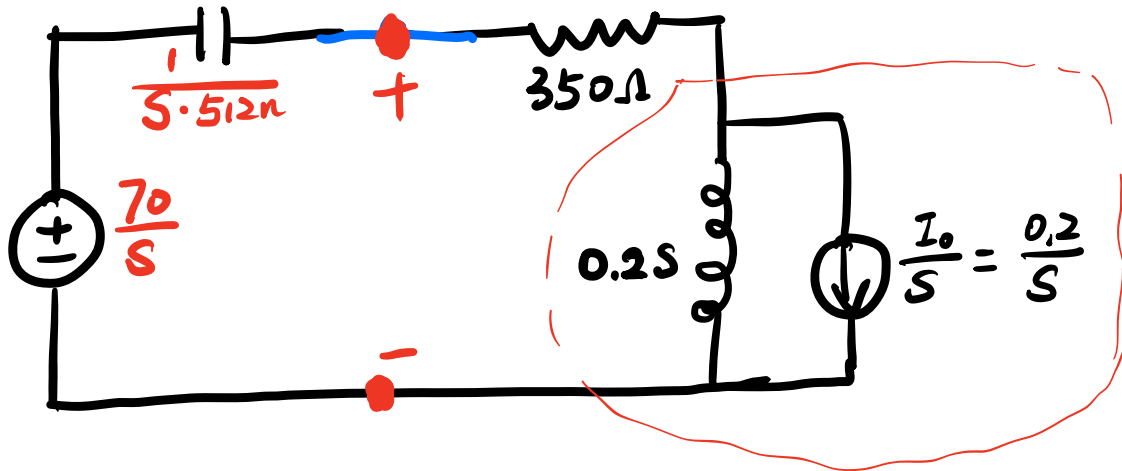

$$I(s) = \frac{\frac{70}{s} + 0.04}{\frac{1}{5.512n} + 350 + 0.2S}$$

$$V(s) = I(s) \cdot (350 + 0.2S) - 0.04$$



$$s_{1,2} = -875 \pm 3000j$$

$$= \frac{k_1}{s - (-875 + 3000j)} + \frac{k_2}{s - (-875 - 3000j)}$$

$\alpha = -875$   
 $\omega = 3000$

↓

$$V_0(s) = \frac{70s - 268,125}{s^2 + 1750s + 9,765,625} = \frac{K_1}{(s + 875 - j3000)} + \frac{K_2}{(s + 875 + j3000)}$$

$$K_1 = \left. \frac{70s - 268,125}{(s + 875 + j3000)} \right|_{s=-875+j3000} = \frac{70(-875 + j3000) - 268,125}{[(-875 + j3000) + 875 + j3000]} = 65.1 \angle 57.48^\circ$$

$|k_1|$   $\varphi_k$

$$K_2 = \left. \frac{70s - 268,125}{(s + 875 - j3000)} \right|_{s=-875-j3000} = \frac{70(-875 - j3000) - 268,125}{[(-875 - j3000) + 875 - j3000]} = 65.1 \angle -57.48^\circ$$

$$V_0(s) = \frac{65.1 \angle 57.48^\circ}{(s + 875 - j3000)} + \frac{65.1 \angle -57.48^\circ}{(s + 875 + j3000)}$$


$$v_0(t) = 2(65.1)e^{-875t} \cos(3000t + 57.48^\circ) = \underline{130.2e^{-875t} \cos(3000t + 57.48^\circ)u(t)} \text{ V}$$


## Example 5

- Example---Find  $i_x$  (S.S.) assuming no initial energy stored

Using (1) phasor method

(2) Laplace transform method

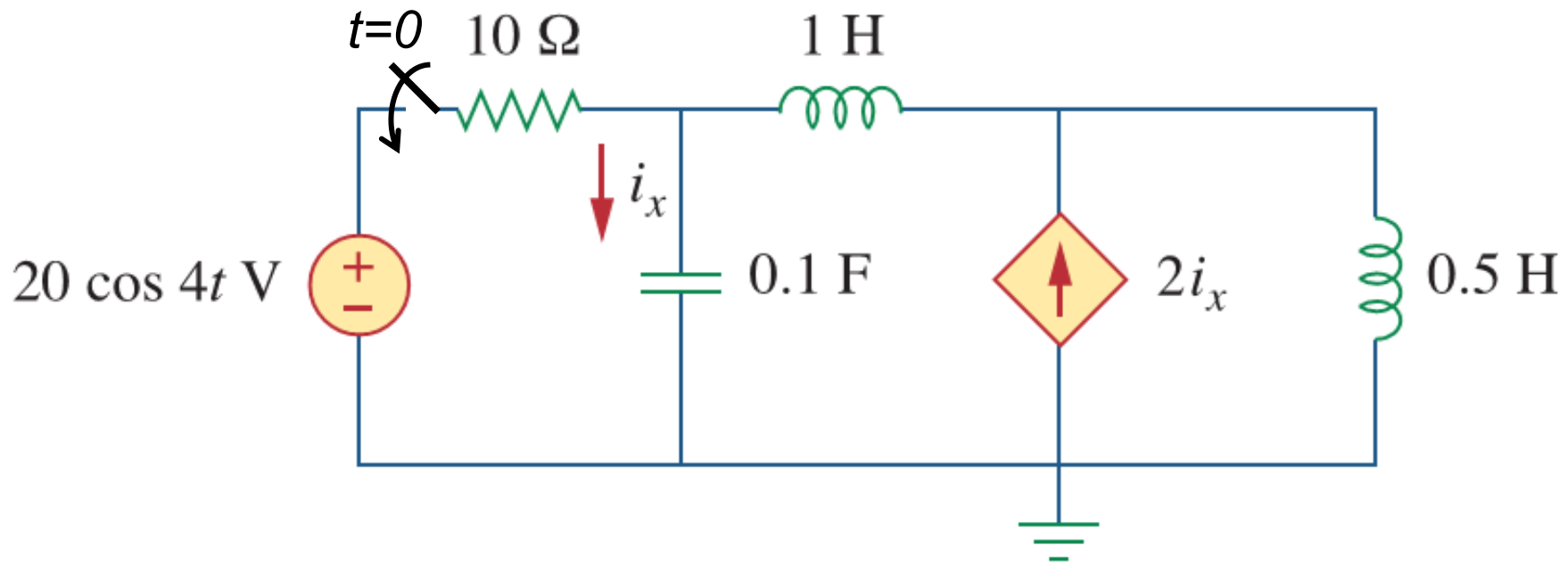


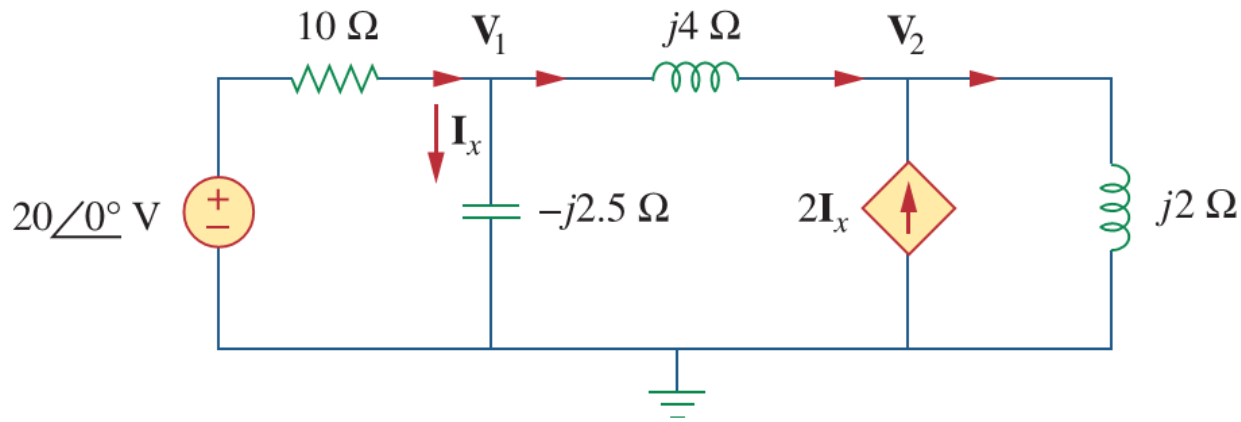

$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$\dot{I}_x = \frac{\dot{V}_1}{-2.5j}$$

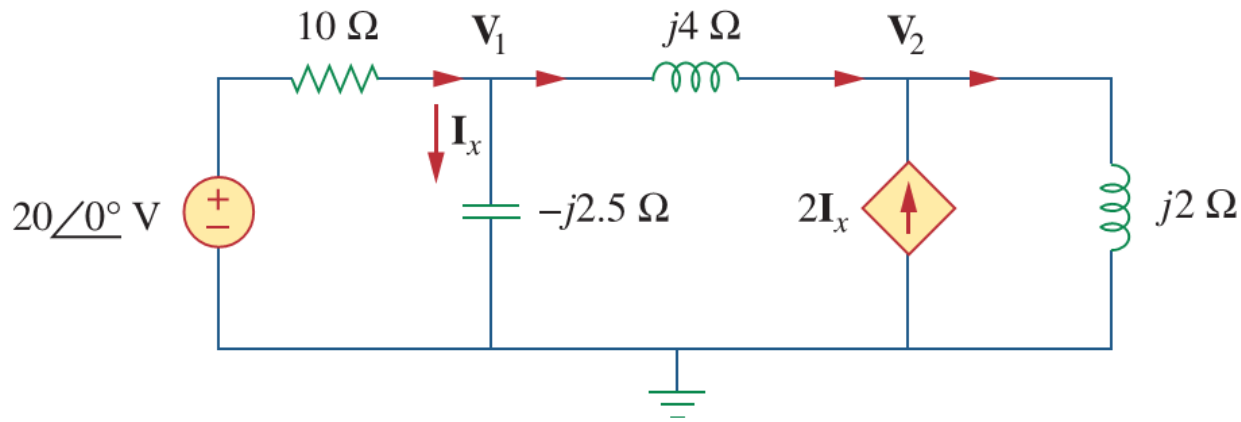


$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$


$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$\dot{I}_x = \frac{\dot{V}_1}{-2.5j}$$
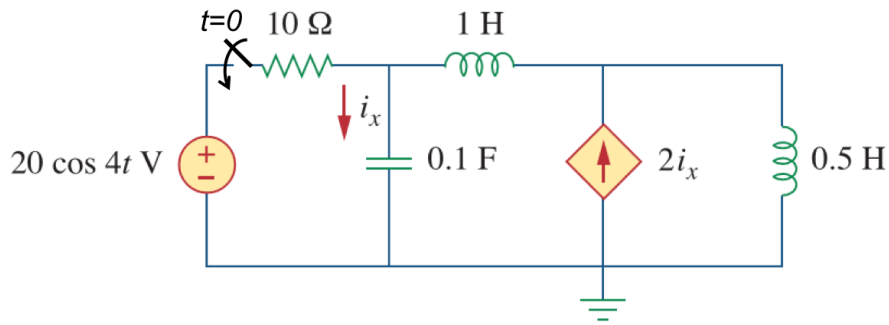
$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$



S.D.

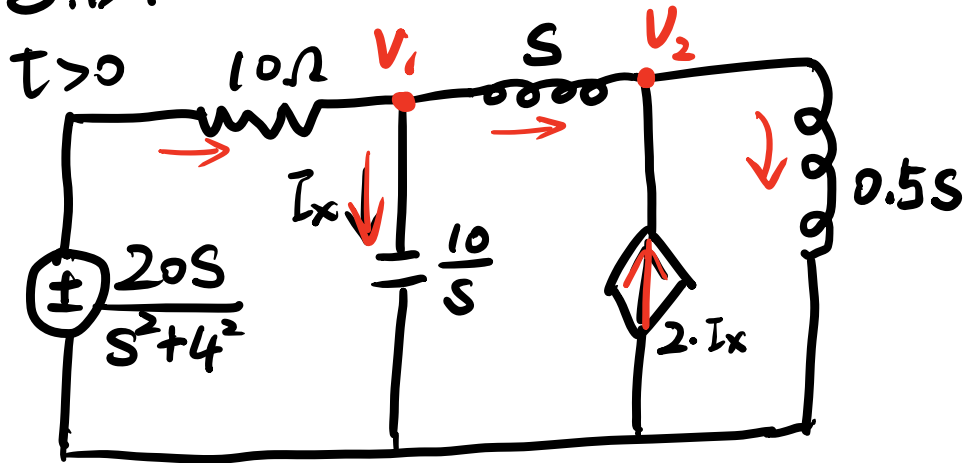

$$\frac{\frac{20S}{S^2+4^2} - V_1}{10} = \frac{V_1}{\frac{10}{S}} + \frac{V_1 - V_2}{S}$$

$$\frac{V_1 - V_2}{S} + 2I_x = \frac{V_2}{0.5S}$$

$$I_x = \frac{V_1}{\frac{10}{S}}$$



$$\tilde{I}_x(s) = \frac{6s^3}{(s^2+4^2)(s^2+3s+20)}$$

$$s_{1,2} = 0 \pm 4j$$

$$s_{3,4} = -1.5 \pm 4.2j$$



$$\tilde{I}_x(s) = \frac{k_1}{s-4j} + \frac{k_1^*}{s-(-4j)}$$

$$+ \frac{k_2}{s-(-1.5+4.2j)} + \frac{k_2^*}{s-(-1.5-4.2j)}$$

$$k_1 = 3.79 \angle 108.43^\circ, \quad k_2 = 5.0 \angle -146.2^\circ$$

$$\mathcal{L}^{-1} \tilde{v}_x(t) = 2|k_1|e^{\alpha_1 t} \cos(\omega_1 t + \varphi_{k_1}) \\ + 2|k_2|e^{\alpha_2 t} \cos(\omega_2 t + \varphi_{k_2})$$

$$\alpha_1 \pm j\omega_1 = 0 \pm 4j$$

$$\underline{\alpha_1 = 0.} \quad \underline{\omega_1 = 4}$$

$$\alpha_2 \pm j\omega_2 = -1.5 \pm 4.2j$$

$$\alpha_2 = -1.5 \quad \omega_2 = 4.2j$$

$$\begin{aligned} \hat{v}_x(t) = & 2|k_1|e^{\alpha_1 t} \cos(\omega_1 t + \varphi_{k_1}) \\ & + 2|k_2|e^{\alpha_2 t} \cos(\omega_2 t + \varphi_{k_2}) \end{aligned}$$

$$= \left[ \overset{\text{S.S.}}{7.58 e^{0t} \cos(4t + 108.43^\circ)} + \right. \\ \left. 10 e^{-1.5t} \cos(4.2t - 146.2^\circ) \right] u(t) \quad \text{A.}$$

T.S. ↑

$$\hat{v}_x(\text{S.S.}) = 7.58 \cos(4t + 108.43^\circ) \quad \text{A}$$

tso



## Example 6

- There is no initial energy stored in this circuit. Find  $i(t)$  if
- $v(t) = e^{-0.6t} \sin 0.8t$  V.

