




Lecture 12

- Transformers/Three-Phase Circuits



Outline

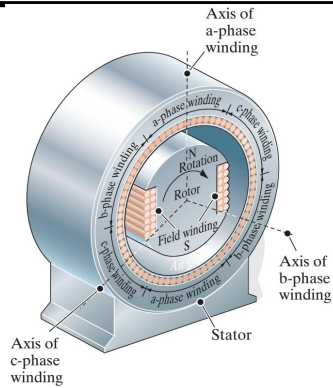- Balanced Three-Phase System (Wye - Wye)
 - Balanced sources
 - Balanced loads
- Circuit analysis (Wye - Wye)
 - Phase voltage/current
 - Line voltage/current




Generating Station
11, 11.5, 12 or 13kV



Step-Up Transformer
(Power Transformer)


220 or
500 kV

Primary Transmission

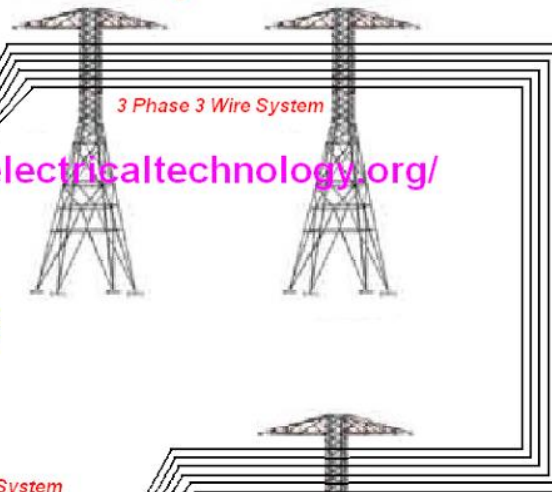


<http://electricaltechnology.org/>

Secondary Transmission

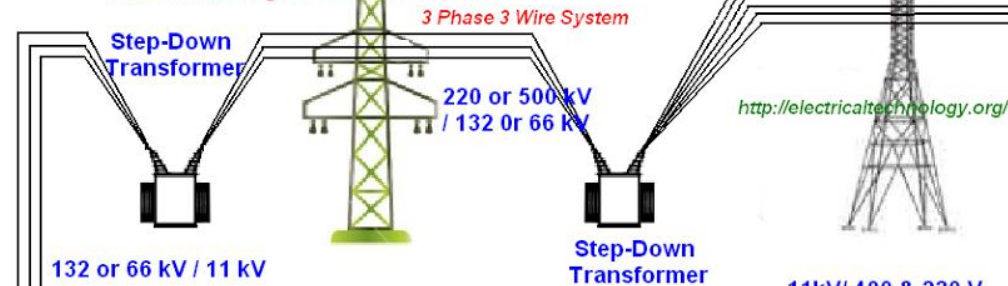

<http://electricaltechnology.org/>

Primary Distribution

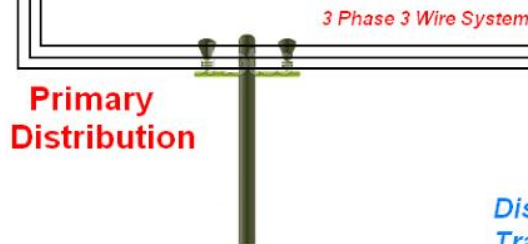

Distribution Transformer

11kV/ 400 & 230 V
3 Phase 4 Wire System


Secondary Distribution

<http://electricaltechnology.org/>

Design By:
Engr Wasim Khan



Copyright Material @ <http://electricaltechnology.org/>

Residential Consumers

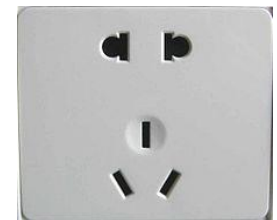




Single Phase vs. Polyphase

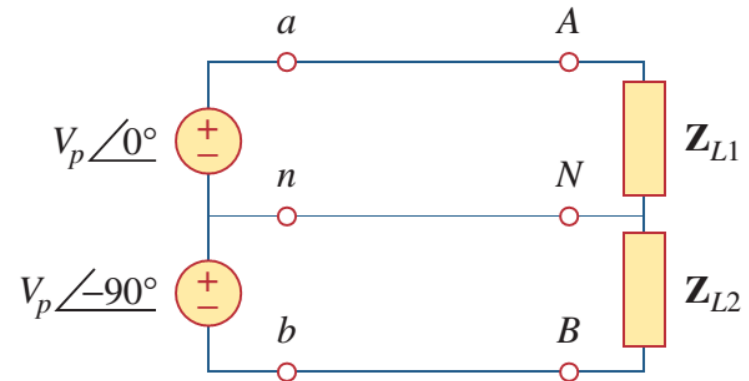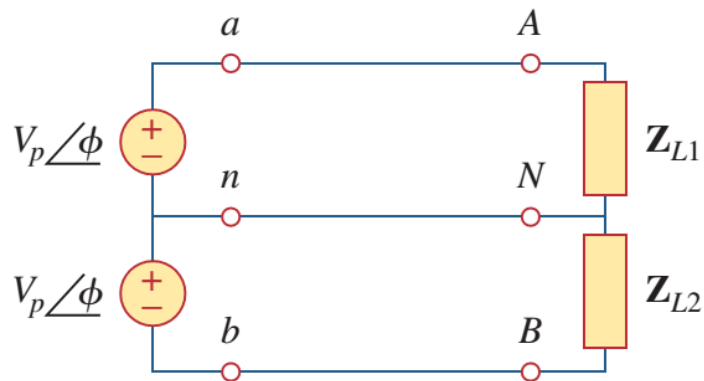- Households have single-phase power supply
 - This typically in a three wire form
- Circuits that operate at the same frequency but with multiple sources at different phases are called polyphase.




Balanced Three-Phase Sources

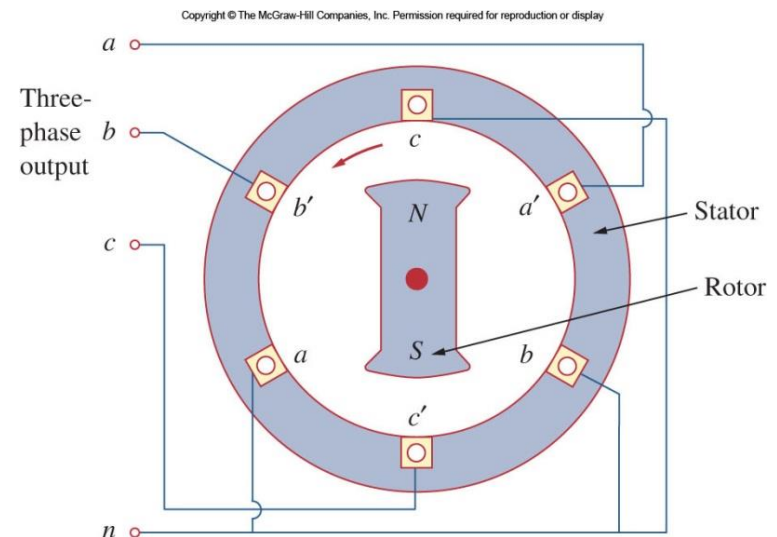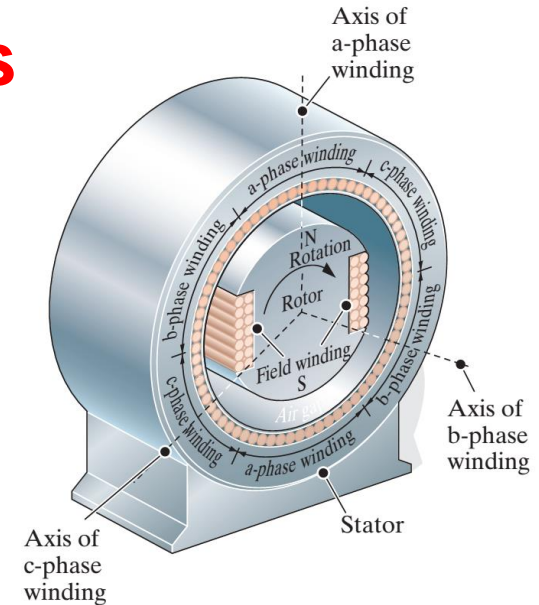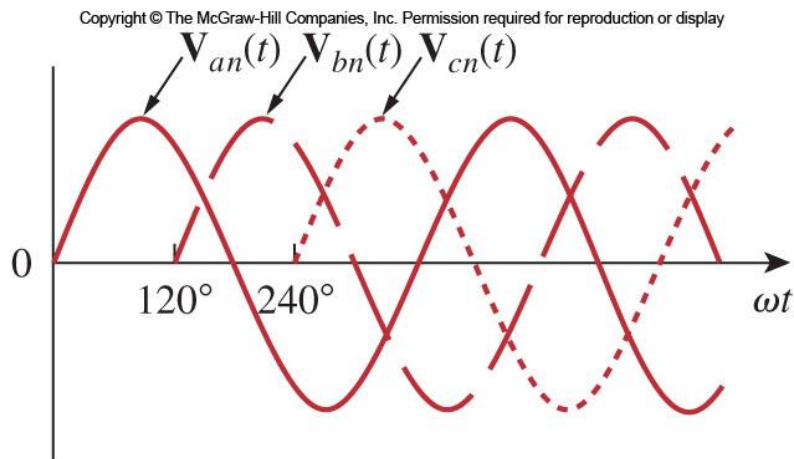- Three phase voltages are typically produced by a three-phase AC generator.
- The output voltages look like below.




Connecting the Sources

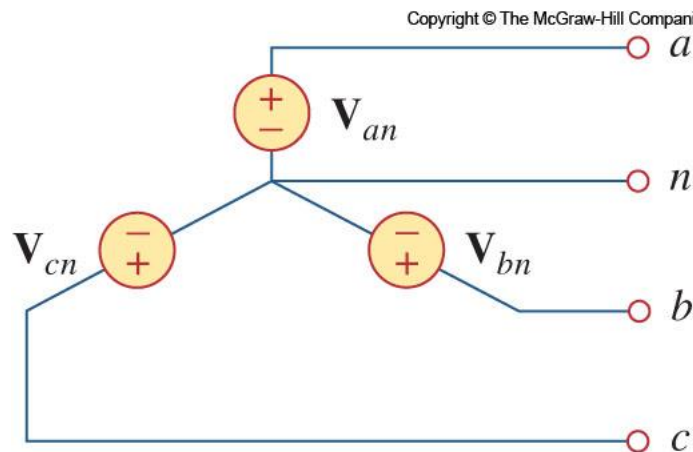- Three phase voltage sources can be connected the loads by either three or four wire configurations.
 - Three-wire configuration accomplished by Delta connected source.
 - Four-wire system accomplished using a Y connected source.



(a)

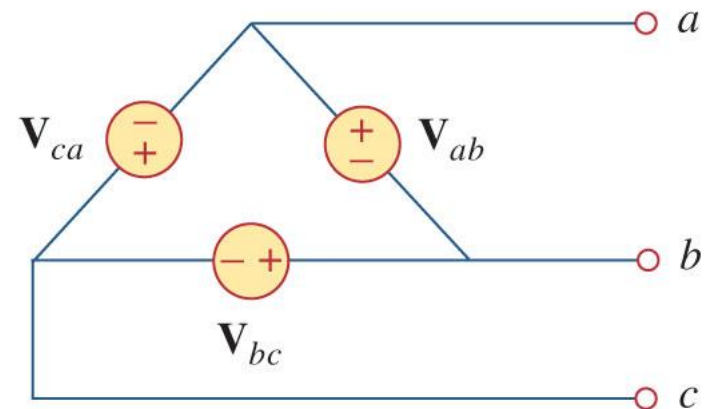


(b)

Balanced Sources

- A wye connected source is said to be balanced when

$$V_{an} + V_{bn} + V_{cn} = 0$$


- Two sequences for the phases:

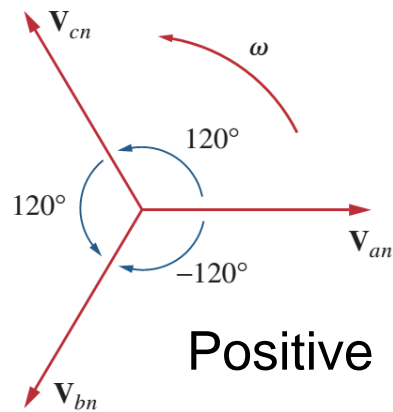

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

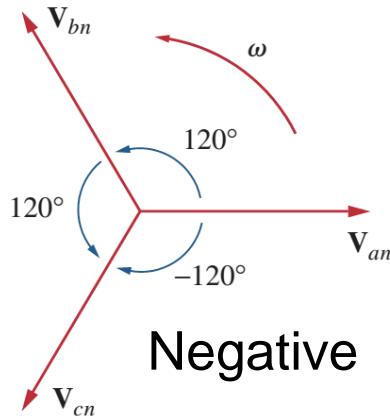
$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$



$$V_{an} = V_p \angle 0^\circ$$

$$V_{cn} = V_p \angle -120^\circ$$


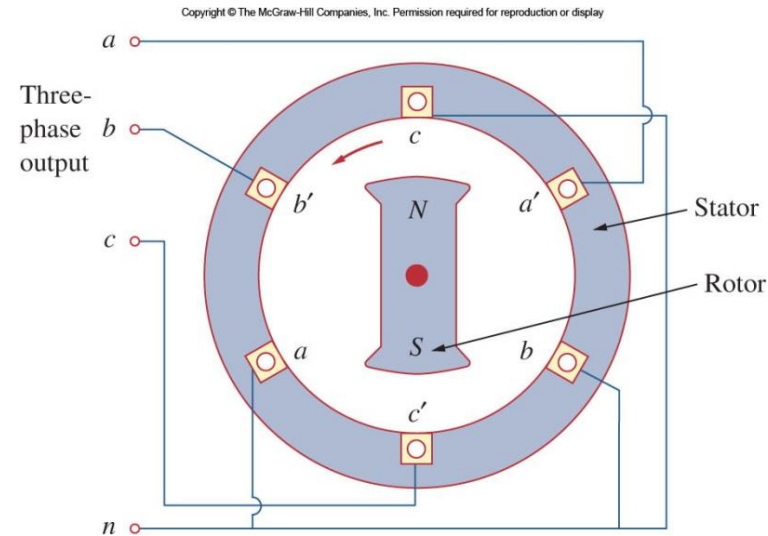
$$V_{bn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$



$$|V_{an}| = |V_{bn}| = |V_{cn}|$$

Balanced Loads

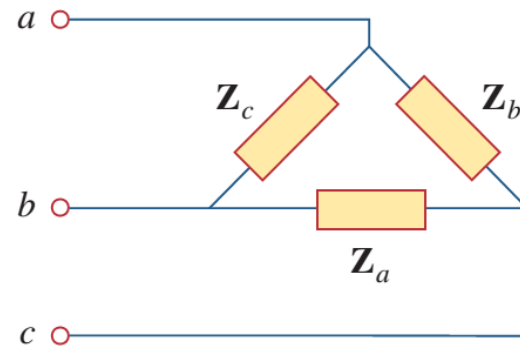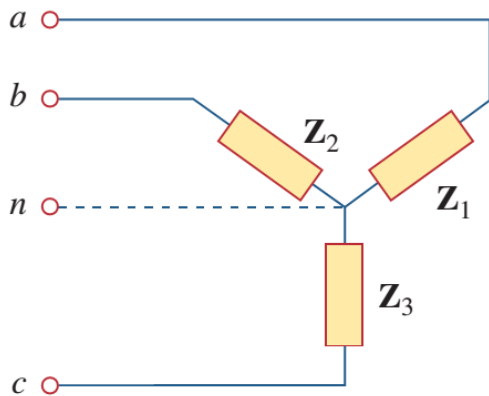- Similar to the source, a balanced load is one that has the same impedance presented to all three voltage sources.
- They may also be connected in either Delta or wye
 - For a balanced wye connected load: $Z_1 = Z_2 = Z_3 = Z_Y$
 - For a balanced delta connected load: $Z_a = Z_b = Z_c = Z_\Delta$



- The load impedance per phase for the two load configurations can be interchanged.




Outline

- Balanced Three-Phase System (Wye - Wye)
 - Balanced sources
 - Balanced loads
- Circuit analysis (Wye - Wye)
 - Phase voltage/current
 - Line voltage/current



Source-Load configurations

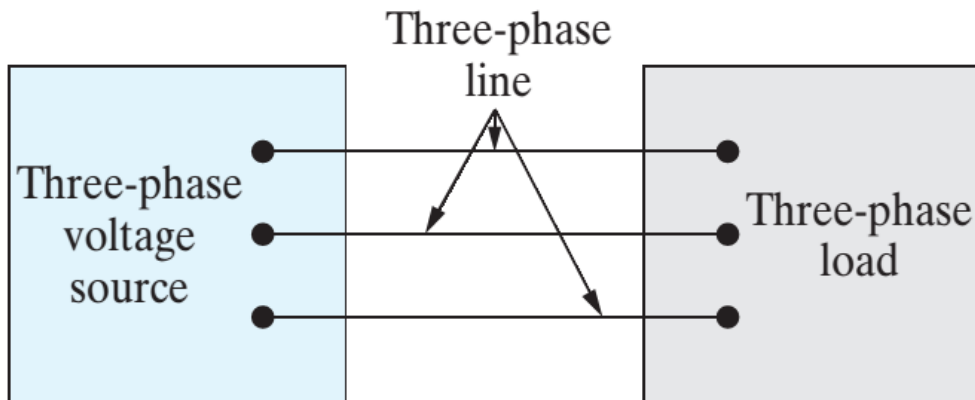


Source	Load
Y	Y
Y	Δ
Δ	Y
Δ	Δ



Source-Load Configurations

Y-Y

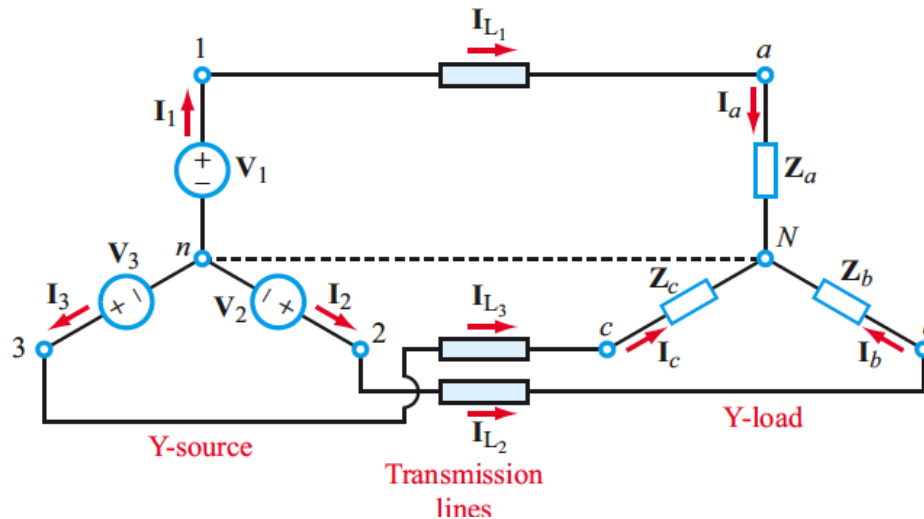


Load Phase Currents

I_a, I_b, I_c
(same as line currents
 $I_{L1}, I_{L2}, \text{ and } I_{L3}$)

Load Phase Voltages

V_{aN}, V_{bN}, V_{cN}

Y-Delta

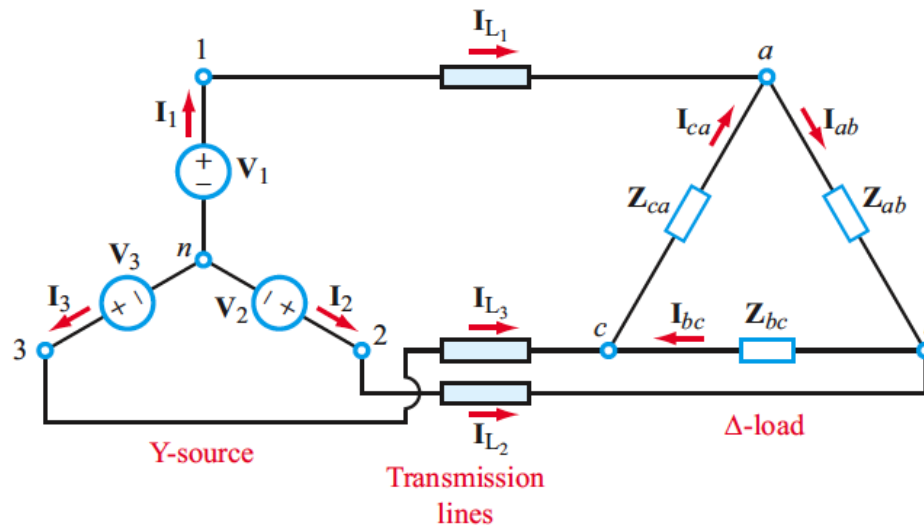

Load Phase Currents

I_{ab}, I_{bc}, I_{ca}


Load Phase Voltages

V_{ab}, V_{bc}, V_{ca}



Source-Load Configurations

Delta-Y

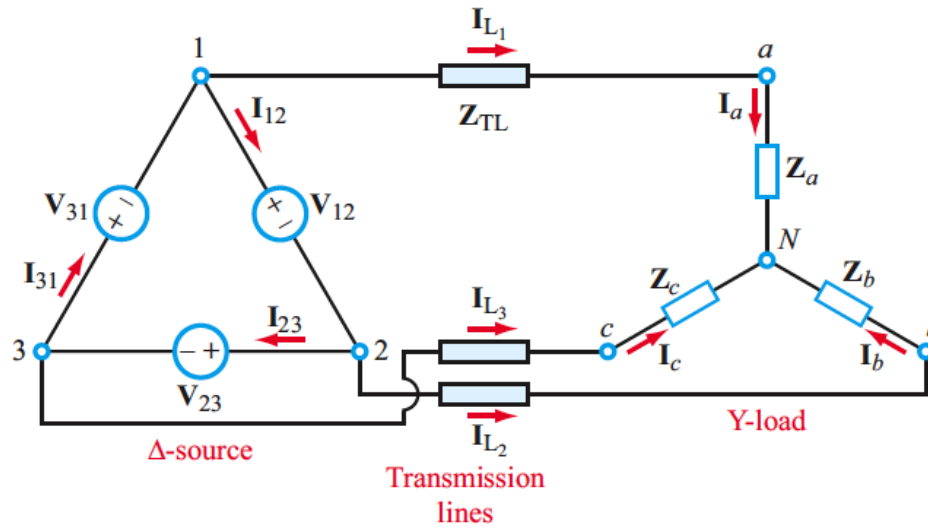


Load Phase Currents

I_a, I_b, I_c
(same as line currents
 $I_{L1}, I_{L2},$ and I_{L3})

Load Phase Voltages

V_{aN}, V_{bN}, V_{cN}

Delta-Delta

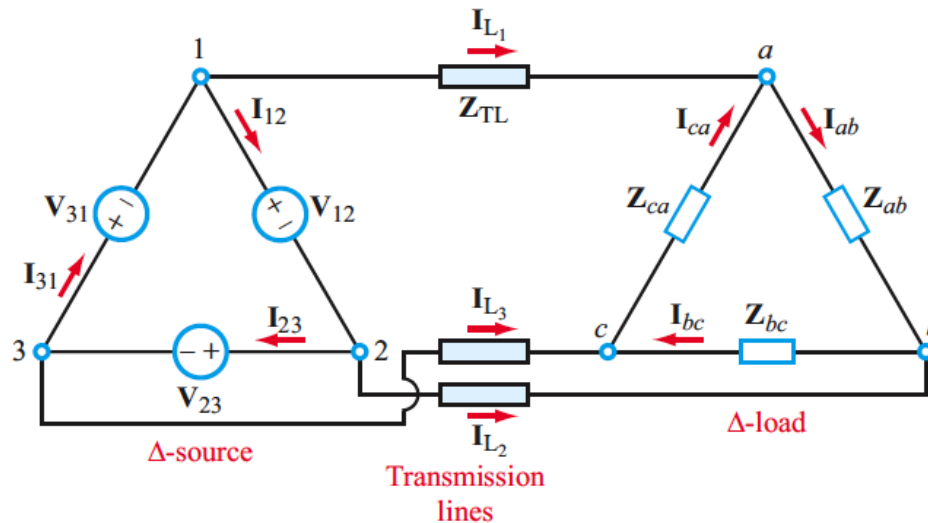

Load Phase Currents

I_{ab}, I_{bc}, I_{ca}

Load Phase Voltages


V_{ab}, V_{bc}, V_{ca}
(same as source voltages
if Z_{TL} is negligible)

Balanced Y-Y connection

- Any three-phase system can be reduced to an equivalent Y-Y system.
- The load impedances Z_y will be assumed to be balanced.
 - This can be the source Z_s , line Z_l and load Z_L together.

$$Z_Y = Z_s + Z_\ell + Z_L$$

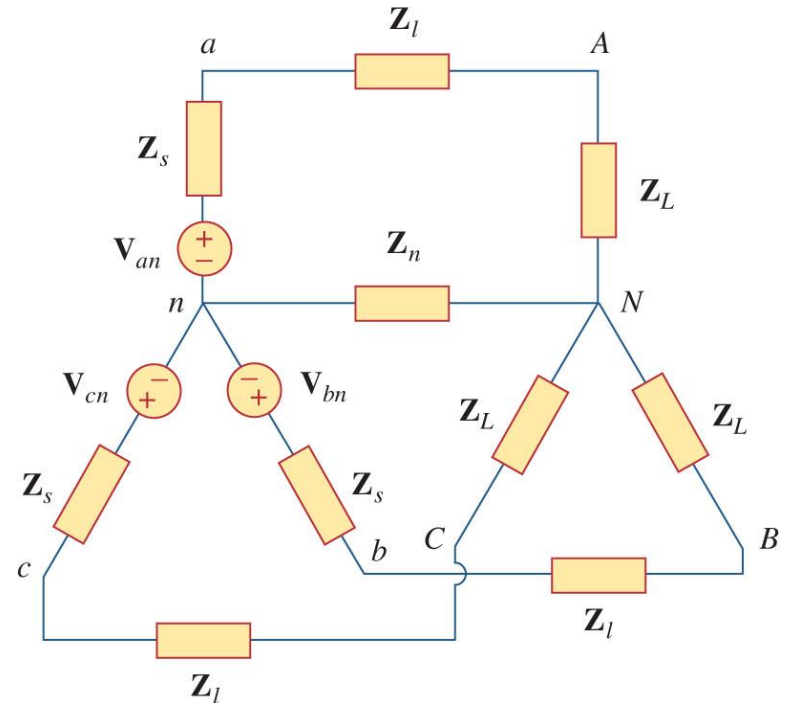Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




Line-to-Line Voltage

- Use the positive sequence:


$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ \quad V_{cn} = V_p \angle +120^\circ$$

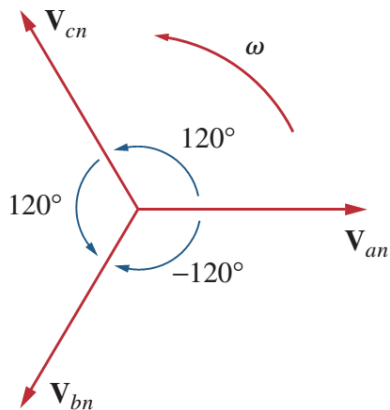The line to line (or line in short) voltages:



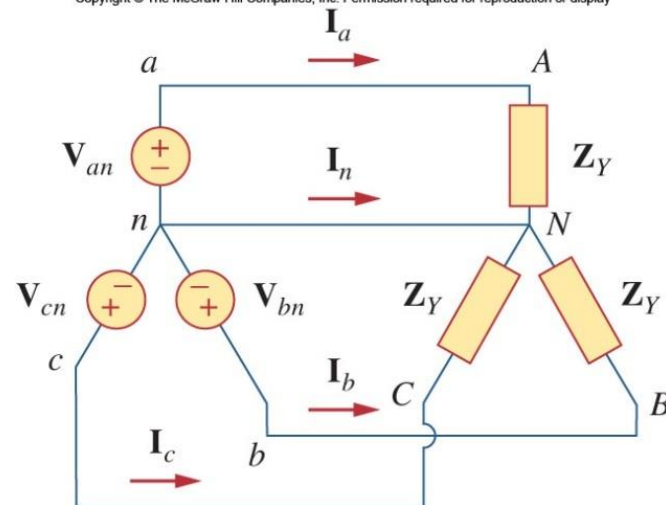
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






Line Currents

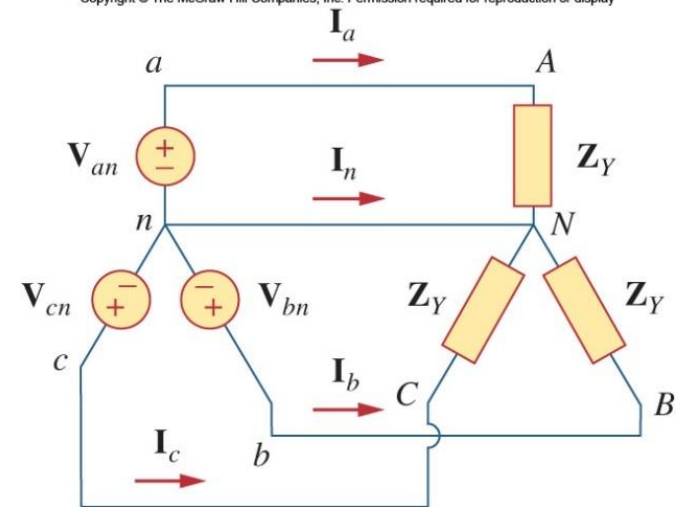Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Example

- Calculate the line currents.




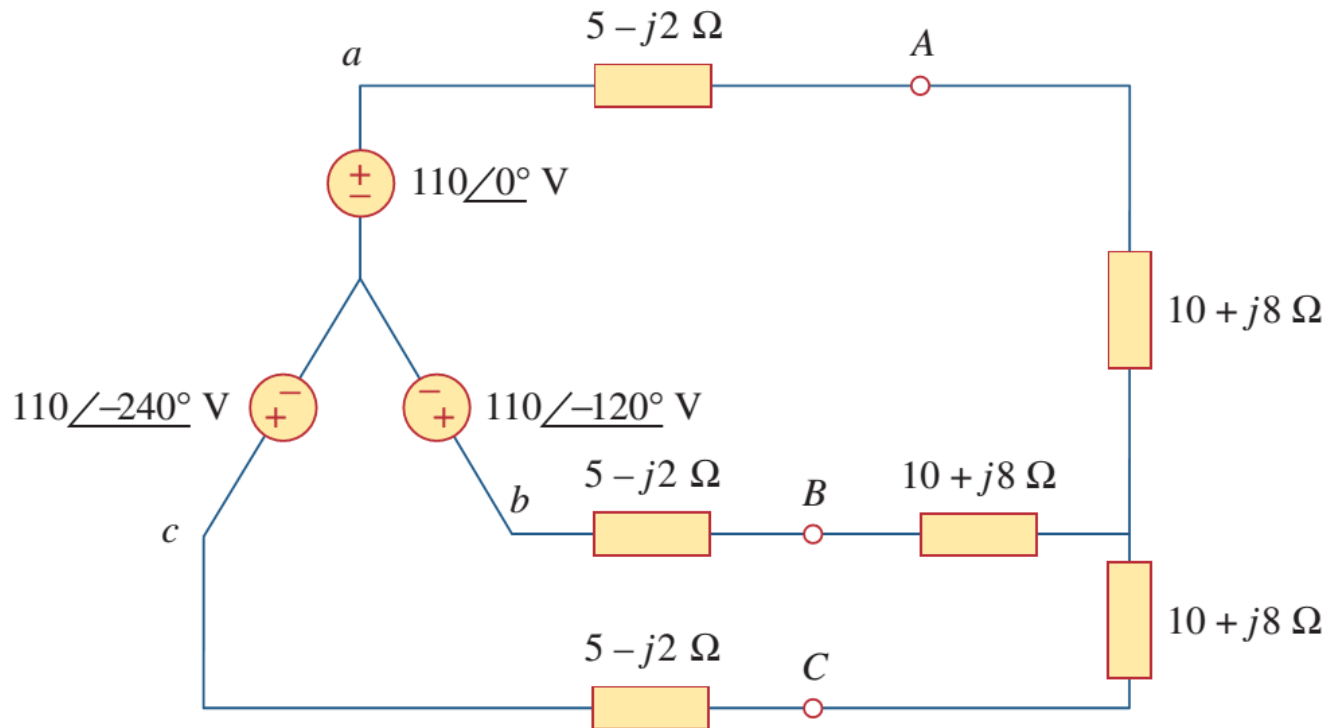




Y-Y	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ <p>Same as line currents</p>	$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{V}_{an} / \mathbf{Z}_Y$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Y-Δ	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{AB} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{BC} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{CA} / \mathbf{Z}_\Delta$	$\mathbf{V}_{ab} = \mathbf{V}_{AB} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{BC} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{CA} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ-Δ	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{ab} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{bc} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{ca} / \mathbf{Z}_\Delta$	<p>Same as phase voltages</p> $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ-Y	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ <p>Same as line currents</p>	<p>Same as phase voltages</p> $\mathbf{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3}\mathbf{Z}_Y}$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$



Y and Δ , Which One Better?

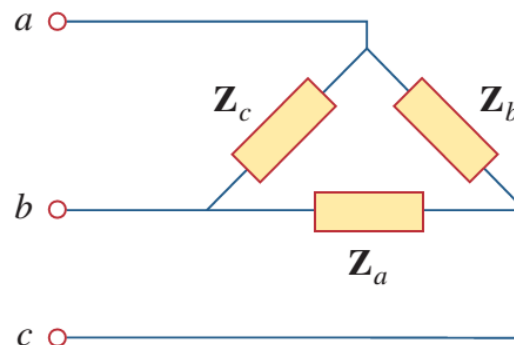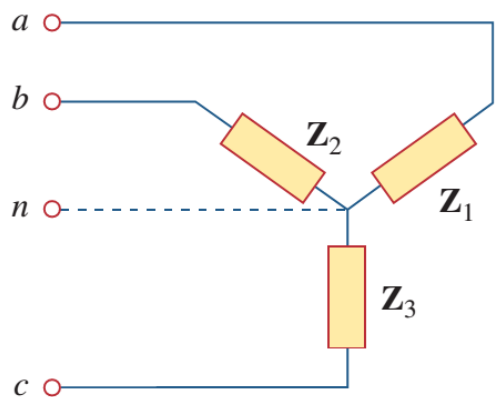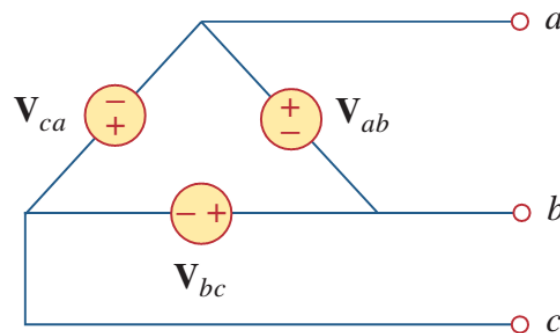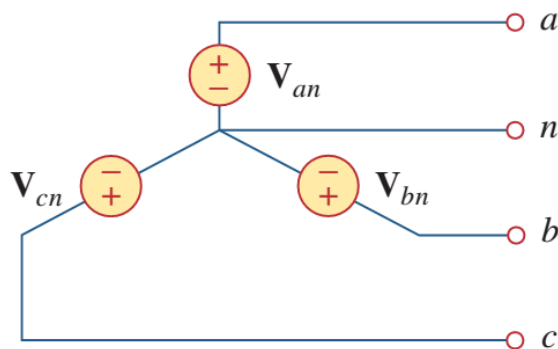

<http://www.allaboutcircuits.com/textbook/alternating-current/chpt-10/three-phase-y-delta-configurations/>