

Homework 3

Due date: 25th, Oct.


Turn in your homework in class

Rules:

- Work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism.
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.


15'

1. (a). A capacitor with 10mF capacitance has the terminal voltage:

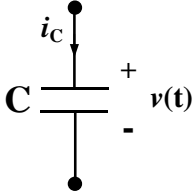
$$v(t) = \begin{cases} 15 \text{ V} & t \leq 0 \\ Ae^{-100t} + Be^{-500t} \text{ V} & t \geq 0 \end{cases}$$


Assuming that the initial current ($t=0s$) on the capacitor is 5 A, please find: (1). constants A and B , (2). the capacitor current for $t > 0$, and (3). the energy of capacitor at $t=1ms$.

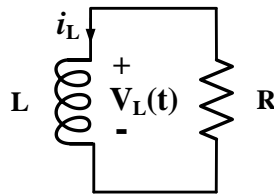- (b). A 200-mH inductor is connected in parallel with a resistor. The current through the inductor is $i_L(t) = 10e^{-800t} \text{ mA}$. Please find the voltage $V_L(t)$ on the inductor with respect to time, as well as the energy of the inductor at $t = 1ms$.



- (c). For the capacitance circuit below, $C_1 = 1 \mu\text{F}$, $C_2 = 0.125 \mu\text{F}$, $C_3 = C_4 = 0.25 \mu\text{F}$. Initially the switch is at “off state”, and the voltage on the capacitor C_1 is 10 V while other capacitors have the same voltage drop of 0 V. At $t=0s$, the switch is closed. Please find the voltage V_2 after the circuit becomes stable. Note that no loss need to be considered.

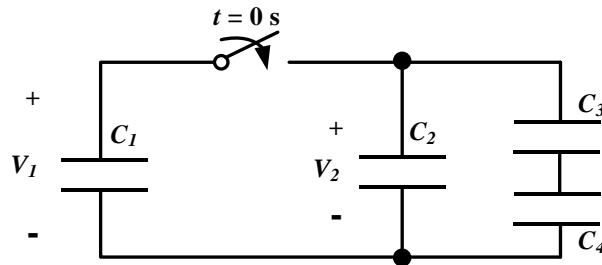

1. (a) 1) $\therefore V(0^+) = V(0^-)$

$\therefore A + B = 15$ ①

4 $\therefore i_C(t) = C \frac{dV(t)}{dt} = 0.01(-100Ae^{-100t} - 500Be^{-500t})$

$\therefore i_C(0) = -A - 5B = 5$ ②

① ② $\Rightarrow A = 20$

$B = -5$

2 (2) $i_C(t) = C \frac{dV}{dt} = -20e^{-100t} + 25e^{-500t}$ A

2 (3) $V(1\text{ms}) = 20e^{-0.1} - 5e^{-0.5} = 15.064$ V

$E = \frac{1}{2} CV^2 = \frac{1}{2} \times 0.01 \times 15.064^2 = 1.135$ J

(b) $V_L(t) = L \frac{di_L(t)}{dt} = 0.2 \times (-800) \times 10e^{-800t} \times 10^{-3} = -1.6e^{-800t}$ V

3 $i_L(1\text{ms}) = 10e^{-0.8} = 4.493$ mA

$E = \frac{1}{2} L i^2 = \frac{1}{2} \times 0.2 \times (4.493 \times 10^{-3})^2 = 2.019 \times 10^{-6}$ J


(c) $C_{2+3+4} = (C_3 \parallel C_4) + C_2 = 0.125 + 0.125 = 0.25$ μF

4 $\therefore Q = C_1 V_1 = C_1 V_1' + C_{2+3+4} V_2$

$V_1' = V_2$

$\Rightarrow V_2 = 8$ V

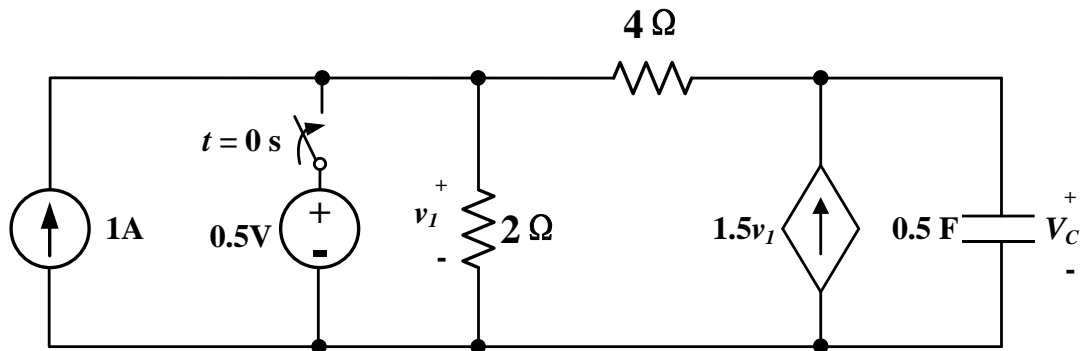2. In the following circuit, the switch is open for a long time for $t < 0$ s. At $t = 0$ s, the switch closes immediately. Please find out the voltage on 0.5 F capacitor ($V_C(t)$) when $t \geq 0$ s.



$$t < 0 \quad \frac{u_I}{2} - 1.5u_I = 1$$

$$u_I = -1 \text{ V}$$

$$u_C(0^-) = 4 \times 1.5u_I + u_I = -7 \text{ V}$$

$$t \rightarrow \infty \quad u_{oc} = 1.5u_I \times 4 + u_I = 7u_I$$

$$\text{and } u_I = 0.5 \text{ V}$$

$$\Rightarrow u_{oc} = 3.5 \text{ V}$$

$$\Rightarrow R_{eq} = 4 \Omega$$


$$\tau = R_{eq} C = 4 \times 0.5 = 2 \text{ s}$$

$$u_C(t) = u_C(\infty) + [u_C(0^-) - u_C(\infty)] e^{-t/\tau}$$


$$= 3.5 - 10.5 e^{-0.5t} \text{ V}$$

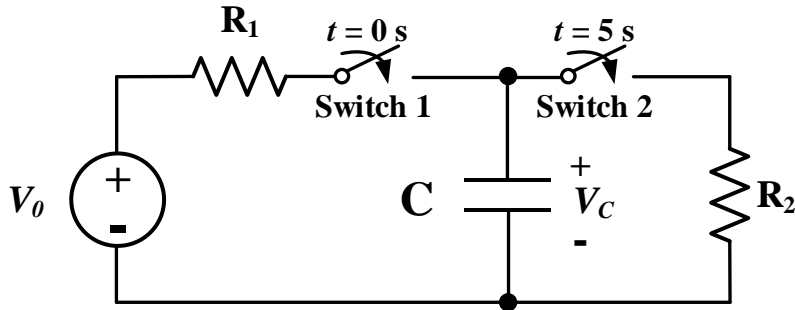3. The circuit contains two switches, both of which have been open for a long time before $t = 0$. **Switch 1** closes at $t = 0$ s, and **switch 2** closes at $t = 5$ s. Determine $V_C(t)$ for $t \geq 0$, given that $V_0 = 24$ V, $R_1 = R_2 = 16$ k Ω , and $C = 250$ μ F. Assume $V_C(0) = 1$ V.


Also, please sketch $V_C(t)$, capacitor current $I_C(t)$, current on R_1 ($I_{R1}(t)$), and voltage on R_1 ($V_{R1}(t)$) for $t > 0$ s, respectively.




$0 \leq t \leq 5$

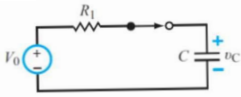

$t \geq 5$

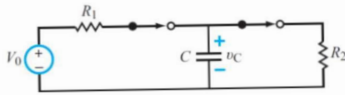

$t = \infty$

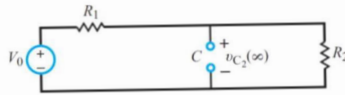

$0 \leq t \leq 5$

$$\tau_1 = R_1 C = 16 \times 10^3 \times 250 \times 10^{-6} = 4 \text{ s}$$

$$V_{C1}(t) = V_{C1}(\infty) + (V_{C1}(0) - V_{C1}(\infty)) e^{-t/\tau_1}$$

$$= V_0 + (1 - V_0) e^{-0.25t}$$

$$= 24 - 23 e^{-0.25t} \text{ V}$$

$t \geq 5$

$$\tau_2 = \frac{R_1 R_2}{R_1 + R_2} C = 8 \times 10^3 \times 250 \times 10^{-6} = 2 \text{ s}$$

$$V_{C2}(\infty) = \frac{V_0 R_2}{R_1 + R_2} = 12 \text{ V}$$

$$V_{C2}(5\text{s}) = V_{C1}(5\text{s}) = 24 - 23 e^{-1.25} = 17.41 \text{ V}$$

$$V_{C2}(t) = V_{C2}(\infty) + (V_{C2}(5\text{s}) - V_{C2}(\infty)) e^{-\frac{t-5}{\tau_2}}$$


$$= 12 + 5.41 e^{-0.5(t-5)} \text{ V}$$

$$i_C(t) = C \frac{dV_C(t)}{dt} = \begin{cases} \frac{23}{16} e^{-0.25t} \text{ mA} = 1.4375 e^{-0.25t} \text{ mA} \\ -0.676 e^{-0.5(t-5)} \text{ mA} \end{cases}$$

$$I_{R1}(t) = \frac{V_0 - V_C}{R_1} = \begin{cases} \frac{23}{16} e^{-0.25t} \text{ mA} \\ \frac{12 - 5.41 e^{-0.5(t-5)}}{16} \text{ mA} = 0.75 - 0.338 e^{-0.5(t-5)} \text{ mA} \end{cases}$$

$$V_{R1}(t) = V_0 - V_C = \begin{cases} 23 e^{-0.25t} \text{ V} \\ 12 - 5.41 e^{-0.5(t-5)} \text{ V} \end{cases}$$

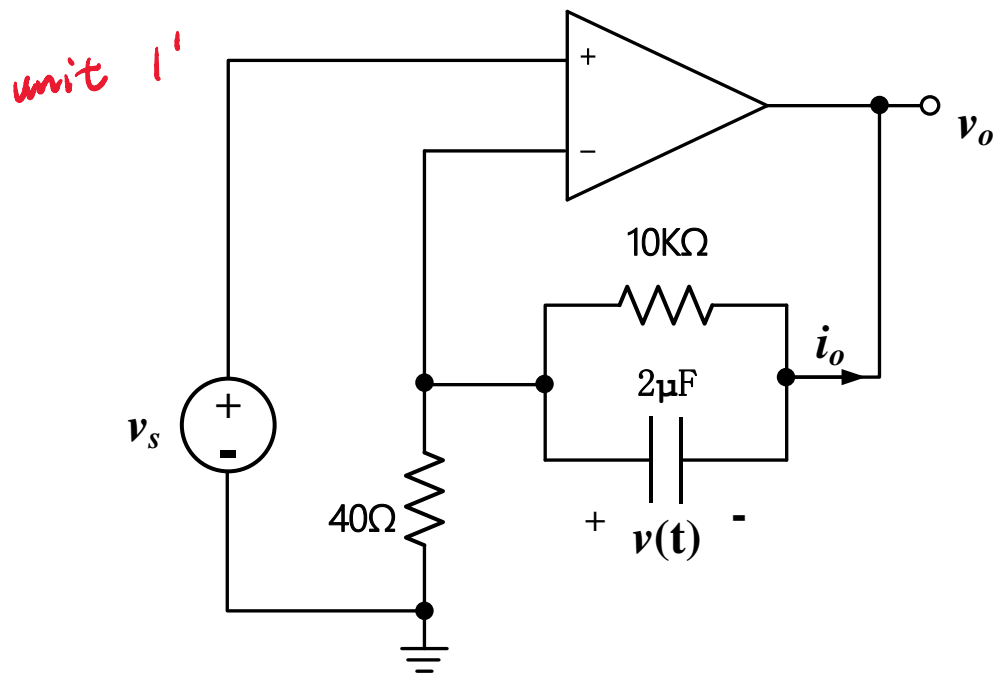10 4. In the circuit below, find $v_o(t)$ and $i_o(t)$, given that $v_s = 4u(t)$ V and $v(0) = 1$ V. (Note that $u(t)$ is step function.)



Solution: ↵

$t \rightarrow \infty$: ↵

$$\frac{0 - v_{40\Omega}}{40} = \frac{v_{40\Omega} - v_0}{10k} \quad \text{1'}$$

$$v_{40\Omega} = v_s = 4V \quad \text{1'}$$

$$v_0 = 1004V \quad \text{1'}$$

$$v_\infty = v_{40\Omega} - v_0 = -1000V \quad \text{1'}$$

$t \geq 0$: ↵

↵

$$R_{eq} = 10k\Omega \quad \text{1'}$$

$$\tau = R_{eq}C = 0.02s \quad \text{1'}$$

$$v(t) = v(\infty) + (v(0) - v(\infty))e^{-\frac{t}{\tau}} = -1000 + 1001e^{-50t}V \quad \text{2'}$$


$$v_0(t) = v_{40\Omega} - v(t) = 1004 - 1001e^{-50t}V \quad \text{1'}$$

$$i_0(t) = \frac{0 - v_{40\Omega}}{40} = -0.1A \quad \text{1'}$$

12' 5. For the circuit below, the independent voltage source has the voltage:

mit 1'
$$V_s(t) = \begin{cases} 0 \text{ V} & t < 0 \text{ s} \\ e^{-100t} \text{ V} & t \geq 0 \text{ s} \end{cases}$$

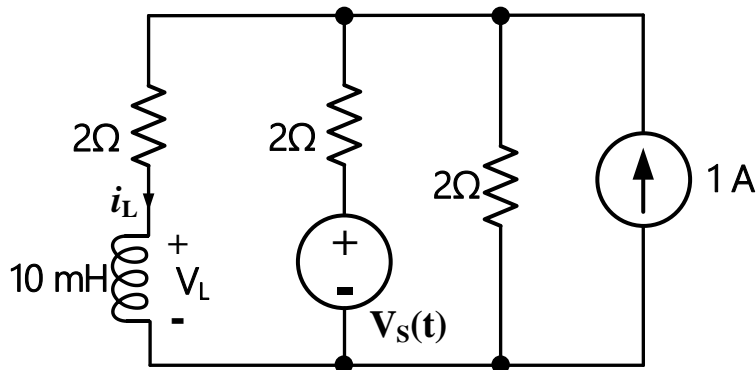Please find the current on the inductor in terms of time ($i_L(t)$) for $t \geq 0 \text{ s}$.



$t < 0 \text{ s}, i_L = \frac{1}{3} \text{ A}$

$\Rightarrow i_L(0^-) = i_L(0^+) = \frac{1}{3} \text{ A}$

$t > 0 \text{ s}$

$$\begin{cases} \frac{V_1}{2} + \frac{V_1 - V_s}{2} + \frac{V_1 - V_L}{2} = 1 \Rightarrow 3V_1 = 2 + V_s + V_L \\ \frac{V_1 - V_L}{2} = i_L \Rightarrow \frac{2 + V_s + V_L}{3} - V_L = 2i_L \\ V_L = L \frac{di_L}{dt} \Rightarrow \frac{2}{3} L \frac{di_L}{dt} + 2i_L = \frac{2}{3} + \frac{V_s}{3} \end{cases}$$

$\Rightarrow \frac{di_L}{dt} + 300 i_L = 100 + 50 e^{-100t}$

$i_L(t) = e^{-300t} \left[\int (100 + 50 e^{-100t}) e^{300t} dt + C \right]$

$= e^{-300t} \left[\frac{1}{3} e^{300t} + \frac{1}{4} e^{200t} + C \right]$

$= \frac{1}{3} + \frac{1}{4} e^{-100t} + C e^{-300t}$

$\therefore i_L(0^+) = \frac{1}{3} + \frac{1}{4} + C = \frac{1}{3}$

$C = -\frac{1}{4}$


$i_L(t) = \frac{1}{3} + \frac{1}{4} e^{-100t} - \frac{1}{4} e^{-300t}$

A.

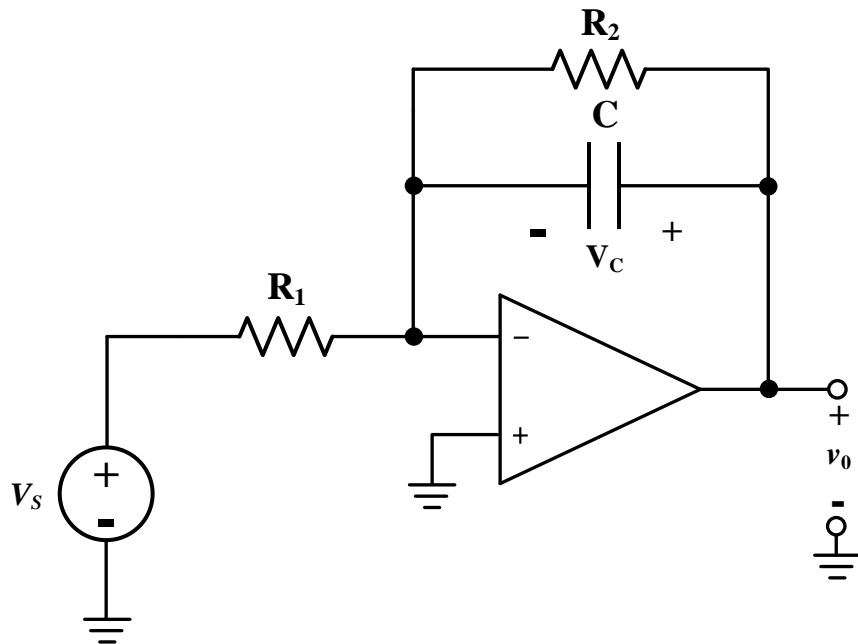6. For the circuit below, assume the operational amplifier is always working in its linear mode, $V_C(0^-) = 5\text{V}$, $R_1 = 5\text{k}\Omega$, $R_2 = 500\Omega$, $C = 5\mu\text{F}$, and

$$V_S(t) = \begin{cases} 0, & t \leq 0 \\ e^{-200t}, & t > 0 \end{cases} \quad (\text{unit for } V_S(t) \text{ is V})$$

Find the output voltage of the operational amplifier $v_0(t)$ for $t > 0$.



$$i_C = C \frac{dv_C}{dt}, \quad V_C = V_0$$

Apply nodal analysis and KCL.

$$\frac{V_S - 0}{R_1} + C \frac{dv_C}{dt} = \frac{0 - V_C}{R_2}$$

$$\frac{e^{-200t}}{5000} + 5 \times 10^{-6} \frac{dv_C}{dt} = -\frac{V_C}{500}$$

$$e^{-200t} + 0.025 \frac{dv_C}{dt} = -10V_C$$

$$\frac{dv_C}{dt} + 400V_C = -40e^{-200t}$$

$$V_C = e^{-400t} \left[\int (40e^{-200t} \cdot e^{400t}) dt + C \right]$$

$$= -\frac{1}{5} e^{-200t} + C e^{-400t}$$

$$V_C(0) = V_C(0^-) = -\frac{1}{5} + C = 5 \text{ V}$$

$$C = 5.2$$

$$V_0 = V_C = 5.2 e^{-400t} - 0.2 e^{-200t} \text{ V}$$