

ShanghaiTech University

EE 115B: Digital Circuits

Fall 2022

Lab 3: Universal Shift Register

Total: 100 Points

Assigned: December 6, 2022. Due: December 18, 2022.

In this lab, you will design a 4-bit universal shift register that implements four operation modes: no change (i.e., hold), right shift, left shift, and parallel load. The block diagram of the register is shown as follows:

 


Figure 1: Block diagram of universal shift register.

The signals are defined as follows:

M(1:0)	Mode selection signal
Serial_in	Serial input
P(3:0)	Parallel input
Clock	Clock signal: positive edge active
CLR	Asynchronous clear signal: active low
Q(3:0)	Output

The four operation modes are defined as follows:

M(1)	M(0)	Mode
0	0	Right shift: Serial_in to Q(3), Q(3) to Q(2), Q(2) to Q(1), Q(1) to Q(0)
0	1	Left shift: Serial_in to Q(0), Q(0) to Q(1), Q(1) to Q(2), Q(2) to Q(3)
1	0	Parallel load: P(3) to Q(3), P(2) to Q(2), P(1) to Q(1), P(0) to Q(0)
1	1	No change

This register can be constructed using four D flip-flops and four 4-to-1 multiplexers. The schematic is shown as follows:

 


Figure 2: Schematic of universal shift register.

To implement this register, you need to complete the following steps:

- (1) Complete the schematic shown in Figure 2 by labeling the **actual inputs** for each multiplexer,
- (2) Write the **behavioral** code for two components: D flip-flop and 4-to-1 multiplexer,
- (3) Write the **structural** code for the register,
- (4) Test the register by simulating it using a testbench. A sample testbench is provided in this document, which tests the asynchronous clear signal (i.e., CLR) and two modes: parallel load and right shift. You need to modify it to test the other two modes: no change and left shift.

Please use the template to prepare your report. You need to include the following items:

- (1) Schematic showing the appropriate signals at the multiplexer inputs,
- (2) Code for the components: D flip-flop and 4-to-1 multiplexer,
- (3) Code for the register,
- (4) Code for the testbench,
- (5) Simulation timing diagram verifying the four operation modes.

Sample testbench code

ENTITY shiftreg_test IS

END shiftreg_test;

ARCHITECTURE behavior OF shiftreg_test IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT shiftreg

PORT(

 P : IN std_logic_vector(3 downto 0);

 Q : OUT std_logic_vector(3 downto 0);

 clock : IN std_logic;

 clr : IN std_logic;

 serial_in : IN std_logic;

 m : IN std_logic_vector(1 downto 0)

);

END COMPONENT;

--Inputs

signal P : std_logic_vector(3 downto 0) := (others => '0');

signal clock : std_logic := '0';

signal clr : std_logic := '0';

signal serial_in : std_logic := '0';

signal m : std_logic_vector(1 downto 0) := (others => '0');

--Outputs

signal Q : std_logic_vector(3 downto 0);

```

-- Clock period definitions
constant clock_period : time := 20ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: shiftreg PORT MAP (
        P => P,
        Q => Q,
        clock => clock,
        clr => clr,
        serial_in => serial_in,
        m => m
    );

    -- Clock process definitions
    clock_process :process
    begin
        clock <= '0';
        wait for clock_period/2;
        clock <= '1';
        wait for clock_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- test CLR
        clr<='0';

```

```
wait for 30ns;

-- test parallel load
clr<='1';
m<="11";
P<="0110";
wait for 40ns;

-- test right shift
m<="01";
serial_in<='1';
wait for 80ns; -- shift 4 bits

wait;
end process;

END;
```