

Homework 7

Due date: Jun. 6th

Turn in your homework online before the class

Rules:

- Please work on your own. Discussion is permissible, but extremely similar submissions will be judged as plagiarism!
- Please show all intermediate steps: a correct solution without an explanation will get zero credit.
- Please submit on time. No late submission will be accepted.
- Please prepare your submission in English only. No Chinese submission will be accepted.

1

[8 points] Find the transfer function $H(\omega)$ with the Bode magnitude plots shown in **Fig 1:a** and **Fig 1:b**. The phase of $H(\omega)$ is 90° at $\omega = 0$ in both figures.

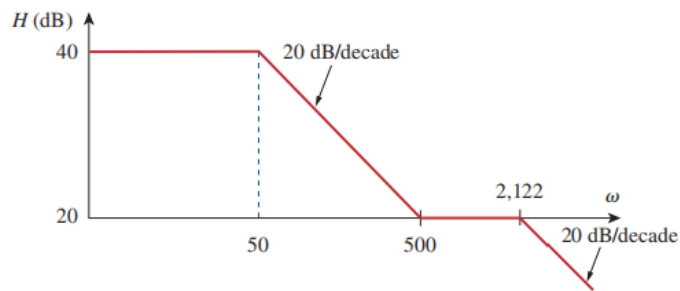


Figure 1: a

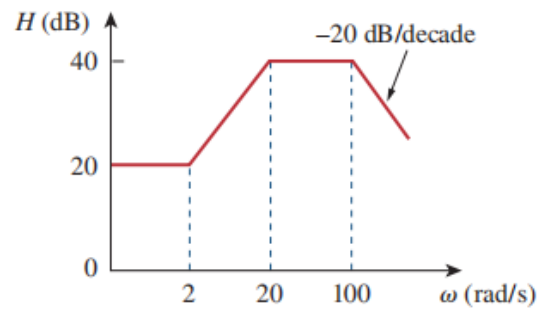


Figure 1: b

2

[12 points] For the circuit shown in **Fig 2**, find:

- (a). The resonant frequency ω_0
- (b). $Z_{in}(\omega_0)$

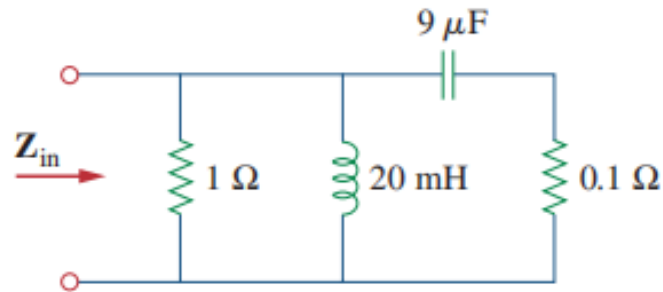


Figure 2:

3

[12 points] An example filter in **Fig 3** has the output of v_o and the input of v_s . Find the transfer function and determine the type of the filter. (Hint: it depends on the parameters, you need to discuss particular cases)

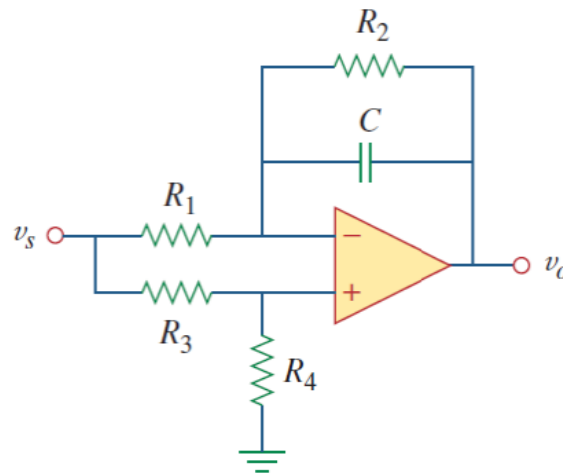


Figure 3:

4

[12 points] Find the transfer function of $\frac{V_o}{V_i}$ and determine the type of the filters shown in **Fig 4:a** and **Fig 4:b**.

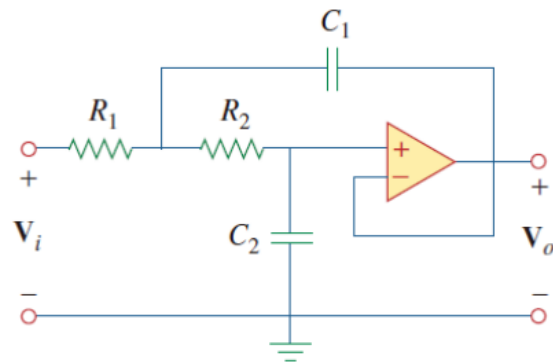


Figure 4: a

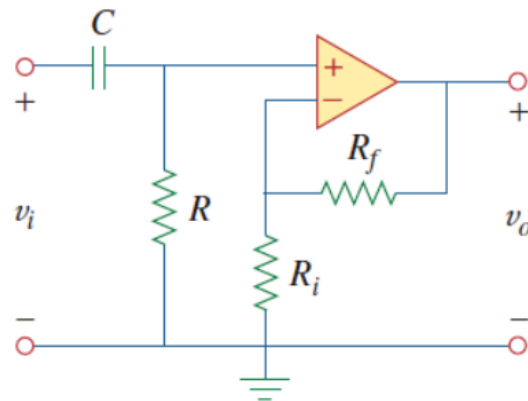


Figure 4: b

5

[14 points]

- (a). Obtain an expression for the transfer function.
- (b). Sketch the Bode Plots for the magnitude and phase of $H(\omega)$, given that $R_1 = R_2 = 100\Omega$, and $C_1 = 10\mu\text{F}$, $C_2 = 0.4\mu\text{F}$.
- (c). What type of filter is it? What is its maximum gain?

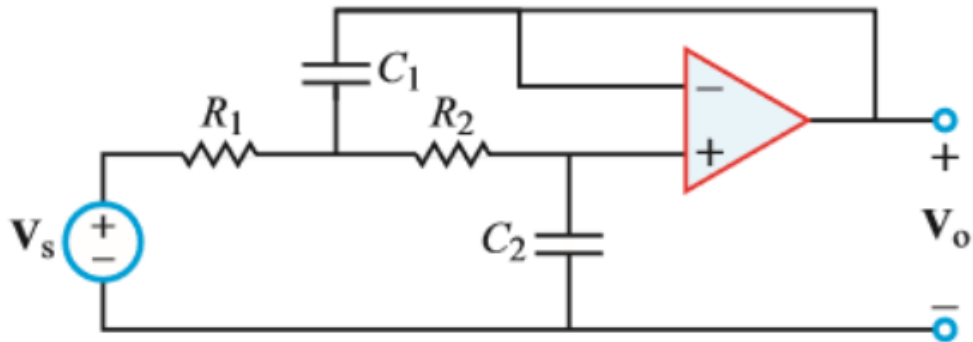


Figure 5:

6

[12 points] The AC circuit is as shown in **Fig 6**. Find:

- (a). The transfer function $H(\omega) = \frac{\dot{V}_o}{\dot{V}_{in}}$,
- (b). The type of the filter,
- (c). The bandwidth of the filter.

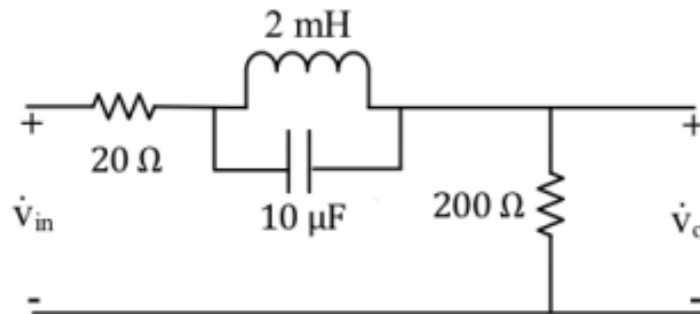


Figure 6:

7

[15points] In the following AC circuit, $R_1 = 10\text{k}\Omega$, $R_2 = 1\text{k}\Omega$, $R_3 = 10\text{k}\Omega$, $R_4 = 100\text{k}\Omega$, $R_5 = 5\text{k}\Omega$, $C_1 = 10\mu\text{F}$, $C_2 = 0.1\mu\text{F}$, $C_3 = 0.2\mu\text{F}$.

- Find $H(\omega) = \frac{\dot{V}_o}{\dot{V}_{in}}$,
- Sketch the Bode plots of $H(\omega)$. Please label the corner frequencies, the gains, phases and slopes of the plot.

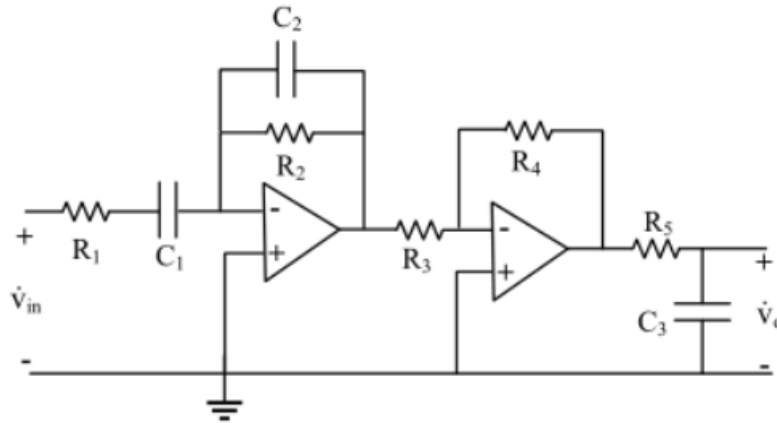


Figure 7:

8

[15 points] For the circuit shown in **Fig 8**

- Write the transfer function $H(\omega) = \frac{V_o}{V_i}$;
- Plot the Bode plots (including magnitude Bode plots and phase Bode plots) of $H(\omega)$, with proper notations on the Bode plots (such as cutoff frequencies, slope of the curves, etc.)
- Specify what type of filter it is.

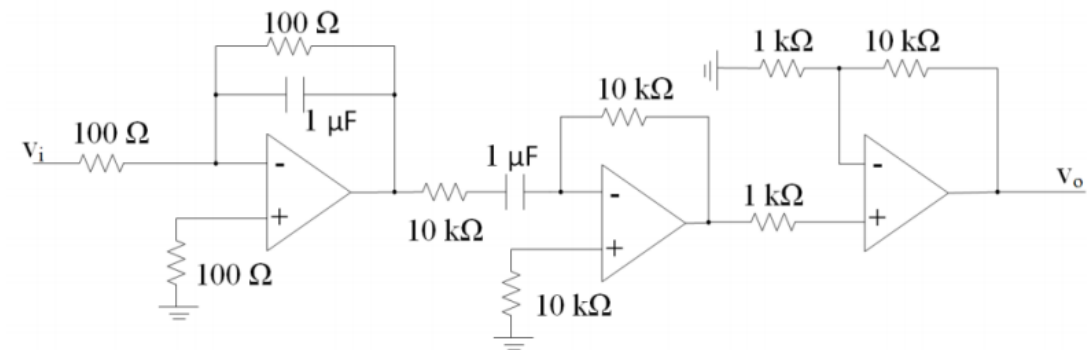


Figure 8: