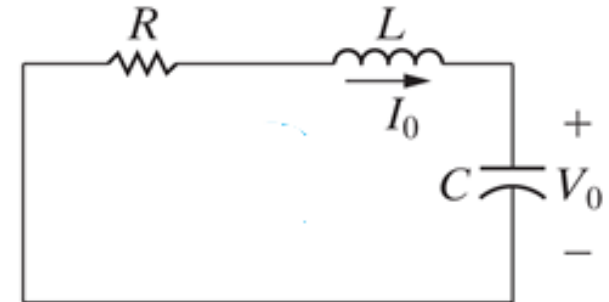


Properties of Series RLC Network - $v(t)$ $V_c(t)$

• Behavior captured by "damping"

- Gradual loss of the initial stored energy V_0
- α determines the rate of damping



$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha \gtrless \omega_0$$

- $\alpha > \omega_0$, overdamped

$$\rightarrow v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\textcircled{1} s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

- $\alpha = \omega_0$, critically damped


$$\rightarrow v(t) = (A_1 t + A_2) e^{-\alpha t}$$

$$\textcircled{2} s_1 = s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha$$

- $\alpha < \omega_0$, underdamped

$$\rightarrow v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$\textcircled{3}$

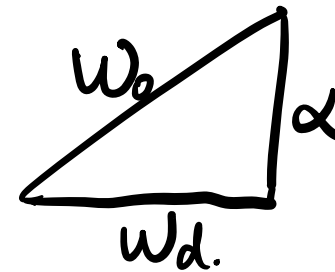


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

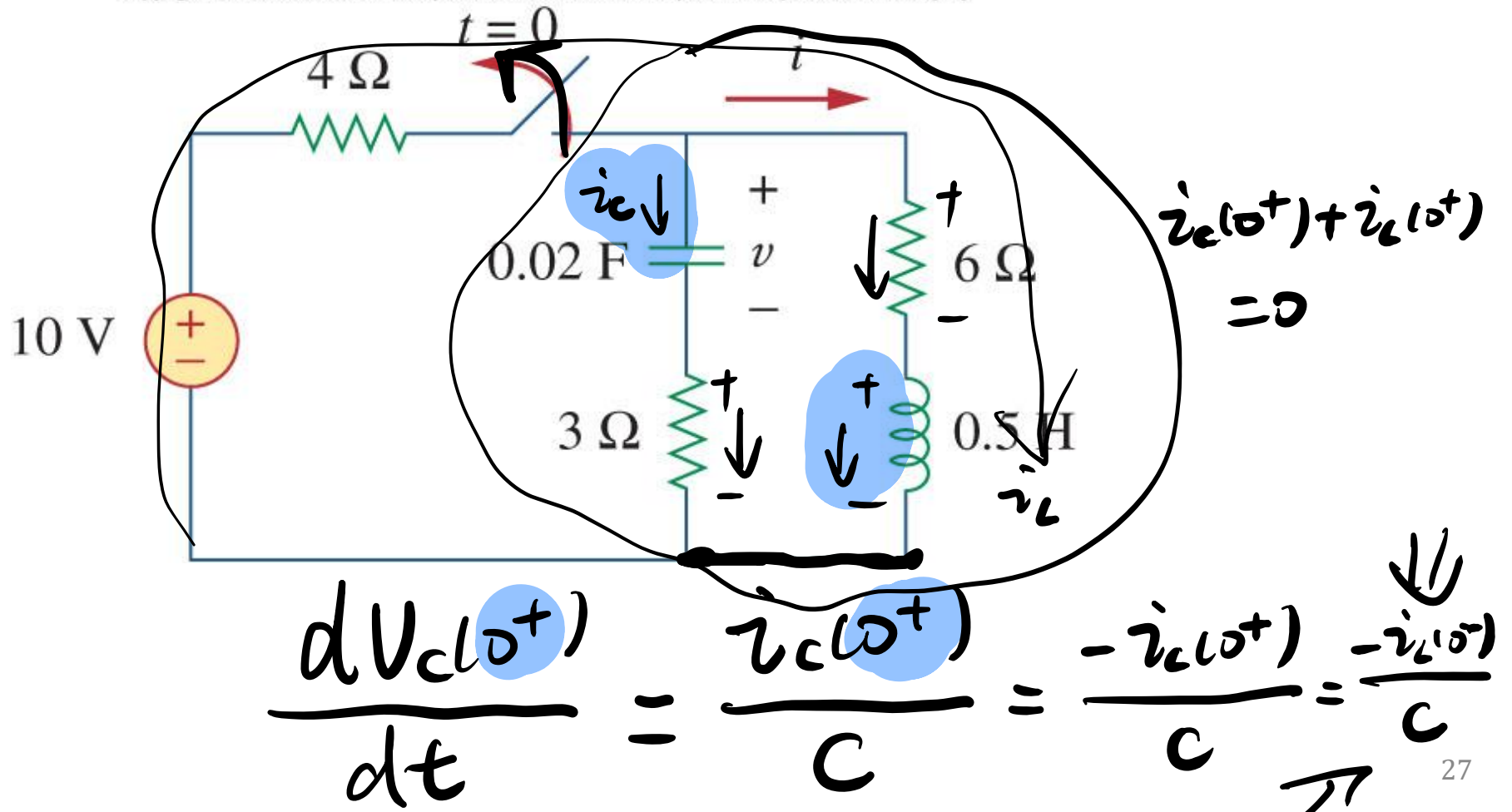Example

- Find $v(t)$ in the circuit below. Assume the circuit has reached steady state at $t = 0^-$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$i_L(0^-) = \frac{10}{4+6} = 1A$$

$$\frac{dV_{CC}(0^+)}{dt} = \frac{-1}{0.02} = 50V/s$$



$t > 0$ S-RLC-Network

$$R = 9\Omega, \quad L = 0.5H, \quad C = 0.02F$$

$$\alpha = \frac{R}{2L} = \frac{9}{1} = 9$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = 10$$

$$\alpha < \omega_0$$

underdamped.

$$V_c(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$
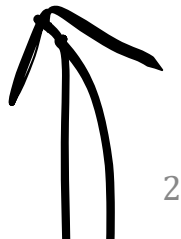
$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 4.36$$



$B_1, B_2?$

$$\langle 1 \rangle V_c(0^+) = V_c(0^-) = 6V$$

$(t < 0)$


$$\langle 2 \rangle \frac{dV_c(0^+)}{dt} = -50 V/s$$

$$\Rightarrow B_1 = 6 \quad B_2 = 0.82$$

$$V_c(t) = e^{-9t} [6 \cos 4.36t + 0.82 \sin 4.36t]$$

$t > 0$

Source-Free Series RLC Circuit

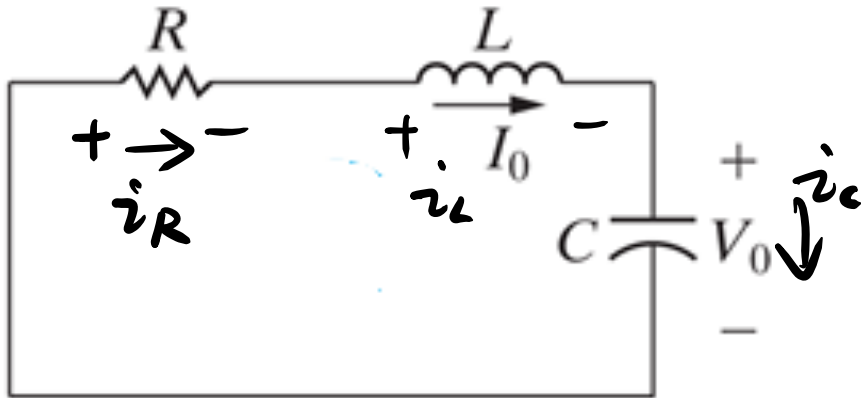

$$\text{Handwritten: } \hat{i}_L(t)$$

$$\mathcal{L} \frac{d\hat{i}_L(t)}{dt} = \underline{V_L(t)}$$

$$\hat{i}_L(t) = i_R = i_C$$

$$i_R \cdot R = \hat{i}_L(t) \cdot R = \underline{V_R(t)}$$

$$\frac{1}{C} \int_{-\infty}^t \hat{i}_L(t) dt = \frac{1}{C} \int_{-\infty}^t \underline{\hat{i}_C(t)} dt = \underline{V_C(t)}$$

$$V_L + V_R + V_C = 0$$

$$\left[L \cdot \frac{di_L(t)}{dt} + \underbrace{i_L(t) \cdot R} + \frac{1}{C} \int_{-\infty}^t i_L(t) \cdot dt \right]' = 0$$

$$\frac{d^2 i_L(t)}{dt^2} + \frac{R}{L} \cdot \frac{di_L(t)}{dt} + \frac{1}{LC} \cdot i_L(t) = 0$$

$$\alpha = \frac{R}{2L}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha \begin{matrix} > \\ = \\ < \end{matrix} \omega_0$$

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \cdot \frac{dv_C}{dt} + \frac{1}{LC} v_C = 0$$

Properties of Series RLC Network - $i(t)$

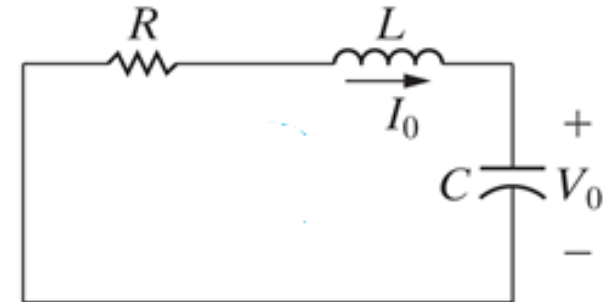- Behavior captured by damping
 - Gradual **loss** of the initial stored energy
 - α determines the rate of damping



$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

- $\alpha > \omega_0$, overdamped

$$\underline{i(t)} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

- $\alpha = \omega_0$, critically damped

$$\underline{i(t)} = (A_1 t + A_2) e^{-\alpha t}$$

- $\alpha < \omega_0$, underdamped


$$\underline{i(t)} = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\begin{aligned} & i_L(0^+) \checkmark \\ & \frac{d i_L(0^+)}{dt} \checkmark \Rightarrow A_1, A_2 \end{aligned}$$

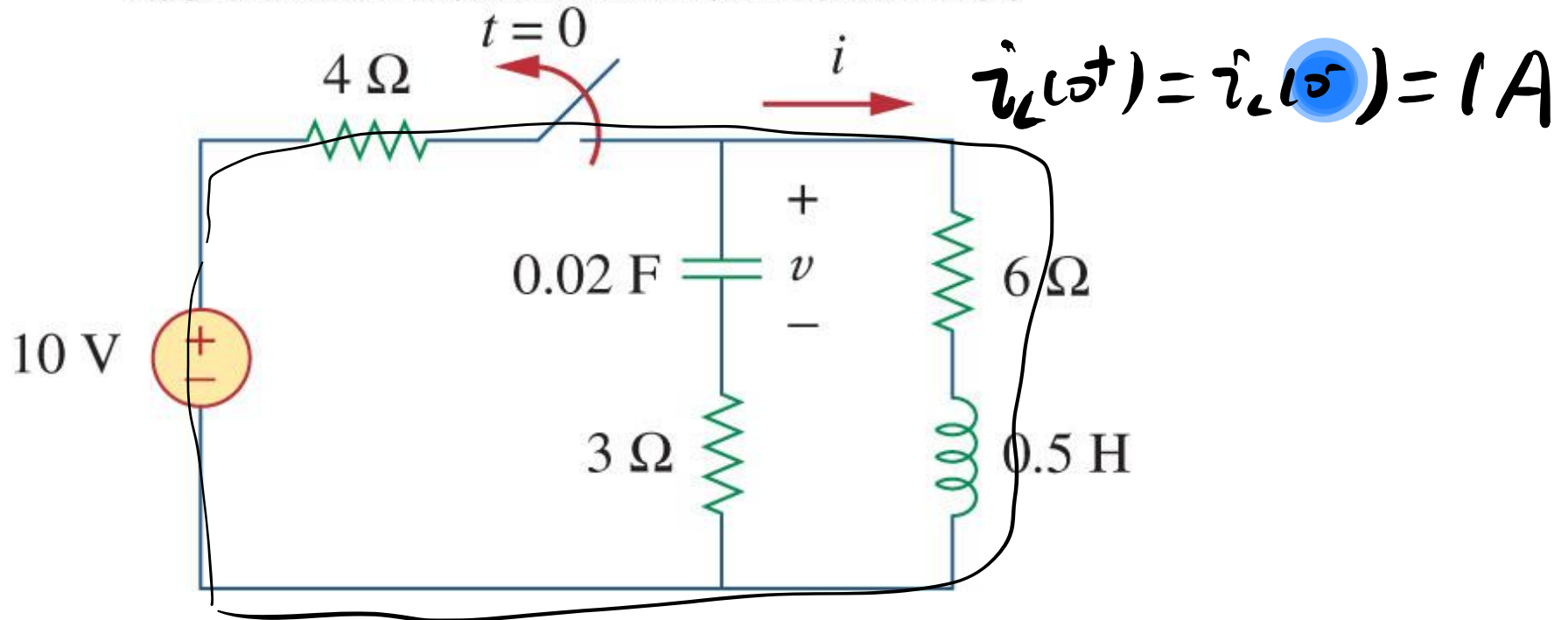Example

- Find $i(t)$ in the circuit below. Assume the circuit has reached steady state at $t = 0^-$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\alpha = \frac{R}{2L} = 9, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10$$

$\alpha < \omega_0$ underdamped \downarrow


- $\alpha < \omega_0$, underdamped

$$\Rightarrow \underline{i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 4.36$$

B_1 B_2 $i_L(0^+) = i_L(0^-) = ?$ **1 A**

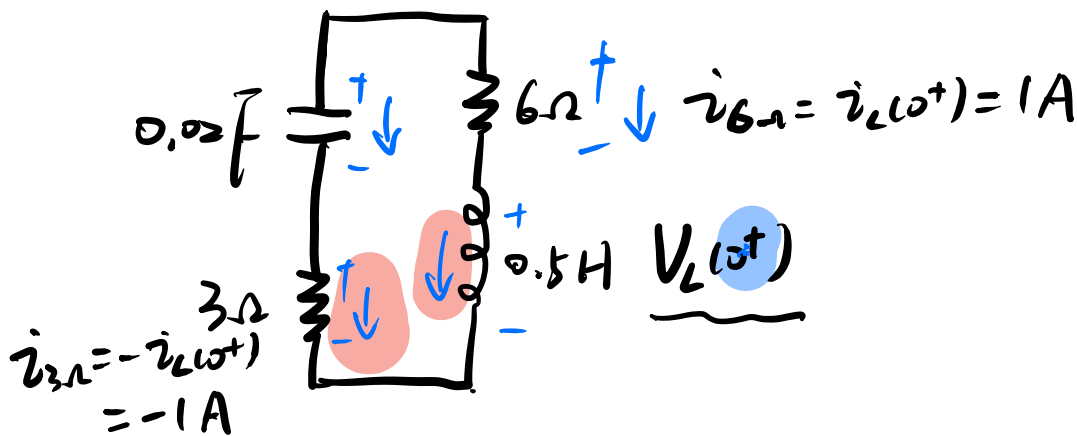? $\frac{di_L(0^+)}{dt} = \frac{V_L(0^+)}{L} = \frac{-3}{0.5} = -6 \text{ A/s}$



$$V_C(0^+) + V_{3\Omega} = V_{6\Omega} + \underline{V_L(0^+)}$$

$$V_L(0^+) = V_C(0^+) + \underline{V_{3\Omega}^{(0^+)}} - V_{6\Omega}^{(0^+)}$$


$$= \underline{V_C(0^-)} + \underline{i_{3\Omega} \times 3\Omega} - \underline{i_{6\Omega} \times 6\Omega}$$

$$= 6 \text{ V} + (-1) \times 3 - 1 \times 6 = \underline{-3 \text{ V}}$$

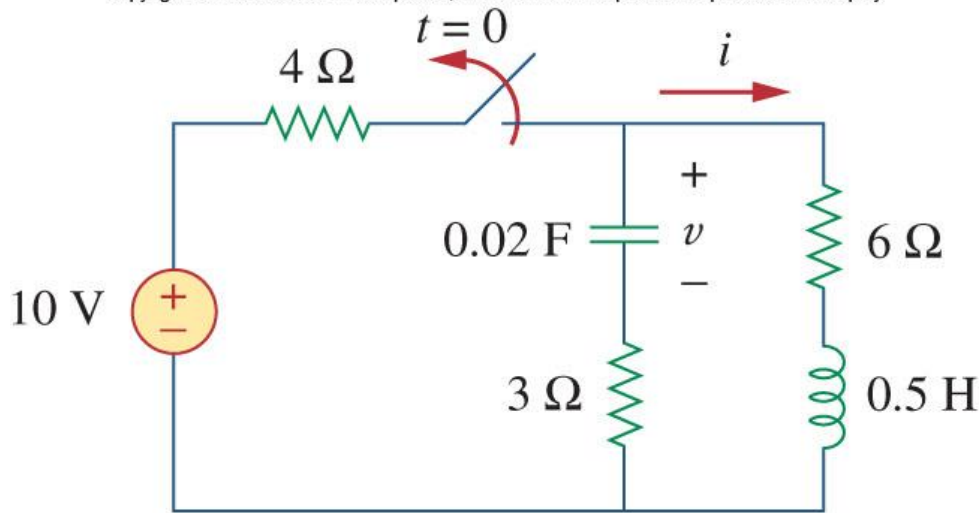Example



- Find $i(t)$ in the circuit below. Assume the circuit has reached steady state at $t = 0^-$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\alpha = \frac{R}{2L} = 9 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10$$
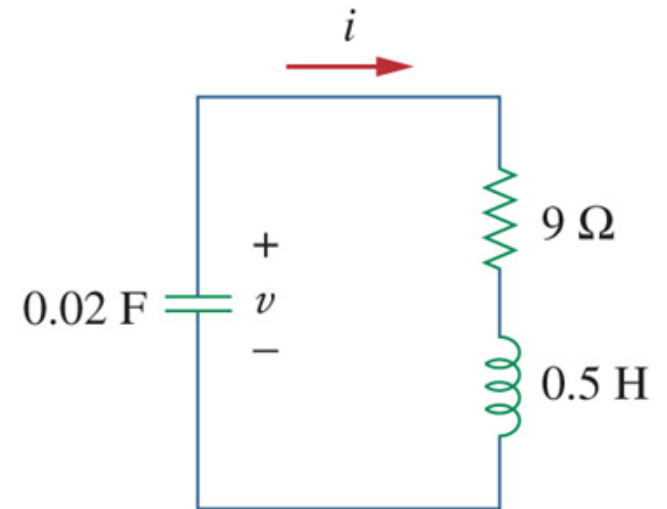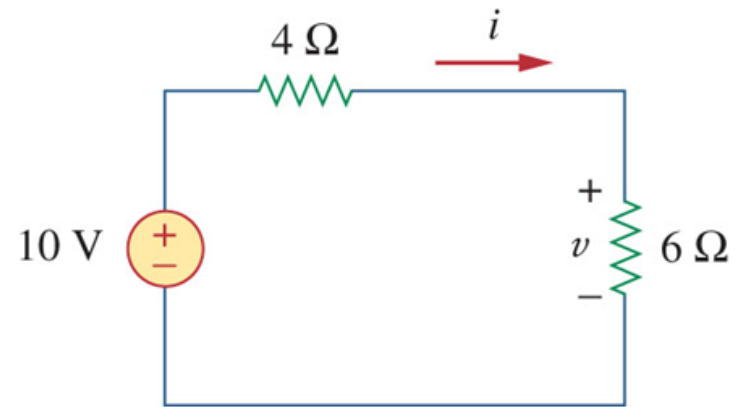
$$s_{1,2} = -\alpha \mp \sqrt{\alpha^2 - \omega_0^2} = -9 \mp j4.359$$








Source-Free Parallel RLC Network

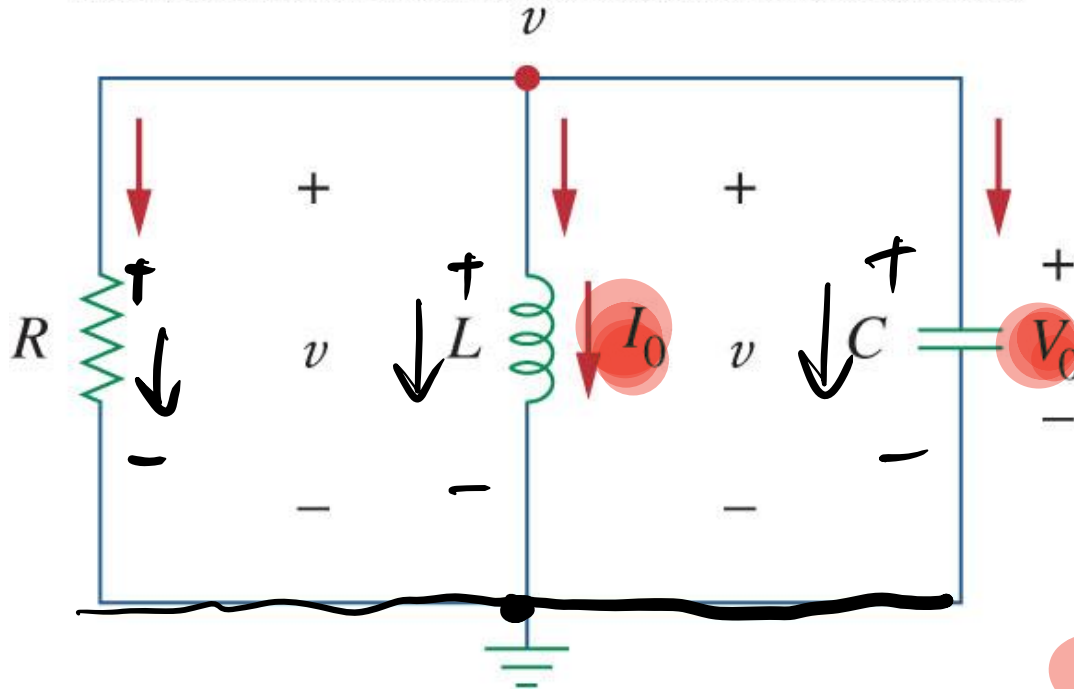Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$V_C(t) ?$$

$$i_C(t) = C \cdot \frac{dV_C(t)}{dt}$$

$$i_R(t) = \frac{V_R(t)}{R} = \frac{V_C(t)}{R}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t V_L(t) dt$$
$$= \frac{1}{L} \int_{-\infty}^t V_C(t) dt$$

KCL:

$$\left[C \cdot \frac{dV_c}{dt} + \frac{V_c}{R} + \frac{1}{L} \int_{-\infty}^t V_c dt \right]' = 0$$

$$\frac{d^2 V_c}{dt^2} + \frac{1}{RC} \frac{dV_c}{dt} + \frac{1}{LC} V_c = 0$$

$$\alpha = \frac{1}{2RC} \quad , \quad \omega_0 = \frac{1}{\sqrt{LC}}$$


$$\alpha \begin{matrix} > \\ = \\ < \end{matrix} \omega_0$$

Source-Free Parallel RLC Network - $v(t)$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

- The characteristic equation is:
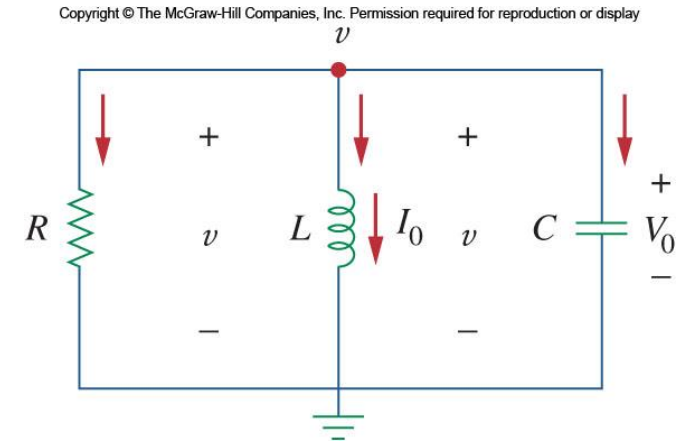
$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$



From this, we can find the roots of the characteristic equation to be:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

As in last time, there are three scenarios to consider.

Three Damping Cases - $v(t)$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\underline{\alpha} = \frac{1}{2RC} \quad \underline{\omega_0} = \frac{1}{\sqrt{LC}}$$

- For the overdamped case, the roots are real and negative,

$\alpha > \omega_0$ $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$


- For critically damped, the roots are real and equal


$\alpha = \omega_0$ $v(t) = (A_1 t + A_2) e^{-\alpha t}$

- In the underdamped case, the roots are complex

$\alpha < \omega_0$ $v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$

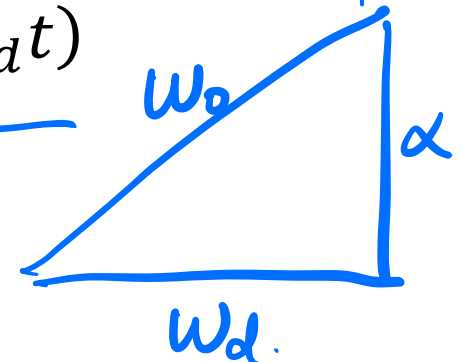$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$



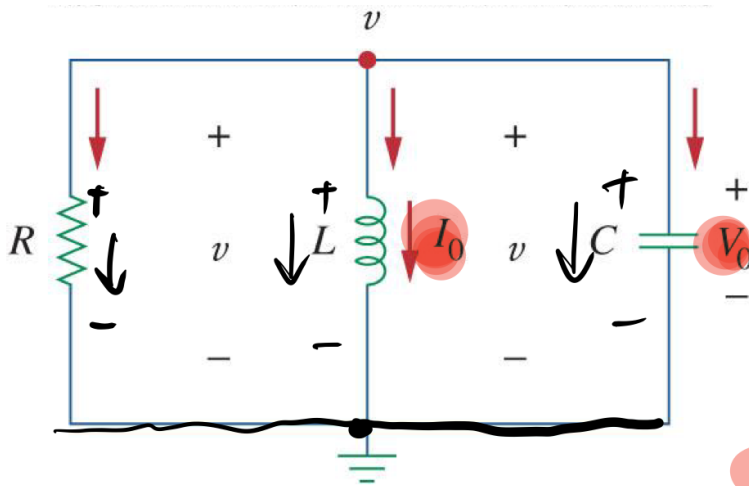

$i_L(t)$?

$$L \frac{d i_L(t)}{dt} = \underline{V_L(t)}$$

$$V_L(t) = \underline{V_R(t)} = \underline{V_C(t)}$$

$$i_R(t) = \frac{V_R(t)}{R} = \frac{V_L(t)}{R} = \frac{L}{R} \cdot \frac{d i_L(t)}{dt}$$

$$i_C(t) = C \cdot \frac{d V_C(t)}{dt} = L C \cdot \frac{d^2 i_L(t)}{dt^2}$$

$$i_L(t) = i_L(t)$$

$$\text{KCL: } i_R + i_C + i_L = 0$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{d i_L}{dt} + \frac{1}{LC} i_L = 0 \quad (i_L)$$

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

α

{

ω_0

$$\frac{d^2 V_c}{dt^2} + \frac{1}{RC} \frac{dV_c}{dt} + \frac{1}{LC} V_c = 0 \quad (V_c)$$

Three Damping Cases - $i(t)$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

- For the overdamped case, the roots are real and negative,


$$\alpha > \omega_0 \quad i(t) = \underline{A_1} e^{s_1 t} + \underline{A_2} e^{s_2 t}$$

- For critically damped, the roots are real and equal

$$\alpha = \omega_0 \quad i(t) = (\underline{A_1} t + \underline{A_2}) e^{-\alpha t}$$

- In the underdamped case, the roots are complex
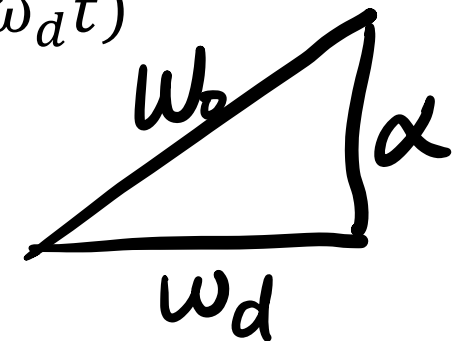
$$\alpha < \omega_0 \quad i(t) = e^{-\alpha t} (\underline{B_1} \cos \omega_d t + \underline{B_2} \sin \omega_d t)$$



Series vs. Parallel (Source-Free RLC Circuit)

• Series


$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$v_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v_c(t) = (A_1 t + A_2) e^{-\alpha t}$$

$$v_c(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

OR $i_L(t)$: 3 cases \uparrow

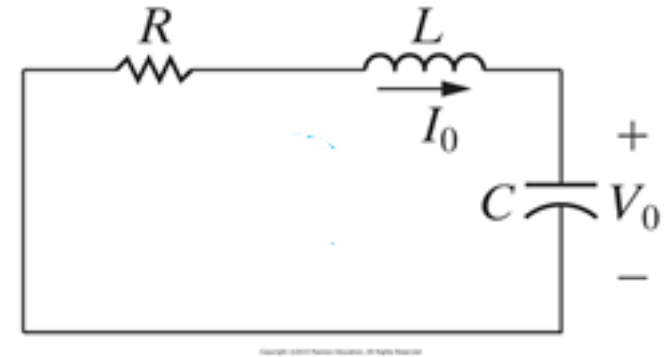

• Parallel

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$v_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v_c(t) = (A_1 t + A_2) e^{-\alpha t}$$

$$v_c(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

OR $i_L(t)$: 3 cases \uparrow

